
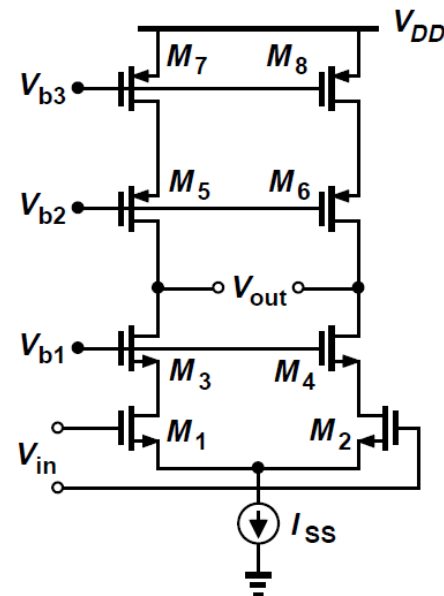


Chapter 9: Operational Amplifiers

- | | |
|-----------------------------------|------------------------------------|
| 9.1 General Considerations | 9.7 Common Feedback |
| 9.2 One-Stage Op Amps | 9.8 Input Range Limitations |
| 9.3 Two-Stage Op Amps | 9.9 Slew Rate |
| 9.4 Gain Boosting | 9.10 High-Slew-Rate Op Amps |
| 9.5 Comparison | 9.11 Power Supply Rejection |
| 9.6 Output Swing | 9.12 Noise in Op Amps |

Op Amp Definition

 - We loosely define an op amp as a “high-gain differential amplifier.”
- Usually employed in a feedback system when precision is a requirement.
- Applications ranging from DC generation, high-speed amplification or filtering.



Op Amp Design Challenge

Three decades ago


- **General-purpose blocks as an “ideal” op amp**
- **Design effort is to satisfy an ideal op amp**
 - **infinite gain**
 - **infinite input impedance**
 - **zero output impedance**

Today

- **Design effort is to make trade-offs for a specific application, often sacrificing the unimportant aspects to improve the critical ones.**
- **E.g., gain error vs speed, open loop gain vs VDD**


Performance Parameter

- Gain(Precision), Bandwidth(Speed): 3-dB/fu
Output Swing, Power dissipation
- Noise, Linearity, Supply Rejection, offset
- Input CM Range, Input/Output Impedance
- Large-Signal behavior (e.g. slew rate)

 

 Example 9.1

The circuit has a nominal gain of 10. i.e., $1 + R_1/R_2 = 10$. Determine the minimal value of A_1 for a gain error 1%:



Solution:


$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1} \\ &= \frac{R_1 + R_2}{R_2} \frac{A_1}{\frac{R_1 + R_2}{R_2} + A_1}\end{aligned}$$

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1}\right)$$

Thus, $A_1 > 1000$. Open-loop gain determines precision.

 Example 9.2

Assume the op amp is a single-pole voltage amplifier. For a small step input, calculate the time required for the output to reach within 1% and its unity-gain bandwidth if $1+R_1/R_2=10$ and its settling time is less than 5ns.





Solution: Speed vs. Bandwidth

$$\tau \approx \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0 \omega_0} \quad \tau \approx 1.09 \text{ ns}$$

$$1 - \exp\left(-\frac{t_{1\%}}{\tau}\right) = 0.99 \quad A_0 \omega_0 \approx (1 + R_1/R_2)/\tau = 9.21 \text{ Grad/s (1.47 GHz)}$$

  Example 9.3

Explain the circuit behavior if we swap the inverting and non-inverting inputs of the op amp.





Solution: Positive feedback destabilizes the circuit.
Output grows exponentially to non-linearity range.

$$\frac{V_{out}}{V_{in}}(s) = \frac{\frac{A_0}{1 - \frac{R_2}{R_1 + R_2} A_0}}{1 - \frac{\frac{R_2}{(1 + \frac{R_2}{R_1 + R_2} A_0) \omega_0}}{s}}$$

$$V_{out}(t) \approx a \left(1 + \frac{R_1}{R_2} \right) \left(\exp \frac{t}{\tau} - 1 \right) u(t)$$


One-Stage Op Amps

- Low-frequency gain: $g_{mN}(r_{ON}||r_{OP})$
- Bandwidth: usually proportional to $1/(C_L \cdot R_{out})$
- Output Swing (single-side): $V_{DD} - 3 \cdot \text{Overdrive}$
- Mirror pole in single-ended circuit
- Power and noise: good, with four devices $\rightarrow$ input noise

  

 Example 9.4

Calculate the input common-mode voltage range and the closed-loop output impedance of the unity-gain buffer.



Solution:



$$V_{ISS} + V_{GS1} < V_{in} < V_{in,max} = V_{DD} - |V_{GS3}| + V_{TH1}$$

Output impedance: $(r_{OP} || r_{ON}) / [g_{mN}(r_{OP} || r_{ON})] = 1/g_{mN}$

The closed-loop pole is independent of open-loop output impedance.


Telescopic Cascode Op Amps

- Low-frequency gain: $g_{mN}[(g_{mN}r_{ON}^2) \parallel (g_{mP}r_{OP}^2)]$
- Speed: Additional poles
- Output Swing (single-side): $V_{DD} - 5V_{\text{Overdrive}}$
- Mirror pole in single-ended
- Difficult to short telescopic op amp output to input
- Power and noise: good, input noise mainly has four devices contribution

  

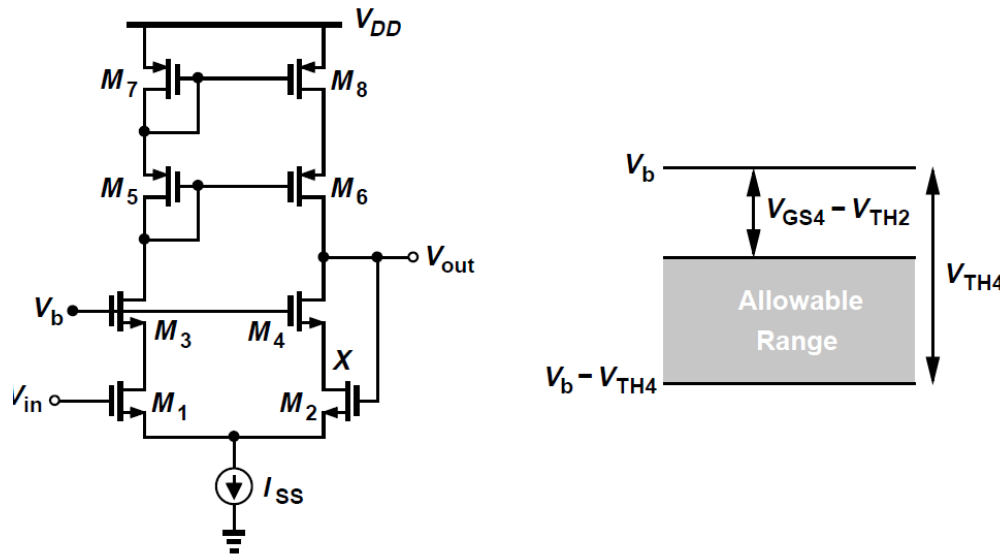Example 9.5

For this unity-gain buffer configuration, explain in which region each transistor operates as V_{in} varies from below $V_b - V_{GS4} + V_{TH2}$ to above $V_b - V_{TH4}$



Solution: Remedy in switched-capacitor circuit


When $V_{in} < V_b - V_{TH4}$, M_4 is in triode, others are saturated;

$V_b - V_{TH4} < V_{in} < V_b - (V_{GS4} - V_{TH2})$ M_2, M_4 are saturated;


$V_{in} > V_b - (V_{GS4} - V_{TH2})$ M_2, M_1 in triode, M_4 is in saturation.

 Example 9.6


Assuming that the op amp has a high open-loop gain, determine the maximum allowable output swing.




(a)

 

(b)

 

(c)

 

(d)

Solution: $\pm(\text{one threshold-one overdrive})$

Telescopic Cascode Op Amps Design


- Generally, power budget determines branch current
- Gain and Output voltage swing
- Deal with I_D , $V_{GS} - V_{TH}$, W/L , g_m and r_O

Design Procedure (Example 9.7)

- Define drain current
- Distribute overdrive voltage
- Calculate the aspect ratio

$$I_D = (1/2)\mu C_{ox}(W/L)(V_{GS} - V_{TH})^2$$

 - Calculate the gain with Lmin
- Iteration by increasing W,L until achieving gain criterion
- Finally, DC bias voltage setup and exam residual goals
- CMFB is necessary



$$g_m r_O = \sqrt{2\mu C_{ox}(W/L)I_D}/(\lambda I_D)$$

PMOS>Cascode_N>Input_N

Linear Scaling

- How to modify design if power budget is different while all the other specifications are the same?
- Only scale the widths of all the transistors while keeping the lengths constant.

Example 9.6


Explain what aspects of the performance degrade for a low-power op amp design when we scale down the transistor width.

Solution:

 - (1) The speed of the op amp in driving a capacitive load
- (2) The input-referred noise voltage rises by a square root factor of scale constant. (for input device)

Gate Bias Voltage Generation

- Ensure bias voltage to track the input CM level
- Choose Mb1 to be a narrow, long, “weak” device





$$V_{b1} = V_P + V_{GS,b1}$$

$$V_{GS,b1} = (V_{GS1,2} - V_{TH1,2}) + V_{GS3,4}$$

Folded Cascode Op Amps

Recall Folded Cascode

 
 
- Not “stack” the cascode transistor on the input device
- Consume higher power
- Output Voltage Swing: $V_{DD} - 4\text{overdrive}$
- Output and input could short together



Folded Cascode Voltage Gain



$$|A_v| = G_m R_{out}$$

- **Since** $(g_{m3} + g_{mb3})^{-1} \parallel r_{O3} \ll r_{O1} \parallel r_{O5}$, **thus** $G_m \approx g_m$
- $|A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3}) r_{O3} (r_{O1} \parallel r_{O5})] [(g_{m7} + g_{mb7}) r_{O7} r_{O9}] \}$
- **Two or three times lower than a telescopic topology**

  



Effect capacitance on the nondominant pole

  - At “folding point”, a large capacitance due to a large current device M_5 would be added to the total capacitance.




NMOS vs. PMOS input

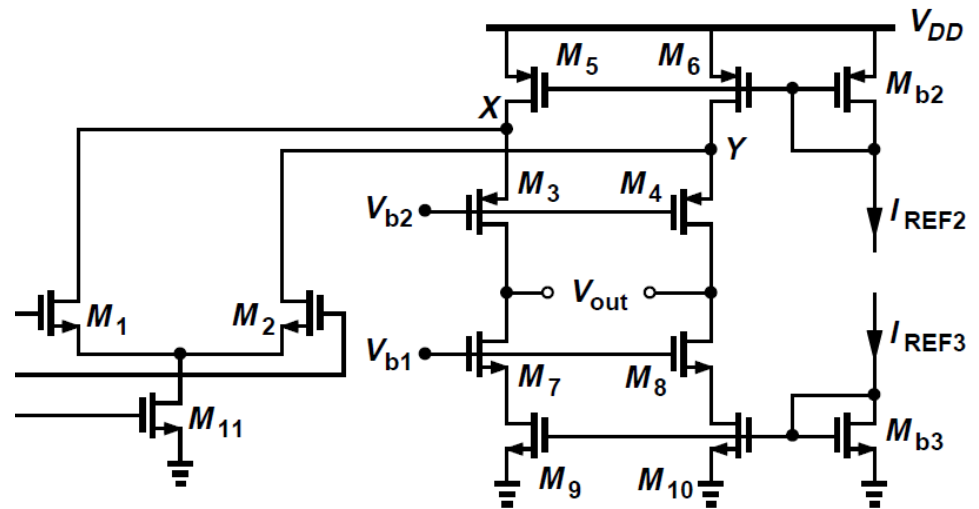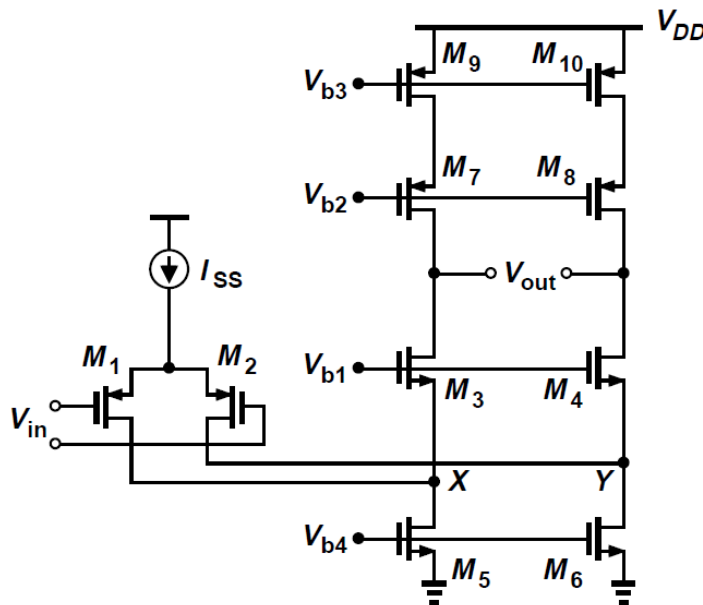- Greater mobility from NMOS input leads to higher gain
- Lowering the pole at folding point
- PMOS input is less sensitive to flicker noise(wider WL)



Folded Cascode Properties

- Slighter Higher Output Swing than telescopic
- Higher Power dissipation, lower voltage gain, lower pole frequency and higher noise
- Input and output can be shorted: 2overdrive from bound
- A better input CM range

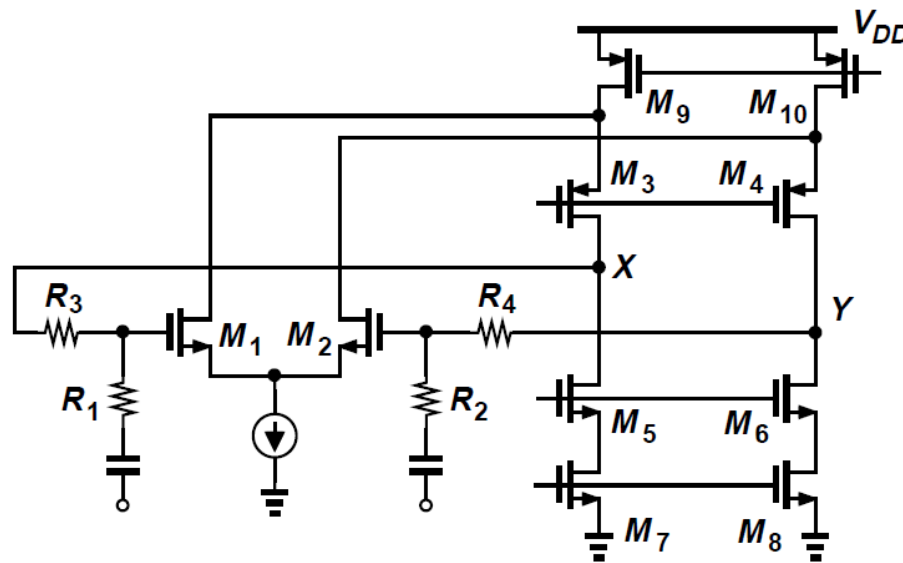

Example 9.9

Design a folded- cascode op amp with an NMOS pair.

Specifications: $V_{DD} = 3V$, differential output swing = $3V$,

Power dissipation = $10mW$, voltage gain = 2000 .

Solution:


(1)Current allocation

(2)Overdrive voltage allocation

(3)Aspect ratio calculation

(4)Small-signal gain with minimal length


 
(5)Iteration by increase $M_5/M_1/M_4$ in turns



Note that the folding point capacitance may limit here.




Low Voltage Single-ended Output

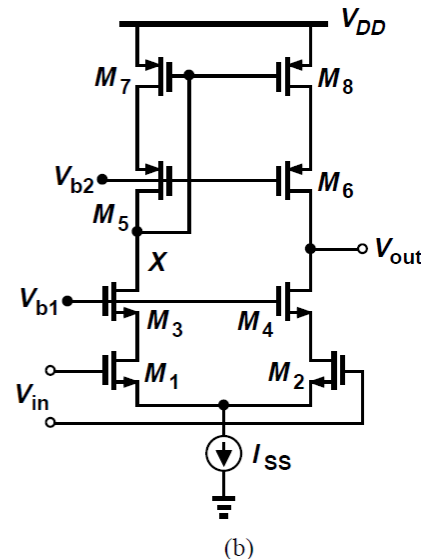 - M7 is biased at the edge of triode
Could M5 always be in saturation?
- Left implementation wastes one threshold voltage
- Still, single-ended output is unfavorable due to half output swing and a mirror pole
- Note that almost all the differential output circuits need a CMFB




Two-Stage Op Amps

   - Voltage headroom in today's design is constrained with low supply voltage and large output swing
- **Gain:** $g_{m1,2}(r_{O1,2} \parallel r_{O3,4}) \cdot g_{m5,6}(r_{O5,6} \parallel r_{O7,8})$
- **Output Swing:** $V_{DD} - 2 \cdot \text{Overdrive}$



Two-Stage Op Amps With cascode devices

 - Voltage headroom in today's design is constrained with low supply voltage and large output swing
- **Gain:** $A_v \approx \{g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{O3,4}r_{O1,2}] \parallel [(g_{m5,6} + g_{mb5,6})r_{O5,6}r_{O7,8}]\} \times [g_{m9,10}(r_{O9,10} \parallel r_{O11,12})]$
- Can we have more stages? Feedback stability limits



Two-Stage Op Amps Design

Example

9.10

Design the two-stage op amp for $V_{DD} = 1V$, $P = 1mW$, a differential output swing of 1 Vpp, and a gain of 100.

Solution:

(1)Current allocation

(2)Voltage allocation:


300mV to M_7 , 200mV to M_5 ,

400mV to M_3 , 100mV to M_1

(noise and gm consideration)


(3)Calculate aspect ratio

(4)Calculate gain > 2000

 

Gain Boosting

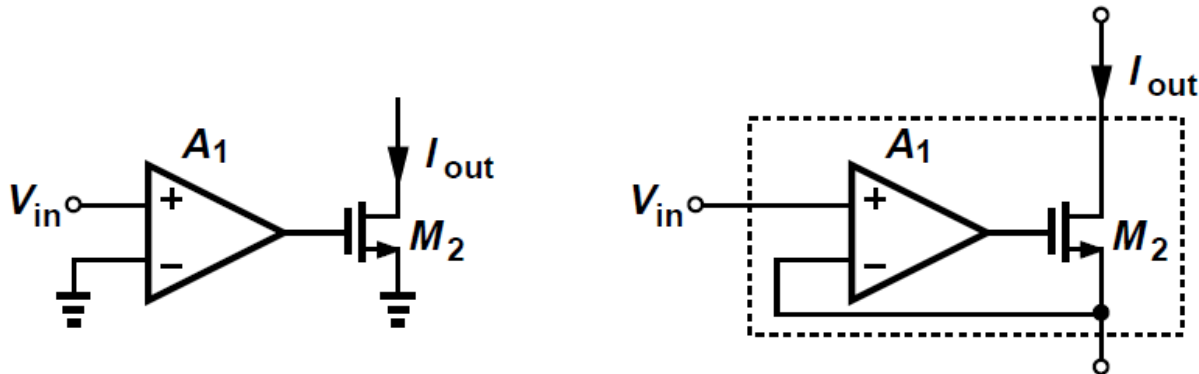- Increase the output impedance without adding more cascode devices. But how?
- A transistor preceded by an ideal voltage amplifier exhibits a transconductance of $g_m A_1$ and a output resistance of r_o .



Gain Boosting



- Increase the output impedance without adding more cascade devices. But how?
- First Perspective:

A degenerated transistor preceded by an ideal voltage amplifier

$$\frac{I_{out}}{V_{in}} = \frac{A_1 g_m}{1 + (A_1 + 1) g_m R_S}$$

$$R_{out} = r_O + (A_1 + 1) g_m r_O R_S + R_S.$$

In fact, the output resistance is “boosted”. The headroom is similar to a simple degenerated transistor

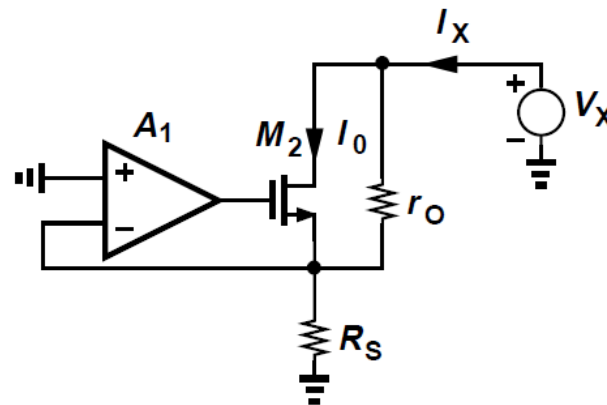 



Example 9.11

Determine the resistance seen at the source of M2 without considering body effect.

Solution:

$$\frac{I_X R_D - V_X}{r_O} + (-A_1 V_X - V_X)g_m + I_X = 0$$
 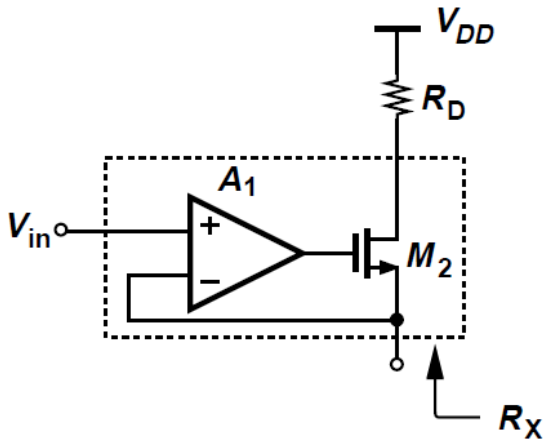
$$R_X = \frac{R_D + r_O}{1 + (A_1 + 1)g_m r_O}$$



Basic gain-boosted stage


- Current-Voltage feedback increase the output impedance by a factor of A_1+1 , while the real g_m raised by A_1 is reduced by A_1+1 when feedback is applied.

- Rout: $R_{out} = r_O + (A_1 + 1)g_m r_O R_S + R_S$.
- Gm: $g_{m1}A_1/(A_1+1) \sim g_{m1}$
- Rp:(look above P, see example 9.11)

$$r_{O2}/[1 + (A_1 + 1)g_{m2}r_{O2}] \approx [(A_1 + 1)g_{m2}]^{-1}$$

($\ll r_{O1}$, can be neglected)



$$\begin{aligned} |A_v| &\approx g_{m1}[r_{O2} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O1}] \\ &\approx g_{m1}g_{m2}r_{O1}r_{O2}(A_1 + 1). \end{aligned}$$

 

Regulated Cascode

Second Perspective

- Loosely view the voltage change divided by R_S and $g_m r_O R_S$.
- Drain current response can be suppressed as
 - V_P is constant
 - Current through R_S is constant
- V_P is “pinned” to V_B by feedback regulation.

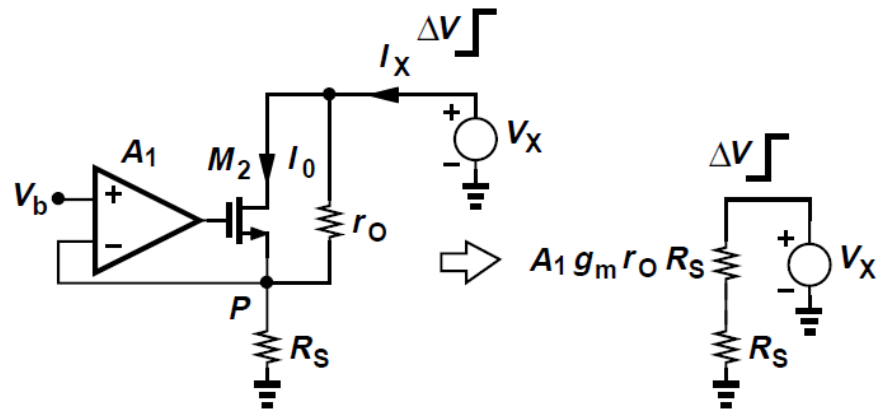 

Example 9.12

Determine the small-signal values of V_P , V_G , I_0 , and I_{ro} .

Assume $(A_1 + 1)g_m r_O R_S$ is large.


Solution: Current circulates M2

$$V_X = [r_O + (A_1 + 1)g_m r_O R_S + R_S]I_X$$

$$\begin{aligned} V_P &= I_X R_S \\ &= \frac{R_S}{r_O + (A_1 + 1)g_m r_O R_S + R_S} V_X. \end{aligned}$$

$$\begin{aligned} V_G &= -A_1 V_P \\ &= \frac{-A_1 R_S}{r_O + (A_1 + 1)g_m r_O R_S + R_S} V_X \end{aligned}$$

$$V_G - V_P \approx -V_X / (g_m r_O).$$

 

$$I_0 \approx -V_X / r_O$$

$$\begin{aligned} I_{ro} &= \frac{V_X - V_P}{r_O} \\ &= \frac{r_O + (A_1 + 1)g_m r_O R_S}{r_O + (A_1 + 1)g_m r_O R_S + R_S} \frac{V_X}{r_O} \\ &\approx \frac{V_X}{r_O}. \end{aligned}$$

Gain boosting Key


- The amplifier boosts the gm of the cascode device
- The amplifier regulates the output current by monitoring and pinning the source voltage

Gain Boosting Circuit Implementation

- Simplest a common-source stage

$$|V_{out}/V_{in}| \approx g_{m1}r_{O1}g_{m2}r_{O2}(g_{m3}r_{O3} + 1)$$

- Avoid headroom limitation, PMOS common-source stage is better, but M3 could go in triode
- Folded-cascode inserts one more stage

 


Example 9.13

Determine the allowable range for V_b .

Solution:


$$V_{b,min} = V_{GS4} + V_{I1}$$

$$V_{b,max} = V_{GS2} + V_P + V_{TH4}$$

 


Gain Boosting with a Differential Pair

 
- One threshold higher than a simple differential circuit
- Merge two gain boosting blocks to differential one



(a)

 



(b)

 


(c)

Gain Boosting in Signal Path and Load

  - Gain boosting can be utilized in the load current source
- To allow maximum swings, A_2 employs NMOS-input.



Gain Boosting Frequency Response

 

$$G_m(s) = g_{m1} \frac{r_{O1}}{r_{O1} + \frac{r_{O2}}{1 + (A_1 + 1)g_{m2}r_{O2}}}$$

$$Z_{out} = [r_{O1} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O2}] \parallel \frac{1}{C_L s}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-g_{m1}r_{O1}[(1 + g_{m2}r_{O2})\frac{s}{\omega_0} + (A_0 + 1)g_{m2}r_{O2} + 1]}{\frac{(r_{O1} + r_{O2})C_L}{\omega_0}[1 + g_{m2}(r_{O2} \parallel r_{O1})]s^2 + [(r_{O1} + r_{O2})C_L + (A_0 + 1)g_{m2}r_{O2}r_{O1}C_L + \frac{1}{\omega_0}]s + 1}$$

• **Zero:**

$$|\omega_z| \approx (A_0 + 1)\omega_0$$

• **Dominant pole:**

$$|\omega_{p1}| = \frac{1}{[r_{O1} + (A_0 + 1)g_{m2}r_{O2}r_{O1} + r_{O2}]C_L + \frac{1}{\omega_0}}$$

$$\approx \frac{1}{A_0 g_{m2} r_{O2} r_{O1} C_L}$$


• **Non-dominant pole: Above the original-3dB bandwidth**

$$|\omega_{p2}| = \frac{[r_{O1} + (A_0 + 1)g_{m2}r_{O2}r_{O1} + r_{O2}]C_L + \frac{1}{\omega_0}}{\frac{(r_{O1} + r_{O2})C_L}{\omega_0}[1 + g_{m2}(r_{O1} \parallel r_{O2})]}$$

$$\approx (A_0 + 1)\omega_0 + \frac{1}{g_{m2}r_{O2}r_{O1}C_L}$$

Frequency Response Bode Plot

- Gain boosting frequency response bode plot
- Two poles, non-dominant is below the original 3dB pole

 

Example 9.15

Is the dominant-pole approximation valid here.

Solution:

$$\begin{aligned}\frac{\omega_{p2}}{\omega_{p1}} &\approx \left[(A_0 + 1)\omega_0 + \frac{1}{g_{m2}r_{O2}r_{O1}C_L} \right] \left[(A_0 + 1)g_{m2}r_{O2}r_{O1}C_L + \frac{1}{\omega_0} \right] \\ &\approx (A_0 + 1)^2 g_{m2}r_{O2}r_{O1}C_L \omega_0 + 2(A_0 + 1) + \frac{1}{g_{m2}r_{O2}r_{O1}C_L \omega_0}.\end{aligned}$$



The second term is typically much greater than unity and the approximation is valid.

Comparison


	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

Output Swing Calculation

  - Be careful about distortion and gain error
- The maximum output amplitude that yields an acceptable distortion or gain error
- Apply a growing sinusoid wave, monitor the resulting output, and calculate the maximum allowable gain





Common-Mode Feed Back

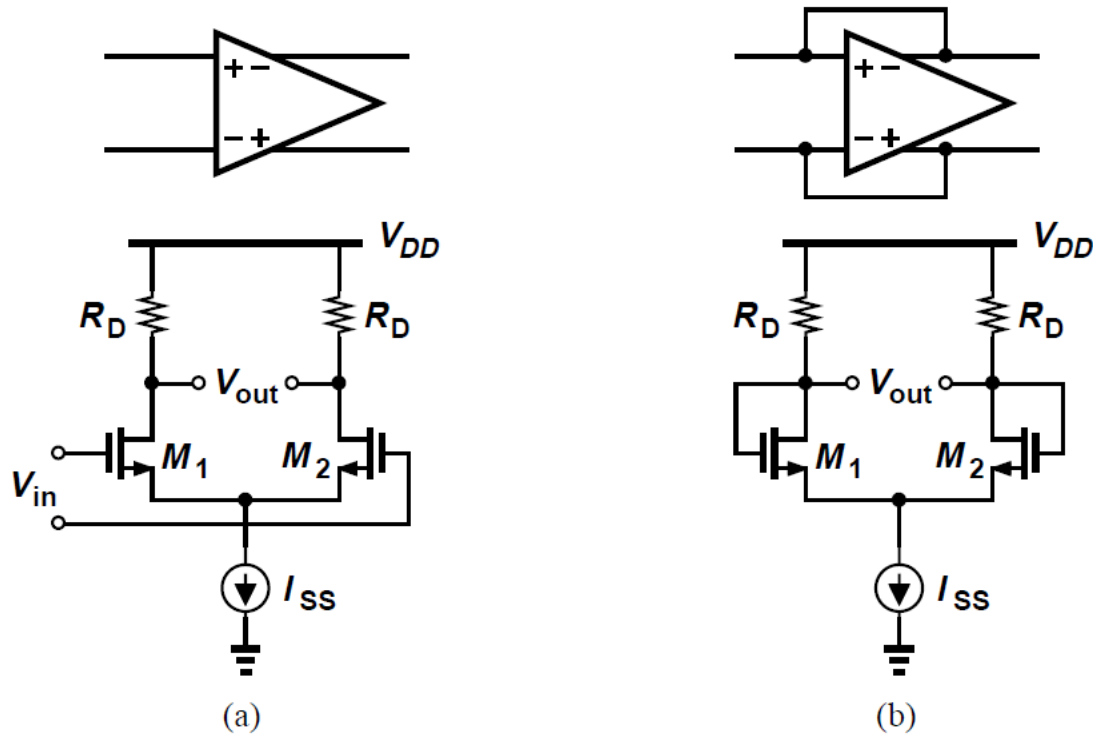

- $V_{cm}(in)$ and $V_{cm}(out)$: $V_{DD} - I_{SS}R_D/2$.


Basic Concepts

  - In fully-differential op amps, the output CM level is usually not well defined.
 - **Case 1:** $I_{D3,4} < I_{SS}/2$, V_x, V_y decreases, I_{SS} triode;
 - **Case 2:** In reverse, V_x, V_y increases, M_3, M_4 triode.



Basic Concepts

- In high-gain amplifiers, CMFB balances the PMOS and NMOS current mismatches, thus avoid driving one of them into triode region.
- Differential feedback cannot define CM level
- In simulation, CM may be well-defined around half V_{DD} , yet in real world, random mismatches and device variations would degrade CM easily without CMFB.

 

Example 9.16


Consider the telescopic op amp below. Suppose M9 suffers from a 1% current mismatch with respect to M10, producing $I_{SS} = 2.97$ mA rather than 3 mA. Assuming perfect matching for the others. Explain what happens in the circuit.

Solution:

Output voltage error: $(I_P - I_N)(R_P || R_N) = 3.99$ V


V_x, V_y must rise so much that M5, M6, M7, M8 go to triode, yielding $I_{D7} = 1.485$ mA.

 Current mismatch is largely depended on different drain-source voltage.



Conceptual topology

 - Measure output CM level;
- Compare with a reference;
- Apply the error to correct the level.



CM Sensing Techniques



- **Resistive sensing**

$$V_{out,CM} = (R_1 V_{out2} + R_2 V_{out1}) / (R_1 + R_2)$$

- large R_1, R_2 to avoid loading effect
- large chip area and parasitic capacitance
- reduce frequency performance


- **Source follower sensing**

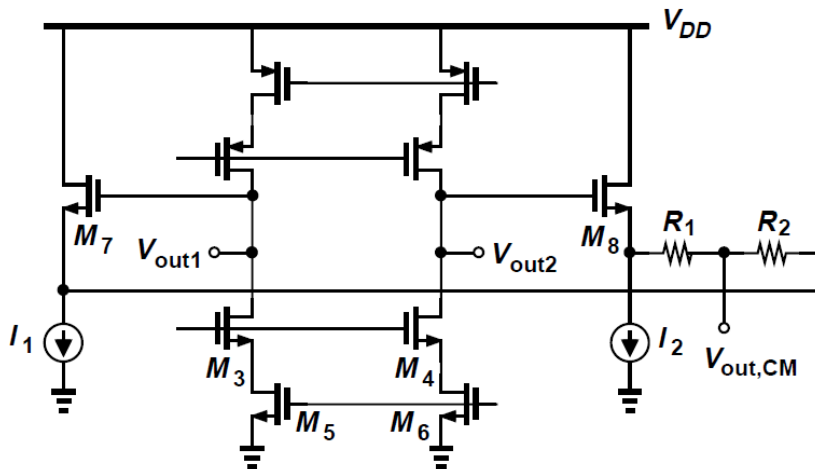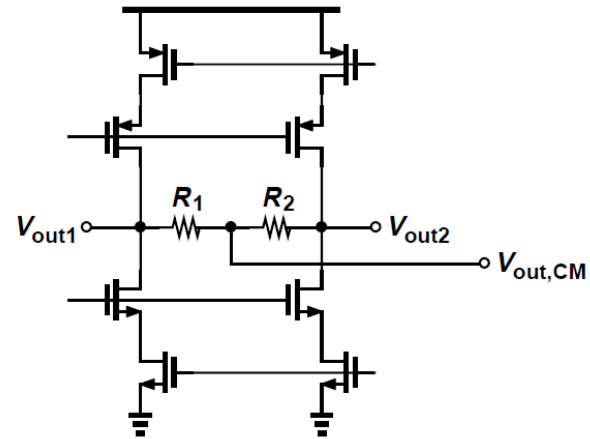- lose one V_{th} in swing
- large R_1, I_1 to avoid “starved”




CM Sensing Techniques

 - Capacitive sensing
 - Switched-capacitor
- Deep triode sensing
 - $R_{tot} \sim v_{out1} + v_{out2}$
 - R_{tot} has no relationship with differential voltage
 - may go to saturation region



$$\begin{aligned}
 R_{tot} &= R_{on7} \parallel R_{on8} \\
 &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out1} - V_{TH})} \parallel \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out2} - V_{TH})} \\
 &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{out2} + V_{out1} - 2V_{TH})},
 \end{aligned}$$

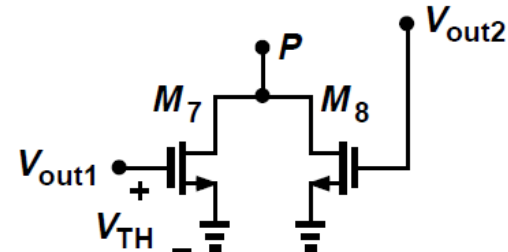


Example 9.17

A student simulates the step response of a closed-loop op amp circuit and observes the output waveforms shown in below. Explain why V_{out1} and V_{out2} do not change symmetrically.

Solution:

 As evident from waveforms, the output CM levels change from t_1 to t_2 , indicating CM sensing mechanism is nonlinear. For example, if M7 or M8 in last slide does not in deep triode at t_2 , the CM level would change because now it is a function of differential output.




CM Sensing Techniques

- Differential pair sensing


- $I_{CM} \propto V_{out1} + V_{out2}$ by small signal analysis
- Under Large swings situation, sensing is not valid due to

large non linearity

 


CM Feedback Techniques

- Control cascade current source

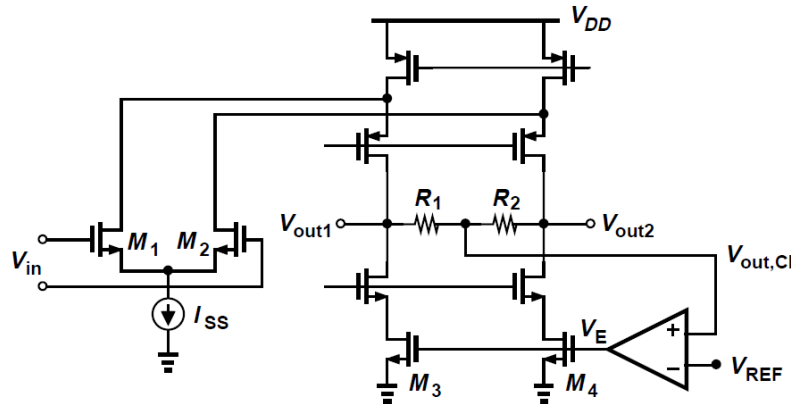



- Control tail current source

 

CM Feedback Techniques

- Deep triode sensing feedback
 - Limited headroom
 - Large C
 - Device variation
- Deep triode folded-cascade sensing feedback
  
$$V_{out1} + V_{out2} = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)_{7,8}} \frac{1}{V_b - V_{GS5}} + 2V_{TH}$$




CMEB small signal analysis

$$\begin{aligned} \beta &= \frac{\sqrt{2}}{V_1} |I_2=0| \\ &= -(g_{m7} + g_{m8})(R_{on7} || R_{on8}) \\ &= -2\mu_n C_{ox} \left(\frac{W}{L} \right)_{7,8} V_{DS7,8} \cdot \frac{1}{2\mu_n C_{ox}(W/L)_{7,8}(V_{GS7,8} - V_{TH7,8})} \\ &= -\frac{V_{DS7,8}}{V_{GS7,8} - V_{TH7,8}}, \end{aligned}$$

$$\left| \frac{dV_{out,CM}}{dV_b} \right|_{closed} \approx \frac{V_{GS7,8} - V_{TH7,8}}{V_{DS7,8}}$$

Maximize $V_{ds7,8}$ for Sensitivity

 


CM Feedback Techniques

- **Modification of deep triode sensing feedback**

$$(W/L)_{15} = (W/L)_9 \qquad (W/L)_{16} = (W/L)_7 + (W/L)_8$$

 - **The output level is relatively independent of device parameters and lowers sensitivity of V_b**




CM Feedback Techniques

- **Modification of deep triode sensing feedback**


$$(W/L)_{15} = (W/L)_9 \quad (W/L)_{16} = (W/L)_7 + (W/L)_8$$

 - **M17, M18 reproduces the drain of M15 a voltage equal to the source voltage of M1 and M2**




CM Feedback Techniques


- Another type of CM feedback topology
- Diode-connected loads' output CM level is well-defined
- Differential small signal gain $g_{m1,2}(r_{O1,2} \parallel r_{O3,4} \parallel R_F)$
- Common-mode work as a diode-connected $R_F \gg r_{O1,2} \parallel r_{O3,4}$
- Low supply voltage design $I_1 R_F / 2 = |V_{TH3,4}|$

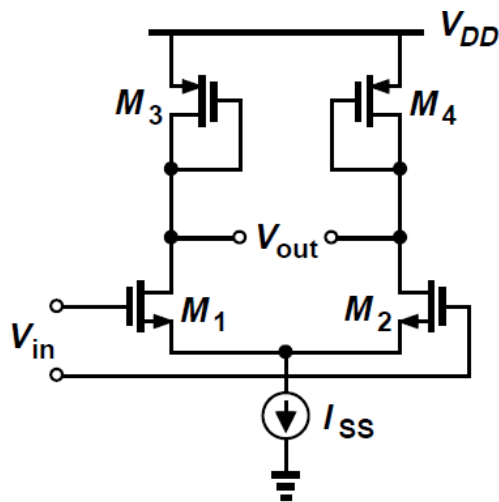

(a)

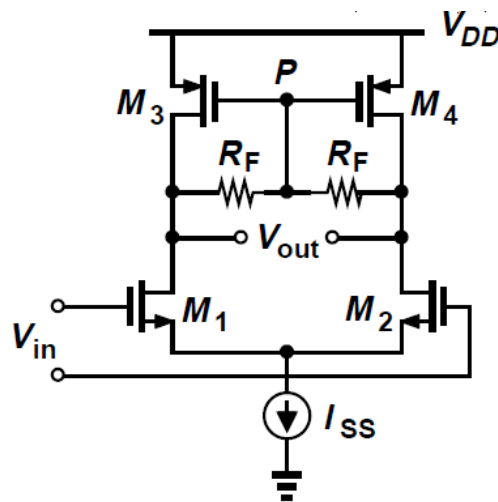

(b)

 

(c)


Example 9.19

Determine the maximum allowable output swings.

Solution:

Each output can fall to two overdrive voltages above ground if $V_{in,CM}$ is chosen to place I_{SS} at the edge of the triode region. The highest level allowed at the output is equal to the output CM level at P plus $|V_{th3,4}|$ (by selecting suitable R_F). Thus, output swing is $V_{DD} - 3V_{ov}$.

(R_F is small, not like previous setup)

 

Example 9.20


Facing voltage headroom limitations, a student constructs the circuits below. Determine the small-signal gain from the input CM level to the output CM level.

Solution: $g_{m5} + g_{m6} = 2\mu_n C_{ox}(W/L)_{5,6}V_P$


$$R_{tail} = [2\mu_n C_{ox}(W/L)_{5,6}(V_{out,CM} - V_{TH5,6})]^{-1}$$

$$\frac{V_{out,CM}}{V_{in,CM}} = -\frac{1}{\frac{2R_{tail}}{r_{O3,4}} + g_{m,tail}R_{tail} + (g_{m1,2}r_{O3,4})^{-1}}.$$


(A poor CMRR)

 

(a)

 



(b)

 

(c)



CMFB in Two-Stage Op Amps

  - CMFB around second stage (not good)
 - May establish a current beyond nominal value
- CMFB from second stage to first stage
 - Global loop control of both stages



CMFB from Second to First Stage

  
- CMFB from second stage to first stage limitation
 - 3 or 4 poles, which makes it difficult for the loop stable



CMFB at both Stages

- All the drain currents are copied from I_{SS}
- The differential voltage gain is equal to

$$g_{m1}(r_{O1}||r_{O3}||R_1)g_{m5}(r_{O5}||r_{O7}||R_3)$$


 


Example 9.21

For the below design explain why the output CM level is inevitably well below $V_{DD}/2$ and hence the output swings are limited. Devise a solution.


Solution:

  The output CM is equal to $V_{G7,8}$, which is only slightly greater than one threshold. The issue can be resolved by drawing a small current from node Q. It can be upwards to desired output and the device is still in saturation.




CMFB for Cascode First Stage

 - First stage use deep triode feedback loop to avoid loading.
- Achieving high gain while not precise





Input Range Limitations

 - Input common-mode level may need to vary over a wide range, e.g. ADC input comparator.
- Input swing limits the total range sometimes.
- In the below single-end unity-gain buffer the input CM minimal voltage is $V_{GS1,2} + V_{ISS}$, which is one threshold greater than $2V_{ov}$ in the output CM.



Extension of Input Range

  - Incorporate both NMOS and PMOS differential pair to keep a necessary transconductance
- The transconductance variation should be concerned
- Gain, speed and noise may vary







Slew Rate

- In a linear circuit, the slope of the step depends on final output value

$$\frac{dV_{out}}{dt} = \frac{V_0}{\tau} \exp \frac{-t}{\tau}$$



- The observation applies to linear feedback system
    
$$V_{out} = V_0 \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \left[1 - \exp \frac{-t}{\frac{C_L R_{out}}{1 + A R_2 / (R_1 + R_2)}} \right] u(t)$$




Slew Rate

  - In a realistic case, with large input steps, the output displays a linear ramp having a constant slope. The slope of ramp is the “slew rate”.
- It seems that the maximum current to charge the load capacitance is limited.
- Nonlinear behavior. Reduce speed and increase distortion.
- Increase SR would consume power and wider device



Slew Rate Example

- A small step rises V_{out} by $g_m \Delta V$ and hence adjusts through R_1 , R_2 negative feedback circuit.
- When M_1 experiences a large step, M_2 turns off. Thus, C_L is charged by a constant current I_{SS} .
- Feedback is broken but after M_2 turns on, the circuit returns to a linear operation.

 

Example 9.22

- (a) Determine the small-signal step response of the circuit.
 (b) Calculate the positive and negative slew rates.

Solution:





$$\frac{V_{out}}{V_{in}}(s) = \frac{A_v}{1 + A_v \frac{C_1}{C_1 + C_2} + \frac{C_1 C_2}{C_1 + C_2} R_{out} s}$$

$$= \frac{A_v / \left(1 + A_v \frac{C_1}{C_1 + C_2}\right)}{1 + \frac{C_1 C_2}{C_1 + C_2} R_{out} s / \left(1 + A_v \frac{C_1}{C_1 + C_2}\right)}$$

$$V_{out}(t) = \frac{A_v}{1 + A_v \frac{C_1}{C_1 + C_2}} V_0 \left(1 - \exp \frac{-t}{\tau}\right) u(t)$$



$$V_{out}(t) = I_{SS} / [C_1 C_2 / (C_1 + C_2)] t$$
 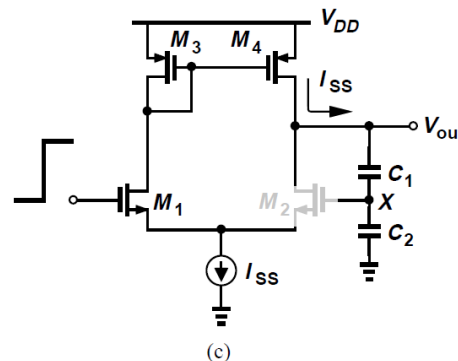  
$$V_{out} = -I_{SS} / [C_1 C_2 / (C_1 + C_2)] t$$






Slew Rate of Telescopic Op Amp

  - Each side appears a ramp with slope equal to $\pm I_{SS}/(2C_L)$
- The total slew rate for Vout1- Vout2 equal to I_{SS}/C_L




Slew Rate of Folded-Cascode Op Amp

   - Yield a slew rate of I_{SS}/C_L if $I_P \geq I_{SS}$
- Otherwise, M3 turns off and tail current source enters the triode region. The settling time increases.




Clamp transistor

 - Limit V_x, V_y to produce large different voltage
- More aggressive design, V_x, V_y higher than $V_{DD} - V_{THN}$



(a)

 

(b)

Example 9.23

As V_{out} rises, so does V_x , eventually turning M2 on. As I_{D2} increases from zero, the plot becomes linear. Considering M1 and M2 becomes linear if difference between their drain current is less than αI_{SS} (e.g., $\alpha = 0.1$).





Calculate the time to linear.

Solution:

$$\alpha I_{SS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2},$$



$$\Delta V_G \approx \alpha \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$
    
$$t = \frac{C_2}{I_{SS}} \left(V_0 - \alpha \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \right)$$




High-Slew-Rate Op Amp

  - Slew rate is limited by power consumption
- The trade-off could be mitigated if the capacitor could be charged to a desired value quickly. And the voltage falls back to original value.
- Complementary topology jumps fast but suffer from poor power supply rejection




Push-Pull Stages

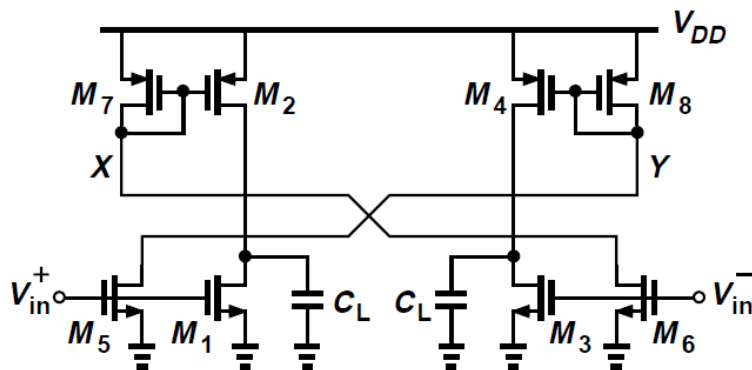- Use current-mirror. E.g. If V_{in+} jumps down, and V_{in-} jumps up then
 - M5 draws less current, lowering I_{D4} ;
 - M3, M6 draws more current;
 - M7 draws more current, raising I_{D2} ;
 - M1 draws less current, charging C_L .




(c)

 


(d)

Push-Pull Stages

 - Improve the input common-mode rejection by adding tail current sources to build differential circuits
- The differential slew rate is $[I_{SS1} + I_{SS2}(W_4/W_8)]/C_L$
- SR increases with a around twofold power penalty



(c)

 

(d)

V_{DD}

Frequency Response and Mirror Pole


- It is not possible to equate zero and pole
- Raise SR would decrease mirror pole frequency

$$g_{m8}/C_Y \quad C_Y \approx 2(W_4 + W_8)LC_{ox}$$

$$H_{mirr}(s) = \frac{W_4}{W_8} g_{m5} (r_{O3} || r_{O4}) \frac{1}{1 + \frac{s}{\omega_{p,X}}} \frac{1}{1 + \frac{s}{\omega_{out}}}$$

$$\omega_{p,X} \approx g_{m8}/C_Y \text{ and } \omega_{out} = [(r_{O3} || r_{O4})C_L]^{-1}$$

$$\begin{aligned} H_{tot}(s) &= H_{main}(s) + H_{mirr}(s) \\ &= \frac{r_{O3} || r_{O4}}{1 + \frac{s}{\omega_{out}}} \left[\frac{W_4}{W_8} \frac{g_{m5}}{1 + \frac{s}{\omega_{p,X}}} + g_{m1} \right] \\ &= \frac{r_{O3} || r_{O4}}{1 + \frac{s}{\omega_{out}}} \cdot \frac{(W_4/W_8)g_{m5} + g_{m1} + g_{m1}s/\omega_{p,X}}{1 + \frac{s}{\omega_{p,X}}} \end{aligned}$$

 

$$|\omega_z| = \left(\frac{W_4}{W_8} \frac{g_{m5}}{g_{m1}} + 1 \right) \omega_{p,X}.$$


Two-Stage Op Amp with High SR

- **Voltage Gain:**

$$|A_v| = g_{m9}(r_{O9}||r_{O11})[g_{m1} + (W_4/W_8)g_{m5}](r_{O1}||r_{O2})$$


- **Slew Rate**

 - If P is low capacitance, it is “agile” enough to go upon to VDD, thus providing a large SR.



Power Supply Rejection

- Power line contains noise
- PSRR(power supply rejection ration):
 - Gain from input to output divided by the gain from supply to the output
- At low frequency $PSRR \approx g_{mN}(r_{OP}||r_{ON})$

 



Example 9.25

Calculate the low-frequency PSRR of the feedback circuit shown below

Solution:
$$\frac{V_{out}}{V_{DD}} = \frac{1}{g_{m2}r_{O4}\frac{C_1}{C_1+C_2} + 1}, \quad PSRR \approx \left(1 + \frac{C_2}{C_1}\right)(g_{m2}r_{O4}\frac{C_1}{C_1+C_2} + 1)$$

$$\approx g_{m2}r_{O4}.$$

  
Feedback reduce $\partial V_{out}/\partial V_{DD}$ and $\partial V_{out}/\partial V_{in}$ the same and PSRR is relatively constant.



Noise in Telescopic Op Amp

- At low frequency the cascode devices contribute negligible noise

 
$$\overline{V_n^2} = 4kT \left(2 \frac{\gamma}{g_{m1,2}} + 2 \frac{\gamma g_{m7,8}}{g_{m1,2}^2} \right) + 2 \frac{K_N}{(WL)_{1,2} C_{ox} f} + 2 \frac{K_P}{(WL)_{7,8} C_{ox} f} \frac{g_{m7,8}^2}{g_{m1,2}^2}$$




Noise in Folded-Cascode Op Amp

- At low frequency the cascode devices contribute negligible noise
 
$$\overline{V_{n,int}^2} = 8kT \left(\frac{\gamma}{g_{m1,2}} + \gamma \frac{g_{m7,8}}{g_{m1,2}^2} + \gamma \frac{g_{m9,10}}{g_{m1,2}^2} \right)$$



(a)

 


(b)

Noise in two-stage Op Amp

- The noise in the second stage contributes negligible noise

$$\overline{V_{n,tot}^2} = 8kT\gamma \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{O1} \parallel r_{O3})^2} \right]$$

 

Example 9.26

A simple amplifier is constructed below. Note that the first stage incorporates diode-connected – rather than current-source loads. Assuming all the transistors in saturation. $(W/L)_1=50/0.6$ $(W/L)_3=10/0.6$ $(W/L)_5=20/0.6$ $(W/L)_7=56/0.6$

Solution:

$$A_{v1} \approx \frac{g_{m1}}{g_{m3}} \quad (8kT/3)(g_{m3} + g_{m1})/g_{m1}^2 = 1.10 \times 10^{-17} \text{ V}^2/\text{Hz}.$$

$$= \sqrt{\frac{50 \times 75}{10 \times 30}} \quad 4kT(2/3)(g_{m5} + g_{m7})/g_{m5}^2 A_{v1}^2 = 2.29 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$\approx 3.54.$$

$$\overline{V_{n,in}^2} = 2(2.29 \times 10^{-18} + 1.10 \times 10^{-17})$$

$$= 2.66 \times 10^{-17} \text{ V}^2/\text{Hz},$$

