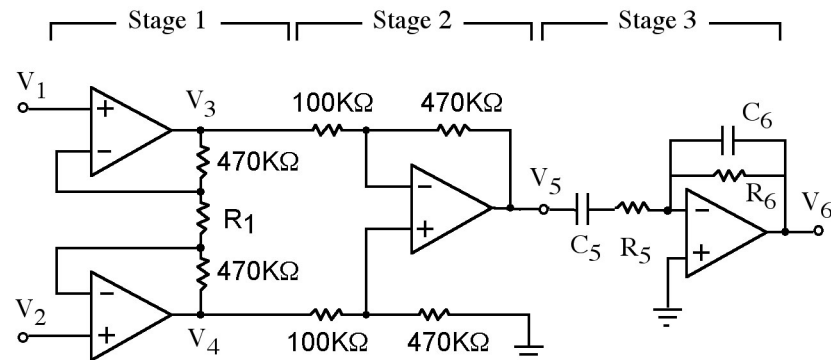


1. As shown on the right, six parameters of an ideal operational amplifier are listed. Circle the correct value for each parameter.

Differential gain	0	∞
Common mode gain	0	∞
Common mode rejection ratio	0	∞
Input impedance	0	∞
Output impedance	0	∞
Bandwidth	0	∞

2. () Refer to the circuit on the right for questions 2 to 5. The stage-1 gain is defined by $(V_3 - V_4) / (V_1 - V_2)$. If we want to set the first-stage gain to 5.7, what value should be chosen for R_1 ? (A) 100 K Ω , (B) 200 K Ω , (C) 330 K Ω , (D) 470 K Ω , (E) none of the above.



3. () The stage-2 gain is defined by $V_5 / (V_3 - V_4)$. What is the gain for stage 2? (A) -4.7, (B) -5.7, (C) -9.4, (D) -11.4, (E) none of the above.
4. () Stage 3 is a bandpass filter with a passing band between 1 Hz and 30 Hz. If we choose $C_5 = 2 \mu\text{F}$, what value should R_5 be set at? (A) 24 K , (B) 33 K , (C) 56 K , (D) 80 K , (E) none of the above.

5. () For stage 3, if choose $C_6 = 0.22 \mu\text{F}$, what value should R_6 be set at? (A) 24 K , (B) 33 K , (C) 56 K , (D) 80 K , (E) none of the above.

6. () The C code on the right implements a digital filter. The input comes from ReadADC() subroutine, which acquires data from the on-chip A/D. The output is sent to port D, which is connected to an external D/A. What kind of filter is this? (A) FIR and causal , (B) FIR and noncausal, (C) IIR and causal, (D) IIR and noncausal, (E) none of the above.

```


uns8 input0, input1;
uns8 output0, output1;
uns16 temp;

... ..
input1 = input0;
input0 = ReadADC();
temp = input0;
temp += input1;
temp += input1;
temp += output1;
temp = temp >> 2;
output0 = temp;
PORTD = output0;
output1 = output0;
    
```

7. () For the above problem, what is the filter equation? (A) $y[n] = (y[n-1] + x[n] + x[n-1]) / 2$, (B) $y[n] = (y[n-1] + 2 x[n] + x[n-1]) / 4$, (C) $y[n] = (y[n] + 2 x[n] + x[n-1]) / 2$, (D) $y[n] = (y[n] + x[n] + x[n-1]) / 4$, (E) none of the above.


8. () We implement a digital filter according to: $y[n] = x[n] - x[n-2] + y[n-2]/4$, where $y[n]$ is the present output and $x[n]$ the present input. Which of the following is the correct transfer function $H(z)$ for this filter? (A) $(z - 1)^2 / (z - 1/4)^2$, (B) $(z^2 - 1) / (z^2 - 1/4)$, (C) $(z + 1)^2 / (z + 1/4)^2$, (D) $(z^2 + 1) / (z^2 + 1/4)$, (E) none of the above.

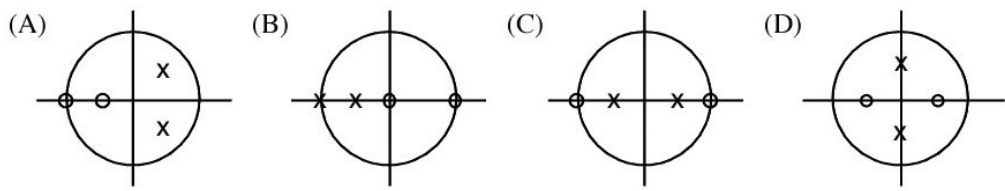9. () For the above problem, which of the following is the correct pole-zero plot for this filter?



(E) none of the above. (The big circle is the unit circle on the z-plane. A zero is shown by o and a pole by x.)

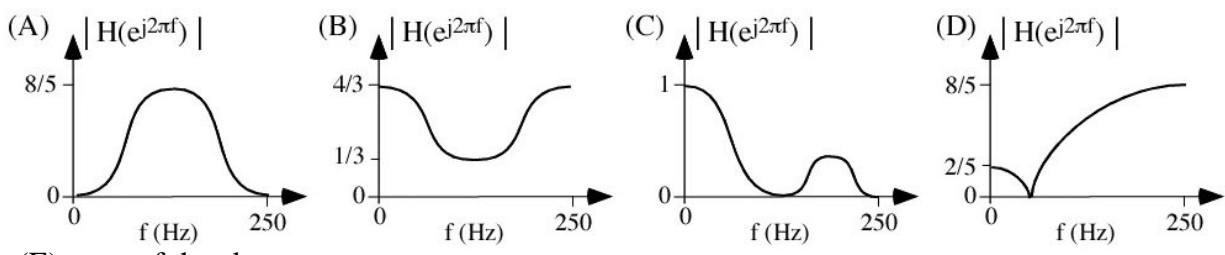10. () For the above problem, we choose a sampling rate of 500 Hz. Which of the following is the correct frequency response, i.e. magnitude of $H(e^{j2\pi f})$, for this filter?



(E) none of the above.