Indirect Measurement of Blood Pressure (see P.317 text)

- · Palpatory method to measure systelic pressure only
- · Auscultatory method to measure both systelic and diastolic pressures



Pressure Measurement Invasive - Catheter & Pressure Transducer ()  
Unit F = ma; pressure = force/area  
For cgs system : pressure : dyne/cm<sup>2</sup>  
dyne = g · cm/s<sup>2</sup>  
I nomHg = (13.6 g/m<sup>3</sup>) (980 cm/s<sup>2</sup>) (
$$\frac{1}{10}$$
 cm)  
duoisty d' mercury acceleration due to gravity at sea level  
I nomHg = 1.01 × 10<sup>5</sup> Ra (Pascal) = 1.01 bar = 760 mmHg  
= 760 torr = 14.7 Psi  
I psi = 51.7 mmHg  
fluman voncus pressure = 5 mmHg ≈ 1/10 psi  
Auman arterial pressure = 80 - 120 mmHg ≈ 2 psi  
- Cousehold water pressure ≈ 60 psi ≈ 3000 mmHg  
car tire pressure ≈ 30 psi ≈ 1500 mmHg  
Direct Pressure Measurement (p.289)  
• Fluid-filled catheter and conventional pressure Hansducer  
Teamp pressure transducer  
- Piezo electric transducer  
- Piezo electric transducer  
- Piezo electric transducer  
- micromanometer-tip  
catheter

Jeroson

pressure piezo dectric sensor

Ø Conventional Fluid-filled catheter/transducer system fluid-filled catheter FERRET dome membrani radius = r cross-sectional area = A Question: Po = P1 ? Preamp Neuton's 2nd law of motions: SF = ma Forces =  $\pi r^2 (P_0 - P_1) - viscous force = m \frac{dv}{dt}$ 5: velocity of fluid flows through the catheter (cm/s) Viscous force ? Assume laminar flow through circular pipe Poiseuille's Law:  $\frac{\Delta P}{Q} = \frac{8 \,\mu l}{\pi r 4}$ ap: pressure gradient (mmHg) Q: volume flow rate (cm3/s) M: Viscosity (poise, dyne.s/cm2) usually 45% (water or saline:  $\mu = 0.01$  poise blood:  $\mu = 0.025$  poise, depending on hematocrit Viscaus force = AP(Rr2) = 8 MlQ/r2; Q=VA  $\pi r^2 (P_0 - P_1) = 8 \mu l Q/r^2 = m \frac{dV}{dt}$ U = Q/A,  $dV/dt = (\frac{1}{A}) dQ/dt = (\frac{1}{\pi r^2}) dQ/dt$  $m = \pi r^2 l \rho$ ,  $\rho$ : density of the fluid Reynolds number: a dimensionless parameter to indicate tendency of turbulent flows { Re< 200, laminar flows  $Re = (2QP)/(\pi\mu r)$ 

Re> 2000, turbulent flows

• 
$$\pi t^{2} (P_{0} - P_{1}) - 8 \mu l Q / t^{2} = l \rho d g_{dt}$$
  
• The compliance (capacitance)  
in the system is usually dominated  
by the transducer compliance  
(the membrane in the dome)  
 $C_{T} = \frac{d V}{dP_{1}} = \frac{1}{E}$ ,  $V$ : volume (cm<sup>3</sup>), fictors  
 $pec.f.d$   
E: modulus of elasticity for the transducer  
 $(Capacitance = 1/elastame)$   
 $= \frac{dV}{dt} = C_{T} \frac{dP_{1}}{dt}$   
•  $\pi tr^{2}(P_{0} - P_{1}) - \frac{8\mu l}{T^{2}}(C_{T} \frac{dP_{1}}{dt}) = l\rho (C_{T} \frac{d^{2}P_{1}}{dt^{2}})$   
after rearranging terms:  
 $P_{0} = (\frac{P_{P}}{\pi r^{2}}) C_{T} \frac{d^{2}P_{1}}{dt^{2}} + (\frac{8\mu l}{\pi r^{4}}) C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{d^{2}P_{1}}{dt^{2}} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{d^{2}P_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{d^{2}P_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{d^{2}P_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{d^{2}P_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = L C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = C_{T} \frac{dP_{1}}{dt} + R C_{T} \frac{dP_{1}}{dt} + P_{1}$   
•  $P_{0} = R C_{1} \frac{dP_{1}}{dt} + L C_{1} \frac{dP_{1}}{dt} + P_{1}$ 

2nd-order system, low-pass filter





• Sinusoidal pressure-generator test system (p.304)



Transient step response (P.30)



#### Circuit Analysis Using Laplace Transform and Fourier Transform: RLC Low-Pass Filter

Ying Sun

The schematic on the right shows a 2nd-order RLC circuit. A constant voltage (V) is applied to the input of the circuit by closing the switch at t = 0. The output is the voltage across the capacitor (C). The circuit can be represented as a linear time-invariant (LTI) system. The input is  $v_i$ . If a constant voltage is applied at t = 0, it is a step input. We further normalize the input voltage V = 1 such that it's unit step function. Thus, the input is the unit step function u(t), and the output is the step response s(t). The LTI system can



be completely characterized by its impulse response h(t). The step response is the convolution between the input step function and the impulse response:  $s(t) = u(t) \otimes h(t)$ .

## Circuit analysis using Laplace transform

The circuit analysis can be done by use of the Kirchhoff's voltage law and the properties of capacitor and inductor:

$$i = C \frac{dv_c}{dt} \text{, and } v_L = L \frac{di}{dt} - \dots$$

$$(1)$$

$$v_i = Ri + v_L + v_c = Ri + L \frac{di}{dt} + v_c - \dots$$

$$(2)$$

By substituting (1) into (2), we have:

$$v_{i} = LC \frac{d^{2}v_{c}}{dt^{2}} + RC \frac{dv_{c}}{dt} + v_{c}$$
(3)

Although a closed form solution can be obtained by solving the above 2nd-order differential equation, we will take the frequency-domain approach. Taking LT on both side, we have:

$$V_{i}(s) = LC s^{2} V_{c}(s) + RC s V_{c}(s) + V_{c}(s)$$
(4)

The transfer function is given by:

$$H(s) = \frac{V_c(s)}{V_i(s)} = \frac{1}{LC s^2 + RC s + 1}$$
(5)

We now use a different set of parameters:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\alpha s + \omega_n^2}$$
(6)

where  $\omega_n = \frac{1}{\sqrt{LC}}$ , natural frequency

$$\alpha = \frac{R}{2L}$$
, damping factor

We further define damped frequency  $\omega_d$ :

$$\omega_d = \sqrt{\omega_n^2 - \alpha^2}$$
; or  $\omega_n^2 = \omega_d^2 + \alpha^2$ ; or  $\omega_n = \sqrt{\omega_d^2 + \alpha^2}$ 

To obtain the impulse response, the transfer function is further extended to:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\alpha s + \omega_n^2} = \frac{\omega_n^2}{(s + \alpha + \sqrt{\alpha^2 - \omega_n^2})(s + \alpha - \sqrt{\alpha^2 - \omega_n^2})} = \frac{\omega_n^2}{(s + \alpha + j\omega_d)(s + \alpha - j\omega_d)} = \frac{\omega_n^2}{(s + \alpha + j\omega_d)(s + \alpha - j\omega_d)} = \frac{\omega_n^2}{(s + \alpha + j\omega_d)(s + \alpha - j\omega_d)}$$

The system has two poles at:  $-\alpha + j \omega_d$  and  $-\alpha - j \omega_d$ .

Taking the ILT, the impulse response is:

$$h(t) = \left(\omega_d + \frac{\alpha^2}{\omega_d}\right) e^{-\alpha t} \sin \omega_d t \quad \dots \tag{8}$$

Next, we want to get a closed form solution for the step response. This will be accomplished by extending H(s) to H(s)/s, or S(s), which is the LT of the step response.

$$S(s) = \frac{H(s)}{s} = (\omega_d + \frac{\alpha^2}{\omega_d})(\frac{1}{s})(\frac{\omega_d}{(s+\alpha)^2 + \omega_d^2}) = \frac{a}{s} + \frac{bs+c}{(s+\alpha)^2 + \omega_d^2}$$
$$\omega_d^2 + \alpha^2 = a(s+\alpha)^2 + a\omega_d^2 + bs^2 + cs = (a+b)s^2 + (2a\alpha+c)s + a(\omega_d^2 + \alpha^2)$$

We have a+b=0,  $2a\alpha+c=0$ , and  $\omega_d^2+\alpha^2=a(\omega_d^2+\alpha^2) \Rightarrow a=1, b=-1$ , and  $c=-2\alpha$ .

$$S(s) = \frac{1}{s} - \frac{s+2\alpha}{(s+\alpha)^2 + \omega_d^2} = \frac{1}{s} - \frac{s+\alpha}{(s+\alpha)^2 + \omega_d^2} - \left(\frac{\alpha}{\omega}\right) \frac{\omega_d}{(s+\alpha)^2 + \omega_d^2}$$
(9)

Using the LT Table, we obtain the step response s(t):

$$s(t) = 1 - e^{-\alpha t} \left[ \cos \omega_d t + \left( \frac{\alpha}{\omega_d} \right) \sin \omega_d t \right]$$
(10)

Next, we want to combine cosine and sine into one term with a phase angle. We further define the damping ratio  $\eta$ ,  $\eta = \frac{\alpha}{\omega_n}$ .

$$\frac{\alpha}{\omega_d} = \frac{\alpha}{\sqrt{\omega_n^2 - \alpha^2}} = \frac{1}{\sqrt{\omega_n^2 / \alpha^2 - 1}} = \frac{1}{\sqrt{1/\eta^2 - 1}} = \frac{\eta}{\sqrt{1 - \eta^2}}$$
(11)  
$$s(t) = 1 - e^{-\alpha t} [\cos \omega_d t + (\frac{\eta}{\sqrt{1 - \eta^2}}) \sin \omega_d t] = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} [\sqrt{1 - \eta^2} \cos \omega_d t + \eta \sin \omega_d t] = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} [\sin \phi \cos \omega_d t + \cos \phi \sin \omega_d t] = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} \sin (\omega_d t + \phi)$$
(12)  
where  $\tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{\sqrt{1 - \eta^2}}{\eta}, \ \phi = \tan^{-1} \frac{\sqrt{1 - \eta^2}}{\eta}.$ 

From the previous circuit course, such as ELE 212, you might have learned what the damping ratio means: a) underdamping  $(\eta < 1)$ ; b) critical damping  $(\eta = 1)$ ; and c) overdamping  $(\eta > 1)$ .

Assume the underdamping situation, s(t) is shown on the right. The 2nd-order system requires two parameters to define, such as the damped frequency  $\omega_d$  and the damping factor  $\alpha$ . These two parameters can be obtained from the s(t) curve by making two measurements. A prominent feature point is the first peak after the onset. We measure the time to peak  $T_p$ and the amount of overshoot (OS). This point occurs when the derivative of the curve is 0.



$$\frac{ds(t)}{dt} = 0$$

$$\frac{ds(t)}{dt} = h(t) = (\omega_d + \frac{\alpha^2}{\omega_d})e^{-\alpha t}\sin\omega_d t = 0.$$
(13)

The peaks and valleys occur when  $\omega_d t = 0, \pi, 2\pi, 3\pi, 4\pi, \dots$  The first peak occurs when  $\omega_d t = \pi$ . Thus,  $T_p = \frac{\pi}{\omega_d}$ , or  $\omega_d = \frac{\pi}{T_p}$  (14)

At the first peak  $T_p$ ,

$$s(T_{p}) = 1 - \frac{e^{-\alpha T_{p}}}{\sqrt{1 - \eta^{2}}} \sin\left(\omega_{d} T_{p} + \tan^{-1} \frac{\sqrt{1 - \eta^{2}}}{\eta}\right) = 1 - \frac{e^{-\alpha T_{p}}}{\sqrt{1 - \eta^{2}}} \sin\left(\pi + \tan^{-1} \frac{\sqrt{1 - \eta^{2}}}{\eta}\right) = 1 + \frac{e^{-\alpha T_{p}}}{\sqrt{1 - \eta^{2}}} \sin\left(\tan^{-1} \frac{\sqrt{1 - \eta^{2}}}{\eta}\right) = 1 + \frac{e^{-\alpha T_{p}}}{\sqrt{1 - \eta^{2}}} \sqrt{1 - \eta^{2}} = 1 + e^{-\alpha T_{p}} = 1 + OS .$$
(15)

Thus,  $e^{-\alpha T_p} = OS$ , or  $\alpha = -\frac{\ln OS}{T_p}$ . (16)

## **Frequency response**

Let's assign values to the circuit components so that we can plot the frequency response as an example. Let's assume:

 $R = 40 K \Omega; L = 1 mH; C = 0.1 \mu F$  -----(17)

Based on these values, we have:

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \, mH \times 0.1 \, \mu F}} = 100000 \text{ radians/s; and}$$

$$\alpha = \frac{R}{2L} = \frac{40 \, K \, \Omega}{2 \times 1 \, mH} = 20000$$

$$\omega_d = \sqrt{\omega_n^2 - \alpha^2} = \sqrt{100000^2 - 20000^2} = 97980 \text{ radians/s.}$$

$$\eta = \frac{\alpha}{\omega_n} = \frac{20000}{100000} = 0.2 \text{ ; } \phi = \tan^{-1} \frac{\sqrt{1 - \eta^2}}{\eta} = \tan^{-1} \frac{\sqrt{1 - 0.2}}{0.2} = 1.35 \text{ radians.}$$

The transfer function is  $H(s) = (\omega_d + \frac{\alpha^2}{\omega_d})(\frac{\omega_d}{(s+\alpha)^2 + \omega_d^2})$ . The system has the poles at  $-\alpha \pm j \omega_d$ , or  $-20000 \pm 97980 j$ . The zeros are at infinity.

# Bode plot

Enter the poles of  $-20000 \pm 97980 j$  at the online Bode plot generator <http://http://www.onmyphd.com/? p=bode.plot>. We obtain the following:

#### **Step response**

$$s(t) = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} \sin(\omega_d t + \phi) = 1 - \frac{e^{-20000t}}{0.9798} \sin(97980t + 1.35) =$$

Due to a range issue with the graphing calculator, we change the time unit from s to ms:

$$s(t) = 1 - \frac{e^{-20t}}{0.9798} \sin(97.98t + 1.35)$$

From the graph, we see that the peak occurs roughly at:  $T_p = 0.0323$  ms, and OS = 0.52.

Using the formula derived previously:

$$\omega_d = \frac{\pi}{T_p} = \frac{3.14159}{0.0000323} = 97263$$

as compare to  $\omega_d = 97980$ .

$$\alpha = -\frac{\ln OS}{T_p} = -\frac{\ln 0.52}{0.0000323} = 20245,$$

as compare to  $\alpha = 20000$ .

