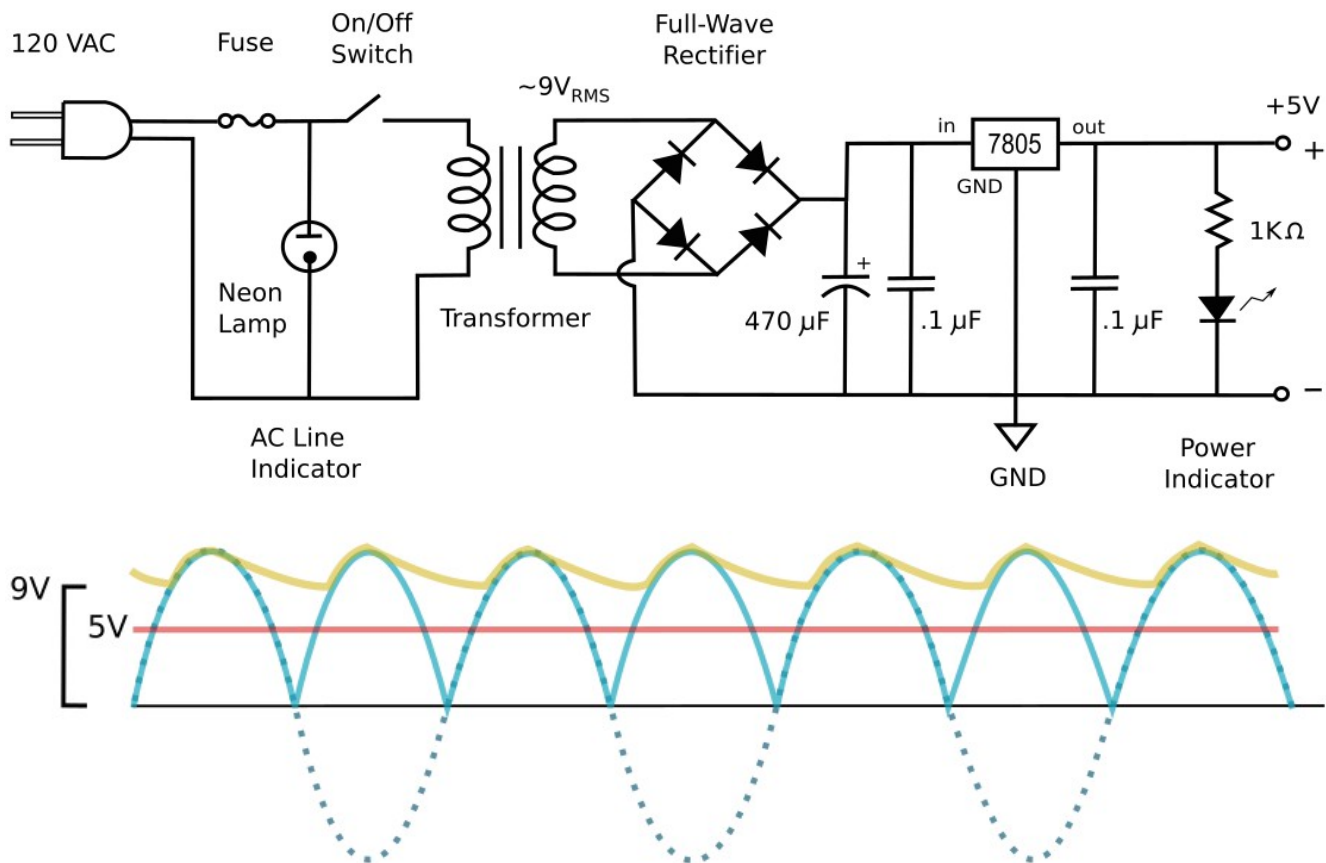


# Power Supply Circuitry

Ying Sun's Lecture Notes


## An Example of a 5V DC Power Supply



The diode bridge provides full-wave rectification as shown above. The 470  $\mu F$  electrolytic capacitor reduces the ripples. The two .1  $\mu F$  ceramic capacitors decouple the high-frequency signals of the load, if present, from the power source. Note that the electrolytic capacitor has equivalent series resistor and inductor (ESR and ESL), making it to behave more like an inductor at high frequencies.

## LM7805 – 5V Voltage Regulator

TO-220 package 1A rating

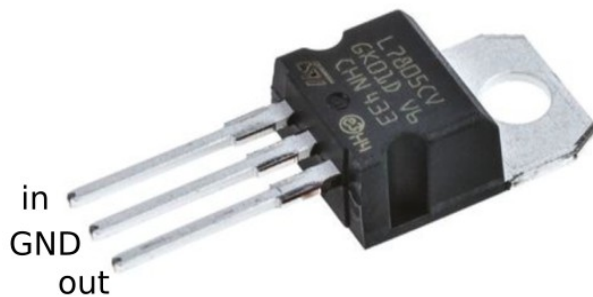


TO-92 package 100 mA rating


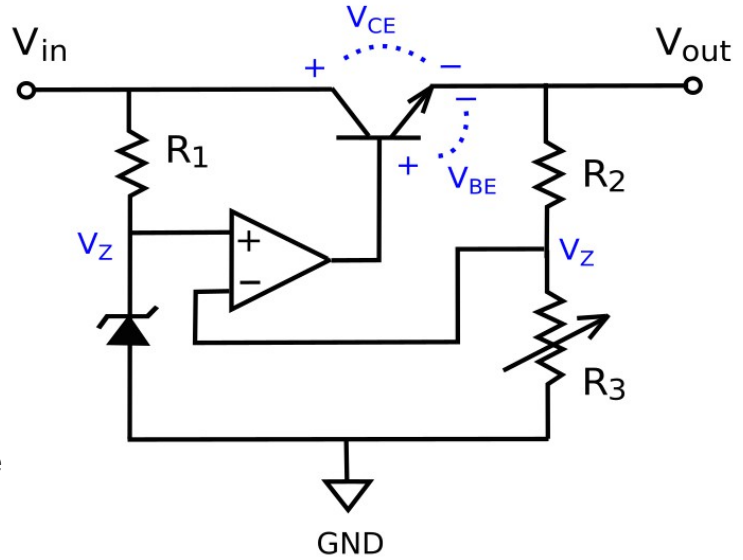
## Voltage Regulator Circuit

$V_{in}$  needs to be sufficiently higher than  $V_{out}$ , typically by 1.5 V in order to maintain a constant  $V_{out}$ .  $R_1$  provides the bias current to keep the zener diode at the constant breakdown voltage  $V_Z$ . Because of the “virtual ground” of the OP amp, the voltage across  $R_3$  also at the constant voltage  $V_Z$ . The output voltage is maintained at a constant value via the negative feedback of the OP amp.  $V_{out}$  can be adjusted via the potentiometer  $R_3$ .



$$V_{out} = V_Z \times (R_2 + R_3) / R_3$$

## Schematic Diagram of LM7805

