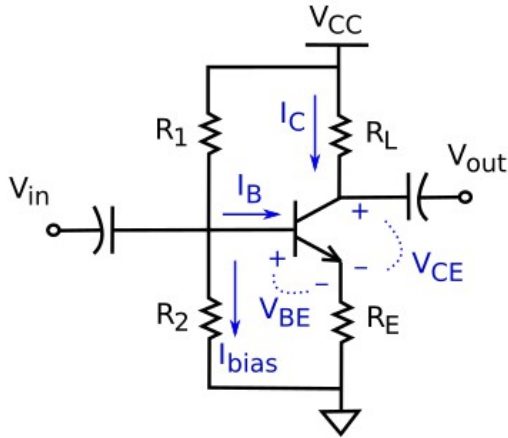


Transistor Circuits

Ying Sun's Lecture Notes

An Example of Common-Emitter NPN Transistor Amplifier



Choose $V_{CC} = 12\text{ V}$. Set the operating point at $I_C = 10\text{ mA}$ and $I_B = 100\text{ }\mu\text{A}$. The current gain is


$$\beta = h_{FE} = \frac{\Delta I_C}{\Delta I_B} = 100$$

Choose $R_L = 620\text{ }\Omega$, voltage across R_L is $10\text{ mA} \times 620 = 6.2\text{ V}$. $V_{CE} = 5\text{ V}$ at the operating point, voltage across R_E is given by $V_{CC} - 6.2\text{ V} - V_{CE} = 0.8\text{ V}$. Thus, R_E should be set at $0.8\text{ V} / 10\text{ mA} = 80\text{ }\Omega$. The bias current I_{bias} is typically set at 10 times of I_B , or 1 mA . V_{BE} is a constant voltage of 0.7 V . Thus, R_2 is $(0.8\text{ V} + 0.7\text{ V}) / 1\text{ mA} = 1.5\text{ K}\Omega$. R_1 should be set at $(12\text{ V} - 1.5\text{ V}) / (1\text{ mA} + 100\text{ }\mu\text{A}) = 9.5\text{ K}\Omega$. The voltage gain is given by:


$$A_V = \frac{V_{out}}{V_{in}} = \frac{\Delta V_C}{\Delta V_B} = -\frac{R_L}{R_E} = -620\text{ }\Omega / 80\text{ }\Omega = -7.75$$

For the AC part (small-signal analysis), the two capacitors block the DC bias voltages from the input and the output. V_{out} is 180° out of phase with V_{in} . R_E serves as a negative feedback for this amplifier. More on next page.

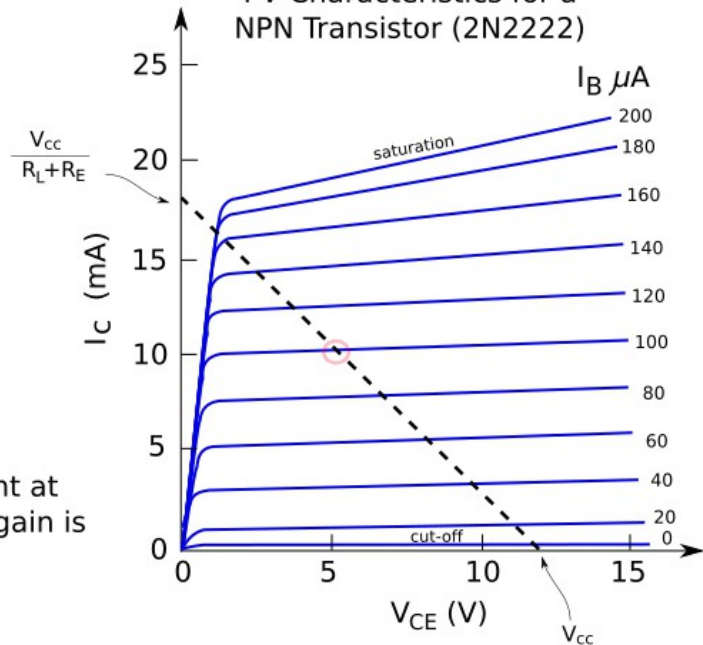
I-V Characteristics for a NPN Transistor (2N2222)




Cut-off

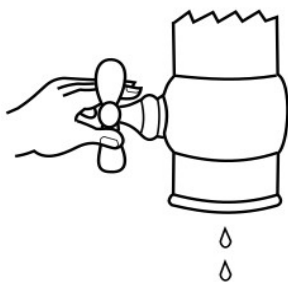

Operating (Linear)

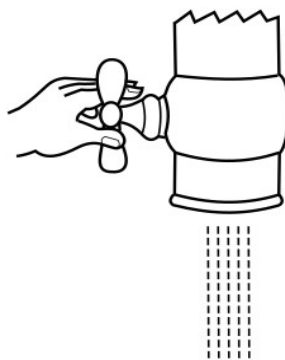


Saturation

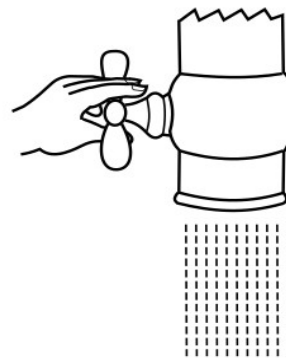

Small-Signal Analysis

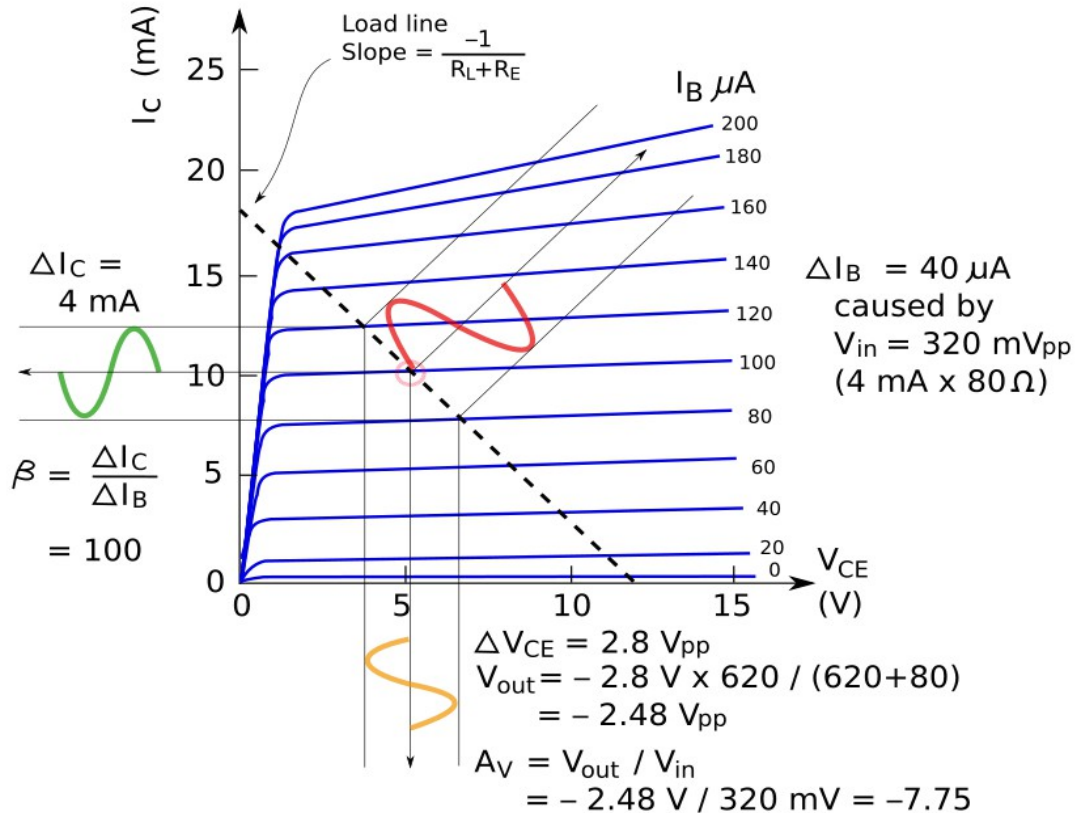The I-V characteristics of a transistor is highly nonlinear. However, if the transistor is biased at an appropriate operating point with DC voltages, a linear input-output relationship can be achieved for small-magnitude AC signals. Thus, this is called the small-signal analysis.



Transistor as a Switch

We use the buzzer circuit on our PIC board as an example. V_{BE} is always 0.7 V. So $I_B = (5\text{V} - 0.7\text{V}) / 10 \text{ K}\Omega = 430 \mu\text{A}$, which sets the transistor into saturation or “turns it on”. At saturation, V_{CE} is 0.2 V and I_C is about 20 mA. $I_{LED} = (5\text{V} - 0.7\text{V} - 0.2\text{V}) / 470 \Omega = 2.5 \text{ mA}$. $I_{buzzer} = 20 \text{ mA} - 2.5 \text{ mA} = 17.5 \text{ mA}$. A 5V buzzer is typically rated at 20 mA. Thus, this transistor switch provides a sufficient current to turn on the buzzer as well as the LED.

The transistor can operate in the nonlinear regions (cut-off and saturation), which acts like an on-off switch.

