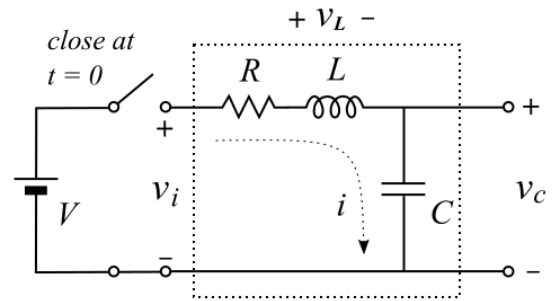


# Circuit Analysis Using Laplace Transform and Fourier Transform: RLC Low-Pass Filter

*Ying Sun*

The schematic on the right shows a 2nd-order RLC circuit. A constant voltage ( $V$ ) is applied to the input of the circuit by closing the switch at  $t = 0$ . The output is the voltage across the capacitor ( $C$ ). The circuit can be represented as a linear time-invariant (LTI) system. The input is  $v_i$ . If a constant voltage is applied at  $t = 0$ , it is a step input. We further normalize the input voltage  $V = 1$  such that it's unit step function. Thus, the input is the unit step function  $u(t)$ , and the output is the step response  $s(t)$ . The LTI system can be completely characterized by its impulse response  $h(t)$ . The step response is the convolution between the input step function and the impulse response:  $s(t) = u(t) \otimes h(t)$ .



## Circuit analysis using Laplace transform

The circuit analysis can be done by use of the Kirchhoff's voltage law and the properties of capacitor and inductor:

$$i = C \frac{dv_c}{dt}, \text{ and } v_L = L \frac{di}{dt} \text{----- (1)}$$

$$v_i = Ri + v_L + v_c = Ri + L \frac{di}{dt} + v_c \text{----- (2)}$$

By substituting (1) into (2), we have:

$$v_i = LC \frac{d^2v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c \text{----- (3)}$$

Although a closed form solution can be obtained by solving the above 2nd-order differential equation, we will take the frequency-domain approach. Taking LT on both side, we have:

$$V_i(s) = LC s^2 V_c(s) + RC s V_c(s) + V_c(s) \text{----- (4)}$$

The transfer function is given by:

$$H(s) = \frac{V_c(s)}{V_i(s)} = \frac{1}{LC s^2 + RC s + 1} \text{----- (5)}$$

We now use a different set of parameters:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\alpha s + \omega_n^2} \text{----- (6)}$$

where  $\omega_n = \frac{1}{\sqrt{LC}}$ , natural frequency

$$\alpha = \frac{R}{2L}, \text{ damping factor}$$

We further define damped frequency  $\omega_d$  :

$$\omega_d = \sqrt{\omega_n^2 - \alpha^2}; \quad \text{or} \quad \omega_n^2 = \omega_d^2 + \alpha^2; \quad \text{or} \quad \omega_n = \sqrt{\omega_d^2 + \alpha^2}$$

To obtain the impulse response, the transfer function is further extended to:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\alpha s + \omega_n^2} = \frac{\omega_n^2}{(s + \alpha + \sqrt{\alpha^2 - \omega_n^2})(s + \alpha - \sqrt{\alpha^2 - \omega_n^2})} = \frac{\omega_n^2}{(s + \alpha + j\omega_d)(s + \alpha - j\omega_d)} = \frac{\omega_d^2 + \alpha^2}{s^2 + 2\alpha s + \alpha^2 + \omega_d^2} = (\omega_d + \frac{\alpha^2}{\omega_d}) (\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}) \text{-----} (7)$$

The system has two poles at:  $-\alpha + j\omega_d$  and  $-\alpha - j\omega_d$ .

Taking the ILT, the impulse response is:

$$h(t) = (\omega_d + \frac{\alpha^2}{\omega_d}) e^{-\alpha t} \sin \omega_d t \text{-----} (8)$$

Next, we want to get a closed form solution for the step response. This will be accomplished by extending  $H(s)$  to  $H(s)/s$ , or  $S(s)$ , which is the LT of the step response.

$$S(s) = \frac{H(s)}{s} = (\omega_d + \frac{\alpha^2}{\omega_d}) (\frac{1}{s}) (\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}) = \frac{a}{s} + \frac{bs + c}{(s + \alpha)^2 + \omega_d^2}$$

$$\omega_d^2 + \alpha^2 = a(s + \alpha)^2 + a\omega_d^2 + bs^2 + cs = (a + b)s^2 + (2a\alpha + c)s + a(\omega_d^2 + \alpha^2)$$

We have  $a + b = 0$ ,  $2a\alpha + c = 0$ , and  $\omega_d^2 + \alpha^2 = a(\omega_d^2 + \alpha^2) \Rightarrow a = 1$ ,  $b = -1$ , and  $c = -2\alpha$ .

$$S(s) = \frac{1}{s} - \frac{s + 2\alpha}{(s + \alpha)^2 + \omega_d^2} = \frac{1}{s} - \frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2} - (\frac{\alpha}{\omega_d}) \frac{\omega_d}{(s + \alpha)^2 + \omega_d^2} \text{-----} (9)$$

Using the LT Table, we obtain the step response  $s(t)$ :

$$s(t) = 1 - e^{-\alpha t} [\cos \omega_d t + (\frac{\alpha}{\omega_d}) \sin \omega_d t] \text{-----} (10)$$

Next, we want to combine cosine and sine into one term with a phase angle. We further define the damping ratio  $\eta$ ,  $\eta = \frac{\alpha}{\omega_n}$ .

$$\frac{\alpha}{\omega_d} = \frac{\alpha}{\sqrt{\omega_n^2 - \alpha^2}} = \frac{1}{\sqrt{\omega_n^2/\alpha^2 - 1}} = \frac{1}{\sqrt{1/\eta^2 - 1}} = \frac{\eta}{\sqrt{1 - \eta^2}} \text{-----} (11)$$


$$s(t) = 1 - e^{-\alpha t} [\cos \omega_d t + (\frac{\eta}{\sqrt{1 - \eta^2}}) \sin \omega_d t] = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} [\sqrt{1 - \eta^2} \cos \omega_d t + \eta \sin \omega_d t] =$$

$$1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} [\sin \phi \cos \omega_d t + \cos \phi \sin \omega_d t] = 1 - \frac{e^{-\alpha t}}{\sqrt{1 - \eta^2}} \sin(\omega_d t + \phi) \text{-----} (12)$$

$$\text{where } \tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{\sqrt{1 - \eta^2}}{\eta}, \quad \phi = \tan^{-1} \frac{\sqrt{1 - \eta^2}}{\eta}.$$

From the previous circuit course, such as ELE 212, you might have learned what the damping ratio means: a) underdamping ( $\eta < 1$ ); b) critical damping ( $\eta = 1$ ); and c) overdamping ( $\eta > 1$ ).

Assume the underdamping situation,  $s(t)$  is shown on the right. The 2nd-order system requires two parameters to define, such as the damped frequency  $\omega_d$  and the damping factor  $\alpha$ . These two parameters can be obtained from the  $s(t)$  curve by making two measurements. A prominent feature point is the first peak after the onset. We measure the time to peak  $T_p$  and the amount of overshoot (OS). This point occurs when the derivative of the curve is 0.

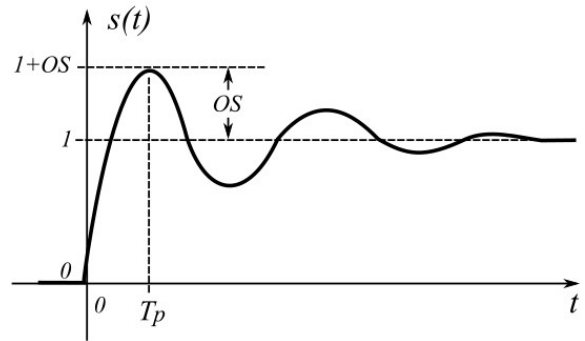

$$\frac{ds(t)}{dt} = 0$$

$$\frac{ds(t)}{dt} = h(t) = (\omega_d + \frac{\alpha^2}{\omega_d})e^{-\alpha t} \sin \omega_d t = 0 \dots\dots\dots (13)$$

The peaks and valleys occur when  $\omega_d t = 0, \pi, 2\pi, 3\pi, 4\pi, \dots$ . The first peak occurs when  $\omega_d t = \pi$ . Thus,  $T_p = \frac{\pi}{\omega_d}$ , or  $\omega_d = \frac{\pi}{T_p}$  ..... (14)

At the first peak  $T_p$ ,

$$s(T_p) = 1 - \frac{e^{-\alpha T_p}}{\sqrt{1-\eta^2}} \sin(\omega_d T_p + \tan^{-1} \frac{\sqrt{1-\eta^2}}{\eta}) = 1 - \frac{e^{-\alpha T_p}}{\sqrt{1-\eta^2}} \sin(\pi + \tan^{-1} \frac{\sqrt{1-\eta^2}}{\eta}) =$$

$$1 + \frac{e^{-\alpha T_p}}{\sqrt{1-\eta^2}} \sin(\tan^{-1} \frac{\sqrt{1-\eta^2}}{\eta}) = 1 + \frac{e^{-\alpha T_p}}{\sqrt{1-\eta^2}} \sqrt{1-\eta^2} = 1 + e^{-\alpha T_p} = 1 + OS \dots\dots\dots (15)$$

Thus,  $e^{-\alpha T_p} = OS$ , or  $\alpha = -\frac{\ln OS}{T_p}$  ..... (16)

**Frequency response**

Let's assign values to the circuit components so that we can plot the frequency response as an example. Let's assume:

$$R = 40 \Omega ; L = 1 \text{ mH} ; C = 0.1 \mu F \dots\dots\dots (17)$$

Based on these values, we have:

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \text{ mH} \times 0.1 \mu F}} = 100000 \text{ radians/s; and}$$

$$\alpha = \frac{R}{2L} = \frac{40 \Omega}{2 \times 1 \text{ mH}} = 20000$$


$$\omega_d = \sqrt{\omega_n^2 - \alpha^2} = \sqrt{100000^2 - 20000^2} = 97980 \text{ radians/s.}$$

$$\eta = \frac{\alpha}{\omega_n} = \frac{20000}{100000} = 0.2 ; \phi = \tan^{-1} \frac{\sqrt{1-\eta^2}}{\eta} = \tan^{-1} \frac{\sqrt{1-0.2^2}}{0.2} = 1.35 \text{ radians.}$$

The transfer function is  $H(s) = (\omega_d + \frac{\alpha^2}{\omega_d}) (\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2})$ . The system has the poles at  $-\alpha \pm j\omega_d$ , or  $-20000 \pm 97980j$ . The zeros are at infinity.
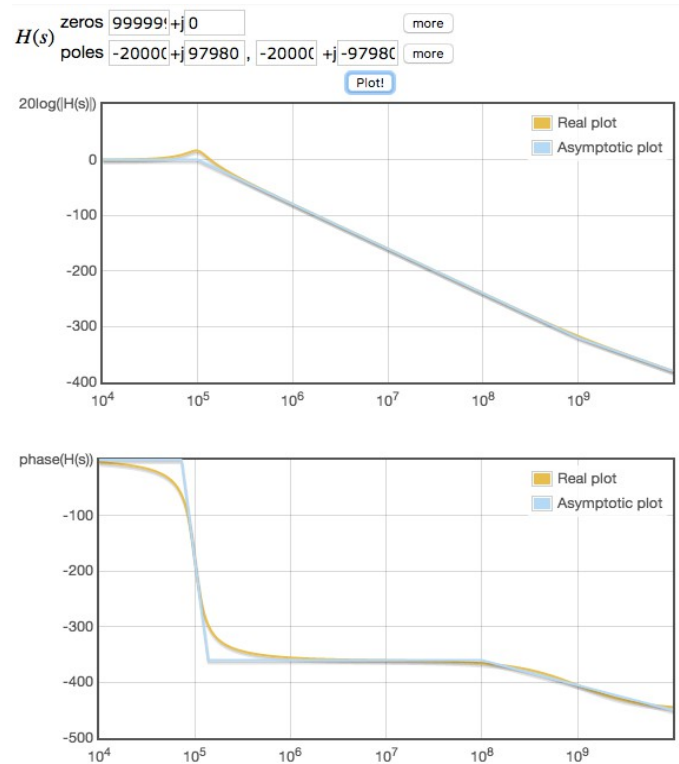
### Bode plot

Enter the poles of  $-20000 \pm 97980j$  at the online Bode plot generator <http://http://www.onmyphd.com/?p=bode.plot>. We obtain the following:



### Step response

$$s(t) = 1 - \frac{e^{-\alpha t}}{\sqrt{1-\eta^2}} \sin(\omega_d t + \phi) = 1 - \frac{e^{-20000t}}{0.9798} \sin(97980t + 1.35) =$$

Due to a range issue with the graphing calculator, we change the time unit from s to ms:

$$s(t) = 1 - \frac{e^{-20t}}{0.9798} \sin(97.98t + 1.35)$$

From the graph, we see that the peak occurs roughly at:  $T_p = 0.0323$  ms, and  $OS = 0.52$ .

Using the formula derived previously:

$$\omega_d = \frac{\pi}{T_p} = \frac{3.14159}{0.0000323} = 97263,$$

as compare to  $\omega_d = 97980$ .

$$\alpha = -\frac{\ln OS}{T_p} = -\frac{\ln 0.52}{0.0000323} = 20245,$$

as compare to  $\alpha = 20000$ .

