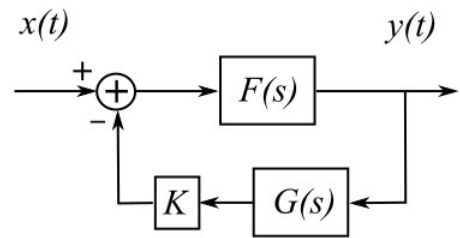


A gain parameter (K) is added to the feedback loop as shown. We have negative feedback for $K > 0$, positive feedback for $K < 0$. In order to explore the stability of the feedback system, K is adjusted over a wide range. For a given K , the roots of the system are plotted. As K is varied, the roots follow certain trajectories called root locus. The overall transfer function is:



$$H(s) = \frac{F(s)}{1 + K G(s) F(s)}$$

For those K 's where the root locus gets on the $j\omega$ axis or into the right side of the s -plane, the system becomes unstable. The roots of the system are given by:

$$1 + K G(s) F(s) = 0, \text{ or } G(s) F(s) = -\frac{1}{K} \quad (G(s)F(s) \text{ is called the loop gain.})$$

Example

Plot the root locus for $G(s) F(s) = \frac{s-1}{(s+1)(s+2)}$.

$$G(s) F(s) = \frac{s-1}{(s+1)(s+2)} = -\frac{1}{K} \Rightarrow -Ks + K = s^2 + 3s + 2 \Rightarrow$$

$$s^2 + (3+K)s + (2-K) = 0$$

$$\text{The roots are at: } s = \frac{-K-3 \pm \sqrt{(K+3)^2 + 4K-8}}{2} = \frac{-K-3 \pm \sqrt{K^2 + 10K + 1}}{2}.$$

For $K = 0$ (no feedback):

$$\text{roots at } s = \frac{-3 \pm 1}{2} = -1, -2; \text{ zeros at } 1, \infty.$$

For $K > 0$ (negative feedback):


Now we find the root locus for positive K starting from 0. Because the zeros are at 1 and ∞ , the root locus must enter either 1 or ∞ , as $K \rightarrow \infty$.

$K = 2 \Rightarrow s = 0, -5$. This is where one of the roots moves cross to the right side.

$K = 5 \Rightarrow s = 0.4, -8.4$.


$K \rightarrow \infty \Rightarrow s \rightarrow 1.0, -\infty$. $G(s)F(s) \rightarrow -0$ (approaching 0 from the negative side).

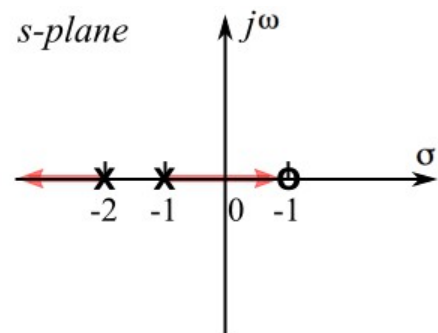The root locus plot is shown on the right.







Negative Capacitance: Compensation for Microelectrode Capacitance

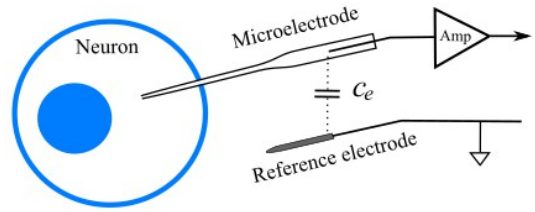The standard technique for recording action potentials from a neuron is to insert a microelectrode, which is made from a glass pipette by using an electrode puller. The microelectrode tapers and becomes very small at the tip ($\sim 1 \mu\text{m}$). The microelectrode has a large resistance R_e as well as a large stray capacitance C_e with respect to the surrounding bath solution.



The equivalent circuit is shown on the right, where R_m = membrane resistance, C_m = membrane capacitance, v_s = voltage signal to be measured, and v_i = input voltage to the amplifier. The equivalent circuit can be further reduced, where the source impedance Z_s includes R_e , R_m and C_m . If v_s is a square pulse, v_i would show a low-pass filtered waveform because of the presence of C_e . To recover the lost higher frequency components, an amplifier is designed such that the output voltage v_o resembles v_s , as illustrated.

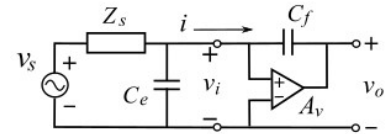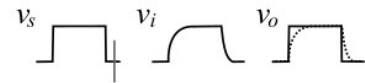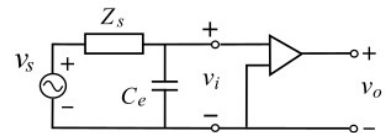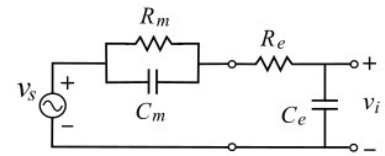

A technique typically used for this situation is based on a positive feedback circuit that creates a “negative capacitance” to cancel out C_e . As shown in the equivalent circuit, the gain of the amplifier is A_v , where $v_o = A_v \times v_i$. A positive feedback is created by connecting C_f from the output to the positive input terminal of the amplifier.

Let i be the current through C_f , we have

$$v_i = v_o + \frac{1}{C_f} \int i \, dt = A_v v_i + \frac{1}{C_f} \int i \, dt$$

$$(1 - A_v) v_i = \frac{1}{C_f} \int i \, dt \Rightarrow v_i = \frac{1}{(1 - A_v) C_f} \int i \, dt$$

$$\text{Choose } A_v = 1 + \frac{C_e}{C_f} \Rightarrow \frac{1}{(1 - A_v) C_f} = \frac{1}{-C_e}$$

The final equivalent circuit is shown on the right, where the negative capacitance $-C_e$ cancels out the electrode capacitance C_e , if the gain of the positive feedback A_v is properly set.

The gain should be set at $A_v = 1 + C_e/C_f$ in order to reproduce the square wave. Too low or too high a gain would affect the wave shape as shown on the right.

