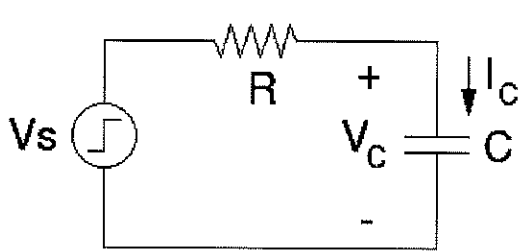


Name

Score

1) Linear Circuit Theory



V_s is a 5 V step function engaged at $t=0$.


$R=1\text{ k}\Omega$, $C=1\text{ nF}$

Assume $V_c(t=0) = 0$

Recall: $I_c = C\text{ d}V_c/\text{d}t$

- Find a value for the current I_c **immediately after** the source V_s stepped up to 5 V.
- What is the value of I_c **a long time after** the step has been applied ($t \rightarrow \infty$).
- Write down the **time-domain KVL** equation for the given circuit and derive a **symbolic solution** for the voltage $V_c(t)$ for $t \geq 0$.
- Find a value for the **time t_{90}** , where the **voltage V_c** has reached **90%** of its final value.


2) Voltage Regulator

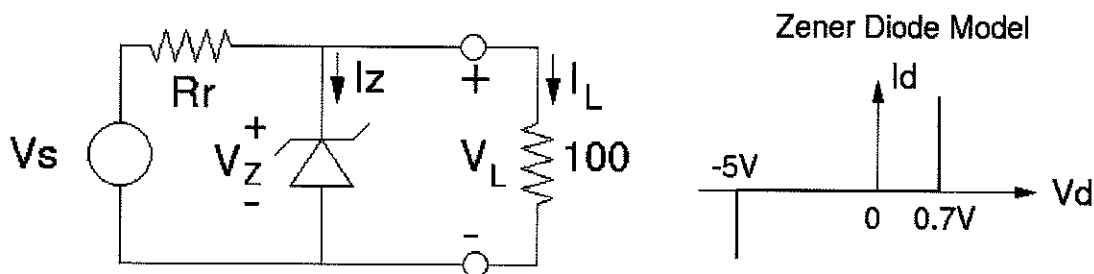

V_s is an unregulated dc voltage, which varies between 6.3 V and 7.0 V.

- What is the **minimum** value of V_L if $R_r = 50\Omega$? (Hint: Check if the Zener diode is on or off).
- Find a value for the **maximum** of the Zener diode current I_z if $R_r = 16\Omega$.
- What is the **minimum** of the Zener diode current I_z if $R_r = 16\Omega$?
- Derive a **value** for the **maximum** of R_r such that $V_L = V_Z = 5\text{ V}$ for all values of V_s between **6.3V** and **7.0 V**.

3) Voltage Reference with Diodes

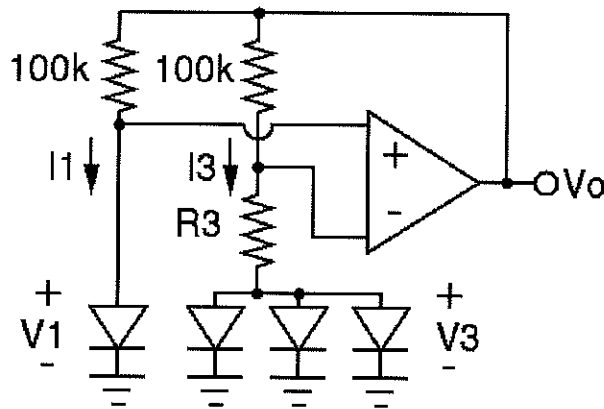

OpAmp is ideal and
all diodes are identical

@ $T=300\text{K}$ $nV_T=30\text{ mV}$

@ $T=400\text{K}$ $nV_T=40\text{ mV}$

$$I_d = I_s \exp(V_d/nV_T)$$

$$dV_d/dT = -1.7\text{ mV/K}$$

- Use the given **diode equation** to find a **symbolic expression** for the diode voltage difference $\Delta V_d = V_1 - V_3$.
- The output **voltage** V_o can be written as $V_o = V_1 + \dots$. Fill in the missing part of this equation. (Assume that V_1 and all resistor values are known).
- If $R_3 = 1.5\text{ k}\Omega$ and $V_1 = 670\text{ mV}$ at $T = 300\text{ K}$, find the values of V_o at the 2 temperatures i) $T_1 = 300\text{ K}$, and ii) $T_2 = 400\text{ K}$, respectively.
- Derive a value for R_3 such that the output **voltage** V_o becomes approximately **temperature independent** (i.e. remains constant), between $T_1 = 300\text{ K}$ and $T_2 = 400\text{ K}$.

$$1) \quad a) \quad \left\| \bar{I}_C(t=0^+) = \frac{V_{step}}{R} = 5 \text{ mA} \right\| \quad 2$$

$$b) \quad \left\| \bar{I}_C(t \rightarrow \infty) = 0 \right\| \quad 2$$

$$c) \quad \left| V_s = \bar{I}_C R + V_C = C \cdot R \frac{dV_C}{dt} + V_C \right| \quad 1$$

$$\text{for } t \geq 0 \quad |V_s = V_{step}|$$

$$\therefore \left\| V_C(t) = V_{step} (1 - e^{-\frac{t}{RC}}) \right\| \quad t \geq 0 \quad 3$$

$$d) \quad \left| V_C(t_{90}) = V_{step} (1 - e^{-\frac{t_{90}}{RC}}) = 0.9 V_{step} \right|$$

$$\therefore \left| e^{-\frac{t_{90}}{RC}} = 0.1 \right| \quad 2$$

$$\left\| t_{90} = RC \cdot \ln(10) = 2.3 \mu\text{s} \right\| \quad 2$$

12

2) a) $V_{S \min} = 6.5V$

If Zener is on $I_r = \frac{V_{S \min} - V_z}{R_r} = 26mA$

$\therefore I_r < I_L = 50mA$ for proper operation

\therefore | Zener is off |

$\| V_{L \min} = V_{S \min} \cdot \frac{R_L}{R_r + R_L} = 4.2V \|$

b) Zener is on $\therefore | I_{r \max} = \frac{V_{S \max} - V_z}{R_r} = 125mA |$

$| I_L = 50mA |$

$\therefore \| I_z = I_{r \max} - I_L = 75mA \|$

c) Zener is on: $| I_{r \min} = \frac{V_{S \min} - V_z}{R_r} = 81.25mA |$

$I_L = 50mA$

$\therefore \| I_z \min = I_{r \min} - I_L = 31.25mA \|$

d) Zener turn on: $| V_z = 5V ; I_z = 0 |$

$\therefore | I_{r \min} = \frac{V_{S \min} - V_z}{R_{r \max}} = I_L |$

$\therefore \| R_{r \max} = \frac{V_{S \min} - V_z}{I_L} = 26\Omega \|$

12

$$\begin{aligned} 3) \text{ a) } V_i - V_s &= nV_T \ln\left(\frac{I_i}{I_s}\right) - nV_T \ln\left(\frac{I_s}{I_s \cdot 3}\right) \\ &= nV_T \ln\left(\frac{I_i}{I_s} \cdot \frac{3I_s}{I_s}\right) \end{aligned}$$

$$\text{Ideal OpAmp } \therefore I_i \cdot 100k = I_s \cdot 100k$$

$$\therefore \Delta V_d = V_i - V_s = nV_T \ln(3) \quad 3$$

$$\text{b) } |V_o = V_i + 100k \cdot I_i = V_i + 100k \cdot I_s|$$

$$|I_s R_s = \Delta V_d|$$

$$\therefore I_s = \frac{\Delta V_d}{R_s}$$

$$\therefore |V_o = V_i + \frac{100k}{R_s} \Delta V_d = V_i + \frac{100k}{R_s} nV_T \ln(3) \quad 3$$

$$\text{c) i) } |V_{o1} = 0.67V + \frac{100}{1.5} 0.03 \ln(3)V = 2.867V \quad |$$

$$\text{ii) } |V_{o2} = 0.5V + \frac{100}{1.5} 0.04 \ln(3)V = 3.430V \quad |$$

$$\text{d) } \left| \frac{dV_o}{dT} = 0 \right| \therefore \left| \frac{dV_i}{dT} + n \frac{V_T}{T} \ln(3) \cdot \frac{100k}{R_s} = 0 \right|$$

$$\left| R_s = -100k \cdot \frac{nV_T}{T} \ln(3) \cdot \frac{1}{dV_i/dT} \right|$$

$$\left| R_s \right|_{R_s=300k} = 100k \cdot \ln(3) \cdot \frac{0.1mV}{1.7mV} = 6.46k\Omega \quad 4$$

121