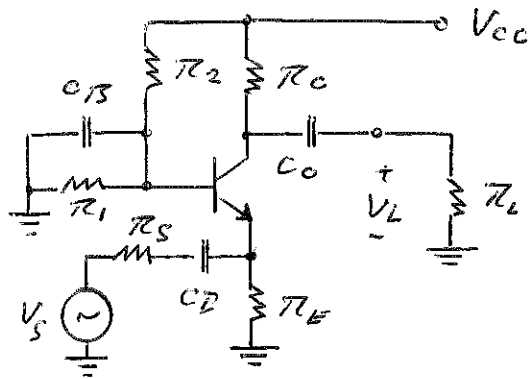


CIS Amplifier Example



Transistor

$$\beta = 100$$

$$V_A = 75V$$

$$V_{BEQ} \approx 0.7V$$

$$r_{V_T} \approx 30mV$$

| | | | |
|-------------------------|------------------------|------------------|---------------|
| $V_{CC} = 10V$ | $r_{\pi} = 5.6k\Omega$ | $C_2 = 27\mu F$ | $f_L = 100Hz$ |
| $R_C = R_L = 10k\Omega$ | $R_2 = 27k\Omega$ | $C_0 = 2\mu F$ | |
| $R_E = 2k\Omega$ | $R_S = 40\Omega$ | $C_B = 4.7\mu F$ | |

Find: • Q-point (I_{CQ}, V_{CEQ})

• $A_V = \frac{V_L}{V_S}$

Step 1: DC Analysis

$$I_{CQ} = \frac{V_{CC} \frac{R_1}{R_1 + R_2} - V_{BEQ}}{\frac{R_B}{\beta} + (1 + \frac{1}{\beta}) R_E}$$

$$R_B = 4.6k\Omega$$


$$\| I_{CQ} \approx 0.49 \|$$

$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E [1 + \frac{1}{\beta}])$$

$$\| V_{CEQ} \approx 4.1V \|$$

Step 2: AC Analysis (caps act as shorts)

Small Signal eq. Circuit

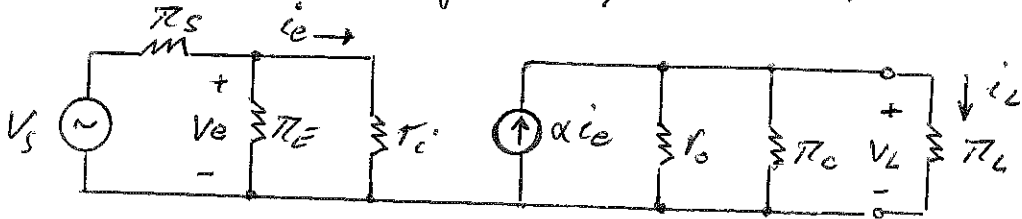

$$\left| \begin{array}{l} r_i = \frac{\alpha}{f_m} \approx \alpha \frac{V_T}{I_{CE}} \approx 60 \Omega \quad r_o = (1/\beta) \frac{V_A}{I_{CE}} \approx 15 \text{ M}\Omega \\ \tilde{r}_L = r_o \parallel r_c \parallel r_L \approx 5 \text{ k}\Omega \quad r_o \text{ is typically neglected} \end{array} \right|$$

Equations

$$\left| \begin{array}{l} V_e = i_e r_i \\ V_L = \alpha i_e \tilde{r}_L \\ V_e = V_s \cdot \frac{r_{in}}{r_s + r_{in}} \end{array} \right| \quad \text{where } r_{in} = r_e \parallel r_i \approx 59 \Omega$$

$$\left| A_V = \frac{V_L}{V_s} = \frac{r_{in}}{r_s + r_{in}} \cdot \frac{\alpha \tilde{r}_L}{r_i} \approx 49 \right|$$

$$\left| A_I = \frac{i_L}{i_e} \approx \alpha \frac{r_c}{r_c + r_L} \approx 0.50 \right|$$

$$\left| r_{out} = r_c \parallel r_o \approx 10 \text{ k}\Omega \right|$$

Note: Due to the low input resistance, the CC gain stage is frequently preceded by a CE or a CC gain stage