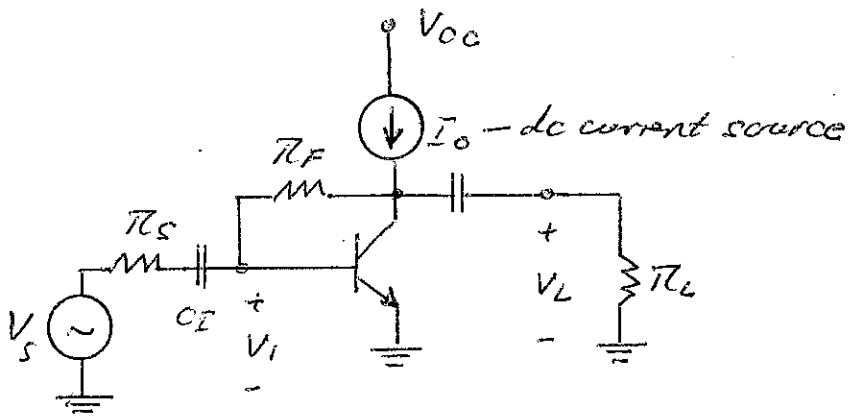


CE Amplifier with active Load

Basic Configuration



Transistor

$$\beta = 150$$

$$V_A = 75V$$

$$nV_T = 30mV$$

$$V_{BEQ} \approx 0.7V$$

Find : • Q-point (I_{CQ} and V_{CEQ})

• AC voltage gain $A_V = \frac{V_L}{V_i}$

$$R_S = 50\Omega$$

$$R_F = 560k\Omega$$

$$R_L = 100k\Omega$$

$$I_O = 1mA$$

Step 1: Q-point Analysis

$$KCL: I_O = I_{CQ} + I_{BQ} = I_{CQ} \left(1 + \frac{1}{\beta}\right)$$


$$\| I_{CQ} \approx I_O \left(1 - \frac{1}{\beta}\right) \approx 1.0mA \|$$

$$KVL: V_{CEQ} = V_{BEQ} + I_{CQ} R_F$$

$$\| V_{CEQ} = V_{BEQ} + I_{CQ} \frac{R_F}{\beta} \approx 4.4V \|$$

Step 2: AC Analysis (Caps act as shorts)

Small signal eq. circuit

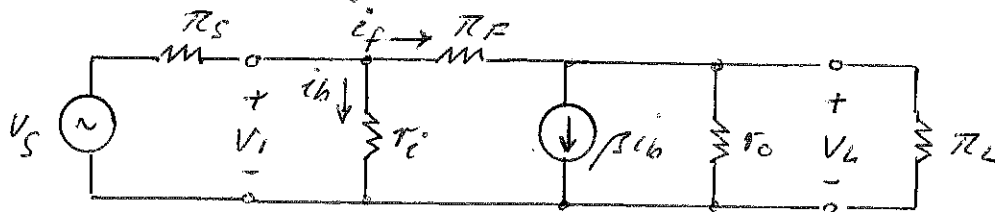

Equations

$$\begin{array}{l}
 (1) \quad V_1 = i_b \pi_i \\
 (2) \quad V_L = -\beta i_b \tilde{\pi}_L + i_f \tilde{\pi}_L \\
 (3) \quad i_f = (V_1 - V_L) \frac{1}{\pi_F}
 \end{array}
 \quad \left| \quad \begin{array}{l}
 \pi_i = \frac{\beta}{g_m} \approx 4.5 \text{ k}\Omega \\
 \tilde{\pi}_L = \pi_o \parallel \pi_L = 42.9 \text{ k}\Omega
 \end{array}
 \right.$$

$$\begin{array}{l}
 (3) \rightarrow (2) \\
 (1) \rightarrow
 \end{array}
 \quad V_L = -\beta i_b \tilde{\pi}_L + (i_b \pi_i - V_L) \frac{\tilde{\pi}_L}{\pi_F}$$

$$\text{or} \quad V_L = \left(-\beta i_b + i_b \frac{\pi_i}{\pi_F} \right) \frac{\tilde{\pi}_L \pi_F}{(\tilde{\pi}_L + \pi_F)}$$

$$\text{since } \frac{\pi_i}{\pi_F} \ll 1$$

$$|V_L| \approx -\beta i_b \tilde{\pi}_L \parallel \pi_F$$


and

$$\|A_V\| = \frac{V_L}{V_1} = -\frac{\beta}{\pi_i} \tilde{\pi}_L \parallel \pi_F = -g_m \tilde{\pi}_L \parallel \pi_F$$

$$\tilde{\pi}_L \parallel \pi_F \approx 39.8 \text{ k}\Omega$$

$$\therefore \|A_V\| \approx -1,327 \quad \text{very high gain!}$$

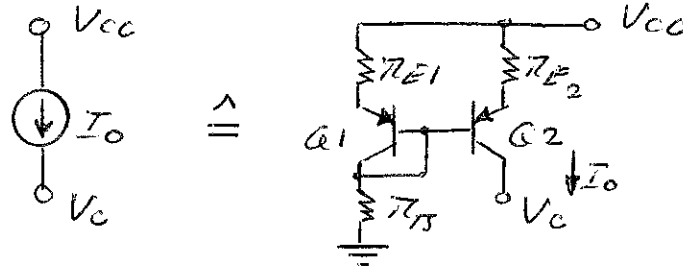Step 3: Replace ideal current source with current mirror



If Q_1 and Q_2 are reasonably well matched and $r_{E1} = r_{E2}$, then

$$\left\| \bar{I}_o \approx \frac{V_{CC} - V_{BEQ}}{r_{E1} + r_{E3}} \right\|$$

$$\left\{ \begin{array}{l} V_{CC} = 10V \\ V_{BEQ} \approx 0.7V \\ r_{E1} = r_{E2} = 310\Omega \\ r_{E3} \approx 9k\Omega \end{array} \right.$$

$$\therefore \bar{I}_o \approx 1mA$$

Note: This current source implementation yields an equivalent source resistance of

$$\left\| r_{out} = r_{o2} + \tilde{r}_E (1 + \beta m_2 r_{o2}) \right\|$$

$$\tilde{r}_E = r_{E2} \parallel V_{i2}$$

$$I_{CQ2} = 1mA$$

$$r_{o2} = \frac{V_{A2}}{I_{CQ2}}$$

$$V_{A2} = 40V$$

$$nV_T = 30mV$$

$$\beta = 150$$

$$\therefore \left\| r_{out} \approx 450k\Omega \right\|$$

$$\beta m_2 = \frac{I_{CQ2}}{nV_T}$$

CE Amplifier with active load

```
.model mod1 npn (bf=180 is=100f nf=1.2 va=80)
.model mod2 pnp (bf=180 is=100f nf=1.2 va=40)

.MODEL Q2N3904 NPN (Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)

.MODEL Q2N3906 PNP ((Is=1.41f Xti=3 Eg=1.11 Vaf=18.7 Bf=180.7 Ne=1.5 Ise=0
+ Ikf=80m Xtb=1.5 Br=4.977 Nc=2 Isc=0 Ikr=0 Rc=2.5 Cjc=9.728p
+ Mjc=.5776 Vjc=.75 Fc=.5 Cje=8.063p Mje=.3677 Vje=.75 Tr=33.42n
+ Tf=179.3p Itf=.4 Vtf=4 Xtf=6 Rb=10)

Vcc 1 0 dc 10

*Io 1 2 dc 1m
Rb 9 0 9k
Re1 1 8 330
Re2 1 10 330
q2 9 9 8 q2n3906
q3 2 9 10 q2n3906

Vs 5 0 dc 0 ac 1 sin(0,1.5m,1k)
rs 5 6 50
cs 6 3 4.7u
co 2 7 1u
r0 7 0 100k
rf 2 3 560k

q1 2 3 0 q2n3904


.opt probe post=1
.op
.ac dec 20 10 10meg
.tran 4u 4m 2m
.four 1k v(7)
.print tran v(2) v(3) v(7)
.print ac vm(7) vp(7)
.end
```

CE Amplifier with active Load

(Mag(V)) : f(Hz)

vm(7)

vm(7)

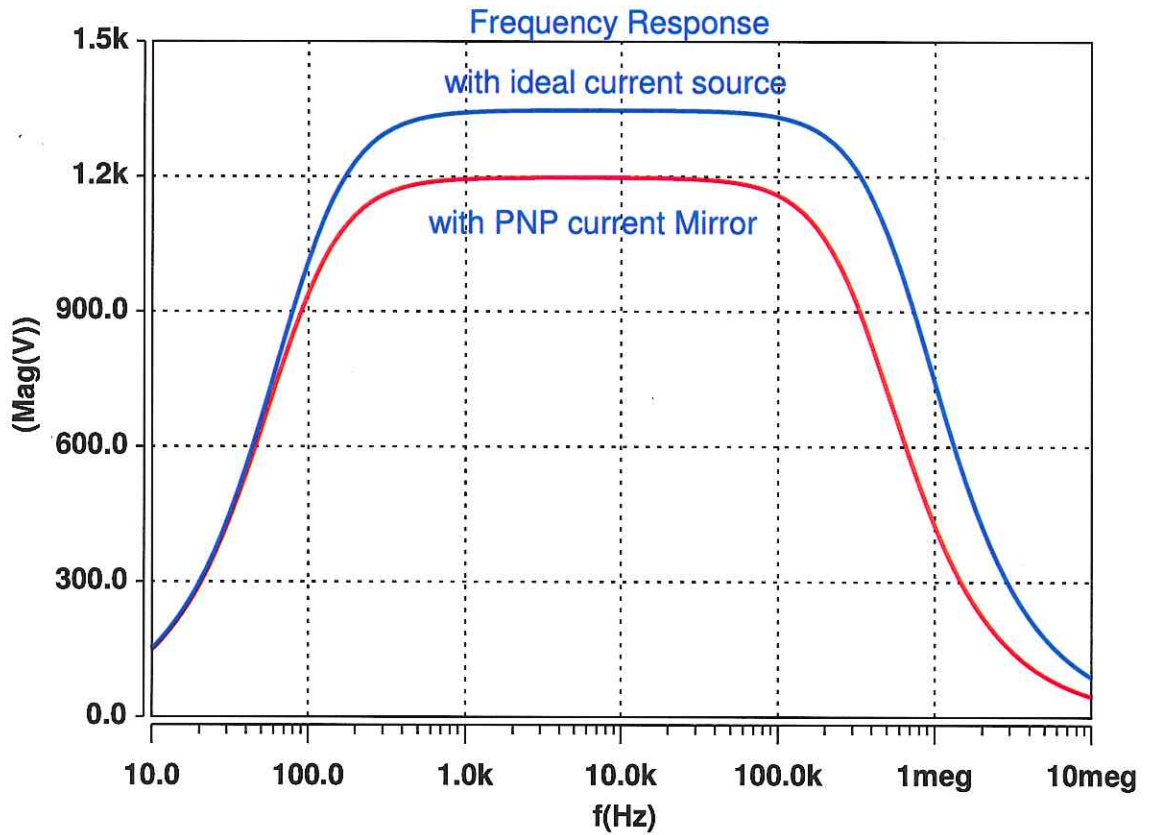

(V) : t(s)

v(7)

v(7)

