

CE Amplifier Example

Given: | Supply Voltage 10V
 $R_L = 10k\Omega$ |

Required: | $|A_V| > 100$
 100Hz - 100kHz Passband |

Transistor


$$100 < \beta < 400$$

$$V_{BE} \approx 0.7V$$

$$r_{V_T} \approx 30m\Omega$$

$$V_A \approx 80V$$

Topology

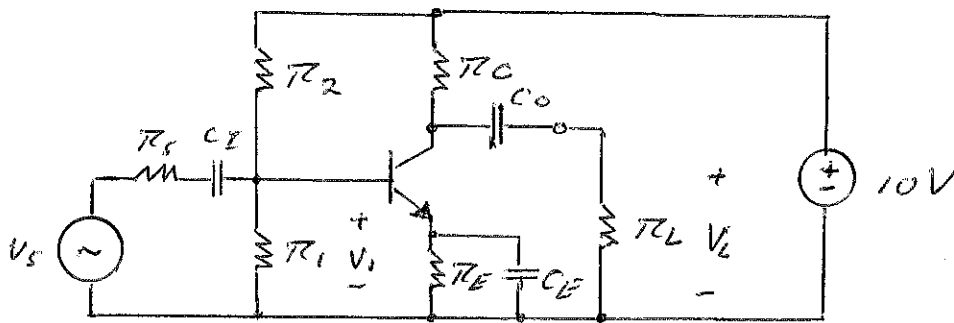

$$|A_V = \frac{V_o}{V_i}|$$

Note: C_1 , C_C and C_E are dc decoupling caps. Their values will depend on the required frequency band of the amplifier and the operating point (Q-point) values of the transistor.

To simplify the analysis, we will first assume that they act as shorts for all frequencies of interest. Subsequently, we will determine their proper values.

Step 1 Select Q-point

$$\text{e.g. } \begin{cases} I_{CQ} \approx 1 \text{ mA} \\ V_{CEQ} \approx 5 \text{ V} \end{cases}$$

Step 2 Determine values of biasing resistors.

$$\begin{cases} I_{CQ} = \frac{V_{CC} \frac{\pi_1}{\pi_1 + \pi_2} - V_{BEQ}}{\frac{\pi_1 \pi_2}{\beta} + (1 + \frac{1}{\beta}) \pi_E} \\ V_{CE} = V_{CC} - I_{CQ} [\pi_C + (1 + \frac{1}{\beta}) \pi_E] \end{cases}$$

Since you have 4 free parameters, namely π_1 , π_2 , π_C and π_E , there exists no unique solution!

We will use the 2 degrees of freedom to optimize the circuit performance with regard to Q-point stability and (possibly) power dissipation. The first objective requires $\pi_3 = \pi_1 \pi_2$ to be much smaller than $\beta \pi_E$, the second would require π_3 to be large (less current)

Practical Compromise:

$$\left| \begin{array}{l} R_1 = 10k\Omega \\ R_2 = 47k\Omega \end{array} \right|$$

$$\therefore R_{B3} \approx 8.2k\Omega$$

$$\left| R_E = 1k\Omega \right|$$

$$\left| I_{CQ} (\beta = 100) = 0.97 \text{ mA} \right|$$

$$\left| I_{CQ} (\beta = 400) = 1.03 \text{ mA} \right|$$

$$\therefore \| I_{CQ} = 1.00 \pm 0.03 \text{ mA} \|$$

Select $R_C = 4.7k\Omega$


$$\left| V_{CEQ} (\beta = 100) = 4.45 \text{ V} \right|$$

$$\left| V_{CEQ} (\beta = 400) = 4.11 \text{ V} \right|$$

$$\therefore \| V_{CEQ} = 4.28 \pm 0.17 \text{ V} \|$$

Step 3 Small Signal Analysis

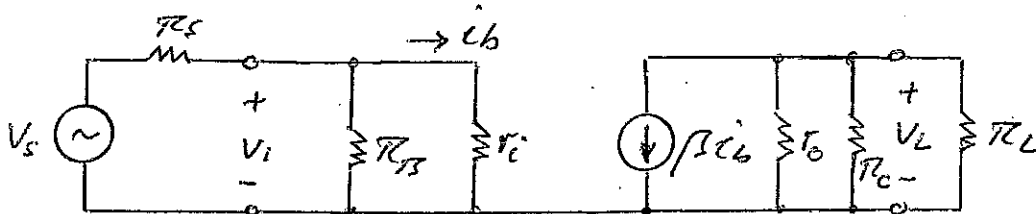Linear equivalent circuit (capacitors shorts)



where $r_{\pi} = \beta \frac{nV_T}{I_{CQ}}$

Note: $\beta i_b = g_m V_i$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{nV_T}$$

simplify, $r_o \parallel R_C \parallel R_L = \tilde{r}_L = 3.07k\Omega$

CE-4

$$|V_i = i_b r_i = i_b \frac{\beta}{g_m}| \quad |V_L = -\beta i_b \tilde{\pi}_L|$$

or

$$|V_L = -g_m V_i \tilde{\pi}_L|$$

$$\| A_v = \frac{V_L}{V_i} = -g_m \tilde{\pi}_L = -\frac{I_{ca}}{nV_T} \tilde{\pi}_L \|$$

$$\left| \begin{array}{l} I_{ca} = 1.00 \text{ mA} \\ nV_T = 30 \text{ mV} \\ \tilde{\pi}_L = 3.07 \text{ k}\Omega \end{array} \right| \quad \therefore \| A_v \approx -102.3 \pm 3 \|$$

Note: If magnitude of voltage gain would have been too small, we could have increased the bias current, I_{ca} .

$$\text{e.g.} \quad \left| \begin{array}{l} I_{ca} \approx 2 \text{ mA} \\ \pi_C \approx 2.2 \text{ k}\Omega \\ \pi_E \approx 500 \Omega \\ \tilde{\pi}_L \approx 1.73 \text{ k}\Omega \end{array} \right| \quad \left| \begin{array}{l} V_{CEA} \approx 3.9 \text{ V} \\ \therefore \| A_v \approx -115 \text{ V} \| \end{array} \right|$$

or

$$\left| \begin{array}{l} I_{ca} \approx 5 \text{ mA} \\ \pi_C \approx 1 \text{ k}\Omega \\ \pi_E \approx 200 \Omega \\ \tilde{\pi}_L \approx 960 \Omega \end{array} \right| \quad \left| \begin{array}{l} V_{CEA} \approx 3.3 \text{ V} \\ \therefore \| A_v \approx -144 \| \end{array} \right|$$

To keep Q-point β independent, π_1 and π_2 have to be reduced accordingly in the latter 2 cases.

Step 4 Determine values of decoupling caps

All 3 decoupling caps form a highpass filter with their respective resistor counterpart, that is

C_i and $r_{in} \approx 2.2 - 5.2 k\Omega$	for $I_{CQ} = 1mA$
C_o and $r_L \approx 10 k\Omega$	
C_E and $r_E \parallel \frac{1}{g_m} \approx \frac{1}{g_m} \approx 33 \Omega$	

Since C_E turns out to have the smallest resistor counterpart, we select it to set the low frequency corner at 100Hz

$$\| C_E = \frac{g_m}{2\pi f_L} = 48 \mu F \|$$

To avoid overlaps with the corner frequency f_L , we select the values of C_i and C_o such that they form a corner at around $1/10$ of f_L . Hence

$$\| C_i = \frac{10}{2\pi f_L r_{in}} \approx 5.3 \mu F \|$$


$$\| C_o = \frac{10}{2\pi f_L r_L} \approx 1.6 \mu F \|$$

CE Amplifier Design Example

Frequency Response

(Mag(V)) : f(Hz)

vm(7)

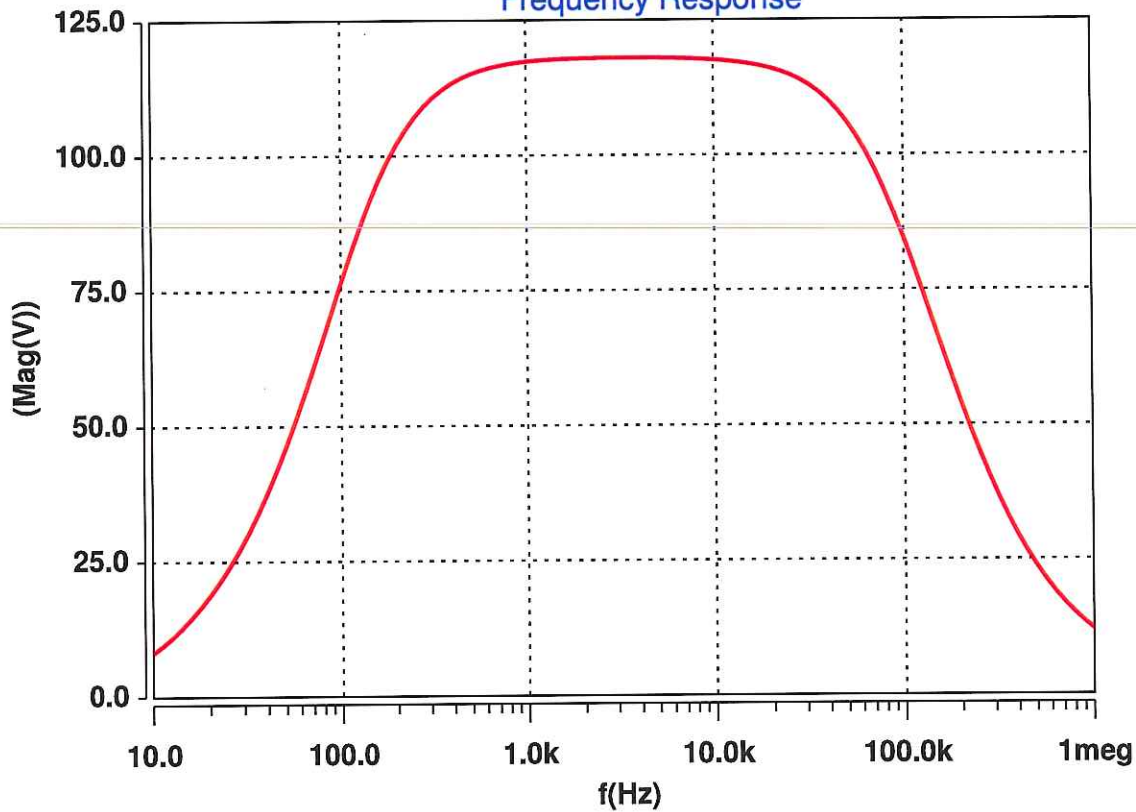


Transient Response


(V) : t(s)

v(7)

v(5)

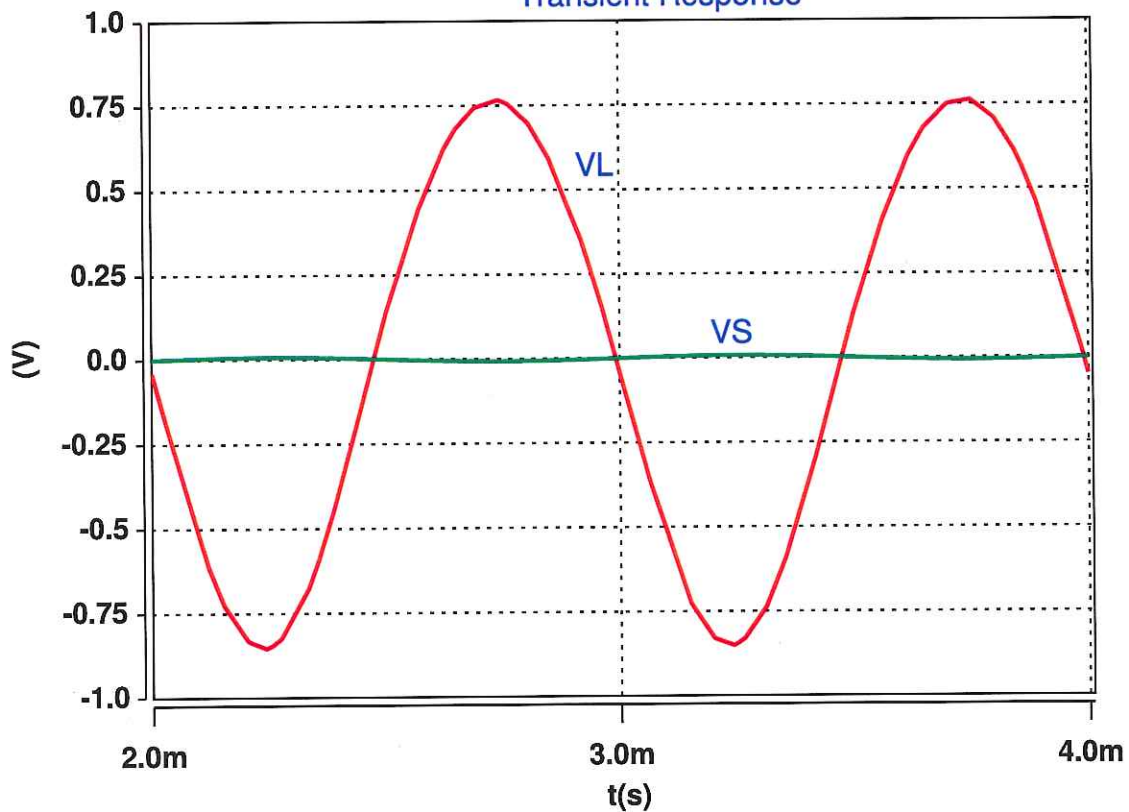

CE Amplifier with Emitter Degeneration

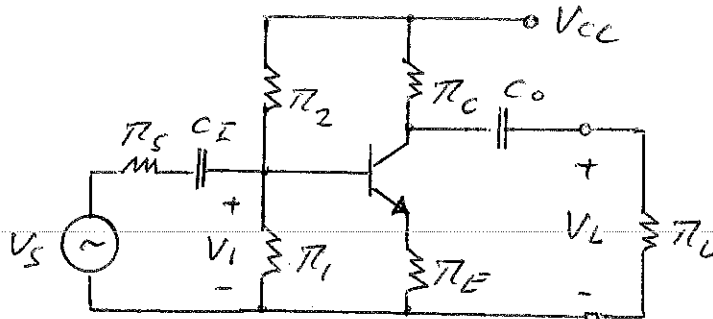

Transistor

$$\beta = 150$$

$$V_A = \infty$$

$$V_{BEQ} \approx 0.7V$$

$$r_{V_T} \approx 30mV$$

$$V_{CC} = 10V$$

$$\pi_1 = 10k\Omega$$

$$\pi_c = 10k\Omega$$

$$\pi_2 = 75k\Omega$$

$$\pi_L = 10k\Omega$$

$$\pi_E = 1k\Omega$$

Find:

- Q-point (I_{CQ}, V_{CEQ}) DC Analysis

- $A_v = \frac{V_L}{V_i}$ AC Analysis

Step 1: DC Analysis


$$|\pi_B = 8.8k\Omega|$$

$$(\pi_B = \pi_1 // \pi_2)$$

$$\left\| \begin{aligned} I_{CQ} &= \frac{V_{CC} \frac{\pi_1}{\pi_1 + \pi_2} - V_{BEQ}}{\frac{\pi_B}{\beta} + (1 + \frac{1}{\beta})\pi_E} \approx 0.52mA \\ V_{CEQ} &= V_{CC} - I_{CQ}(\pi_c + [1 + \frac{1}{\beta}]\pi_E) \approx 4.3V \end{aligned} \right\|$$

Step 2: AC Analysis (Capacitors as shorts)

Small Signal eq. Circuit

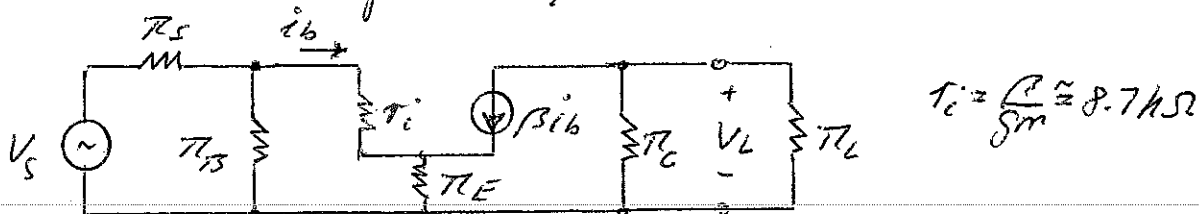

Equations:

$$(1) \quad \left| \begin{array}{l} V_i = i_b r_{\pi} + (1 + \beta) i_b r_E \\ V_L = -\beta i_b \tilde{r}_L \end{array} \right|$$

$$\tilde{r}_L = r_C \parallel r_L = 5 \text{ k}\Omega$$

$$\therefore A_v = - \frac{\beta \tilde{r}_L}{r_{\pi} + (1 + \beta) r_E}$$

$$= - \frac{\tilde{r}_L}{11 g_m + (1 + \frac{1}{\beta}) r_E}$$

$$\| A_v \approx - \frac{\tilde{r}_L}{\frac{\Delta V_T}{I_{CQ}} + r_E} = -4.7 \|$$

Note: The emitter resistor r_E significantly reduces the gain. In return, it keeps the output voltage (V_L) more linear since the denominator of the voltage gain varies less with I_{CQ} .