
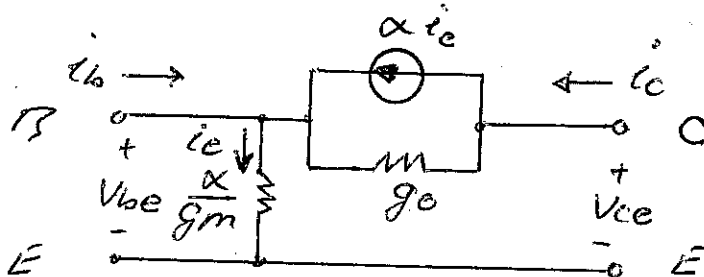


# CE Model Parameters

from Physics (small signal equivalent)

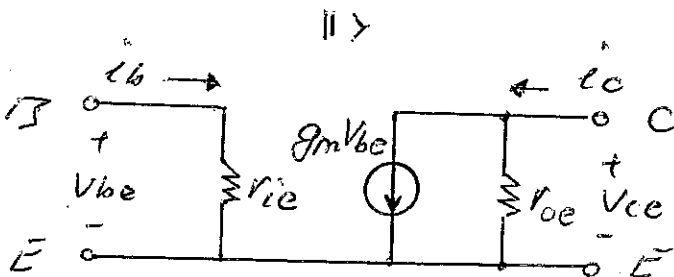

Note:  $g_o$  is conductance of reverse biased CB junction



Note:  $\alpha i_e = g_m V_{be}$

$$\left\| \begin{aligned} r_{oe} &= \left. \frac{V_{ce}}{i_c} \right|_{V_{be}=0, i_b=0} & r_{ie} &= \left. \frac{V_{be}}{i_b} \right|_{V_{ce}=0} = \frac{\alpha}{g_m} (1 + \beta) = \frac{\beta}{g_m} \end{aligned} \right\|$$

Applying the above definition the the original circuit yields:

$$V_{ce} \Big|_{i_b=0} = i_c \left( \frac{\alpha}{g_m} + [1-\alpha] \frac{1}{g_o} \right)$$

or

$$\left\| \frac{V_{ce}}{i_c} \Big|_{i_b=0} = \frac{\alpha}{g_m} + [1-\alpha] \frac{1}{g_o} \approx [1-\alpha] \frac{1}{g_o} \right\|$$

$$\left| r_{ce} \approx [1-\alpha] r_o \right| \quad 1-\alpha = \frac{1}{1+\beta}$$

$$r_o = 1/g_o$$

# NPN BJT Output Characteristics (CE Configuration)

