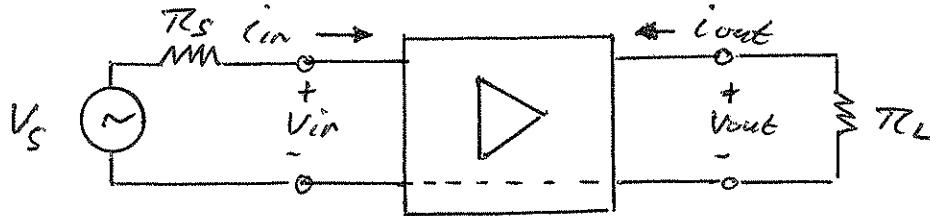
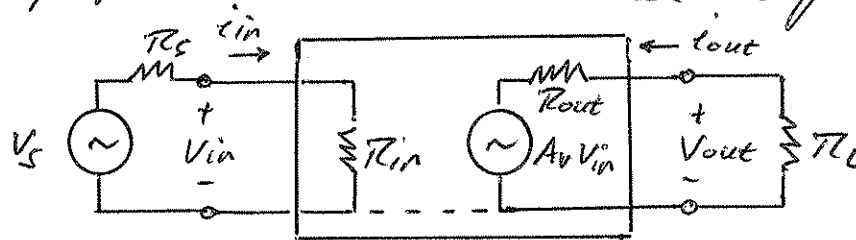


# Amplifier Classification

Amplifiers feature an input and an output port and thus can be modeled as a 2-port



If we treat the amplifier as a box, we can only observe the input current  $i_{in}$ , the input voltage  $V_{in}$ , the output current  $i_{out}$  and the output voltage  $V_{out}$ . The interior circuitry of the amplifier can be modeled as follows:



The depicted parameters are defined as

$$\left| \begin{array}{ll} A_V = \frac{V_{out}}{V_{in}} & R_{in} = \frac{V_{in}}{i_{in}} \Big|_{R_L} \\ A_I = \frac{i_{out}}{i_{in}} & R_{out} = \frac{V_{out}}{i_{out}} \Big|_{V_s=0} \end{array} \right|$$

Note:  $V_s$  and  $R_s$  as well as  $R_L$  are frequently decoupled from the amplifier bias circuitry by capacitors, which only pass the AC signals.

## Measuring $\pi_{in}$ and $\pi_{out}$

$\pi_{in}$  and  $\pi_{out}$  can readily be computed by replacing the amplifier circuit by a linear equivalent circuit and imposing the specific operating condition based on the definitions of  $\pi_{in}$  and  $\pi_{out}$ .

When measuring  $\pi_{in}$  and  $\pi_{out}$ , we have to make sure we are not altering the operating conditions of the amplifier. An effective way to measure  $\pi_{in}$  and  $\pi_{out}$  is to apply a single (AC) source  $V_S$  and record the open loop and closed loop voltage at the input and output, respectively. The unknown resistors  $\pi_{in}$  and  $\pi_{out}$  can then be computed as follows:

$$\left| \begin{array}{l} V_{in}(\text{open}) = V_S \\ V_{in}(\text{closed}) = V_S \cdot \frac{\pi_{in}}{\pi_S + \pi_{in}} \end{array} \right| \quad \left\| \pi_{in} = \pi_S \frac{V_{in}(\text{closed})}{V_{in}(\text{open}) - V_{in}(\text{closed})} \right\|$$

and

$$\left| \begin{array}{l} V_{out}(\text{open}) = A_V \cdot V_{in} \\ V_{out}(\text{closed}) = A_V \cdot V_{in} \frac{\pi_L}{\pi_{out} + \pi_L} \end{array} \right| \quad \left\| \pi_{out} = \pi_L \frac{V_{out}(\text{open}) - V_{out}(\text{closed})}{V_{out}(\text{open})} \right\|$$

For best accuracy select  $\pi_S \approx \pi_{in}$  (expected)

$\pi_L \approx \pi_{out}$  (expected)