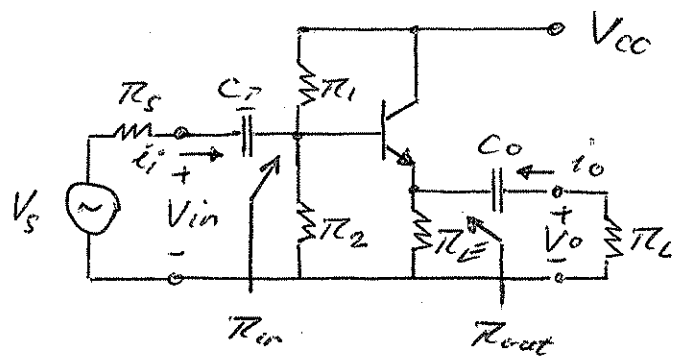


2.6 Common Collector Amplifier (Emitter Follower)


The CC amplifier is typically used as the output stage of an amplifier cascade. It provides a comparatively high input resistance paired with a small output resistance and thus yields a high current gain.

Basic Configuration



Assumption:
The 2 coupling caps C_2 and C_0 act as AC shorts

Small signal equivalent circuit

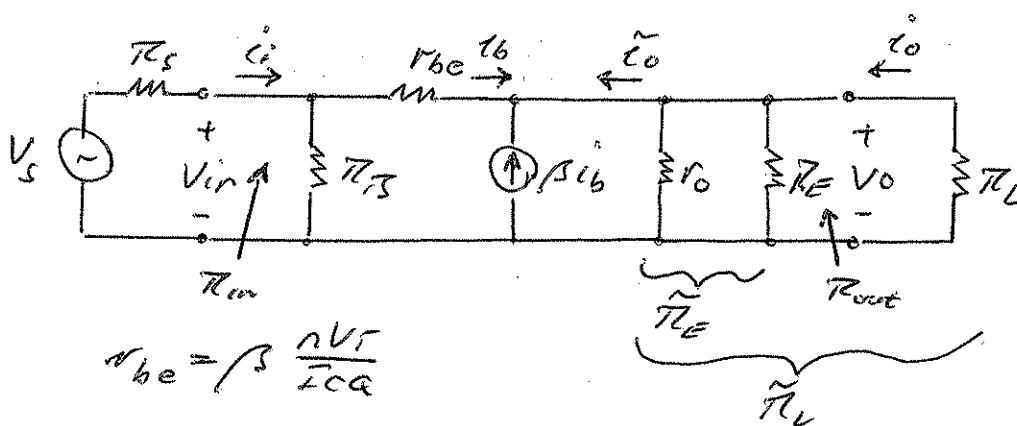

$$r_{be} = \beta \frac{nV_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

Equations:

$$V_{in} = i_b [\beta_{be} + (1+\beta)\tilde{r}_c] \quad (1)$$

$$i_i = i_b + \frac{V_{in}}{\tilde{r}_B} \quad (2)$$

$$\| \tilde{r}_{in} = \frac{V_{in}}{i_i} = \tilde{r}_B \parallel \frac{V_{in}}{i_b} = \tilde{r}_B \parallel [\beta_{be} + (1+\beta)\tilde{r}_c] \| \quad (3)$$

$$V_o = (1+\beta) i_b \tilde{r}_L \quad (4)$$

$$-i_o \tilde{r}_L = (1+\beta) i_b \tilde{r}_L \quad \text{or} \quad i_o = -(1+\beta) \frac{\tilde{r}_E}{\tilde{r}_E + \tilde{r}_L} i_b \quad (5)$$

Internal Current Gain:

$$\| A_I = \frac{i_o}{i_b} = -(1+\beta) \frac{\tilde{r}_E}{\tilde{r}_E + \tilde{r}_L} \| \quad \text{Notes: } A_I = \left. \frac{i_o}{i_i} \right|_{\tilde{r}_B = \infty} \quad (6)$$

Voltage Gain:

$$\| A_V = \frac{V_o}{V_{in}} = \frac{(1+\beta)\tilde{r}_L}{\beta_{be} + (1+\beta)\tilde{r}_L} \cong \frac{\tilde{r}_L}{\beta_{ve}/\beta_{ce} + \tilde{r}_L} \| \quad (7)$$

Output Resistance:

$$\| \tilde{r}_{out} = \left. \frac{V_o}{i_o} \right|_{V_s=0} = \tilde{r}_E \parallel \frac{V_o}{i_o} = \tilde{r}_E \parallel \frac{\beta_{be} + \tilde{r}_B \parallel \tilde{r}_S}{1+\beta} \| \quad (8)$$

CC Amplifier Design Example

Realize a CC gain stage that can drive an 8Ω speaker and yield an output voltage swing of at least 1V. $V_{CC} = 10V$, $\beta = 150$; $V_{BE} = 60V$, $r_s = 50\Omega$;

1. Select I_{CQ} large enough to yield an output swing of 1V

choice: $|I_{CQ} = 250mA|$

2. Select R_1 & R_2 such that $V_{EQ} \approx 5V$ and $\frac{R_1 R_2}{\beta} \ll R_E$

Select $|R_1 = R_2 = 270\Omega| \rightarrow R_B = 155\Omega$

3. From $I_{CQ} \approx \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BEQ}}{\frac{R_B}{\beta} + R_E}$ we obtain $R_E = 16.3\Omega$

choose $|R_E = 15\Omega|$ (availability) $\rightarrow I_{CQ} \approx 270mA$

Performance Parameters:

$A_V \approx 0.98$	$R_{in} \approx 117\Omega$
$A_I \approx -72.7$	$R_{out} \approx 0.24\Omega$

Note: R_{in} could be made significantly larger if we could increase R_B . Solution: Use bipolar supply voltages (see Lab 7, Fig. 1)