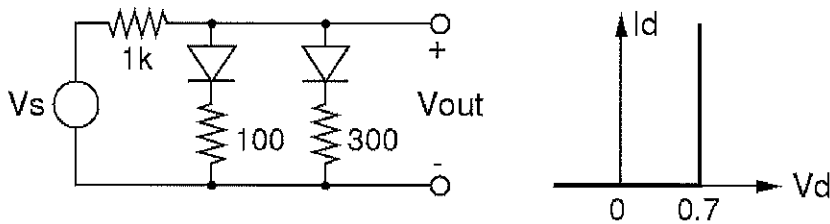


Note: Only solve 4 of the 5 problems given!


Name:

1) Diode Application




- a) Find a value for the current I_S flowing through the $1\text{ k}\Omega$ resistor if V_S is a **dc voltage** of 5 V .
- b) Determine the **maximum value** of V_{out} if V_S is a **sinusoidal voltage** of 5V amplitude.
- c) What is the **minimum value** of V_{out} for the operating conditions given in b)?
- d) Based on the given diode model, we can replace the 2 diode branches by a **single branch** comprising **one** diode in series with a resistor R_x . What is the **value** of this equivalent resistor R_x ?

2) Cascade of two CC Gain Stages

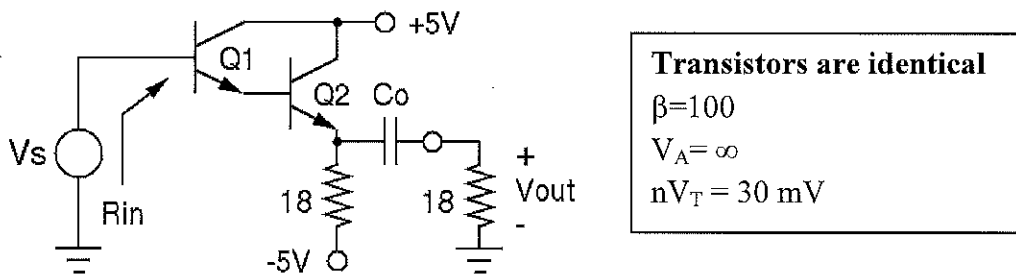

- a) Find a value for the **dc collector current** I_{C2} of **Q2** if V_s is an **ideal ac source** (To simplify matters, you can assume that **both transistors** feature the same **base-emitter voltage** of 0.7 V).
- b) What is the **actual difference** ΔV_{BE} of the two **base-emitters voltages** if we know that Q2 carries **100 times** more current than Q1 but also features a **4 times higher** saturation current I_s due to an elevated junction temperature? (Hint: You can neglect the change in V_T for this calculation since it has little impact).
- c) Find a value for the **maximum ac output swing** (amplitude in V) of this circuit? (Assume that the cap C_o acts as an ac short)
- d) Find the numerical value of the **input resistance** R_{in} (C_o acts as an ac short).


3) **MOSFET Current Mirror**

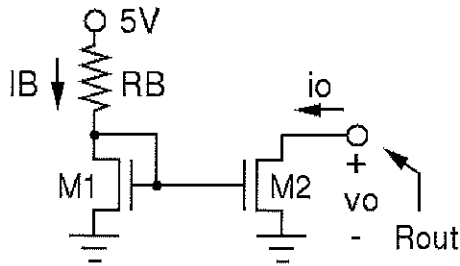

Transistors are identical
 $\mu C_{ox} W/L = 400 \mu A/V^2$
 $V_t = 0.8 V$
 $\lambda = 0.02 V^{-1}$

- Find **RB** such that M1 features a **dc drain current IB** of **100 μA** .
- Find the **minimum value of Vo** that keeps **both transistors in saturation**.
- Derive a numerical value for the **output resistance Rout**.
- By **how much** would **Rout increase** if you were to switch a resistance **Rs of 3k Ω** between the source and ground of **each transistor**? (**IB** remains at **100 μA**)


4) **BJT Amplifier**

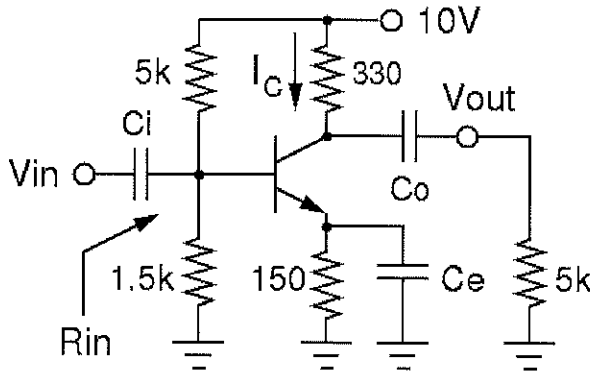

Transistor Parameters:
 $V_{BEQ} = 0.7 V$
 $\beta = 100$
 $V_A = \infty$
 $nV_T = 30 mV$

- What is the value of the **equivalent base resistor RB**?
- Find the Q-point values **ICQ** and **VCEQ** of the depicted NPN transistor.
- Sketch the ac equivalent circuit under the assumption that all three **capacitors** represent **shorts for ac** frequencies and find a numerical value for the voltage gain **AV=Vout/Vin**.
- Find a value for the **input resistance Rin at dc** (**Ci** is not included in **Rin**).

5) MOSFET Amplifier

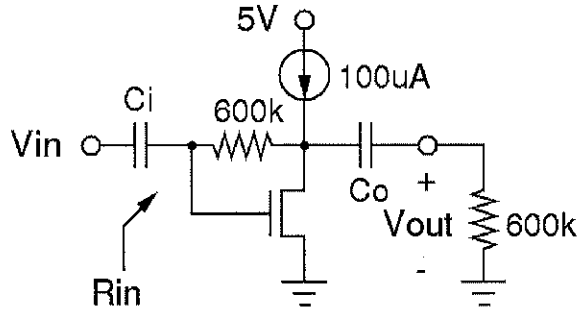

MOSFET Parameters:

$$\mu C_{ox} W/L = 800 \mu A/V^2$$

$$V_t = 0.8 V$$

$$\lambda = 0.02$$

- Find the **dc value** of the **drain voltage** V_D of the depicted MOS transistor (Note: the depicted current source is an **ideal dc source**).
- Sketch the **small signal or ac equivalent circuit** under the assumption that both **capacitors** represent **ac shorts**.
- Derive a **symbolic expression** and a numerical value for the voltage gain $A_v = V_{out}/V_{in}$.
- Find a numerical value for the input resistance (Recall that C_o acts as a short for ac frequencies).

