

# ELE 344 - LAB 1

---

## COMMON-EMITTER AMPLIFIER

Kevin Sylvestre

Section 2

**PURPOSE OF EXPERIMENT:**

The purpose of the experiment is to be exposed to typical design problems with multiple degrees of freedom, where it is the job of the designer to find a compromise between sometimes conflicting performance requirements. In this case, the manipulation of a common-emitter amplifier's component values had to be manipulated to meet the requirements of each task.

## EXPERIMENTAL PROCEDURES:

### TASK 1:

ANALYSIS: Task 1 required consideration of the given circuit model, and the derivation of an expression for the bias current  $I_C$ , containing only  $R_1$ ,  $R_2$ ,  $R_{E1}$ ,  $R_{E2}$ ,  $V_{BE}$  and  $\beta$ . This required DC analysis, so the DC equivalent model had to be drawn. Then, from here, considering the Kirchhoff voltage loop formed between the upper rail voltage and ground, through  $R_1$  and  $R_2$ , the expression could be derived.

DATA AND CALCULATION: The KVL equation is shown below.

$$V_{TH} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}, \quad R_{TH} = R_1 || R_2, \quad R_E = R_{E1} + R_{E2}$$

$$V_{TH} = R_{TH}I_B + V_{BE} + R_E I_E(1 + \beta)$$

From this equation, the derivation was straightforward. The idea is to simply isolate  $I_C$  and use values which are either known or allowed to be included.

$$V_{TH} - V_{BE} = R_{TH}I_B + R_E I_E(1 + \beta)$$

$$V_{TH} - V_{BE} = R_{TH} \frac{I_C}{\beta} + R_E \frac{I_C}{\beta} (1 + \beta)$$

$$V_{TH} - V_{BE} = I_C \frac{R_{TH}}{\beta} + I_C R_E \left( \frac{1}{\beta} + 1 \right)$$

$$V_{TH} - V_{BE} = I_C \left( \frac{R_{TH}}{\beta} + R_E \left( \frac{1}{\beta} + 1 \right) \right)$$

$$I_C = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta} + R_E \left( \frac{1}{\beta} + 1 \right)}$$

RESULTS: The resulting expression for  $I_C$  is shown above.

## TASK 2:

**ANALYSIS:** Task 2 requires an analysis of the voltage gain at mid-band frequencies. This implies AC analysis. The small signal equivalent circuit was drawn and subsequently analyzed.

**DATA AND CALCULATION:** A few steps led to the voltage gain equation. First,  $V_{out}$  and  $V_{in}$  had to be calculated separately before their ratio could be found.

$$A_{V_{in}} = \frac{V_{out}}{V_{in}}, \quad V_{out} = R_C \parallel R_L (-g_m V_{\pi}), \quad V_{in} = V_{\pi} + V_{\pi} \left( g_m + \frac{1}{R_{\pi}} \right)$$

From here, putting  $V_{out}$  over  $V_{in}$  and making a few cancellations will result in the voltage gain equation in question.

$$A_{V_{in}} = \frac{V_{out}}{V_{in}} = \frac{-g_m R_C \parallel R_L}{\left( 1 + g_m + \frac{1}{R_{\pi}} \right) R_{E1}}$$

$$A_{V_{in}} = \frac{-R_C \parallel R_L}{\frac{V_{\pi}}{I_C} + R_{E1}}$$

**RESULTS:** The resulting expression for the voltage gain of this common-emitter circuit is shown above. It is important to note that the value of  $R_{E1}$  should be considerably larger than the value of  $1/g_m$  so that the gain is stable and controlled.

## TASK 3:

**ANALYSIS:** Task 3 calls for an expression for the input impedance of the circuit,  $Z_{in}$ . This also requires AC analysis. First, the input resistance, not including the base resistors ( $R_1$  and  $R_2$ ). Then, the base resistors are included to complete the expression.

**DATA AND CALCULATION:** The input resistance without the base resistors is shown below. It was acquired by inspection of the small signal model.

$$r_{in} = \frac{V_{in}}{i_b} = (1 + \beta) \frac{V_{\pi}}{I_C} + (1 + \beta) R_{E1}$$

From here, this needs to be put in parallel with the base resistors. This is shown below, and concludes the derivation.

$$Z_{in} = \frac{V_{in}}{i_{in}} = r_{in} \parallel R_1 \parallel R_2$$

**RESULTS:** The resulting expression for the input resistance can be seen above. It is in a simplified form, making it easier to read.

#### TASK 4:

**ANALYSIS:** Task 3 is when the designing and choice-making must begin. Given the voltage swing must be at least 4V, one can derive a value for  $I_C$  based on  $R_C$  and the swing. With this value, and with the knowledge that when the rail voltage is above 5V,  $V_{CE}$  and  $V_{RE}$  are about equal, one can divide the remaining voltage from the upper rail between  $V_{CE}$  and  $V_{RE}$ , from which resistance can be calculated, since current values are known. With knowledge of these values, both  $R_{E1}$  and  $R_{E2}$  can be given initial estimates, which, combined with the restriction on  $Z_{in}$ , will lead to the calculation of  $R_1$  and  $R_2$ .

**DATA AND CALCULATION:** First, IC must be selected according to the values given. Since the swing must be at least 4V, we have chosen 5V.

$$I_C = \frac{V_{swing}}{R_C} = \frac{5V}{3.9k\Omega} = 1.28mA$$

From here, this can be used in a rearranged gain equation, to estimate a value for  $R_{E1}$ .

$$R_{E1} = \frac{-R_C || R_L}{A_{vin}} - \frac{V_T}{I_C} = \sim 120\Omega$$

Using another equation, one for  $V_{RE}$ , we can find the value of  $R_{E1}$  and  $R_{E2}$  in series, and, with a value for  $R_{E1}$ , we can determine  $R_{E2}$ . We have the value for  $V_{RE}$ , with the knowledge that when the rail voltage is above 5V,  $V_{CE}$  and  $V_{RE}$  are about equal.

$$V_{RE} = \frac{I_B + I_C}{R_E} \Rightarrow R_{E2} = \frac{I_B + I_C}{V_{RE}} - R_{E1} = 1.82k\Omega$$

Setting  $Z_{in} = 6k\Omega$ , which is greater than  $5k\Omega$ , the restriction, one can finally determine values for  $R_1$  and  $R_2$ . The following equations are solved for  $R_{TH}$  then for  $R_1$  and  $R_2$ .

$$V_{TH} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$V_{TH} = R_{TH}I_B + V_{BE} + R_E I_B(1 + \beta)$$

$$\text{If } Z_{in} = 6k\Omega, \quad R_1 = 25.7k\Omega, \text{ and } R_2 = 12.4k\Omega$$

**RESULTS:** The following results were acquired from this section:

$$R_{E1} = 120\Omega$$

$$R_{E2} = 1.82k\Omega$$

If  $Z_{in} = 6k\Omega$ ,  $R_1 = 25.7k\Omega$ , and  $R_2 = 12.4k\Omega$

These values will be close to those used in the practical circuit and the PSpice model. Not all of these resistor values are available, however, and will have to be substituted.

### TASK 5:

**ANALYSIS:** In task 4, the transistor output resistance was neglected. Task 5 asks for justification for this decision. One can determine the impact of  $r_o$  by finding its value with an estimated early voltage, then comparing that value to  $R_C$ .

**DATA AND CALCULATION:** Assuming the early voltage was fairly reasonable, say 80V, one can calculate  $r_o$  to determine its impact on the circuit.

$$r_o = \frac{V_A}{I_C} = \frac{80V}{1.28mA} = \sim 80k\Omega$$

If  $r_o$  was put in parallel with  $R_C$  the way it would be in the circuit, we see immediately that it would only affect about a 5% change to the value of  $R_C$ .

**RESULTS:** Obviously, this justifies the removal of  $r_o$ ; it's inclusion would only change the results by about +5%.

### TASK 6:

**ANALYSIS:** Given that the frequency is the inverse of the product of the resistance, capacitance, and a scaling factor ( $2\pi$ ), we can calculate the capacitance based on the corner frequency of 100Hz. However, since it is desirable to have smaller capacitance values for  $C_O$  and  $C_I$ , we should evaluate these for 10Hz.

**DATA AND CALCULATION:** The following equations show the capacitance calculations.


$$f = \frac{1}{2\pi RC}$$

$$100Hz = \frac{1}{2\pi R_{E1} C_E} \Rightarrow C_E = 13\mu F$$

$$10Hz = \frac{1}{2\pi R_L C_O} \Rightarrow C_O = 4\mu F$$

$$10\text{Hz} = \frac{1}{2\pi Z_{in} C_I} \Rightarrow C_I = 2.7\mu\text{F}$$

**RESULTS:** From what we can see above,  $C_O$  and  $C_I$  were smaller than  $C_E$ , and all of them were reasonable values. This was enough to work with until the values are simulated. Upon simulation, the values were adjusted to reflect standard values available for the practical circuit. On the next page are the bode plot, and the plot of the phase angle. Both demonstrate the requirements of the design. Notice, specifically, the value of the corner frequency; it is just about 100Hz, which was the target corner

 

frequency.

On top if the phase angle vs. frequency, and on the bottom is the voltage vs. frequency, which shows the corner frequency at about 100Hz.


It is also important to note the operating point acquired for the .out file of the PSpice simulation. By inspection, one can see that the values calculated and the PSpice values were quite close.

## TASK 7:

**ANALYSIS:** By building slowly and carefully, we were able to simulate the circuit on the Protoboard. The following values were used in place of the calculated values, since not all of them were available.


Name	Calculated Value	Practical Value
$R_1$	27.5k $\Omega$	27k $\Omega$
$R_2$	12.4k $\Omega$	12k $\Omega$
$R_{E1}$	120 $\Omega$	120 $\Omega$
$R_{E2}$	1.82k $\Omega$	1.8k $\Omega$
$R_C$	3.9k $\Omega$	3.9k $\Omega$
$R_L$	10k $\Omega$	10k $\Omega$
$C_E$	13 $\mu$ F	15 $\mu$ F
$C_O$	4 $\mu$ F	4.7 $\mu$ F
$C_1$	2.7 $\mu$ F	2.2 $\mu$ F

**RESULTS:** Using the oscilloscope and function generator, we were able to verify the gain at, above and below 100Hz. The gain was -20 above 100Hz, slightly less at 100Hz, and about 10 at 50Hz. This verified the lower corner frequency was indeed at 100Hz. Below is a scope screen capture, as the gain was about -20 above 100Hz.

 

TDS 2012B - 3:15:38 PM 2/9/2010

This image confirms that at frequencies above 100Hz, the gain is -20. Also, this screen capture was taken at a mid-band frequency between 1kHz and 10kHz, namely 5kHz. The gain here is measured at -20, and the input resistance measured 6.48k $\Omega$ .

 

TDS 2012B - 3:18:57 PM 2/9/2010

This screen capture demonstrates the gain degeneration at frequencies below 100Hz. At the frequency of 50Hz, there this was captured, the gain is about -10. The phase angle isn't correct, and the gain is half of what it should be.

### TASK 8:


**ANALYSIS:** Normally, our system would be linear and time-invariant; however, since a non-linear device is in use, there is some small distortion. Total harmonic distortion is the measure of that distortion in the system. In order to calculate the harmonic distortion of the system, the FFT view of the oscilloscope must be used. More details can be found in the results section.

**DATA AND CALCULATION:** There is a great deal of calculation which goes into the harmonic distortion, and it involves the FFT graph in the results section. The method for calculation is as follows: Take the square root of the sum of the squares of harmonic component voltages. This is because power is proportional to the square of the voltage, and normally the distortion would be calculated with power.

$$TDH = \%2.833, \pm 1V$$

$$TDH = \%1.467, \pm 2V$$

**RESULTS:** The following shows the FFT plot for the system, which is used in the calculation of THD.

 

TDS 2012B - 4:10:36 PM 2/9/2010



As you can see from the calculations above and the FFT, the distortion of the output is minimal. There are very clear harmonics, but they do not cause high distortion.

## TASK 9:

**ANALYSIS:** The non-linearity of the system can be expressed as a Taylor Series.

**RESULTS:** With knowledge of the Taylor Series overall, it is simple to express the AC current  $i_c$  as a Taylor polynomial. Firstly, the system must be expressed as a Taylor polynomial, then it must be related to  $i_c$ .

$$e^{\frac{V_{be}}{V_T}} = \sum_{n=0}^{\infty} \frac{1}{n!} \left( \frac{V_{be}}{V_T} \right)^n, \quad i_c = I_C e^{\frac{V_{be}}{V_T}}$$

$$\therefore i_c = \frac{\sum_{n=0}^{\infty} \frac{1}{n!} \left( \frac{V_{be}}{V_T} \right)^n}{I_C}$$

$$\text{OR } i_c = \frac{1 + \frac{V_{be}}{V_T} + \frac{1}{2} \left( \frac{V_{be}}{V_T} \right)^2 + \frac{1}{6} \left( \frac{V_{be}}{V_T} \right)^3 + \frac{1}{24} \left( \frac{V_{be}}{V_T} \right)^4 + \dots}{I_C}$$

Thus, the nonlinearity of the voltage gain could be expressed.

## CONCLUSION:

In sum, this lab looked at many aspects of amplifier design, and guided us through the process, from choosing the bias current all the way to building the circuit. It is important to remember the specifications of the design when building the circuit, as reflected in the numerous expressions and definitions. Ultimately, however, having considered the restrictions, there is still a great number of possible configurations. There is no unique answer when designing the amplifier circuits. Interestingly, this circuit was, looking back, relatively easy to design. The restrictions were relatively non-conflicting, making it easy to choose values. Also, the chosen values were close to standard values, so even the simulations were accurate. Moreover, designs with more transistors may multiply in complexity, so it is important to take away the basics for design from this lab before moving on.