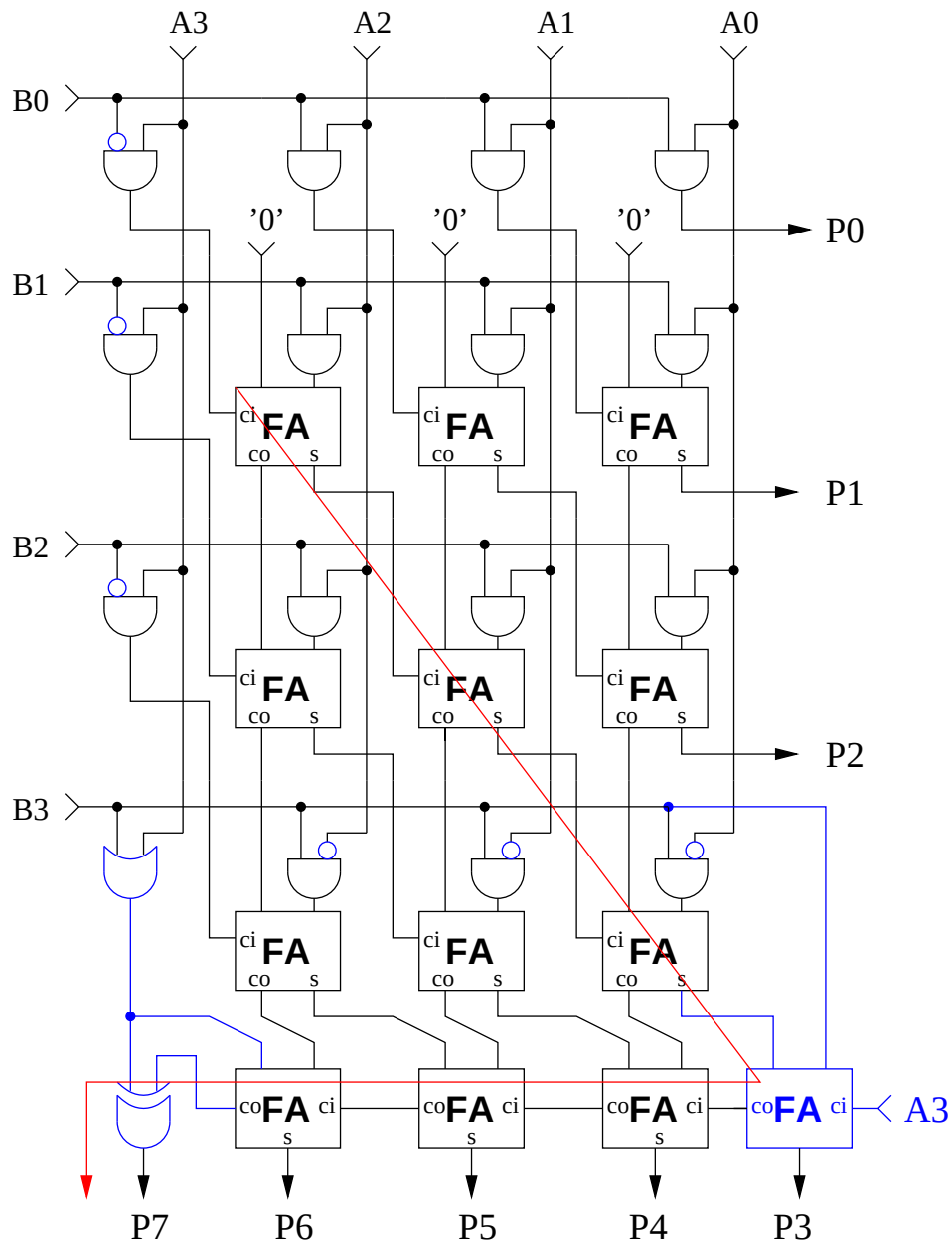


2's Complement Array Multiplier

(Baugh–Wooley Multiplier)

4x4-Bit Binary Multiplication



Worst Case Propagation Delay: $T_{pd} = (2N-1) \cdot t_{pd}(FA)$