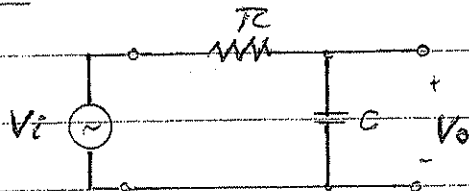


VII Switched-Capacitor Networks

1. Introduction


A) Problems in continuous time filters

Example 1st order LP



$$\frac{V_o}{V_i} = \frac{1}{(1 + sRC)} = \frac{1}{(1 + s/\omega_p)}$$

$$\omega_p = \frac{1}{RC}$$

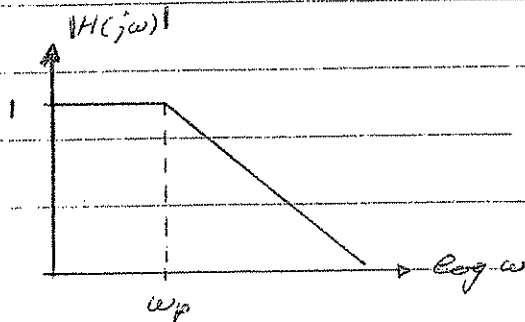


e.g. $\omega_p = 2\pi \cdot 10 \text{ kHz}$
 $C = 1 \text{ pF}$
 $\Rightarrow \underline{\underline{R = 16 \text{ M}\Omega}}$


Problems: - R too big
 - Absolute control of R and C required

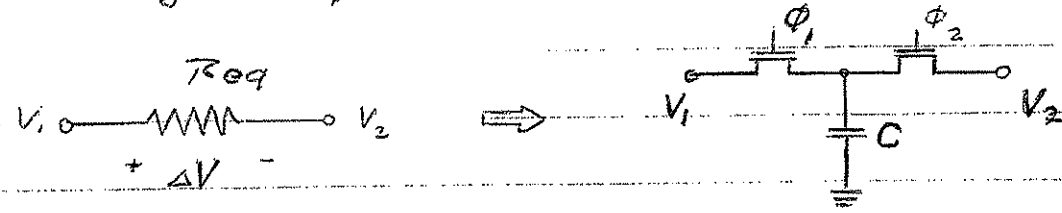B) Solution

Replace resistors by periodically charged and discharged capacitors



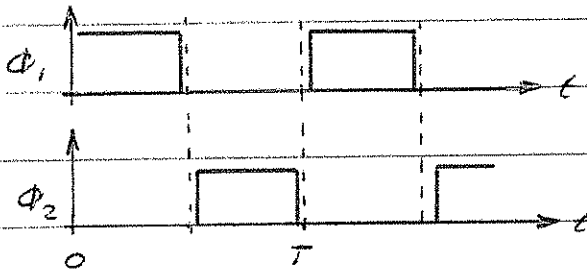Φ_1, Φ_2 Nonoverlapping 2-phase Clock signal



Resistor - Capacitor Relationship: (ideal switches)

ΔQ : Transferred Charge per Cycle

$$\Delta Q = C(V_1 - V_2) \quad \left| \quad \frac{1}{T} \right.$$

$$\underline{\frac{\Delta Q}{T} = \bar{I} = \frac{C}{T} \Delta V} \quad \text{where } \Delta V = V_1 - V_2$$

Compare with Ohm's Law:



$$\underline{\bar{I} = \frac{1}{R} \Delta V}$$

$$\Rightarrow \boxed{R_{eq} = \frac{T}{C} = \frac{1}{C \cdot f_0}}$$


Note: The average current $\bar{I}$ is not a quantity that can physically be measured; it is the equivalent current that transfers the charge ΔQ in time T from node 1 to node 2 with $V_1 - V_2 = \Delta V$.

if we assume ideal switches ($\tau_{on} = 0$), the charge transfer is realized by a train of delta functions.

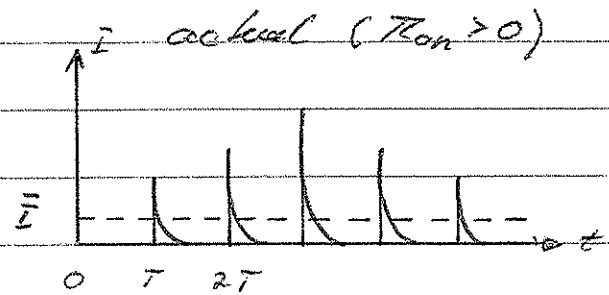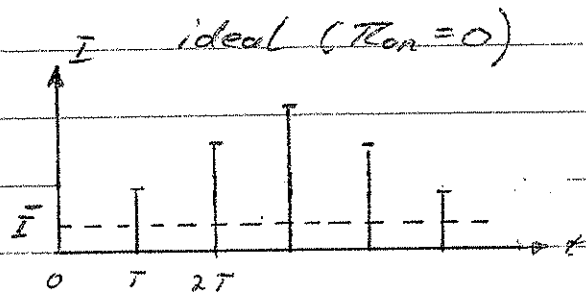if τ_{on} is included in the analysis, the charge transfer is realized by a train of exponentially damped functions.



Example: 1st order LP

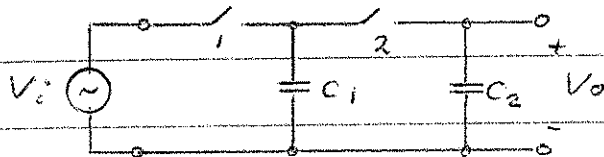

$$H'(s) = \frac{1}{(1 + s\tau_{eq}C_2)} = \frac{1}{(1 + s \cdot T \frac{C_2}{C_1})} \hat{=} \frac{1}{(1 + s/\omega_p')}$$

$$\omega_p' = \frac{1}{T} \frac{C_1}{C_2} = f_c \frac{C_1}{C_2}$$

e.g. $\omega_p' = 2\pi \cdot 10 \text{ kHz}$

$C_2 = 1 \text{ pF}$

$f_c = 200 \text{ kHz}$

$$\Rightarrow C_1 = C_2 \frac{\omega_p'}{f_c} = C_2 \cdot \frac{2\pi}{20} = 0.314 \text{ pF}$$

Advantages


- Requires control of ratios of C only
- Small area (small C -spread)
- Frequency scaling is possible with clock

Disadvantages


- Requires continuous time anti-aliasing filter
- Requires "quartz-stable" nonoverlapping 2-phase clock

2. CMOS Implementation

A) Switches: composite CMOS switch

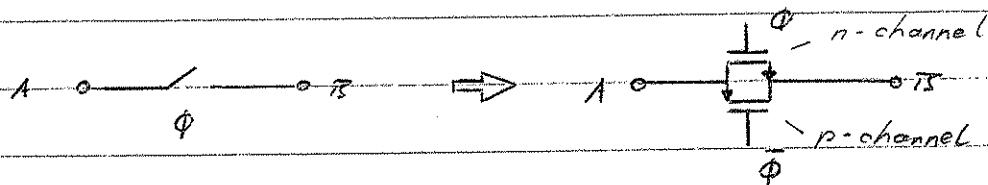

$R_{on} [k\Omega]$

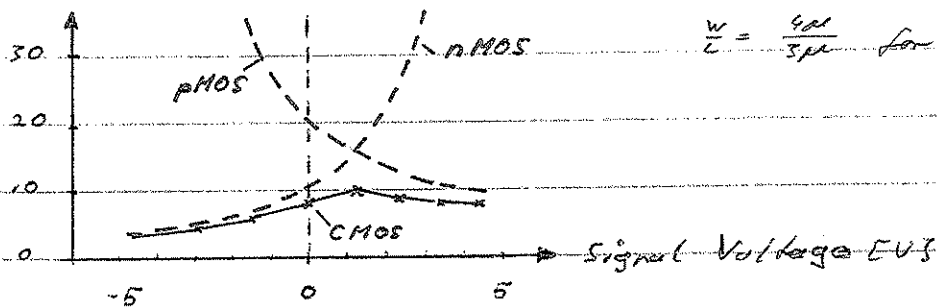



$\frac{W}{L} = \frac{4\mu}{3\mu}$ for p and n-channel

Advantages

- MOSFETs exhibit no DC offset
- extremely small leakage currents in off-state
- R_{on} variations acceptable over full signal swing
- 1st order elimination of clock-feedthrough

13) Nonoverlapping 2-phase clock

Example with NOR Gates

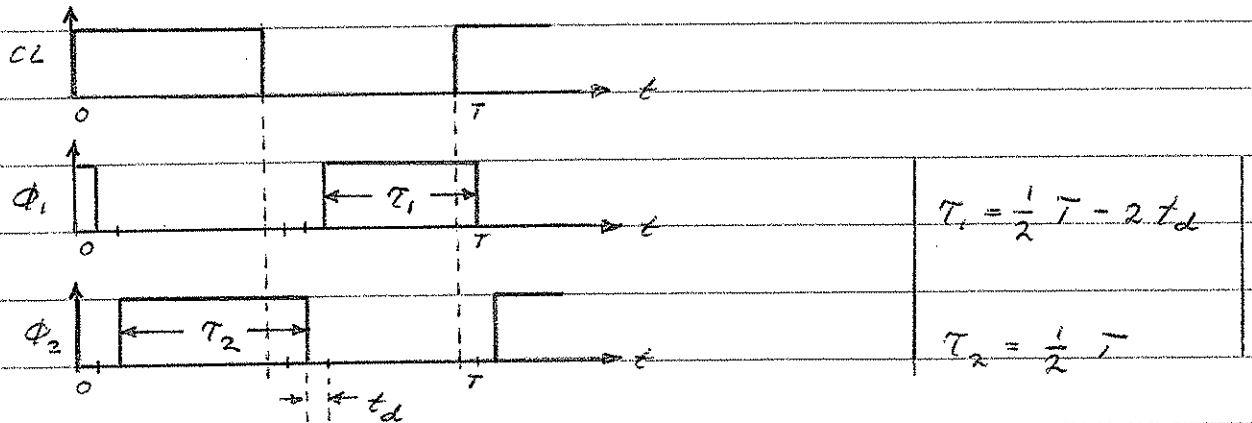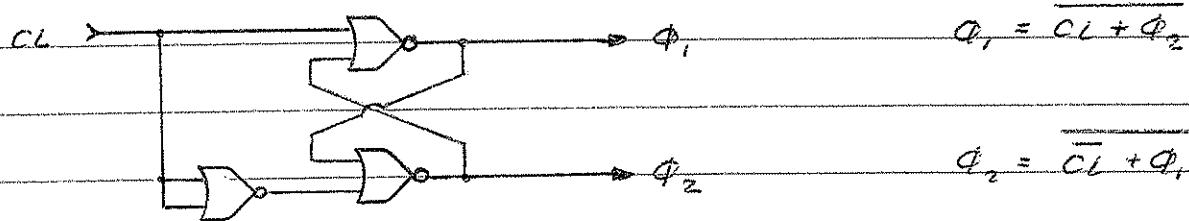

t_d : Gate delay of NOR


Notes if the delay of a single gate is too small, the above scheme can be modified to yield a longer nonoverlapping time by including an even number of inverters in the crossed-over feedbacks.

$t_{\text{nonoverlap}} = (1+N)t_d$	$N \text{ even } \{0, 2, 4, \dots\}$
$\tau_1 = \frac{1}{2}T - (2+N)t_d$	
$\tau_2 = \frac{1}{2}T - Nt_d$	

To reduce the clock-feedthrough effect, it is also important to realize symmetrical edges for Φ_1 and Φ_2

c) Capacitors

Undercut insensitive structure

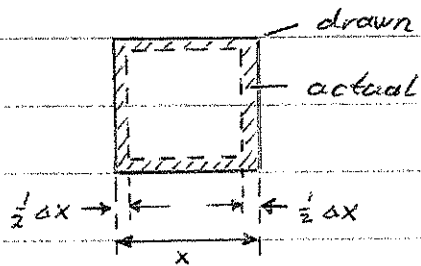


Uniform undercut ($0.2 - 0.5 \mu$)


$$C_{ac} = C_{ox} (x - \Delta x)^2$$

Ex: Realize 2 Cap. with ratio 4

a) Minimum Area

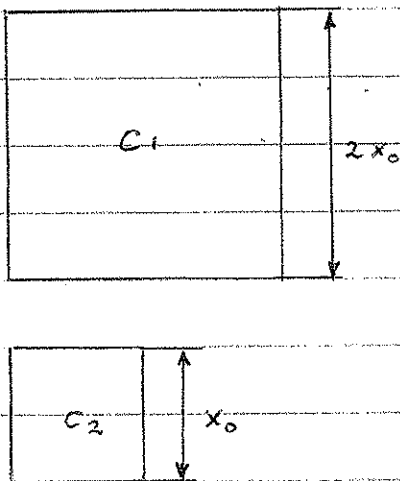

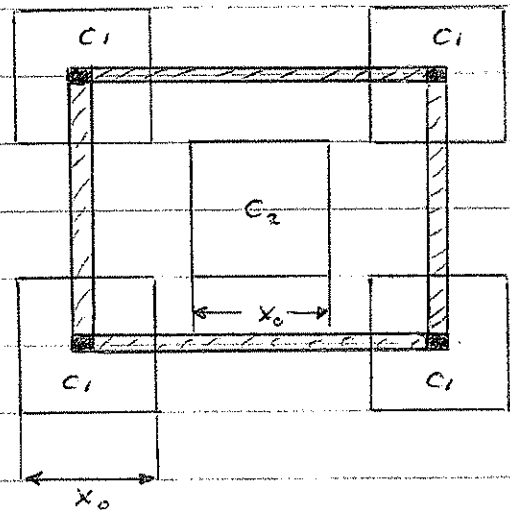b) Undercut insensitive
+ Gradient insensitive



$$\frac{C_1}{C_2} = \frac{(2x_0 - \Delta x)^2}{(x_0 - \Delta x)^2} = 4 \frac{(1 - \frac{\Delta x}{x_0} + \frac{1}{4} \frac{\Delta x^2}{x_0^2})}{(1 - 2 \frac{\Delta x}{x_0} + \frac{\Delta x^2}{x_0^2})}$$

$$\frac{C_1}{C_2} = 4 \frac{(x_0 - \Delta x)^2}{(x_0 - \Delta x)^2} = 4$$

$$\approx 4 (1 - \frac{\Delta x}{x_0}) (1 + 2 \frac{\Delta x}{x_0}) \approx 4 (1 + \frac{\Delta x}{x_0})$$



In general:

$$\Rightarrow \underline{\underline{C_1 \approx \frac{\Delta x}{x_0} \cdot 2 [1 - \sqrt{\frac{C_2}{C_1}}]}} \quad C_2 \leq C_1 \quad C_1 \geq C_2 \Rightarrow C_k = 0$$

VII-7

capacitors with fractional ratios
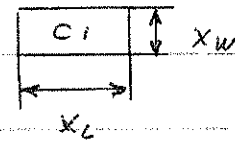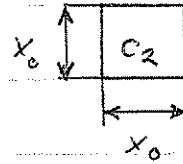
$$\frac{C_1}{C_2} = \pi \quad 1 \leq \pi < 2$$



$$C_1 = C_{ox} (x_W - ax)(x_L - ax)$$

$$C_2 = C_{ox} (x_0 - ax)^2$$

$$\pi = \frac{C_1}{C_2} = \frac{(x_W - ax)(x_L - ax)}{(x_0 - ax)^2}$$

Def:

$w = \frac{x_W}{x_0}$	normalized width of C_1
$L = \frac{x_L}{x_0}$	normalized length of C_1
$e_u = \frac{ax}{x_0}$	undercut error of C_2

Thus:

$$\pi = \frac{(w - e_u)(L - e_u)}{(1 - e_u)^2} \quad (1)$$

condition for zero undercut error: undercut area C_1

$$\pi(4x_0 \frac{1}{2} ax - 4 \frac{1}{4} ax^2) = (x_W \frac{1}{2} ax + x_L \frac{1}{2} ax)2 - 4 \frac{1}{4} ax^2 \quad \left| \frac{1}{x_0^2} \right.$$

$$\pi(2e_u - e_u^2) = (w e_u + L e_u) - e_u^2$$

$$\pi(2 - e_u) + e_u = w + L \quad (2)$$

Solve for w and L in (1) + (2)

more precise:

Solution:

$$\left\{ \begin{array}{l} w \cong \pi \left(1 - \sqrt{1 - \frac{1}{\pi}} \right) \\ L \cong \pi \left(1 + \sqrt{1 - \frac{1}{\pi}} \right) \end{array} \right\} \quad \left\{ \begin{array}{l} w = \pi(1 - e_u) \left(1 + \frac{e_u}{\pi} - \sqrt{1 - \frac{1}{\pi}} \right) \\ L = \pi(1 - e_u) \left(1 + \frac{e_u}{\pi} + \sqrt{1 - \frac{1}{\pi}} \right) \end{array} \right.$$

e.g. $\pi = 1.5$

$$\left\{ \begin{array}{l} w_{1.5} \cong 0.634 \\ L_{1.5} \cong 2.366 \end{array} \right.$$

$$x_0 = 25 \mu m$$

$$\Rightarrow \left\{ \begin{array}{l} x_W = 15.85 \mu m \\ x_L = 59.15 \mu m \end{array} \right.$$

5. SC Filter Design

A) The z-Transform

Def

$$X(z) = \mathcal{Z}[x(t)] = \mathcal{Z}[x(n)] = \sum_{n=-\infty}^{\infty} x(n) z^{-n}$$

Note: Very often $x(t) = 0$ for $t < 0$

Then

$$X(z) = \sum_{n=0}^{\infty} x(n) z^{-n}$$

one-sided z-Transf.

Recall: Laplace transf of a discrete function

$$X(s) = \mathcal{L}[x(t)] = \mathcal{L}[x(n)] = \sum_{n=-\infty}^{\infty} x(n) e^{-snT}$$

Relationship between s- and z-domain:

$$z = e^{sT}$$

Inverse function:

$$s = \frac{1}{T} \ln[z]$$


nonlinear functn

i.e. polynomial in s does not transform into polynomial in z

Mapping between s- and z-domain

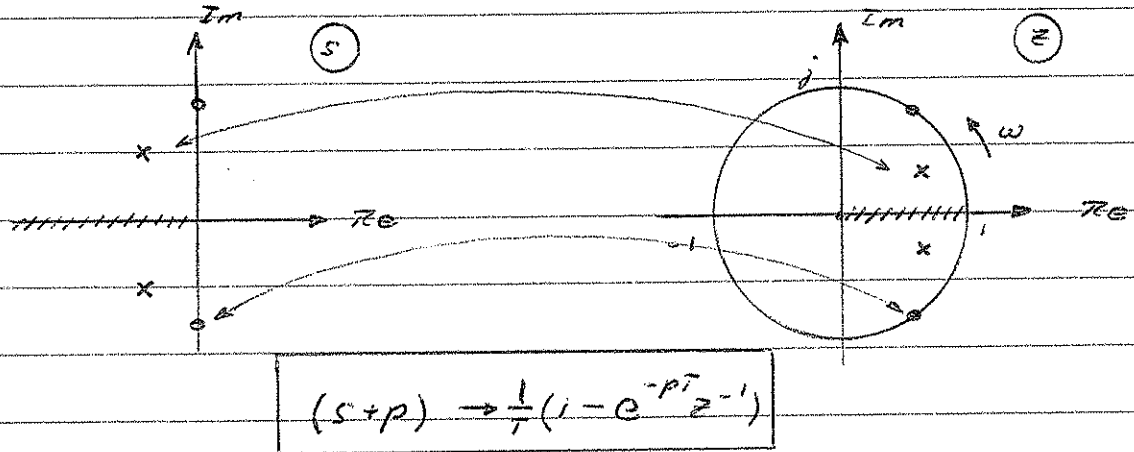a) Matched z-transform (MzT)

Poles and zeros in s are exactly mapped into poles and zeros in z.



b) Bilinear z-transform (BLT)

The nonlinear function $s = \frac{1}{T} \ln[z]$ is approximated by a bilinear function:

Recall: $\ln x = 2 \left[\left(\frac{x-1}{x+1} \right) + \frac{1}{3} \left(\frac{x-1}{x+1} \right)^3 + \dots \right]$ $x > 0$

$$s \rightarrow \frac{2}{T} \frac{(1 - z^{-1})}{(1 + z^{-1})}$$

Frequency warping:

$$s = j\omega \rightarrow j \frac{2}{T} \tan \left[\frac{T}{2} \omega' \right]$$

c) Lossless discrete int. z-transform (LDI)

The nonlinear function $s = \frac{1}{T} \ln[z]$ is approximated by a linear function


Recall: $\ln x = \left(\frac{x-1}{x} \right) + \frac{1}{2} \left(\frac{x-1}{x} \right)^2 + \dots$ $x \gg \frac{1}{2}$

$$s \rightarrow \frac{1}{T} \frac{(1 - z^{-1})}{z^{-1/2}}$$






Frequency warping:

$$s = j\omega \rightarrow j \frac{2}{T} \sin \left[\frac{T}{2} \omega' \right]$$

Mapping of the Frequency Axis

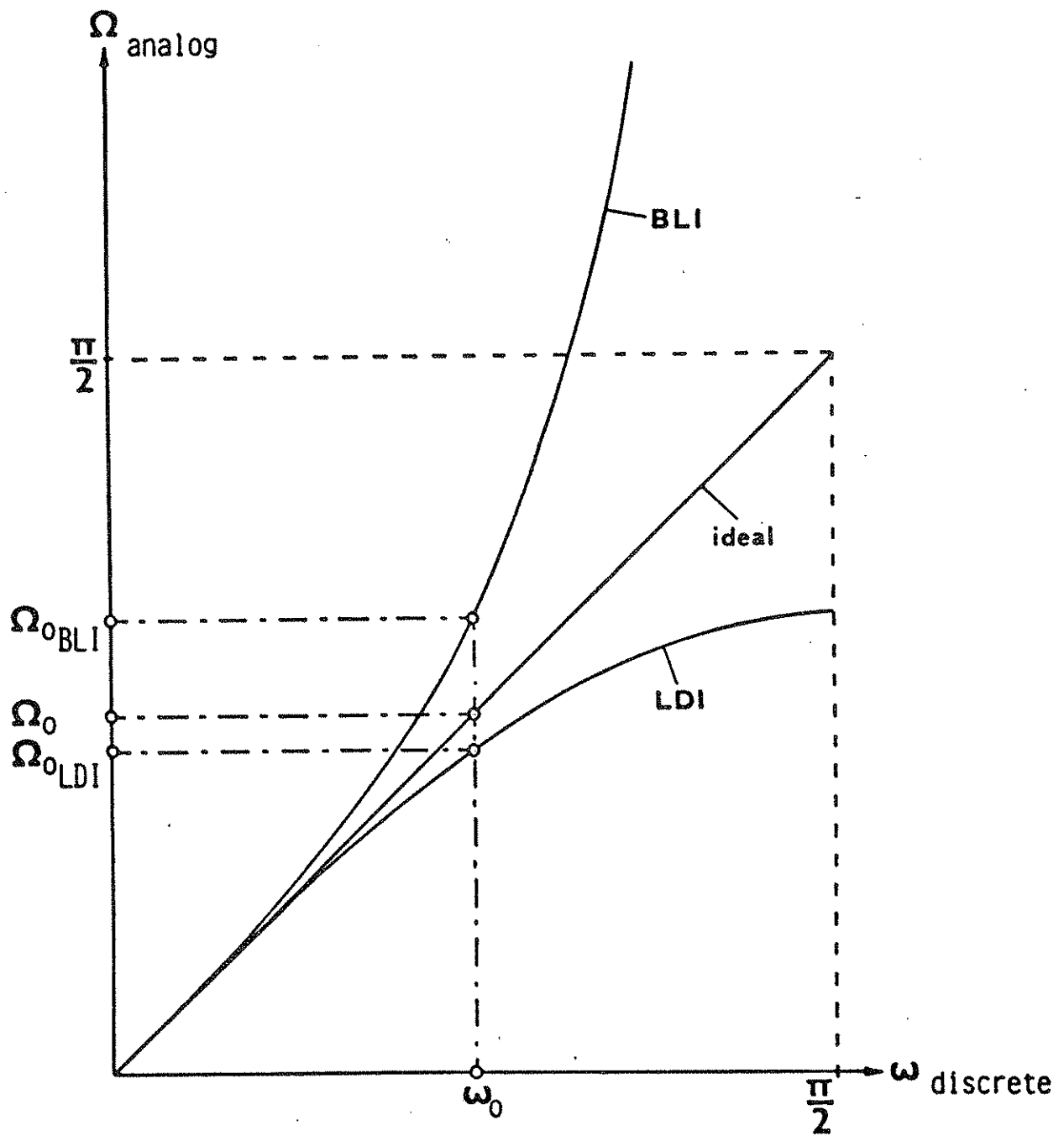

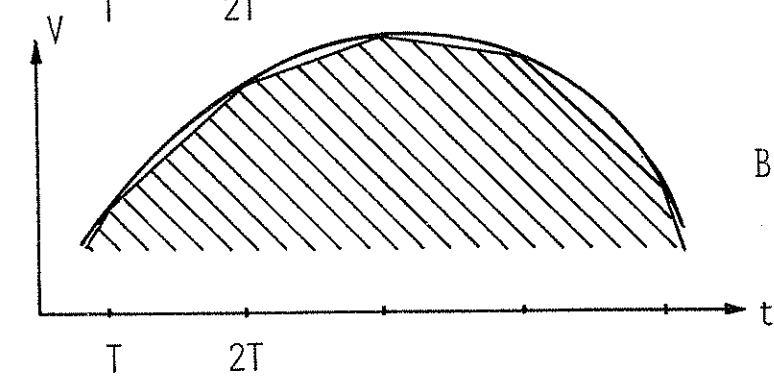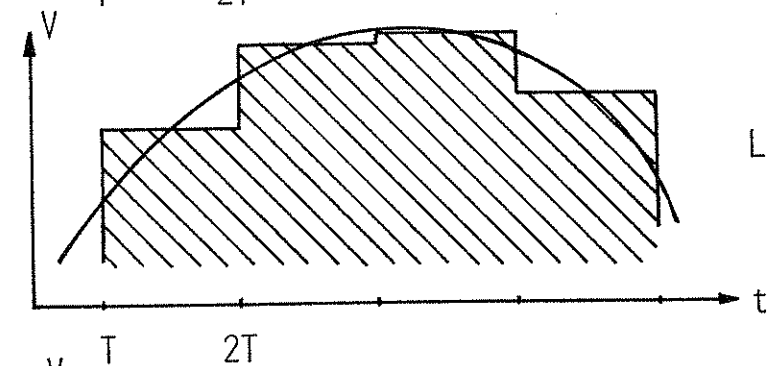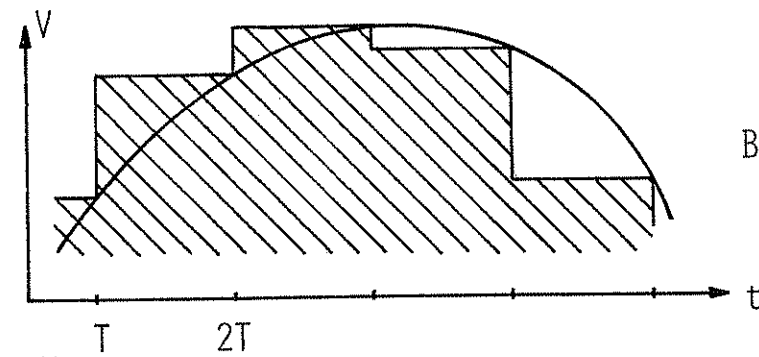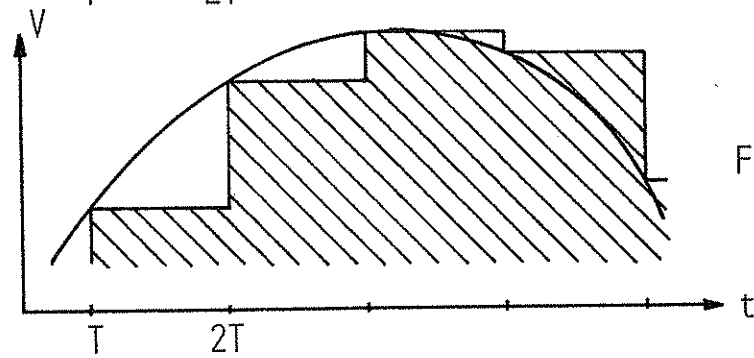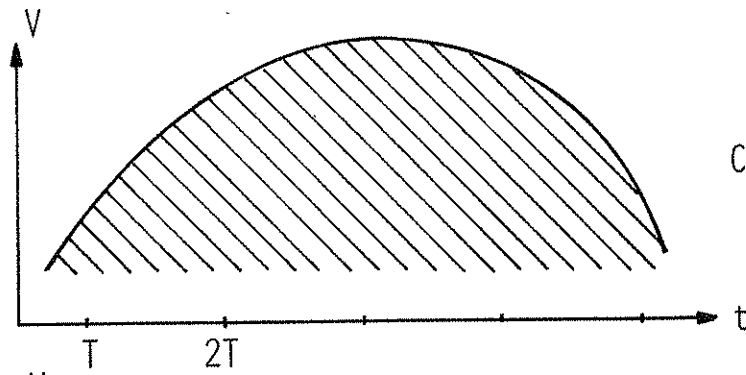
$$\omega_{LDI} = \left[\frac{T}{2} \right]^{-1} \sin \omega \frac{T}{2}$$




13) The time-discrete Integrator

continuous-time

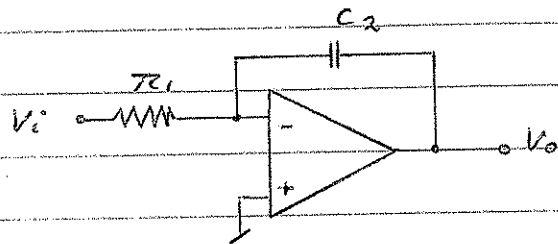

discrete-time

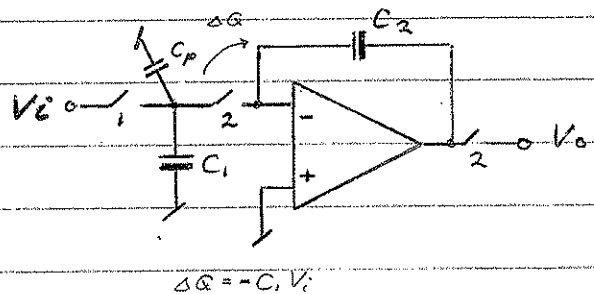

$$\frac{d}{dt} V_o(t) = -\frac{1}{R_1 C_2} V_i(t)$$

$$V_o(t) = -\frac{1}{R_1 C_2} \int V_i(t) dt$$



$$V_o(s) = -\frac{1}{R_1 C_2} \frac{1}{s} V_i(s)$$

$$V_o(n) - V_o(n-1) = -\frac{C_1}{C_2} V_i(n - \frac{1}{2})$$

$$\sum_n [V_o(n) - V_o(n-1)] = -\frac{C_1}{C_2} \sum_n V_i(n - \frac{1}{2})$$



$$V_o(z) = -\frac{C_1}{C_2} \frac{z^{-1/2}}{(1-z^{-1})} V_i(z)$$

Realized $s \leftrightarrow z$ domain mapping

$$s \rightarrow \frac{1}{T} \frac{(1-z^{-1})}{z^{-1/2}}$$

LTI z -transform


Integrator constant

$$\frac{1}{R_1 C_2} \rightarrow \frac{1}{T} \frac{C_1}{C_2}$$


$$\omega_I \rightarrow f_c \frac{C_1}{C_2}$$

The parasitic insensitive integrator

inverting

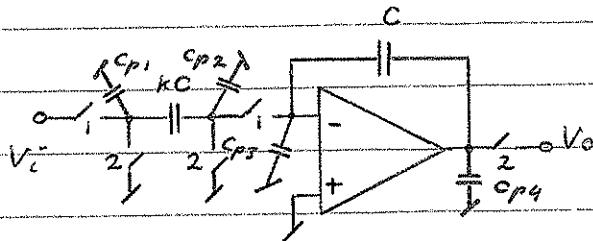

noninverting

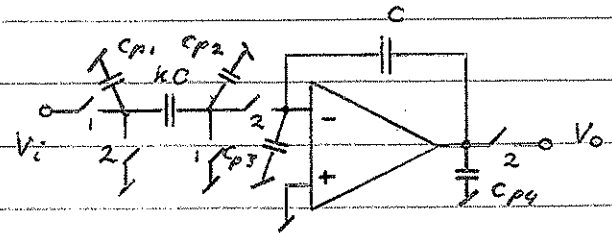

we assume amplifier gain $A_o \gg 1$

influence of the different parasitics:

C_{p1} : does not contribute to charge balance at ampl. input node

C_{p2} : switched between ground and virtual ground
 $\Rightarrow$ does not accumulate charge

C_{p3} : connected to virtual ground (amp. neg. input)
 $\Rightarrow$ does not accumulate charge

C_{p4} : charged by ampl. to V_o but does not contribute to charge balance at amp. input

$$\Rightarrow \underline{H^-(z) = -K \frac{z^{-1/2}}{(1-z^{-1})}}$$







$$\underline{H^+(z) = K \frac{z^{-1/2}}{(1-z^{-1})}}$$


Rule to obtain parasitic insensitive circuits:

All effective capacitors in a SC network must be connected to nodes which are

grounded or virtually grounded (amplifier input)


or connected to a voltage source (amplifier output)

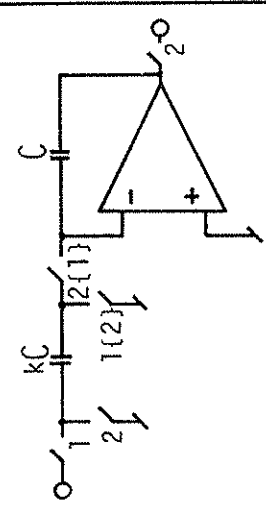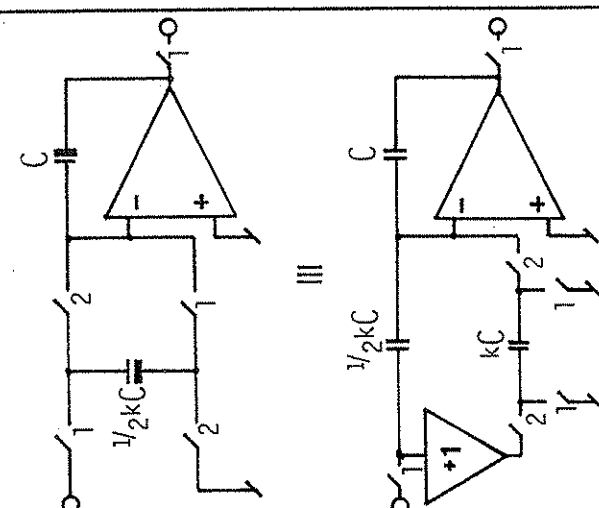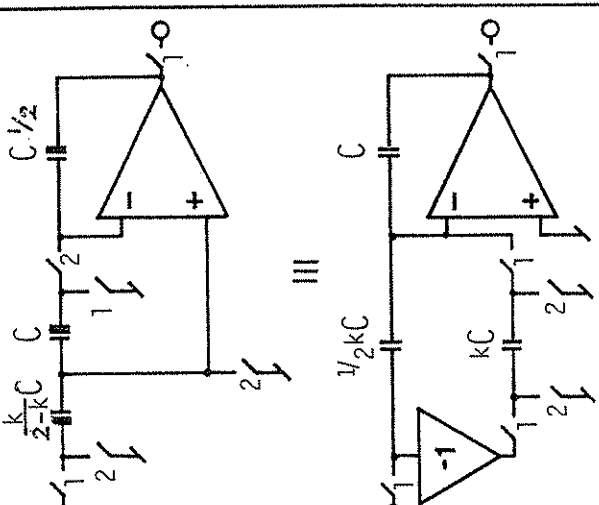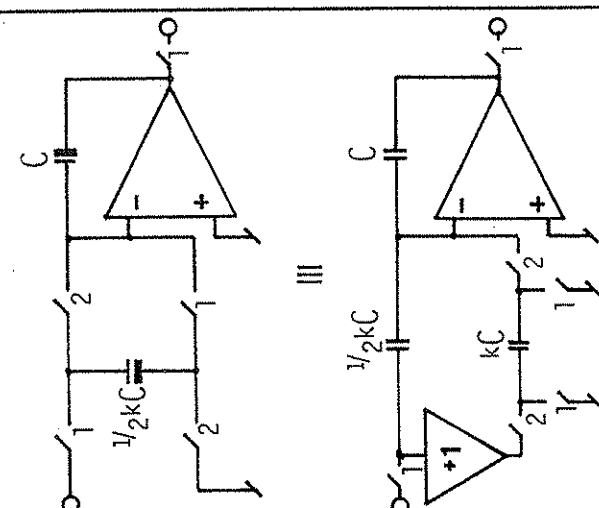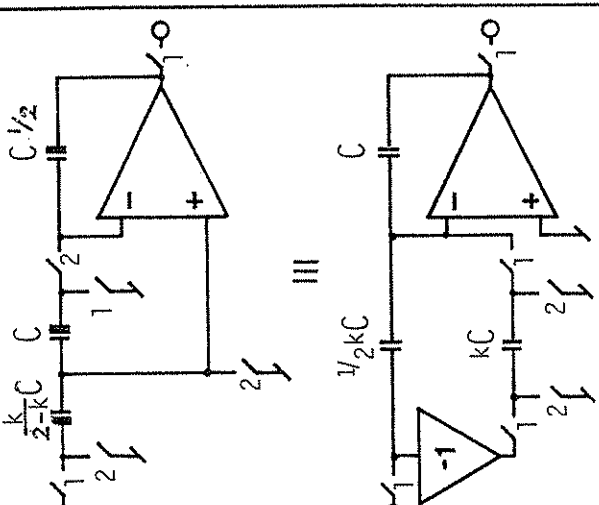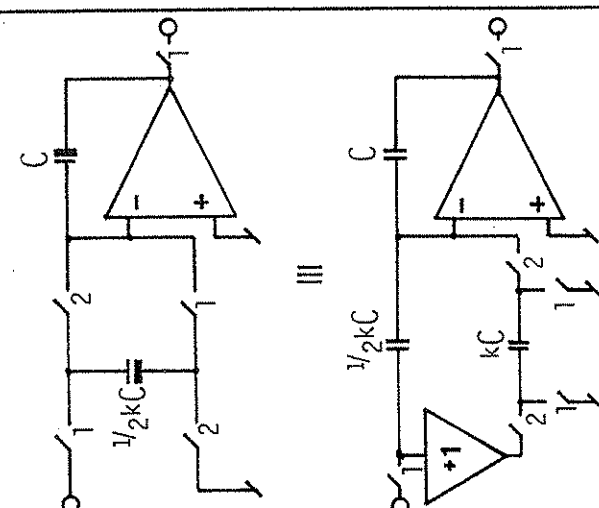LOSSLESS DISCRETE INTEGRATOR	BI-LINEAR INTEGRATOR	
		$H(z) = +k \frac{z^{-1/2}}{1-z^{-1}}$
		$H(z) = -k \frac{1}{2} \frac{1+z^{-1}}{1-z^{-1}}$
		$H(z) = +k \frac{1}{2} \frac{1+z^{-1}}{1-z^{-1}}$

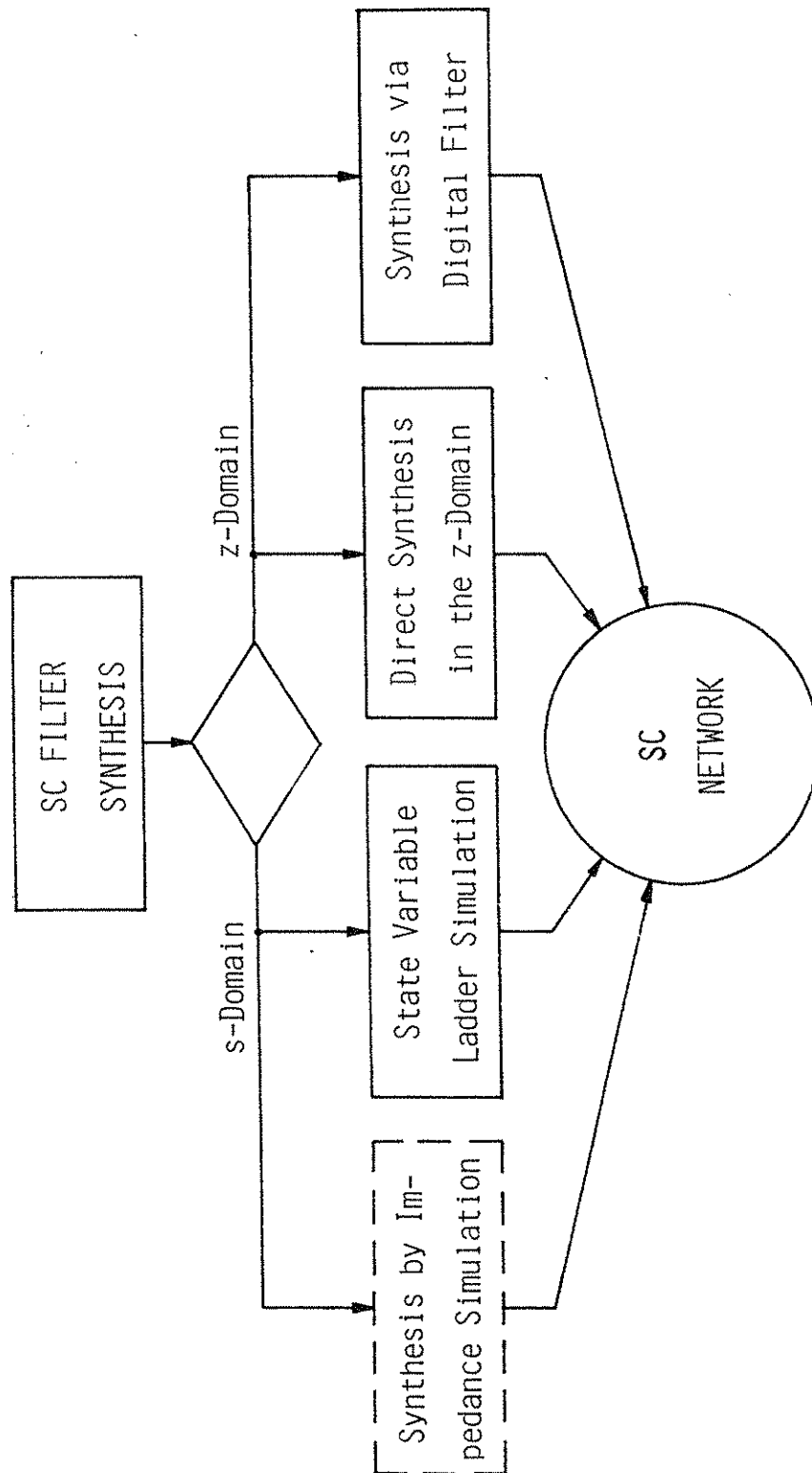


1. Synthesis by Impedance Simulation

1.1 Resistance

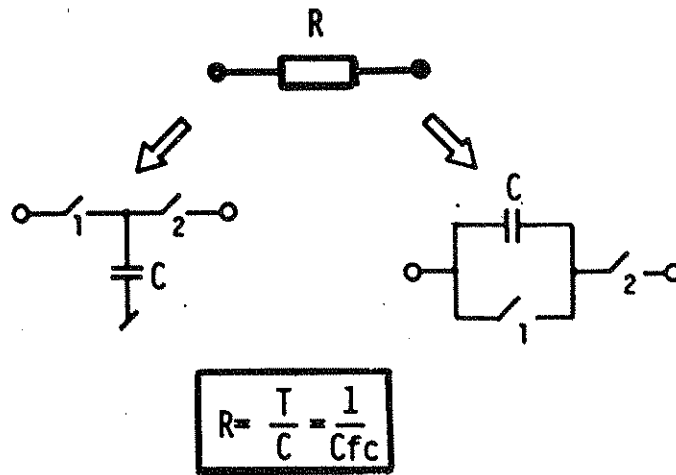

1.2 Inductance

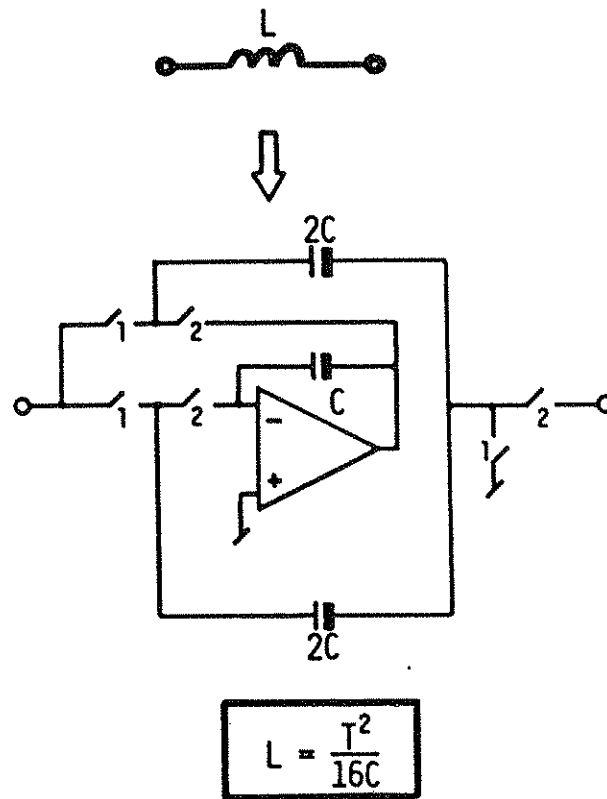

Synthesis by Impedance Simulation

Advantages:

- simple Synthesis Procedure
- requires few active Elements (Amplifiers)

Disadvantages:

- SC Circuits are adversely affected by Stray-Capacitances (top- and bottom-plate Parasitics).
- requires always a Predistortion Procedure (even for very high rates of Sampling- to Signal Frequency).
- may yield unstable SC Circuits.

2. Synthesis of SC Ladder Filters

General Procedure

- i) Start with general doubly terminated LC-R ladder filter.
- ii) Reduce given network to minimum reactance structure (by introducing controlled voltage-sources).
- iii) Realize remaining reactive elements by SC integrators and controlled sources by SC summers.
- iv) Calculate capacitor ratios according to the relationship between time continuous integrator and chosen SC realization.

Simulation of LC- π Ladder Filters

Example 3rd order Lowpass Filter


cut-off frequency: $f_c = 1 \text{ kHz}$

sampling rate: $f_s = 16 \text{ kHz}$

1. Prewarping of cut-off frequency for LDI z-transform

$$f_c' = \frac{f_s}{\pi} \sin \left[\pi \frac{f_c}{f_s} \right] = 0.994 \text{ kHz}$$

2. LC- π Prototype Filter

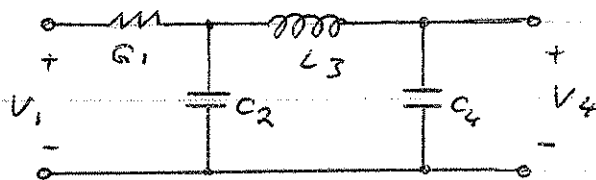


$$G_1 = 1 \Omega$$

$$C_2 = 1.621 \times 10^{-4} \text{ F}$$

$$L_3 = 2.136 \times 10^{-4} \text{ H}$$

$$C_4 = 2.417 \times 10^{-4} \text{ F}$$

3. SFG in s-domain

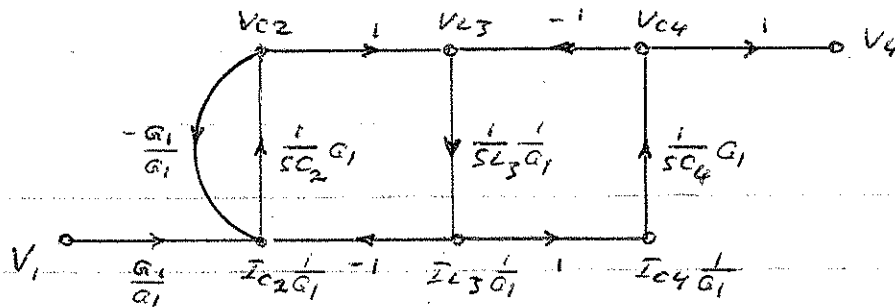

NW equations:

$$V_{c2} = I_{c2} \frac{1}{sC_2}$$

$$I_{c2} = (V_1 - V_{c2}) G_1 - I_{L3}$$

$$I_{L3} = V_{L3} \frac{1}{sL_3}$$

$$V_{L3} = V_{c2} - V_{c4}$$


$$V_{c4} = I_{c4} \frac{1}{sC_4}$$

$$I_{c4} = I_{L3}$$

$$V_4 = V_{c4}$$

Impedance scaling by G_1


4. SFG in z-domain

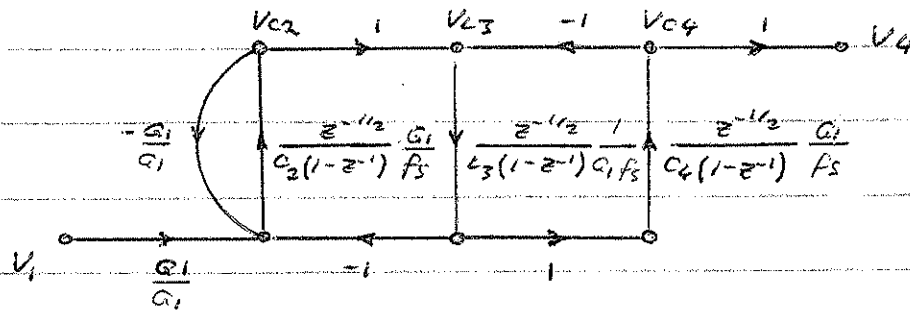

Frequency scaling by f_s

5. Implementation of discrete-time integrator

(LTI equivalent)

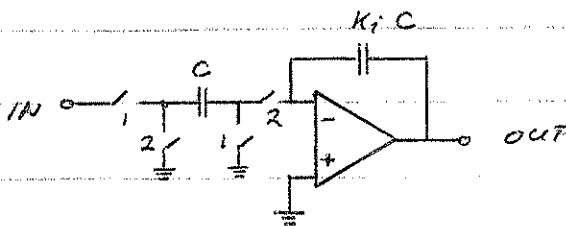

equivalent integrator constant:

$$K_i = \begin{cases} \frac{f_s}{G_1} C_i & i \text{ even} \\ f_s G_1 L_i & i \text{ odd} \end{cases}$$

6. equivalent element values:

passive

active SC

$$\begin{aligned} G_1 &= 1 \Omega^{-1} \\ C_2 &= 1.621 \times 10^{-4} \text{ F} \\ L_3 &= 2.156 \times 10^{-4} \text{ F} \\ C_4 &= 2.417 \times 10^{-4} \text{ F} \end{aligned}$$

$$\begin{aligned} G_{1n} &= G_1 / Q_1 = 1 \\ K_2 &= \frac{f_s}{G_1} C_2 = 2.593 \\ K_3 &= f_s G_1 L_3 = 3.417 \\ K_4 &= \frac{f_s}{G_1} C_4 = 3.867 \end{aligned}$$

7. Implementation of resistive Termination (G_1)

Problem: Input loop in z -domain SFG comprising G_1 and C_2 is not realizable as LDI equivalent circuit, since each loop delay must be an integer multiple of the sampling period.

Solution ①: Multiply G_1 by $z^{+1/2}$

$$G_1 \rightarrow G_1 z^{+1/2} = G_1 (\cos \omega T/2 + j \sin \omega T/2)$$

Solution ②: Multiply G_1 by $z^{-1/2}$

$$G_1 \rightarrow G_1 z^{-1/2} = G_1 (\cos \omega T/2 - j \sin \omega T/2)$$


Note: In both cases the passive real termination G_1 becomes complex.

Solution ③: Combine solution ① and ② to eliminate a complex termination by multiplying G_1 by $\frac{1}{2}(z^{+1/2} + z^{-1/2})$


$$G_1 \rightarrow G_1 \frac{1}{2}(z^{+1/2} + z^{-1/2}) = G_1 \cos \omega T/2$$

(bilinear termination)

SC Implementation

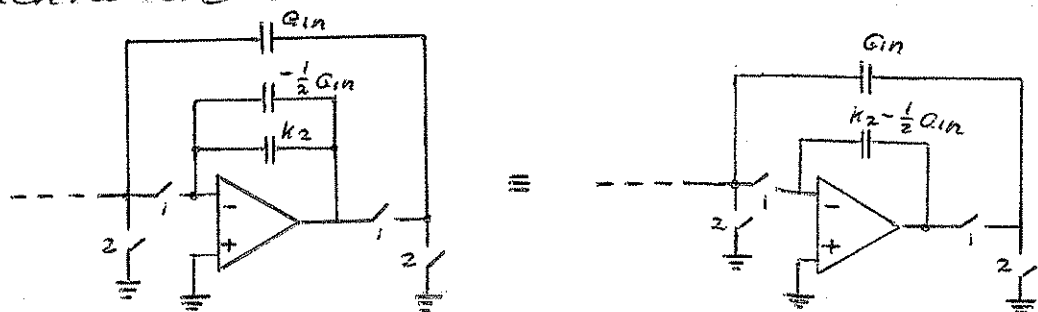

3rd Order SC Ladder Filter

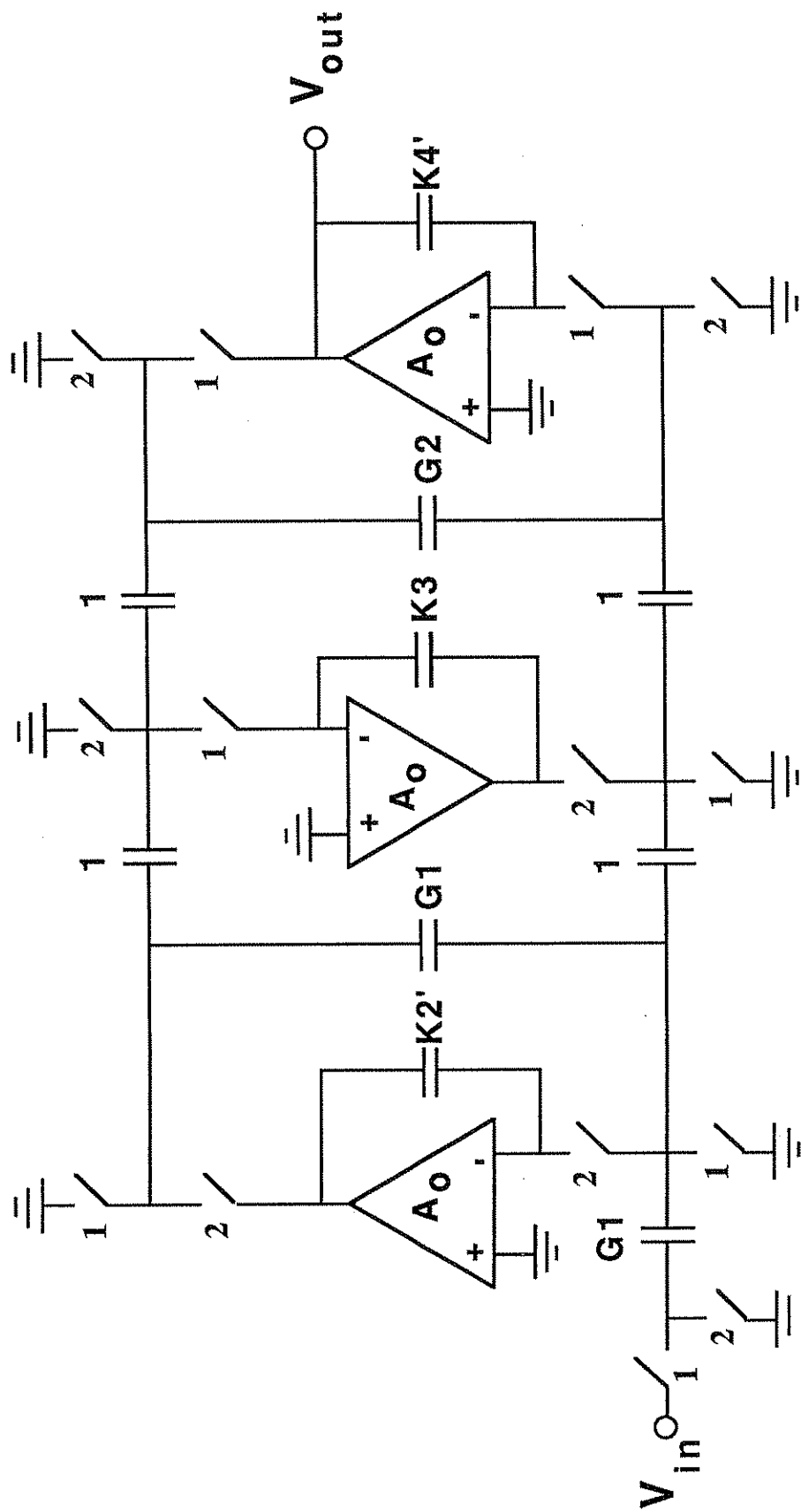

$$K_2' = K_2 - G_1/2$$

$$K_4' = K_4 - G_2/2$$

Example ②: 3rd order lowpass with finite zero

Filter specs: Passband edge: $f_1 = 1\text{kHz}$


Passband ripple: $\leq 0.5\text{dB}$

Stopband edge: $f_2 = 3\text{kHz}$

Stopband loss: $\geq 40\text{dB}$

Sampling rate: $f_s = 20\text{kHz}$

1. R-LC Prototype Filter

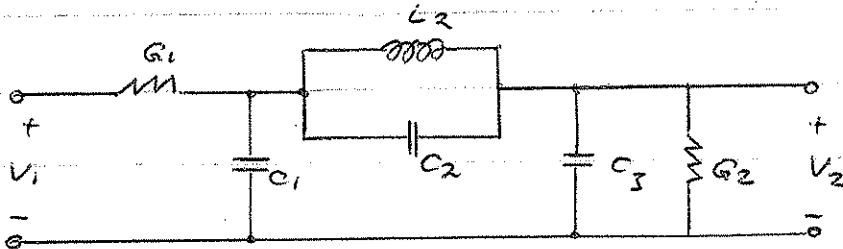

normalized element values: ($G_n = G_i$; $f_n = f_s$)

$$G_1 = G_2 = 1$$

$$C_1 = 4.8948$$

$$L_2 = 3.2807$$

$$C_2 = 0.2611$$

$$C_3 = 4.8948$$

2. Elimination of serial capacitor C_2

NW equations: $I_{C2} = (V_{C1} - V_{C3}) s C_2$

(1)

C_1 branch:

C_3 branch

$$I_{C1} = I_{G1} - I_{L2} - I_{C2}$$

$$I_{C3} = I_{L2} + I_{C2} - I_{G2}$$

(2)

$$V_{C1} = I_{C1} \frac{1}{s C_1}$$

$$V_{C3} = I_{C3} \frac{1}{s C_3}$$

(3)

VII-21

Eliminating I_{C2} and plugging eq. (2) into (3) yields:
 for C_1 branches for C_3 branches

$$V_{C1} = (\bar{I}_{A1} - \bar{I}_{L2}) \frac{1}{sC_1} - (V_{C1} - V_{C3}) \frac{C_2}{C_1}$$

$$V_{C3} = (\bar{I}_{L2} - \bar{I}_{A2}) \frac{1}{sC_3} - (V_{C3} - V_{C1}) \frac{C_2}{C_3}$$


$$\left| \begin{array}{l} V_{C1} = (\bar{I}_{A1} - \bar{I}_{L2}) \frac{1}{s(C_1 + C_2)} + V_{C3} \frac{C_2}{C_1 + C_2} \\ V_{C3} = (\bar{I}_{L2} - \bar{I}_{A2}) \frac{1}{s(C_2 + C_3)} + V_{C1} \frac{C_2}{C_2 + C_3} \end{array} \right|$$

Finally, we substitute $(C_1 + C_2)$ by C_1' and $(C_2 + C_3)$ by C_3' .

We can then write

$$\left\| \begin{array}{l} V_{C1} = (\bar{I}_{A1} - \bar{I}_{L2}) \frac{1}{sC_1'} + V_{C3} \frac{C_2}{C_1'} \\ V_{C3} = (\bar{I}_{L2} - \bar{I}_{A2}) \frac{1}{sC_3'} + V_{C1} \frac{C_2}{C_3'} \end{array} \right\|$$

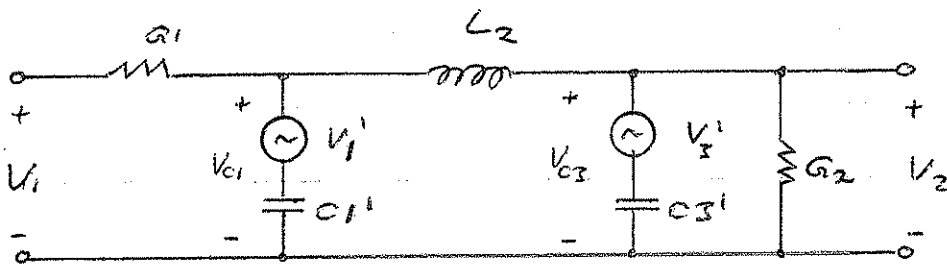
The equivalent circuit of this modified system is shown below



$$\text{where: } \left| \begin{array}{l} C_1' = C_1 + C_2 \\ C_3' = C_2 + C_3 \end{array} \right| \quad \left| \begin{array}{l} V_1' = V_{C3} \frac{C_2}{C_1'} \\ V_3' = V_{C1} \frac{C_2}{C_3'} \end{array} \right|$$

Note: This modified circuit contains only 3 reactive elements and can thus be realized by a 3 integrator circuit

3. Modified SFR

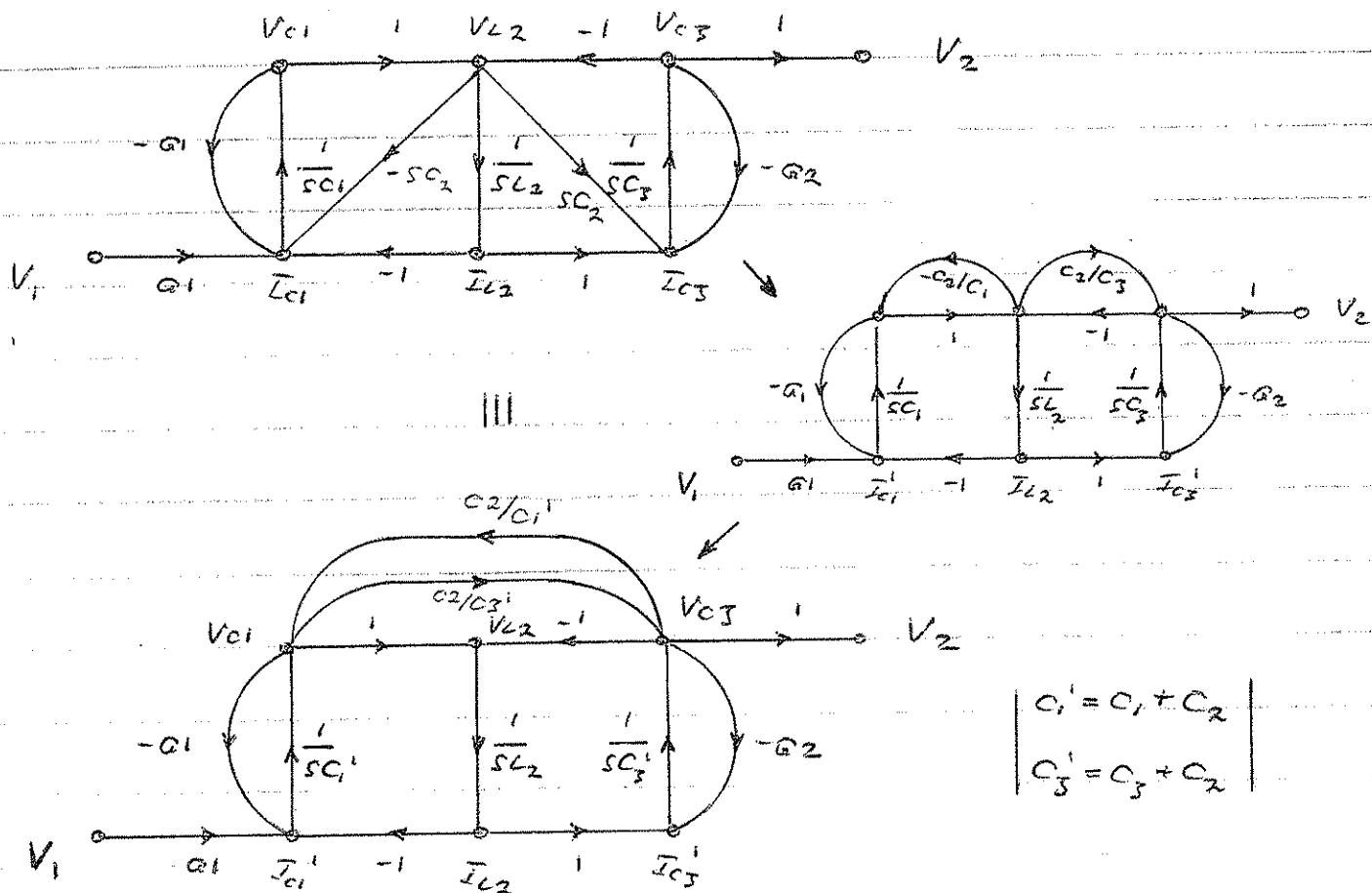


4. SC Implementation (LDE equivalent solution)


Element correspondences: (see Fig. next page)

$C10 = C_1' - \frac{1}{2}G_1$	$C20 = L_2$	$C30 = C_3' - \frac{1}{2}G_2$
$C11 = G_1$	$C21 = 1$	$C31 = 1$
$C12 = 1$	$C22 = 1$	$C32 = G_2$
$C13 = G_1$		$C33 = G_2$
$C14 = C_2$		

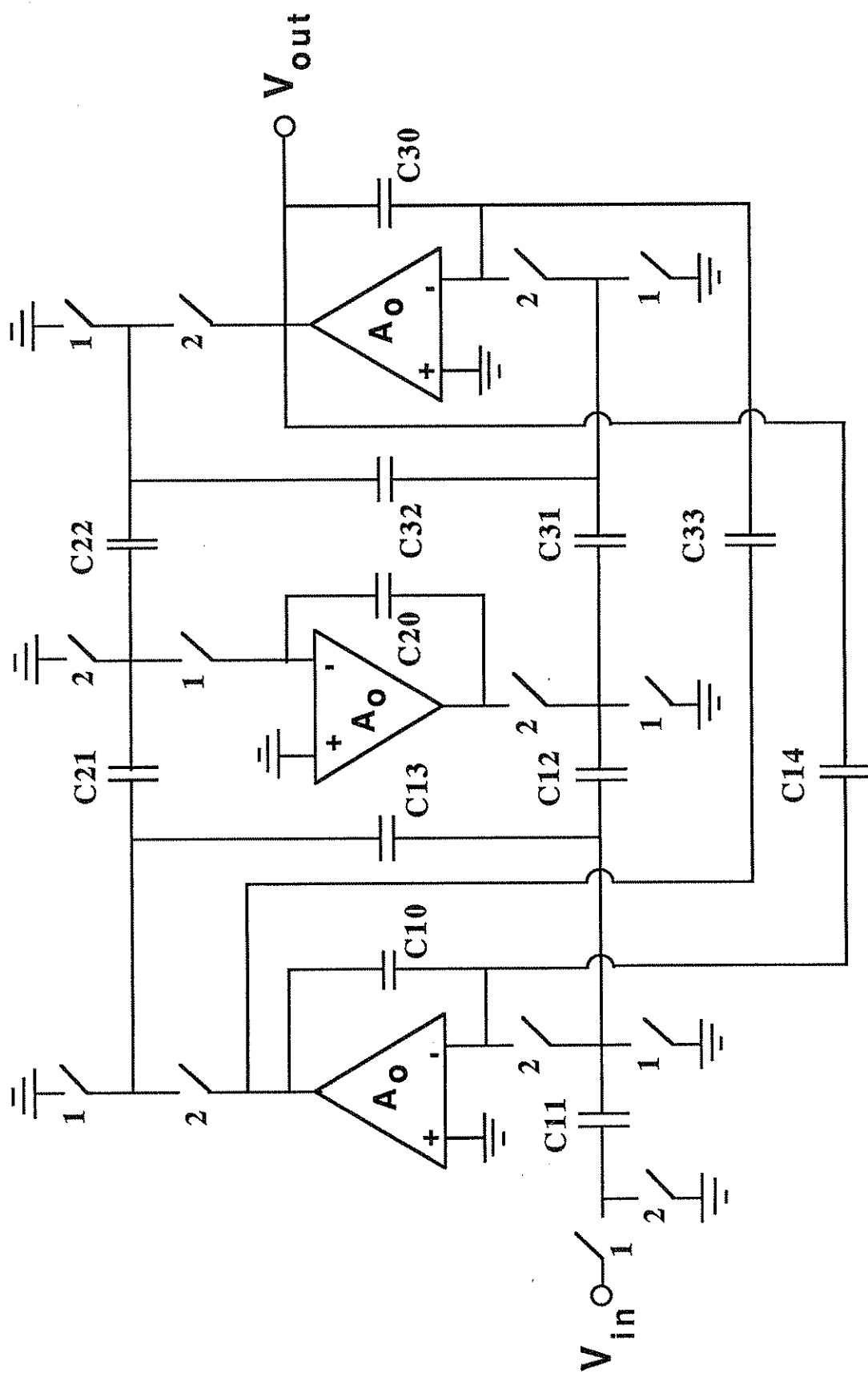
3rd Order SC Ladder Filter with Finite Zero




3. Direct Synthesis in the z -domain

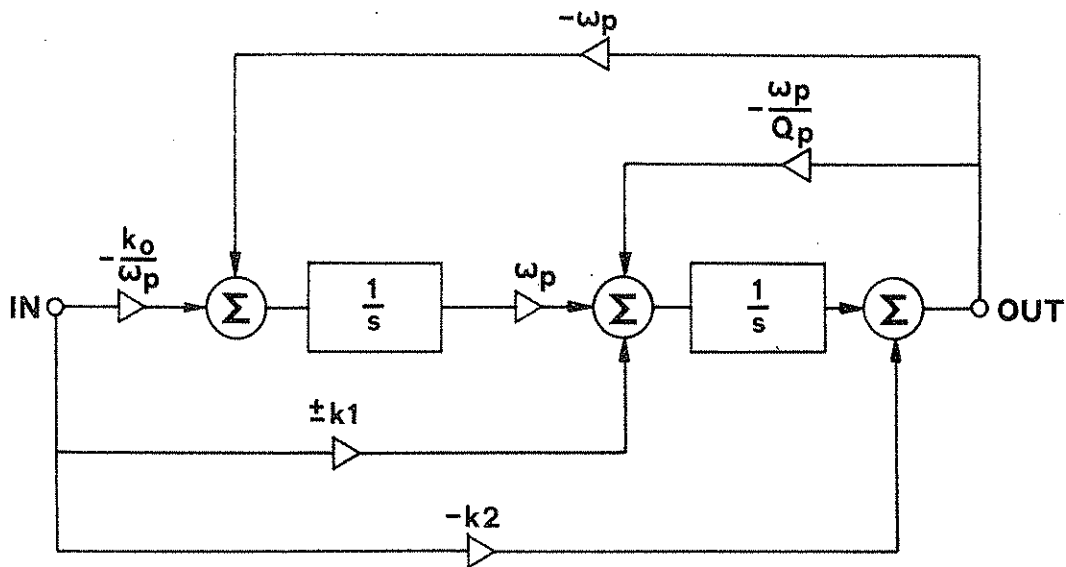

SC Sigquad

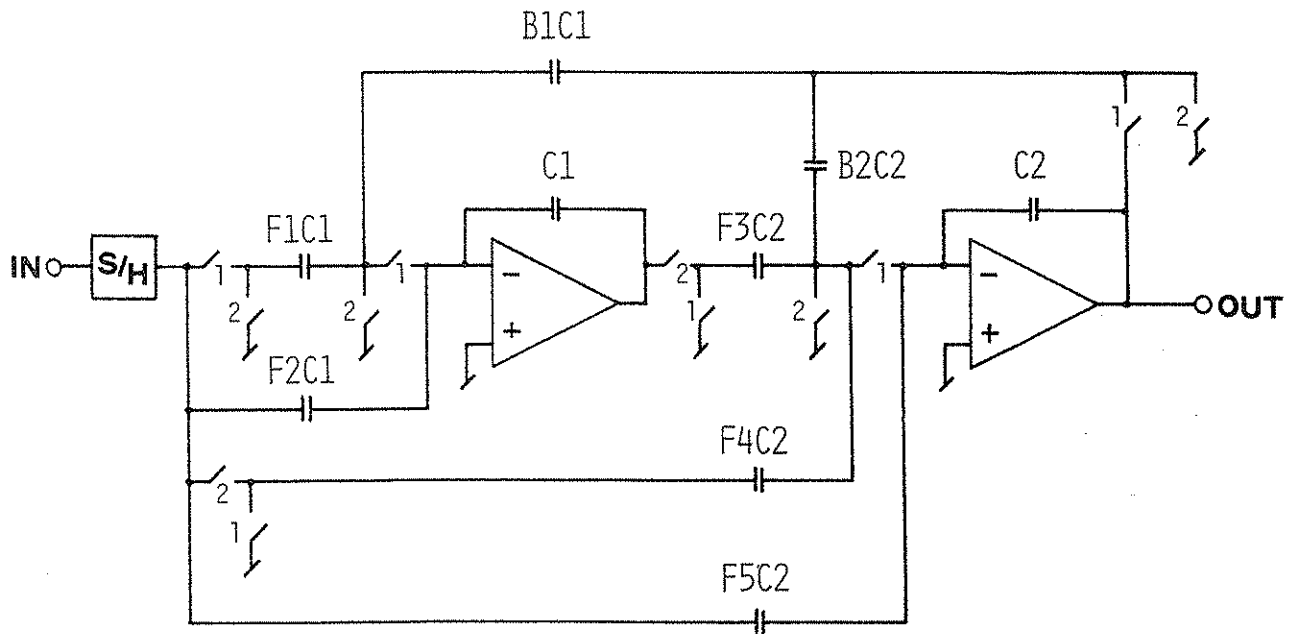

SFG representation:

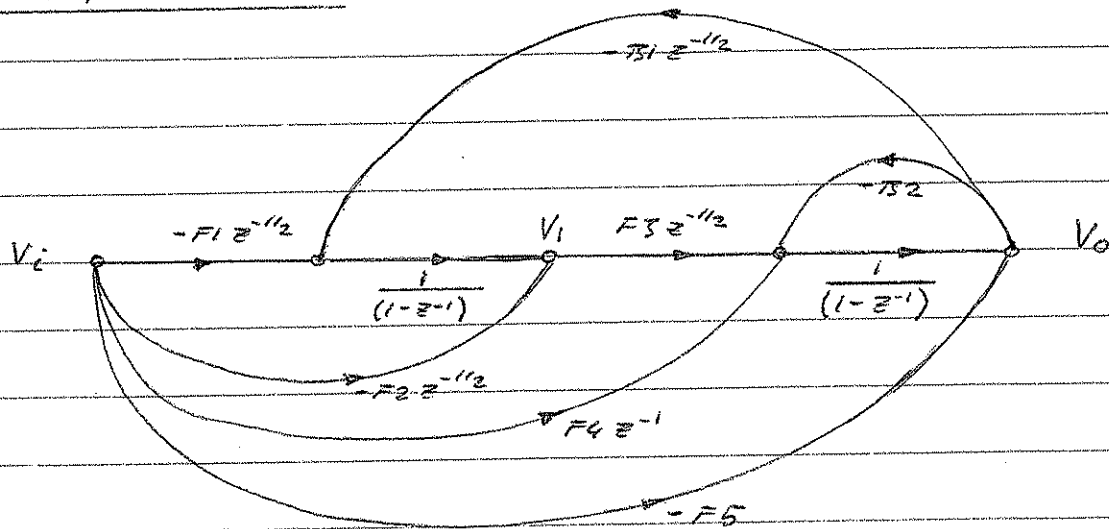

$$\frac{V_o}{V_i} = \frac{-F_1 F_3 z^{-1} - F_2 F_3 z^{-1} (1 - z^{-1}) + F_4 z^{-1} (1 - z^{-1}) - F_5 (1 - z^{-1})^2}{(1 - z^{-1})^2 + \beta_1 F_3 z^{-1} + \beta_2 (1 - z^{-1})}$$

$$\frac{V_o}{V_i} = \frac{F_5}{(1 + \beta_2)} \frac{(1 - z^{-1}) \left[2 - \frac{F_1 F_3 + F_2 F_3 - F_4}{F_5} \right] + z^{-2} \left[1 - \frac{F_2 F_3 - F_4}{F_5} \right]}{(1 - z^{-1}) \left[2 - \frac{\beta_1 F_3 + \beta_2}{1 + \beta_2} \right] + z^{-2} \frac{1}{(1 + \beta_2)}} \quad (1)$$

Biquadratic Function in s

$$\frac{V_o}{V_i} = -k_o \frac{(\omega_z^2 + s \frac{\omega_z}{Q_z} + s^2)}{(\omega_p^2 + s \frac{\omega_p}{Q_p} + s^2)}$$

↓ MZT

$$\frac{V_o}{V_i} = -k_o \frac{(1 - z^{-1})^2 e^{\pm \theta_z T} \cos \tilde{\omega}_z T + z^{-2} e^{\pm 2\theta_z T}}{(1 - z^{-1})^2 e^{-\theta_p T} \cos \tilde{\omega}_p T + z^{-2} e^{-2\theta_p T}} \quad (2)$$

where $\theta_p = \frac{\omega_p}{2Q_p}$ $\tilde{\omega}_p = \omega_p \sqrt{1 - \frac{1}{4Q_p^2}}$ T : clock cycle

$\theta_z = \frac{\omega_z}{2Q_z}$ $\tilde{\omega}_z = \omega_z \sqrt{1 - \frac{1}{4Q_z^2}}$

Compare coefficients of equal power in (1) and (2)

$$\frac{F_5}{1+B_2} = K_0$$

$$1 - \frac{F_1 F_3 + F_2 F_3 - F_4}{2 F_5} = e^{\mp \phi_2 T} \cos \tilde{\omega}_2 T$$

$$1 - \frac{F_2 F_3 - F_4}{F_5} = e^{\mp 2 \phi_2 T}$$

$$1 - \frac{B_1 F_3 + B_2}{2(1+B_2)} = e^{-\phi_p T} \cos \tilde{\omega}_p T$$

$$\frac{1}{1+B_2} = e^{-2 \phi_p T}$$

5 equations

7 unknowns

$\Rightarrow$ 2 free parameters

For optimum dynamic (both amps exhibit equal max. swing)

$B_1 \approx F_3$ (better: $B_1 = F_3 \frac{Q_p}{1+Q_p}$) for lowpass only

Minimum phase network
(zeros in left half plane)

$\phi_2 \leq 0 \Rightarrow \underline{F_4 = 0}$

Nonminimum phase network
(zeros in right half plane)

$\phi_2 > 0 \Rightarrow \underline{F_2 = 0}$

$$B_2 = e^{2 \phi_p T} - 1$$

$$F_3^2 = B_1^2 = 2 e^{2 \phi_p T} - 2 e^{\phi_p T} \cos \tilde{\omega}_p T - B_2$$

$$F_5 = K_0 e^{2 \phi_p T}$$

$$F_2 = \frac{F_5}{F_3} [1 - e^{-2 \phi_2 T}]$$

$$F_1 = \frac{2 F_5}{F_3} [1 - e^{-\phi_2 T} \cos \tilde{\omega}_2 T] - F_2$$

$$B_2 = e^{2 \phi_p T} - 1$$

$$F_3^2 = B_1^2 = 2 e^{2 \phi_p T} - 2 e^{\phi_p T} \cos \tilde{\omega}_p T - B_2$$

$$F_5 = K_0 e^{2 \phi_p T}$$

$$F_4 = F_5 [e^{2 \phi_2 T} - 1]$$

$$F_1 = \frac{2 F_5}{F_3} [1 - e^{\phi_2 T} \cos \tilde{\omega}_2 T] + F_4$$

Example ① Design a 2nd order Lowpass with
 $f_p = 1\text{kHz}$; $Q_p = 1$; Unity Gain at $\omega = 0$
 $f_s = 16\text{kHz}$

a) Transfer function in s and in z:


$$H(s) = - \frac{\omega_p^2}{\omega_p^2 + s \frac{\omega_p}{Q_p} + s^2}$$

↓
MST

$$H(z) = - \frac{1 + e^{-\frac{\omega_p T}{Q_p}} - 2e^{-\frac{\omega_p T}{2Q_p}} \cos[\omega_p T \sqrt{1 - \frac{1}{4Q_p^2}}]}{1 - z^{-1} 2e^{-\frac{\omega_p T}{2Q_p}} \cos[\omega_p T \sqrt{1 - \frac{1}{4Q_p^2}}] + z^{-2} e^{-\frac{\omega_p T}{Q_p}}}$$

$$= \frac{0.12591}{1 - z^{-1} 1.54932 + z^{-2} 0.67523}$$

b) Circuit Topology:

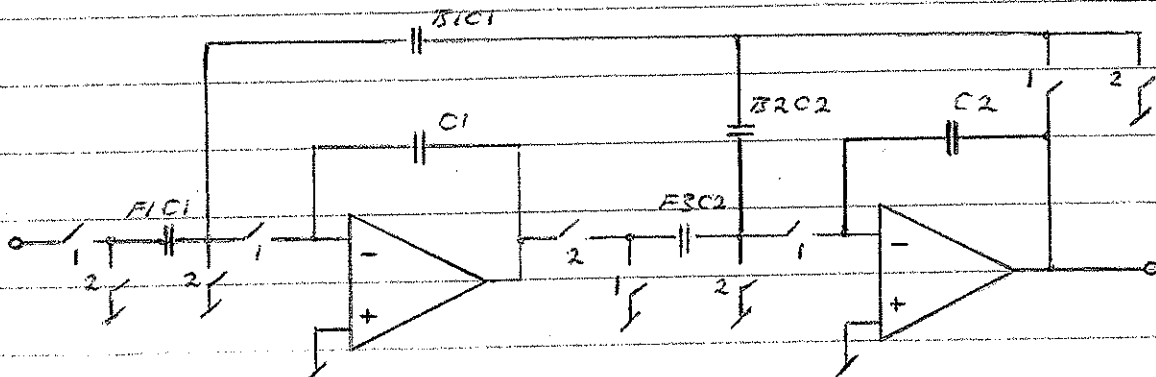

$$H(z) = - \frac{F1F3 z^{-1}}{(1 + \beta z)(1 - z^{-1} [2 - \frac{\beta F1F3 + \beta z}{1 + \beta z}] + z^{-2} \frac{1}{1 + \beta z})}$$

c) coefficient comparison:

Note that the additional factor z^{-1} in the z -domain transfer function numerator has no influence on the filter amplitude response, since it merely adds an excess linear phase

$$z^{-1} \rightarrow e^{-j\omega T}$$

Therefore:

$\frac{F1F3}{1+B2} = 0.12591$ $2 - \frac{B1F3+B2}{1+B2} = 1.54332$ $\frac{1}{1+B2} = 0.57523$ $B1 \approx F3$

(optimum dynamic)

not good for low-Q filters

better
$$B1 = \frac{Q_p}{1+Q_p} F3 \text{ (lowpass only)}$$

Solution:

if
$$B1 = \frac{Q_p}{1+Q_p} F3$$

$F3 = B1 = 0.43182$ $F1 = 0.43182$ $B2 = 0.48038$	$B1 = F1 = 0.30531$ $B2 = 0.48038$ $F3 = 0.61063$
---	---

Capacitors:

$C_{\pi 1} = 1$ (1) $C_{F1} = 1$ (1) $C_1 = 2.516$ (3.275)	$C_{\pi 2} = 1.114$ (1) $C_{F3} = 1$ (1.268) $C_2 = 2.516$ (2.079)
--	--

() dynamically

optimized

Example 2 Design the same low-pass filter by means of the bilinear z-transform

a) Frequency prewarping

$$\omega_p' = \frac{f_s}{\pi} \lg \left[\sqrt{\frac{1}{1-\alpha^2}} \right] = \underline{\underline{1.013 \text{ KHz}}}$$

b) Transfer function in s and z-domain:


$$H(s) = - \frac{\omega_p'^2}{\omega_p'^2 + s \frac{\omega_p'}{Q_p} + s^2}$$

↓ BZT

$$H(z) = - \frac{\frac{\omega_p'^2 T^2}{4(1+Q_p T) + \omega_p'^2 T^2} (1+z^{-1})^2}{1 - z^{-1} \frac{4 - \omega_p'^2 T^2}{4(1+Q_p T) + \omega_p'^2 T^2} + z^{-2} \frac{4(1-Q_p T) + \omega_p'^2 T^2}{4(1+Q_p T) + \omega_p'^2 T^2}}$$

$$= - \frac{0.031944 (1+z^{-1})^2}{1 - z^{-1} 1.55102 + z^{-2} 0.67879}$$

c) Circuit Topology

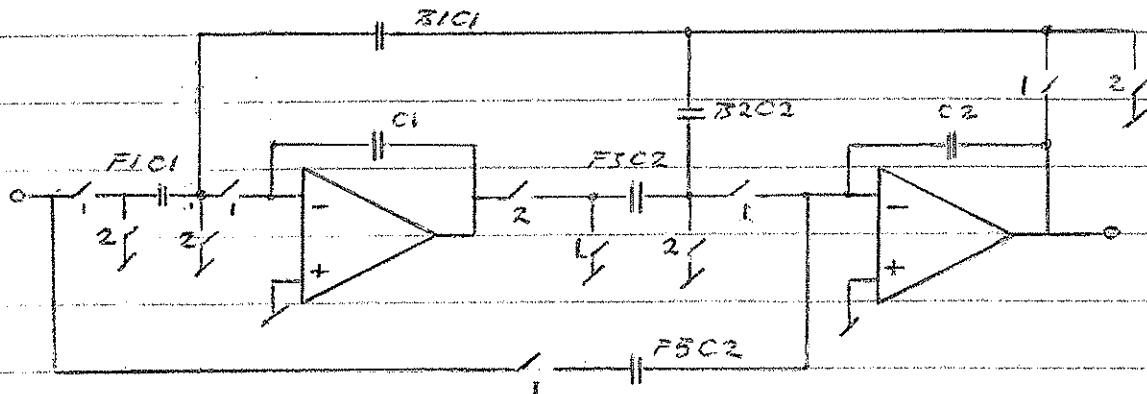

$$H(z) = - \frac{F_5 (1 - z^{-1} [2 - \frac{F_1 F_3}{F_5}] + z^{-2})}{(1 + B_2) (1 - z^{-1} [2 - \frac{B_1 F_3 + B_2}{1 + B_2}] + z^{-2} \frac{1}{1 + B_2})}$$

Thus:

$\frac{F_5}{1 + B_2} = 0.031944$
$\frac{F_1 F_3}{F_5} = 4$
$2 - \frac{B_1 F_3 + B_2}{1 + B_2} = 1.55102$
$\frac{1}{1 + B_2} = 0.67873$
$B_1 \approx F_3$

Solution:

$B_1 = F_3 = 0.43387$
$B_2 = 0.47321$
$F_1 = 0.43387$
$F_5 = 0.047060$

Capacitors:

$C_{B1} = 1$	$C_{B2} = 10.055$
$C_{F1} = 1$	$C_{F3} = 9.220$
$C_L = 2.505$	$C_{F5} = 1$
	$C_2 = 21.250$

Design of a 2nd order SC Bandpass Filter

Filter Specs:

$f_p = 50 \text{ kHz}$	$Q_p = 5$
$f_s = 1 \text{ MHz}$	

Transfer Function:

$$H(z) = \frac{F_2 F_3}{(1+B_2)} \frac{z^{-1}(1-z^{-1})}{(1-z^{-1}[2-\frac{B_1 F_3 + B_2}{1+B_2}] + z^{-2} \frac{1}{1+B_2})}$$

The above specs yields (MST)

$$H(z) = -0.06283 \frac{z^{-1}(1-z^{-1})}{(1-1.84422z^{-1}+0.93910z^{-2})}$$

To balance the 2 amplifier output swings, we set $B_1 = F_3$

By comparing the coefficients of equal power in the above 2 z-domain transfer functions, we obtain:

$B_1 = F_3 = 0.31795$
$B_2 = 0.06495$
$F_2 = 0.19768$

Cap Values:

$C_1 = 5.059$	$C_2 = 15.420$
$B_1 C_1 = 1.608$	$B_2 C_2 = 1$
$F_2 C_1 = 1$	$F_3 C_2 = 4.901$

Example 3 Design a 2nd order Bandpass with
 $f_p = 1 \text{ kHz}$; $Q_p = 5$; Unity Gain in Passband
 $f_s = 16 \text{ kHz}$

a) z-domain transfer function (MAT equivalent)

$$H_{BP}(z) = - \frac{0.078540 (1 - z^{-1})}{1 - z^{-1} 1.77660 + z^{-2} 0.924465}$$

b) SC implementation


Select $F1 = F4 = F5 = 0$

$$H_{BP}(z) = - \frac{F2 F3 z^{-1/2} (1 - z^{-1})}{(1 + B2) (1 - z^{-1}) \left[2 - \frac{B1 F3 + B2}{(1 + B2)} \right] + z^{-2} \frac{1}{(1 + B2)}} \quad \left| \right.$$


c) Result from coefficient comparison:

$$\left| \begin{array}{l} B1 = 0.39993 \\ B2 = 0.081707 \\ F2 = 0.19638 \\ F3 = 0.39993 \end{array} \right| \Rightarrow \left| \begin{array}{ll} C1 = 5.092 & C2 = 12.259 \\ CB1 = 2.036 & CB2 = 1 \\ CF2 = 1 & CF3 = 4.895 \end{array} \right|$$

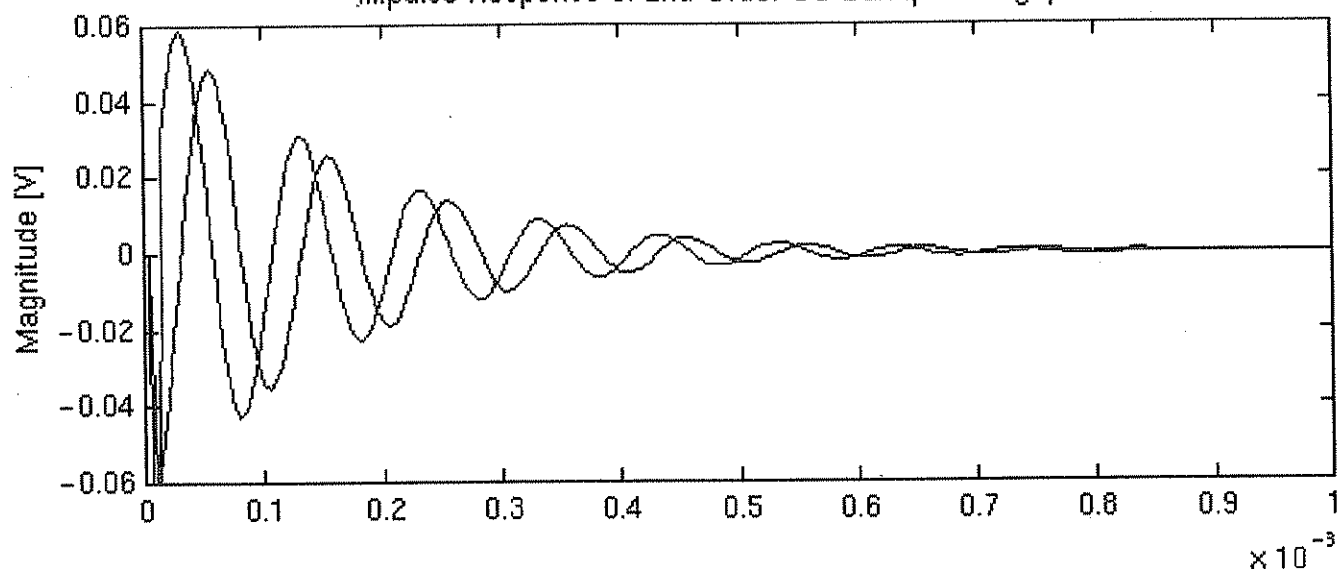
Impulse Response of 2nd Order SC Bandpass/Highpass



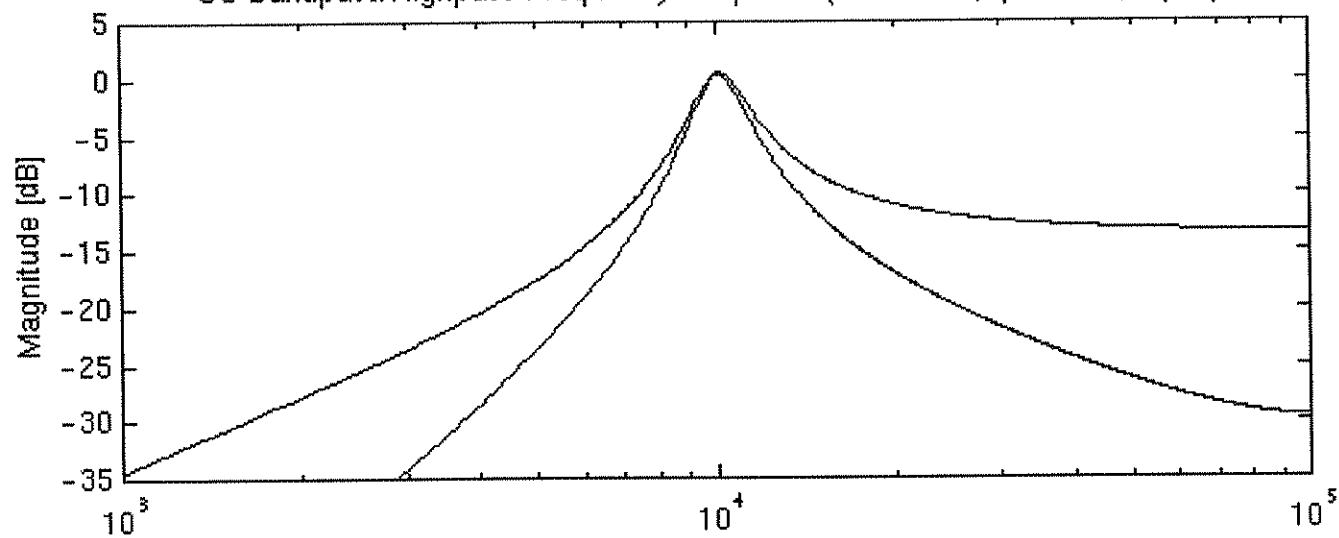SC Bandpass/Highpass Frequency Response ($f_s=200\text{kHz}$, $f_p=10\text{kHz}$, $Q_p=5$)




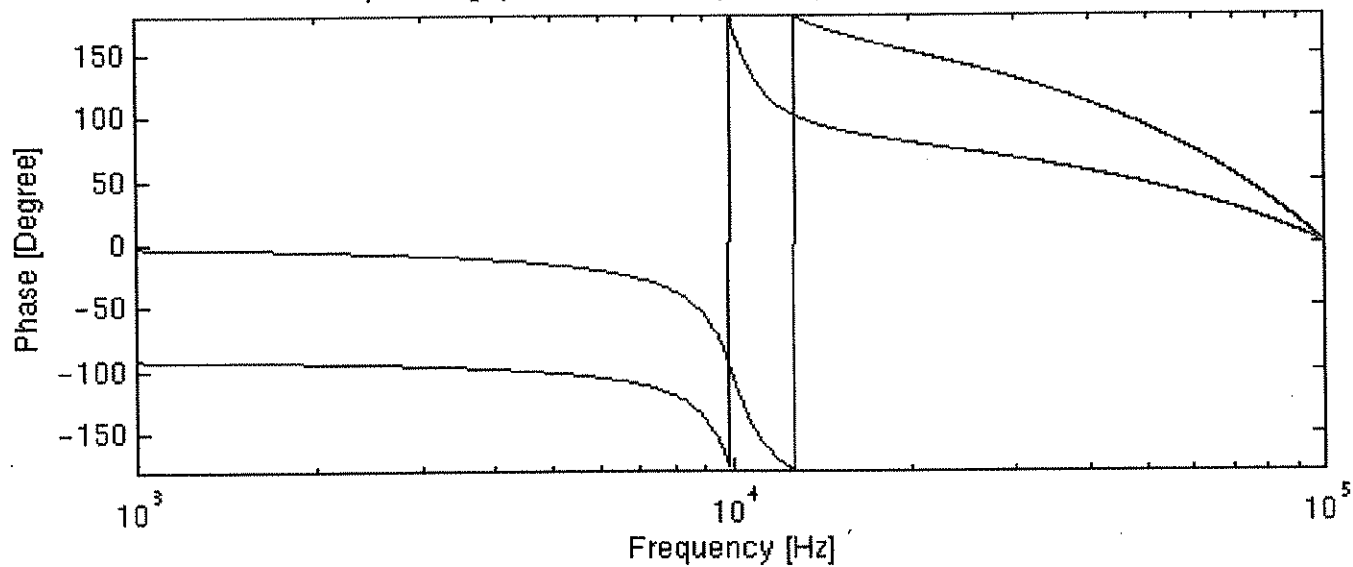SC Bandpass/Highpass Phase Response ($f_s=200\text{kHz}$, $f_p=10\text{kHz}$, $Q_p=5$)



C-Spread Reduction Techniques

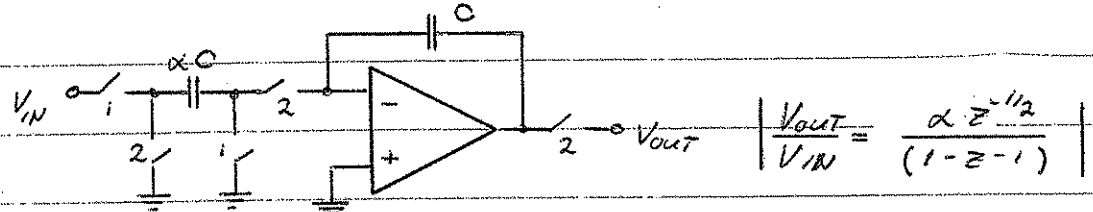Example Noninverting Integrator with $\alpha \ll 1$





Solution A

Solution B

Difference Integrator

Integrator with T-section

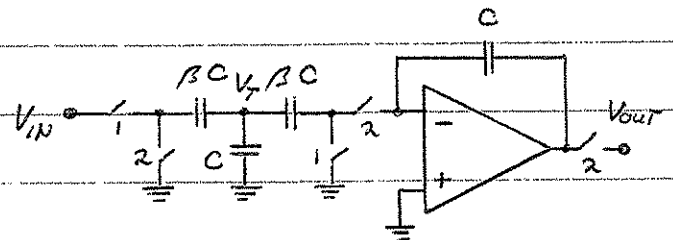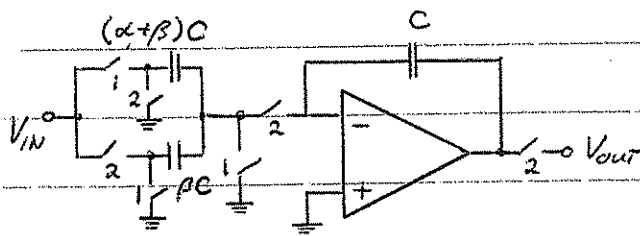

assumption: V_{IN} only changes during phase 1

$$\frac{V_{OUT}}{V_T} = \frac{\beta z^{-1/2}}{(1 - z^{-1})}$$

$$\left\| \frac{V_{OUT}}{V_{IN}} = \frac{[(\alpha + \beta) - \beta] z^{-1/2}}{(1 - z^{-1})} \right\|$$

$$= \frac{\alpha z^{-1/2}}{(1 - z^{-1})}$$

$$\frac{V_T}{V_{IN}} = \frac{\beta}{1 + 2\beta}$$

$$\therefore \left\| \frac{V_{OUT}}{V_{IN}} = \frac{\beta^2}{(1 + 2\beta)} \frac{z^{-1/2}}{(1 - z^{-1})} \right\|$$

$$C\text{-Spread} = \beta^{-1}$$


$$\text{where } \beta = \alpha \left[1 + \sqrt{1 + \frac{1}{\alpha}} \right]$$

e.g. $\alpha = 0.01$
select $\beta = 0.1$
 $\therefore \text{Spread} = 10$


$$C\text{-Spread} = \beta^{-1}$$

e.g. $\alpha = 0.01 \therefore \beta = 0.1105$
 $\therefore \text{Spread} = 9.05$


Leapfrog Structure

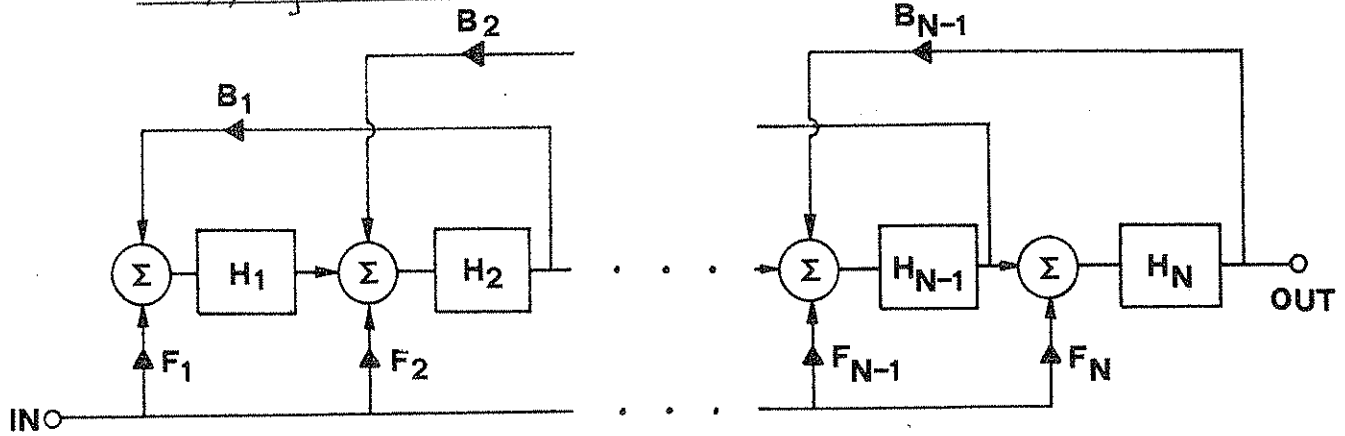

Follow-the-Leader Feedback

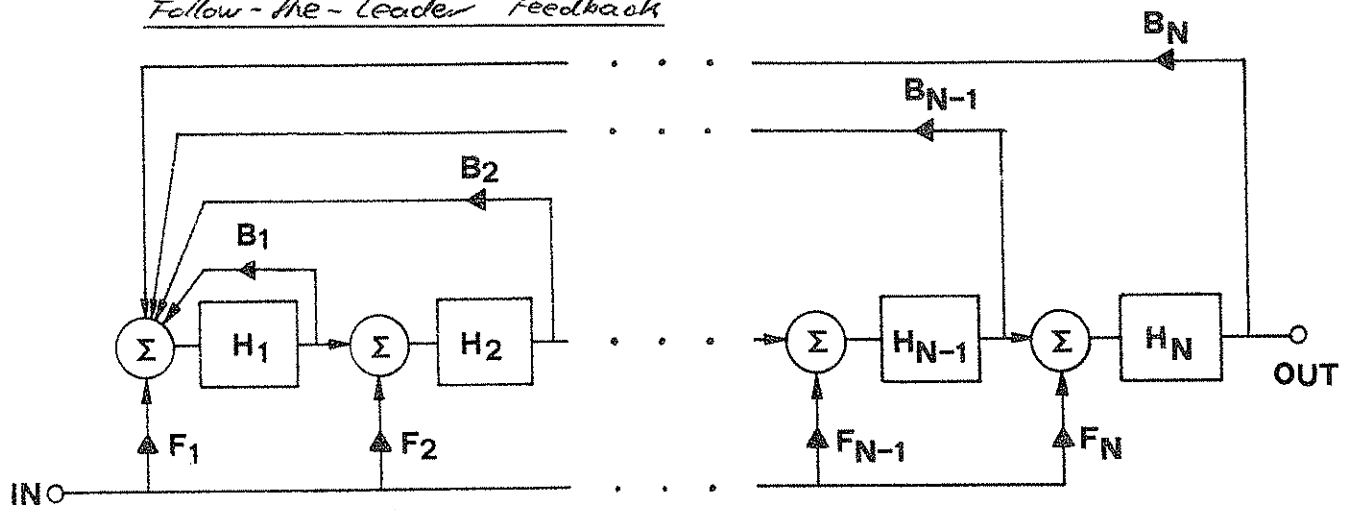


Inverse Follow-the-Leader Feedback

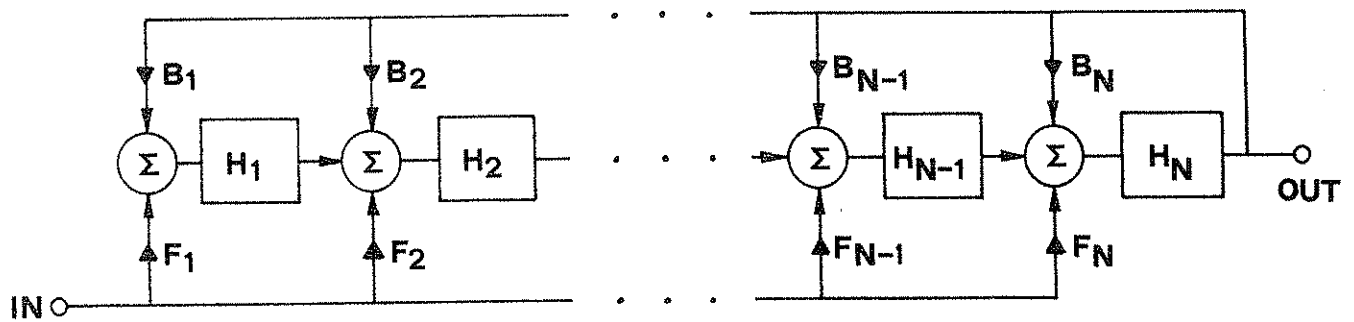


4. Synthesis via Digital Filter Architecture


a) 2-opamp unit delay cell

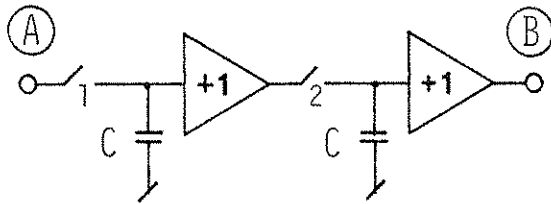


b) single opamp unit delay

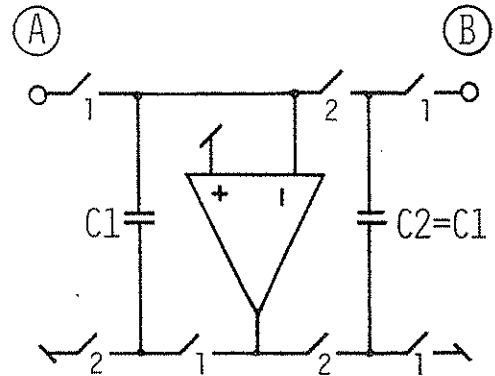

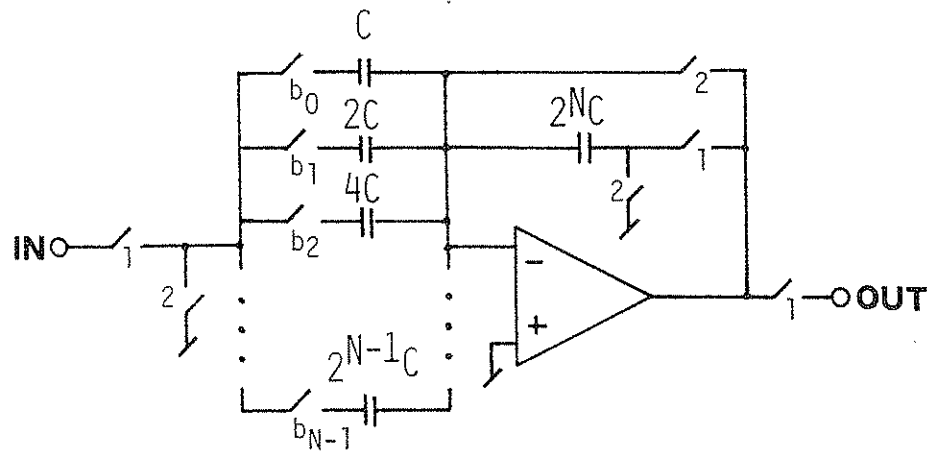
SC Multiplier (digitally controlled) $\therefore$ mult. DAC




a) Direct Form I Topology

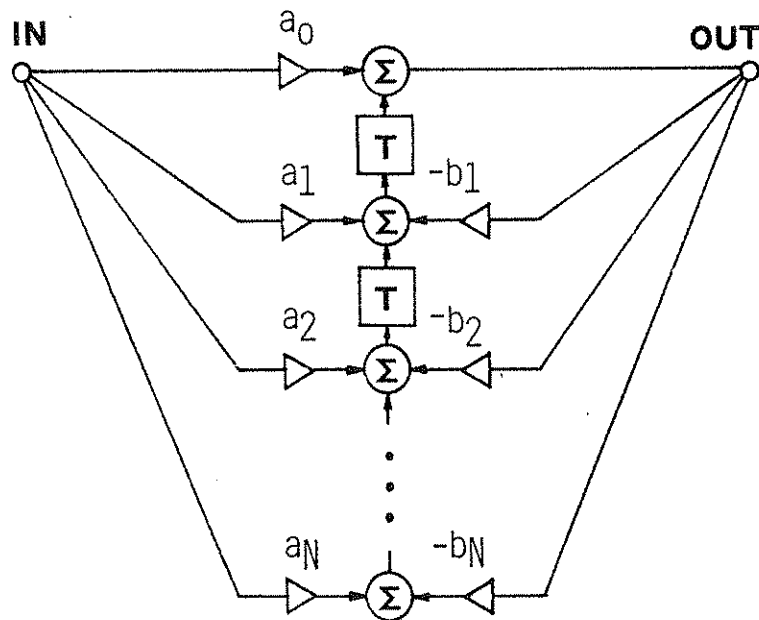


b) Direct Form II Topology

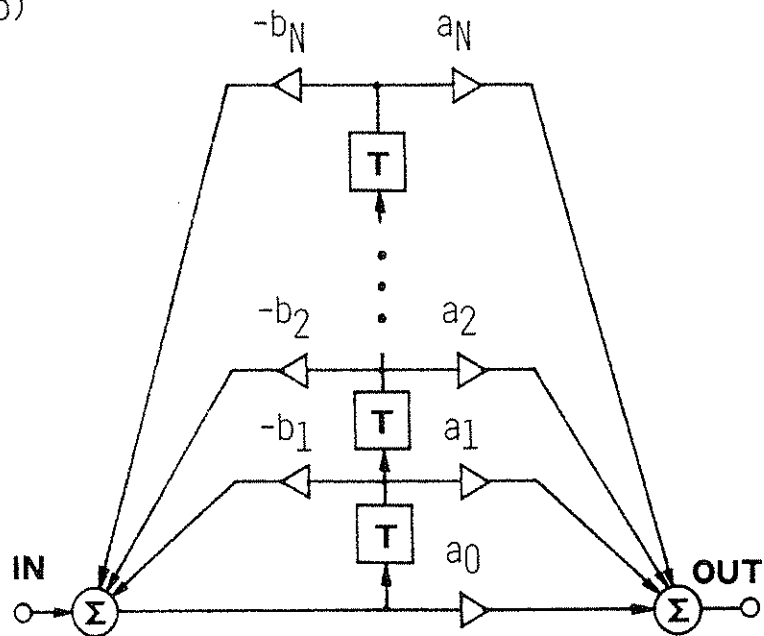

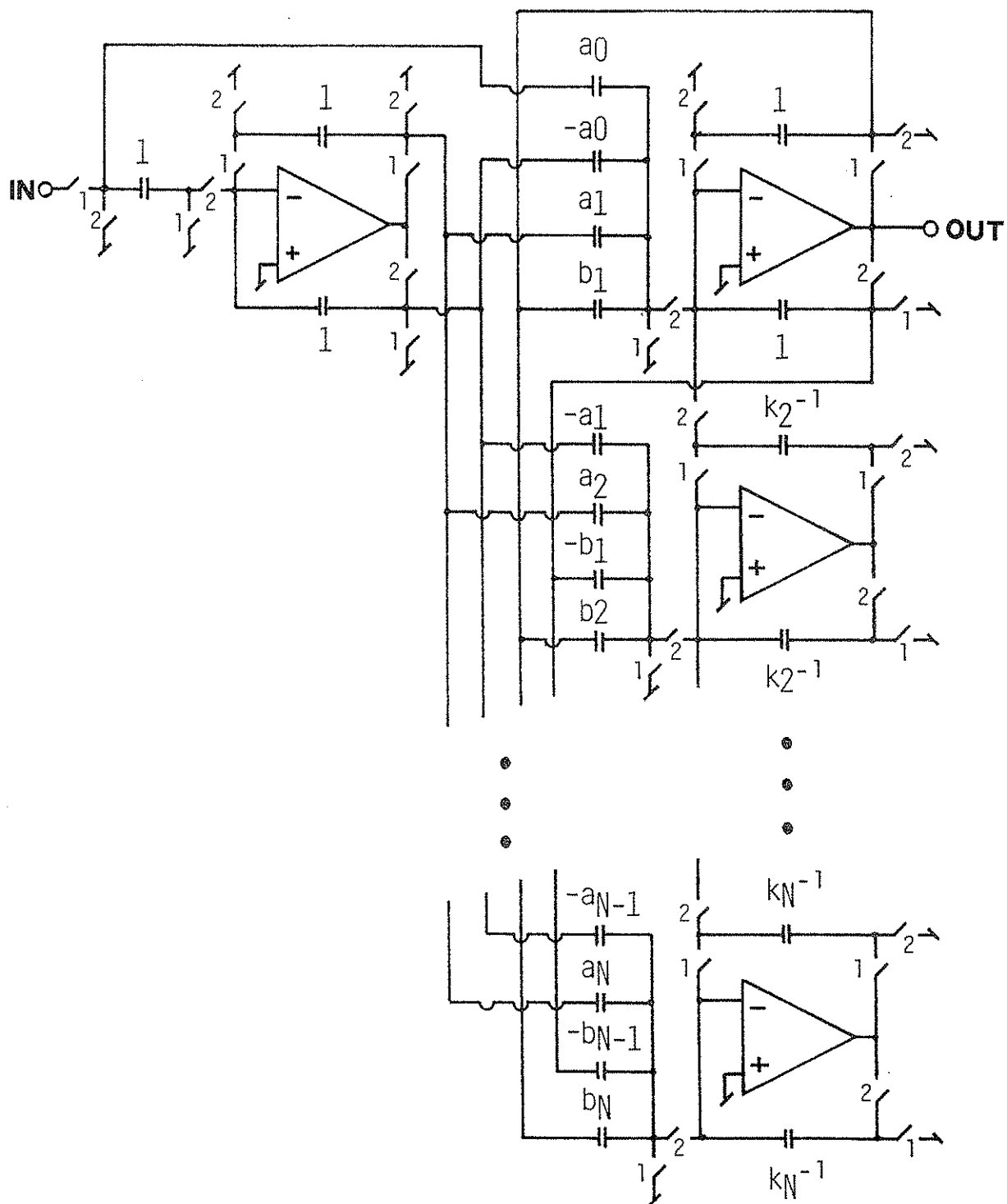N-th order Circuit in Direct Form I Realization




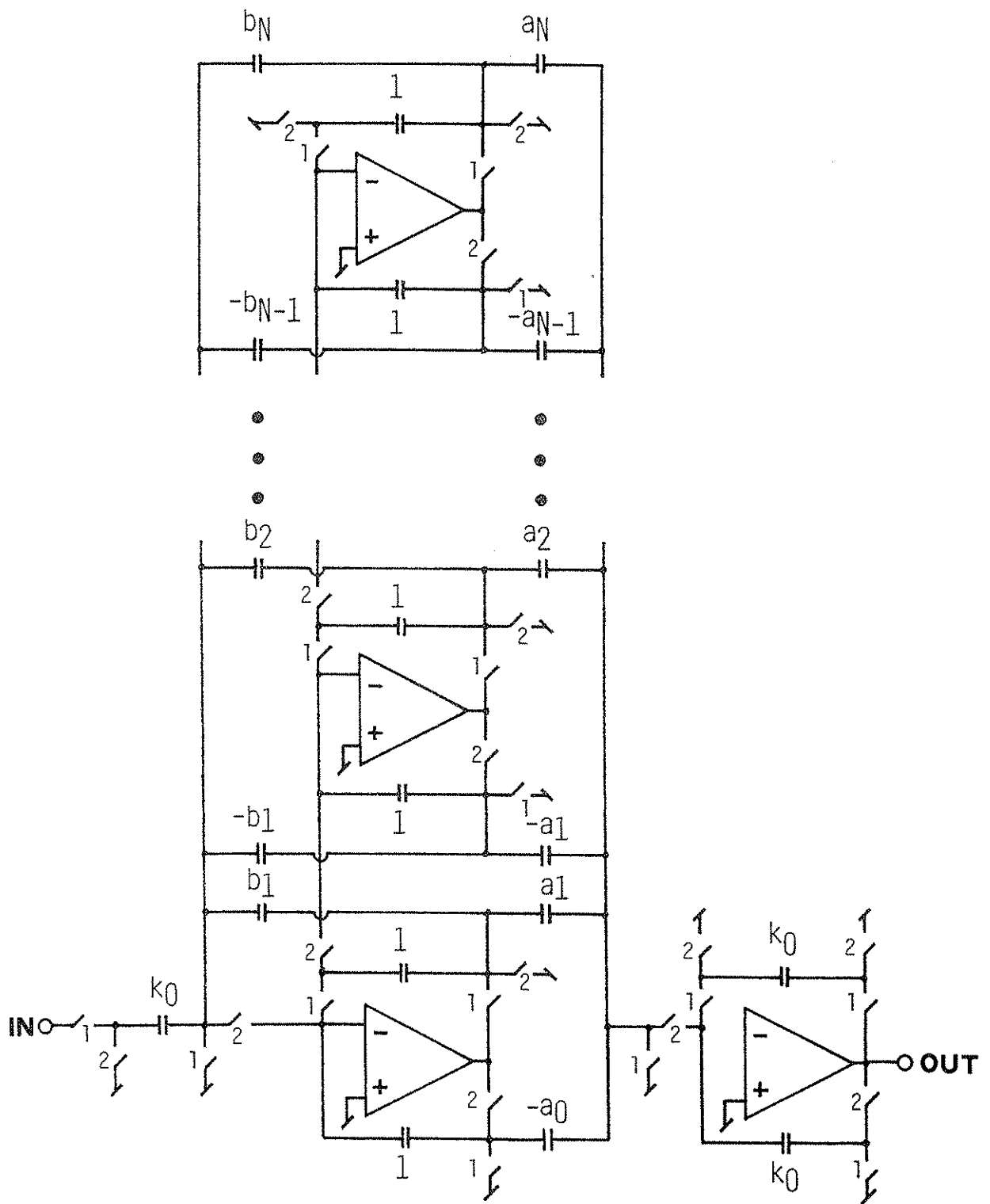N-th order circuit in Direct Form II Realization



Influence of the amplifier finite gain

discrete Integrator

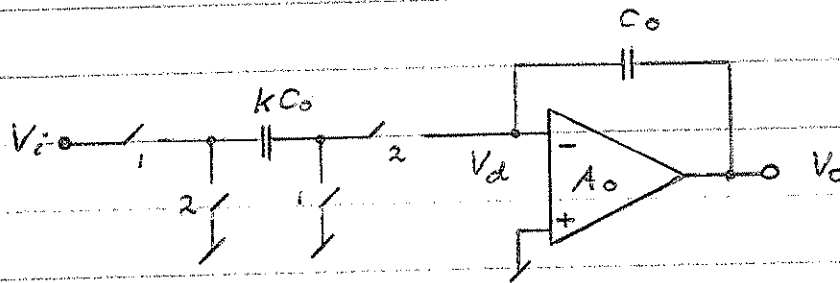

$$V_o = -A_o V_d$$

Analysis

charge at end of ϕ_1 charge at end of ϕ_2

Charge conservation: $Q_1 = Q_2$ $1 \rightarrow 2$

$$\left| \begin{array}{l} Q_1 = Q_1(n + \frac{1}{2}) = kC_0 V_{i1} + C_0 (V_{o1} - V_{d1}) \\ Q_2 = Q_2(n+1) = -kC_0 V_{d2} + C_0 (V_{o2} - V_{d2}) \end{array} \right|$$

replace V_d by $-\frac{1}{A_o} V_o$

$$\left| \begin{array}{l} Q_1 = kC_0 V_{i1} + C_0 V_{o1} (1 + \frac{1}{A_o}) \\ Q_2 = \frac{k}{A_o} C V_{o2} + C_0 V_{o2} (1 + \frac{1}{A_o}) \end{array} \right|$$

V_o does not change during ϕ_1 ; i.e. $V_o(n + \frac{1}{2}) = V_o(n)$

$$\left| \begin{array}{l} Q_1(n + \frac{1}{2}) = kC_0 V_{i1}(n + \frac{1}{2}) + C_0 V_o(n) [1 + \frac{1}{A_o}] \\ Q_2(n+1) = \frac{k}{A_o} C_0 V_o(n+1) + C_0 V_o(n+1) [1 + \frac{1}{A_o}] \end{array} \right|$$

$$Q_1 = Q_2$$

$$\Rightarrow k \phi_0 V_i(n + \frac{1}{2}) + \phi_0 V_o(n) [1 + \frac{1}{\lambda_0}] = \phi_0 V_o(n+1) [1 + \frac{1}{\lambda_0} + \frac{k}{\lambda_0}]$$

↓
z-Transform

$$k V_i(z) z^{+1/2} + V_o(z) [1 + \frac{1}{\lambda_0}] = V_o(z) z^{+1} [1 + \frac{1}{\lambda_0} + \frac{k}{\lambda_0}]$$

$$\begin{aligned} \Rightarrow \frac{V_o(z)}{V_i(z)} &= \frac{k \cdot z^{+1/2}}{z [1 + \frac{1}{\lambda_0} + \frac{k}{\lambda_0}] - [1 + \frac{1}{\lambda_0}]} \\ &= \frac{k z^{+1/2}}{(1 - z^{-1}) (1 + \frac{1}{\lambda_0} + \frac{k}{\lambda_0} - z^{-1} [1 + \frac{1}{\lambda_0}])} \\ &\quad \underbrace{\hspace{10em}}_{\text{Ideo (=Hid(z))}} \quad \underbrace{\hspace{10em}}_{\text{Parasitico = E(z)}} \end{aligned}$$

$$E(z) \cong (1 - \frac{1}{\lambda_0} [1+k]) \frac{(1 - z^{-1})}{1 - z^{-1} [1 - \frac{k}{\lambda_0}]}$$

$$\downarrow$$

$$E(\omega) = (1 - \frac{1}{\lambda_0} [1+k]) \frac{2j e^{-j\omega T/2} \sin \omega T/2}{2j e^{-j\omega T/2} \sin \omega T/2 + \frac{k}{\lambda_0} e^{-j\omega T/2}}$$

$$\cong \frac{1 - \frac{1}{\lambda_0} [1+k]}{1 - j \frac{k}{\lambda_0 2} (\frac{1}{\tan \omega T/2} - j)} = \frac{1 - \frac{1}{\lambda_0} [1+k]}{1 - \frac{k}{\lambda_0 2} - j \frac{k}{\lambda_0 2} [\tan \omega T/2]^{-1}}$$

$$\cong (1 - \frac{1}{\lambda_0} [1+k]) (1 + j \frac{k}{\lambda_0 2} [\tan \omega T/2]^{-1})$$

$$\| E(\omega) \cong 1 - \frac{1}{\lambda_0} [1 + \frac{k}{2}] + j \frac{k}{\lambda_0 2} \frac{1}{\tan \omega T/2} \|$$

$$m_{A_0}(\omega) \cong - \frac{1}{\lambda_0} [1 + \frac{k}{2}]$$

$$\theta_{A_0}(\omega) \cong \tan^{-1} \left[\frac{k}{2 \lambda_0 \tan \omega T/2} \right]$$

Influence of the finite amplifier open-loop Gain A_0

$$m_{A_0}(\omega) \cong -\frac{1}{A_0} \left(1 + \frac{k}{2}\right)$$

$$\theta_{A_0}(\omega) \cong \text{Arc tan} \left(\frac{1}{A_0} \frac{k}{2 \tan \omega T/2} \right)$$


Influence of the Stray-Capacitances

$$m_s(\omega) \cong -\frac{1}{A_0} \left(\frac{C_{sd}}{C_0} + \frac{C_{st}}{2 C_0} \right)$$


$$\theta_s(\omega) \cong \text{Arc tan} \left(\frac{1}{A_0} \frac{C_{st}/C_0}{2 \tan \omega T/2} \right)$$

Influence of the amplifier unity-gain bandwidth and the switch ON resistances


SC Integrator

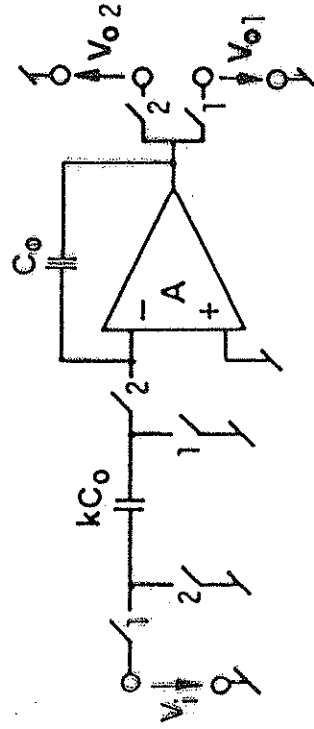

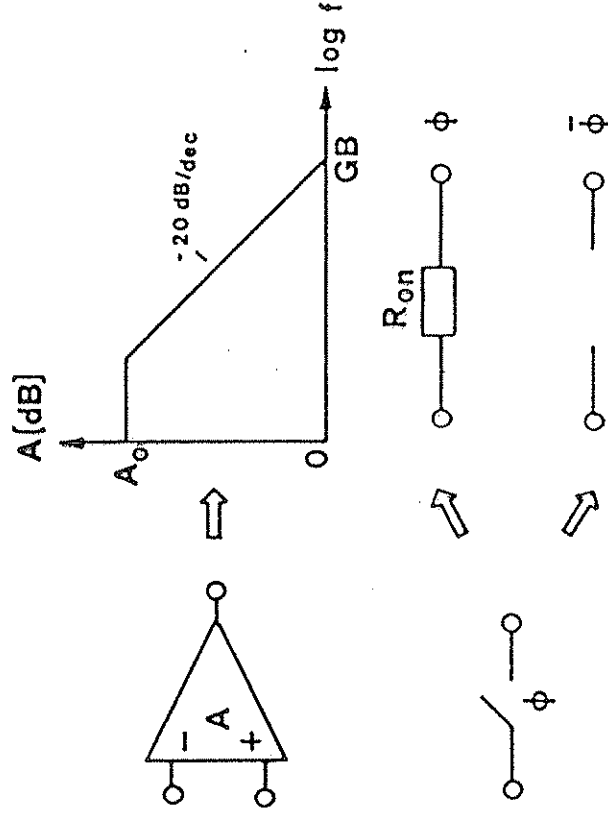
Applied Models for amplifier and switches





SC Integrator during Phase 1


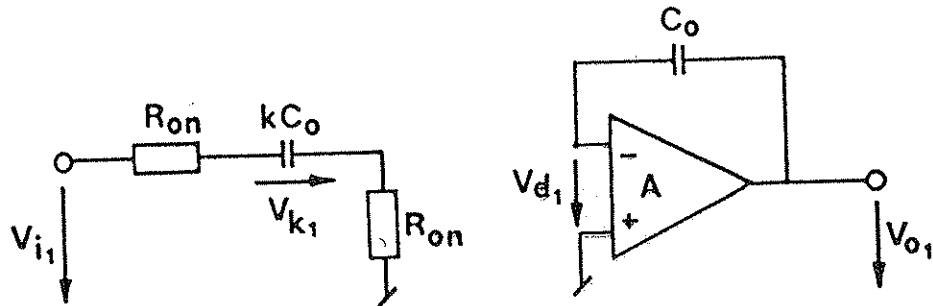


SC Integrator during Phase 2

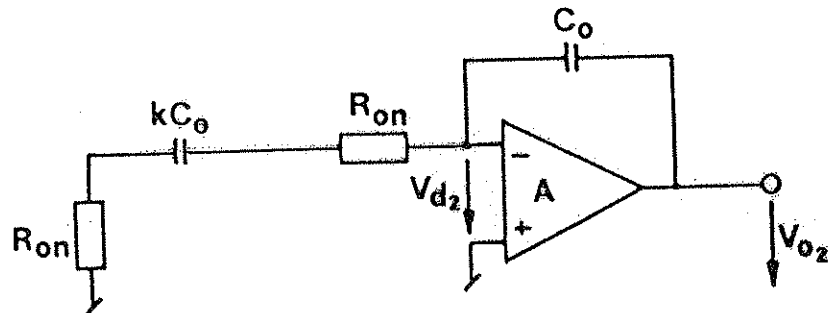


a)

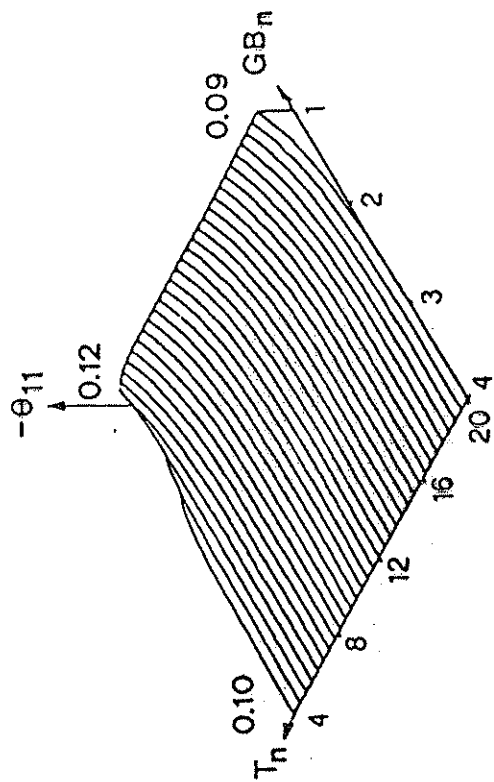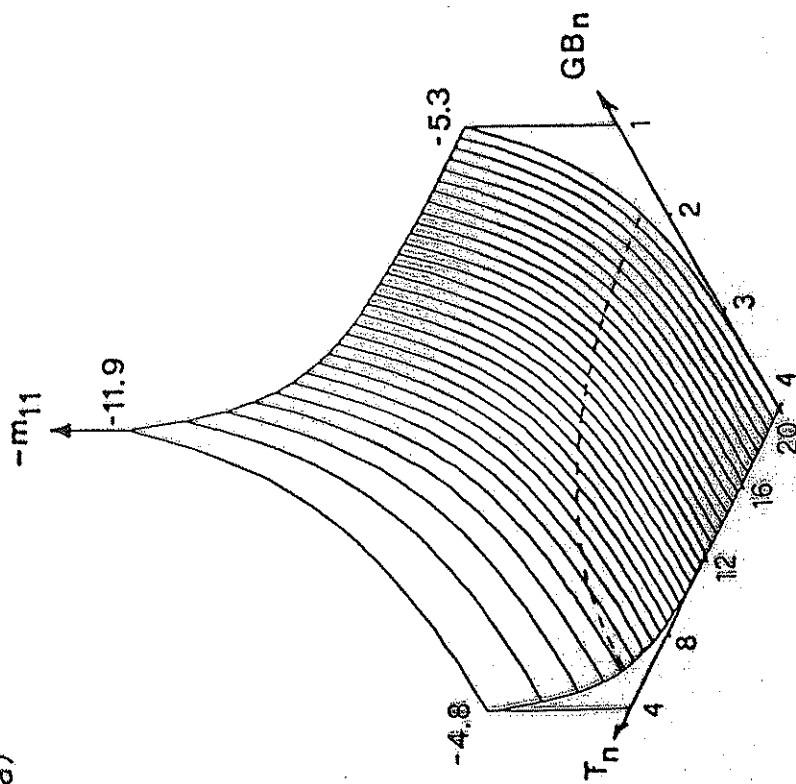


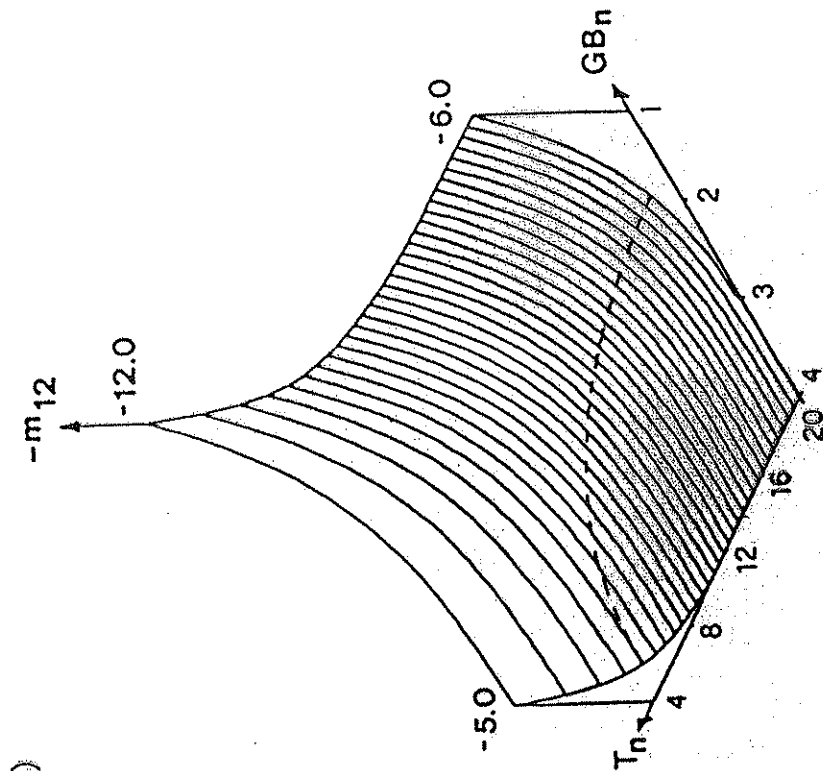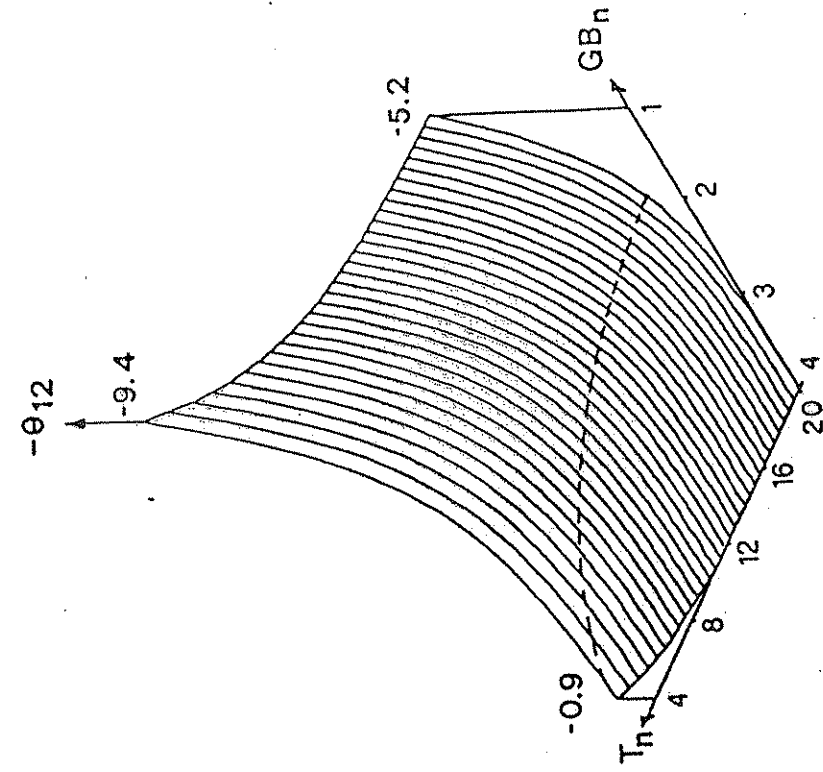

b)

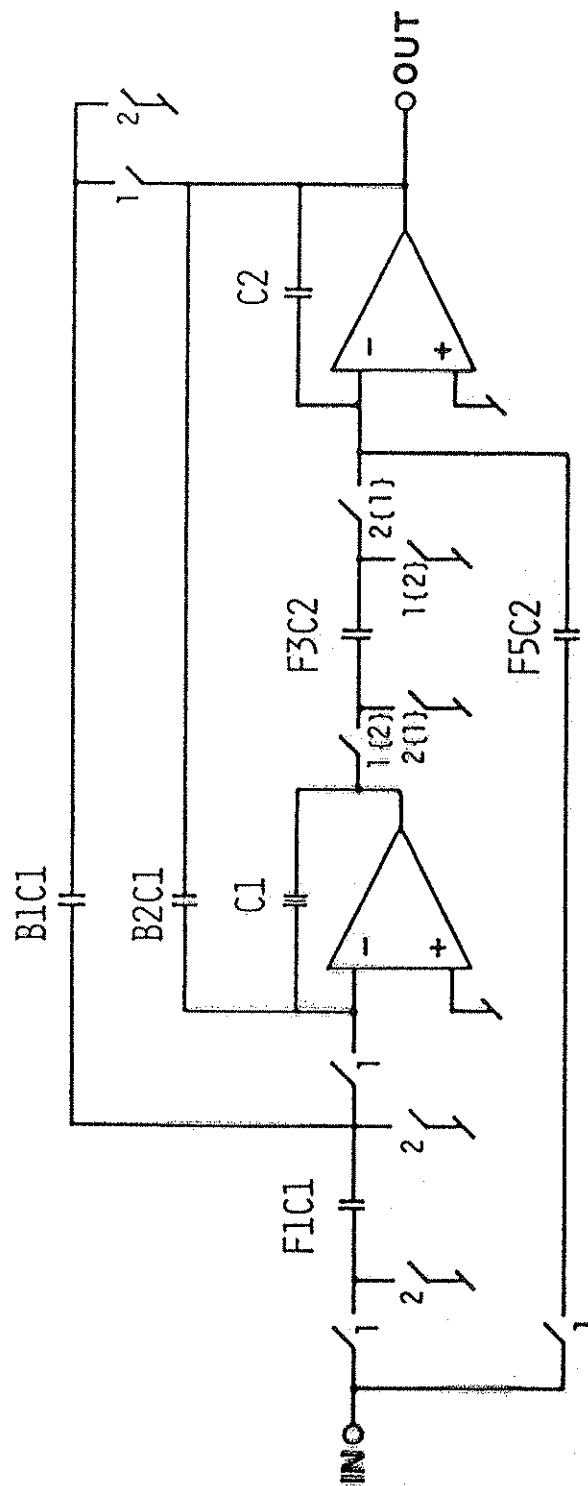Second-order SC Lowpass Circuit with finite Passband Zero



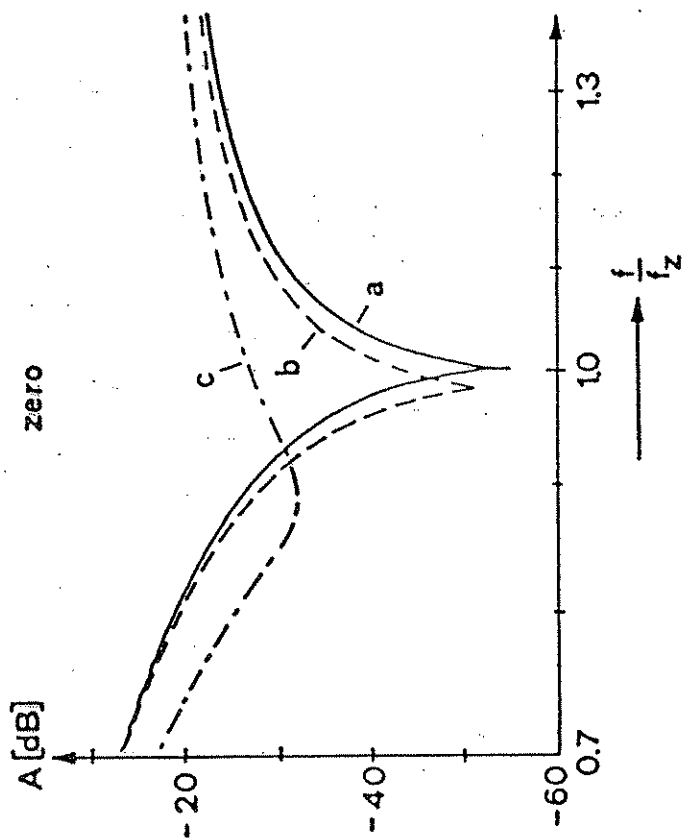

- a) $GB_\eta=4$
- b) $GB_\eta=2$
- c) $GB_\eta=1$
- $A_0=2000$

