

Transconductance-C Filters

A Prototype Filter Implementation

Talk Outline

- Introduction
- Transconductance Elements
- Filter Topologies
- Simulation Results
- Layout of Prototype Filter
- Conclusions

1. Introduction

Why monolithic continuous-time filters?


- Pre- and post filters for sampled-data systems
- Mixed analog digital systems
- Wide frequency range (<100MHz)
- Area and power efficient solution

Continuous-Time Filter Implementation Techniques

- RC-Active Circuits
- MOSFET-C Circuits
- Transconductance-C (Ota-C) Circuits

RC-active Filters

Example: 2nd Order Bandpass

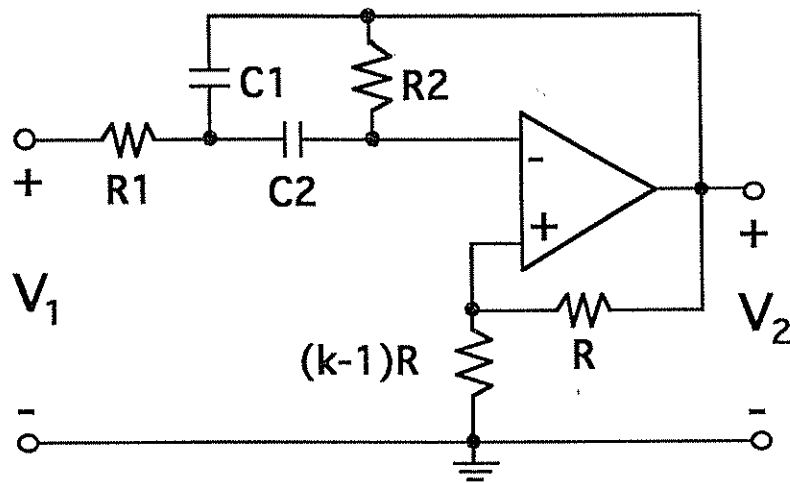

Filter Characteristics


$$T_0 = -\frac{k R_2 C_2}{R_1(C_1 + C_2) - (k-1) R_2 C_2}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{1}{Q_0} = \sqrt{\frac{R_1}{R_2}} \left(\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}} \right) - (k-1) \sqrt{\frac{R_2 C_2}{R_1 C_1}}$$

Summary: Single-opamp negative feedback topologies (2nd order)

Lowpass

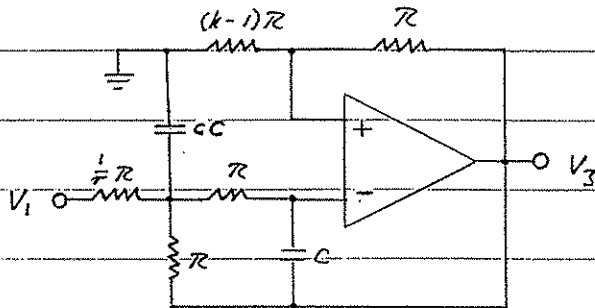


$$\omega_p = \frac{1}{RC} \sqrt{\frac{1-r(k-1)}{C}}$$

$$Q_p = \frac{\sqrt{C(1-r[k-1])}}{2+r-C(k-1)}$$

$$T(s=0) = -\frac{kr}{1-r(k-1)}$$

Bandpass

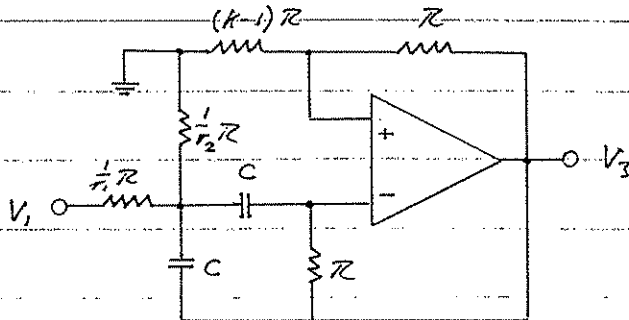


$$\omega_p = \frac{1}{RC} \sqrt{r_1 + r_2}$$

$$Q_p = \frac{\sqrt{r_1 + r_2}}{2-(r_1+r_2)(k-1)}$$

$$T(s=j\omega_p) = -\frac{k \cdot r_1}{2-(r_1+r_2)(k-1)}$$

Highpass

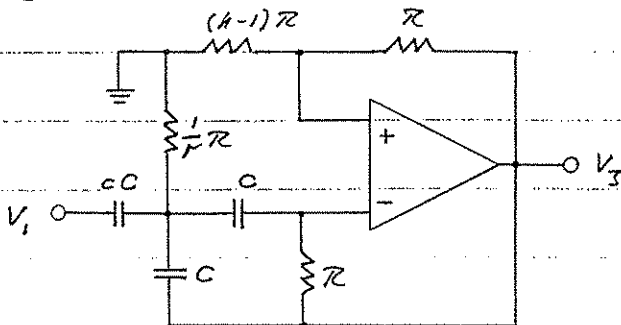


$$\omega_p = \frac{1}{RC} \sqrt{\frac{r}{1-C(k-1)}}$$

$$Q_p = \frac{\sqrt{r(1-C[k-1])}}{2+C-r(k-1)}$$

$$T(s \rightarrow \infty) = -\frac{kC}{1-C(k-1)}$$

Amplifier Finite Gain - Bandwidth Effects (neg. feedback topol.)

Voltage Transfer function:

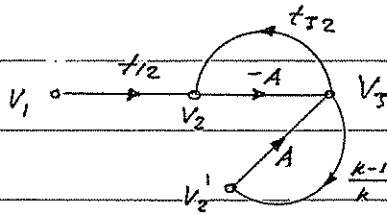

$$T(s) = \frac{V_3}{V_1} = - \frac{A t_{12}}{1 + A(t_{32} - \frac{k-1}{k})} \frac{\frac{k}{A} \hat{d}}{\frac{k}{A} \hat{d}}$$

$$\Rightarrow \left\| T(s) = - \frac{k R_{12}}{\hat{d}(1 + \frac{k}{A}) - k(\hat{d} - t_{32})} \right\|$$

Example: 2nd order Lowpass filter

$$\hat{d} = s^2 + s \frac{1}{RC} (1 + \frac{2+r}{C}) + \frac{1}{(RC)^2} \frac{1+r}{C}$$

$$n_{32} = s^2 + s \frac{1}{RC} \frac{2+r}{C} + \frac{1}{(RC)^2} \frac{1}{C}$$

$$n_{12} = \frac{1}{(RC)^2} \frac{r}{C}$$

Opamp: $A(s) \approx A_0 \frac{\omega_0}{s} = \frac{GB}{s}$

GB: Gain - Bandwidth Pr.

$$\Rightarrow T(s) = - \frac{k \frac{1}{(RC)^2} \frac{r}{C}}{(s^2 + s \frac{1}{RC} [1 + \frac{2+r}{C}] + \frac{1}{(RC)^2} \frac{1+r}{C}) (1 + s \frac{k}{GB}) - k (s \frac{1}{RC} + \frac{1}{(RC)^2} \frac{r}{C})}$$

Approx.

Solution: $\left\| T(s) \approx - \frac{k \frac{1}{(RC)^2} \frac{r}{C}}{(1 + s \frac{k}{GB}) (s^2 [1 + \frac{k^2}{GB RC}] + s \frac{1}{RC} [\frac{2+r-C(k-1)}{C} + \frac{k^2 r}{GB RC C}] + \frac{1}{(RC)^2} \frac{1-r(k-1)}{C})} \right\|$

Poles: neg. real: $\left\| \omega_{p3} \approx \frac{GB}{k} \right\|$

Complex: $\left\| \omega_p \approx \frac{1}{RC} \sqrt{\frac{1-r(k-1)}{C}} \left(1 - \frac{k^2}{2GB RC} \right) \right\|$
 $\left\| Q_p \approx \frac{\sqrt{C(1-r(k-1))} (1 + \frac{k^2}{2GB RC})}{2+r-C(k-1) + \frac{k^2 r}{GB RC}} \right\|$


$$\omega_p \approx \omega_{p0} \left(1 - \frac{k^2}{2GB RC} \right)$$

$$Q_p \approx Q_{p0} \left(1 + \frac{k^2}{2GB RC} \frac{(2-r-C(k-1))}{(2+r-C(k-1))} \right)$$

IX - 6

Summary: Single-opamp positive feedback topologies (2nd order)

Lowpass

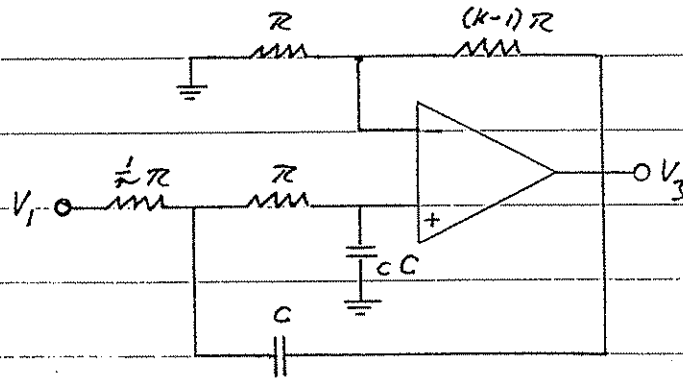


$$\omega_p = \sqrt{\frac{r}{c}} \frac{1}{R C}$$

$$Q_p = \frac{\sqrt{r \cdot c}}{c(1+r) - (k-1)}$$

$$T(s=0) = k$$

Bandpass

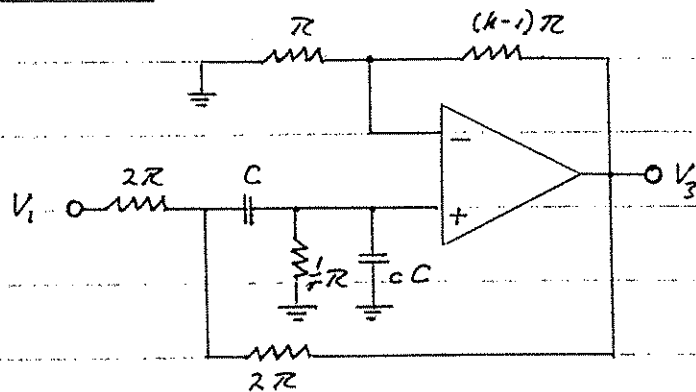


$$\omega_p = \sqrt{\frac{r}{c}} \frac{1}{R C}$$

$$Q_p = \frac{\sqrt{r \cdot c}}{r+c+\frac{1}{2}-\frac{1}{2}(k-1)}$$

$$T(s=j\omega_p) = \frac{k}{2(r+c)+1-(k-1)}$$


Highpass

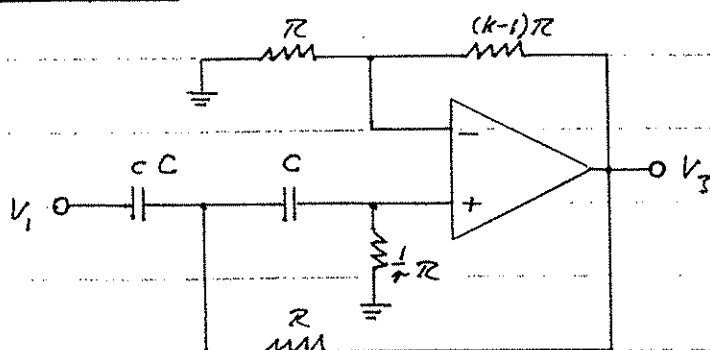

$$\omega_p = \sqrt{\frac{r}{c}} \frac{1}{R C}$$

$$Q_p = \frac{\sqrt{r \cdot c}}{r(1+c) - (k-1)}$$

$$T(s \rightarrow \infty) = k$$

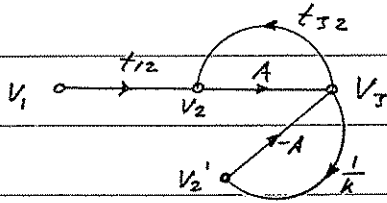Amplifier Finite Gain-Bandwidth Effects (pos. feedback topol.)Voltage Transfer Function:

$$T(s) = \frac{A t_{12}}{1 + A \left(\frac{1}{k} - t_{32} \right)} \frac{\frac{k}{A} \hat{d}}{\frac{k}{A} \hat{d}}$$

$$\Rightarrow \left| T(s) = \frac{k \cdot n_{12}}{\hat{d} \left(1 + \frac{k}{A} \right) - k n_{32}} \right|$$

Example: 2nd order Lowpass Filter

$$\hat{d} = s^2 + s \frac{1}{RC} \left(1 + r + \frac{1}{c} \right) + \frac{1}{(RC)^2} \frac{r}{c}$$

$$n_{32} = s \frac{1}{RC} \frac{1}{c}$$

$$n_{12} = \frac{1}{(RC)^2} \frac{r}{c}$$

$$\text{Opamp: } A(s) \approx A_0 \frac{\omega_0}{s} = \frac{GB}{s}$$

G.B.: Gain-Bandwidth Pr.

$$\Rightarrow \left| T(s) = \frac{k \frac{1}{(RC)^2} \frac{r}{c}}{\left(s^2 + s \frac{1}{RC} \left[1 + r + \frac{1}{c} \right] + \frac{1}{(RC)^2} \frac{r}{c} \right) \left(1 + s \frac{k}{GB} \right) - s \frac{1}{RC} \frac{k}{c}} \right|$$

Approx:

Solution:

$$\left| T(s) \approx \frac{k \frac{1}{(RC)^2} \frac{r}{c}}{\left(1 + s \frac{k}{GB} \right) \left(s^2 \left[1 + \frac{k^2}{GB^2 RC c} \right] + s \frac{1}{RC} \left[1 + r - \frac{(k-1)}{c} \right] + \frac{1}{(RC)^2} \frac{r}{c} \right)} \right|$$

$$\text{Poles: } \text{neg. real: } \left| \omega_{p1} \approx \frac{GB}{k} \right|$$

complex:


$$\left| \omega_p \approx \frac{1}{RC} \sqrt{\frac{r}{c}} \left(1 - \frac{k^2}{2 GB^2 RC c} \right) \right|$$

$$\left| Q_p \approx \frac{\sqrt{rc}}{c(1+r) - (k-1)} \left(1 + \frac{k^2}{2 GB^2 RC c} \right) \right|$$

$$\left| \omega_p \approx \omega_{p0} \left(1 - \frac{k^2}{2 GB^2 RC c} \right) \right|$$

$$\left| Q_p \approx Q_{p0} \left(1 + \frac{k^2}{2 GB^2 RC c} \right) \right|$$


B) Sedra - Espinoza Bandpass Filter

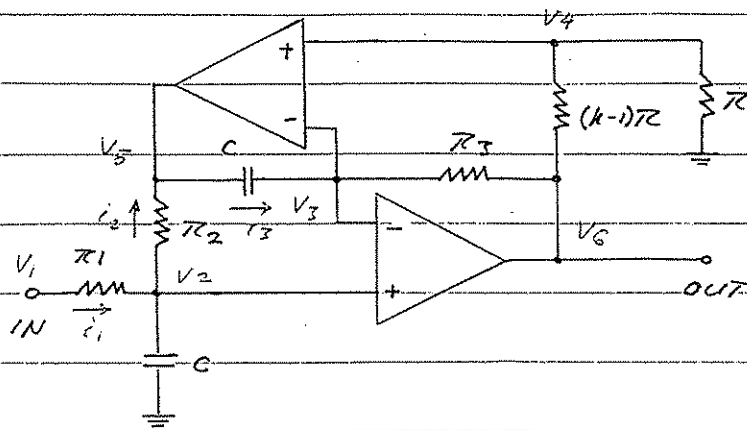

assumption: opamps are ideal

Thus $V_2 = V_3 = V_4$

SFG (for ideal opamps)

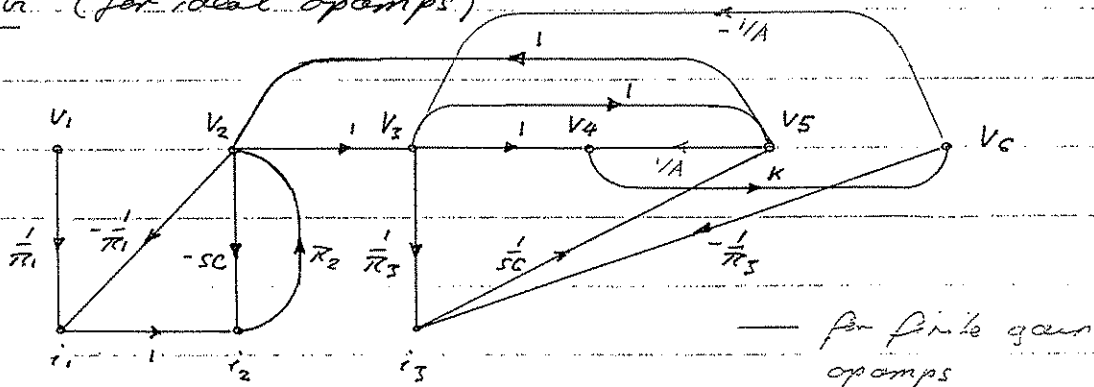

$$T_{16}(s) = \frac{V_6}{V_1} = \frac{k \cdot \frac{R_2}{R_1}}{1 + \frac{R_2}{R_1} + sCR_2 - 1 + \frac{k}{sCR_3} - \frac{1}{sCR_3}} \times \frac{s \frac{1}{CR_2}}{s \frac{1}{CR_2}}$$

$$= \frac{k \cdot s \frac{1}{R_1 C}}{s^2 + s \frac{1}{R_1 C} + \frac{(k-1)}{R_2 R_3 C^2}}$$

Note: k must be larger than 1 otherwise we obtain a 1st order lowpass ($k=1$) or else the element $(k-1)R$ becomes negative!

Filter Parameters:

Sensitivities:

$\omega_p = \sqrt{\frac{(k-1)}{\pi_2 \pi_3}} \cdot \frac{1}{C}$	Special Cases $k=2$ $\pi_2 = \pi_3 = \pi$	$S_{\pi_2}^{\omega_p} = S_{\pi_3}^{\omega_p} = -\frac{1}{2}$
$Q_p = \pi_1 \sqrt{\frac{(k-1)}{\pi_2 \pi_3}}$	$\omega_p = \frac{1}{\pi C}$	$S_{\pi_1}^{Q_p} = 1$
$\bar{T}(s=j\omega_p) = k$	$Q_p = \frac{\pi_1}{\pi}$	$S_{\pi_2}^{Q_p} = S_{\pi_3}^{Q_p} = -\frac{1}{2}$

Influence of amplifier gain-bandwidth product:

$$\bar{T}_{16} = \frac{k \cdot s \cdot \frac{1}{\pi_1 C} \left[1 + \frac{1}{s \pi_5 C} \frac{1}{A} \right]}{s^2 + s \frac{1}{\pi_1 C} + \frac{(k-1)}{\pi_2 \pi_3 C^2} + \frac{k}{A} \left[\frac{s}{\pi_1 C} + \frac{s}{\pi_2 C} + s^2 \right]}$$

Replacing $A(s)$ by $\frac{A_0 \omega_0}{s} = \frac{GB}{s}$ yields:

$$\begin{aligned} \bar{T}_{16} &= \frac{k \cdot s \cdot \frac{1}{\pi_1 C} \left[1 + \frac{1}{GB \pi_5 C} \right]}{s^2 \frac{k}{GB} + s^2 \left[1 + \frac{k}{GB} \left(\frac{1}{\pi_1 C} + \frac{1}{\pi_2 C} \right) \right] + s \frac{1}{\pi_1 C} + \frac{(k-1)}{\pi_2 \pi_3 C^2}} \\ &\approx \frac{k \cdot s \cdot \frac{1}{\pi_1 C} \left[1 + \frac{1}{GB \pi_5 C} \right]}{(s \frac{k}{GB} + 1) \left(s^2 \left[1 + \frac{k}{GB} \frac{1}{\pi_2 C} \right] + s \left[\frac{1}{\pi_1 C} - \frac{k(k-1)}{GB \pi_2 \pi_3 C^2} \right] + \frac{(k-1)}{\pi_2 \pi_3 C^2} \right)} \end{aligned}$$

Poles: $\left| \omega_{p3} \approx \frac{k}{GB} \right|$ neg. real pole

Special case:

$$\omega_p \approx \sqrt{\frac{(k-1)}{\pi_2 \pi_3}} \cdot \frac{1}{C} \left(1 - \frac{1}{2} \frac{k}{GB \pi_2 C} \right)$$

Complex
pole-pair

$$Q_p \approx \pi_1 \sqrt{\frac{(k-1)}{\pi_2 \pi_3}} \left(1 + \frac{1}{2} \frac{k}{GB \pi_2 C} \left[1 - 2(k-1) \frac{\pi_1}{\pi_3} \right] \right)$$

$$\begin{aligned} k=2 \\ \pi_2 = \pi_3 = \pi \\ \pi_1 = Q_p \pi \end{aligned}$$


 $\Rightarrow$

$$\begin{aligned} \omega_p &= \omega_{p0} \left(1 - \frac{\omega_{p0}}{GB} \right) \\ Q_p &= Q_{p0} \left(1 + \frac{\omega_{p0}}{GB} \left[1 - 2Q_{p0} \right] \right) \end{aligned}$$

MOSFET-C Filters


Example: Integrator

RC-active Implementation

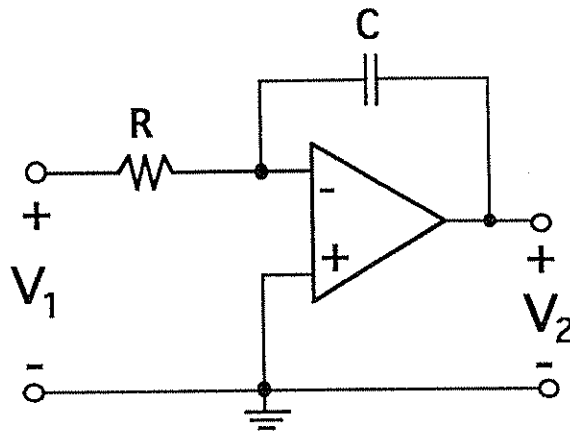

$$T(s) = - \frac{1}{s RC}$$

MOSFET-C Implementation

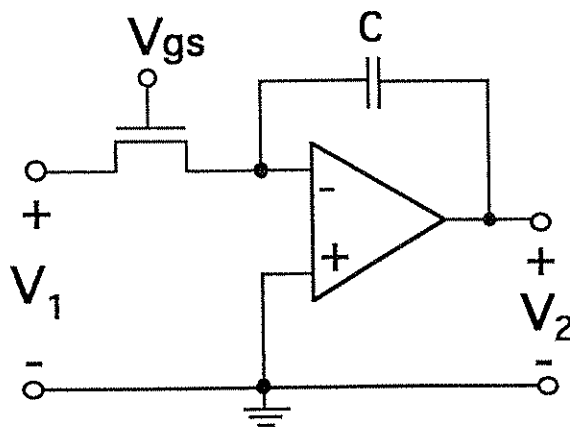

$$T(s) = - \frac{g_{ds}}{s C}$$

where:

$$g_{ds} \cong \mu C_{ox} \frac{W}{L} [V_{gs} - V_T - V_{ds}]$$

RC-Active Filters

Properties

- Many filter topologies available
- Few active elements (op-amps)
- Excellent linearity and dynamic range (90dB)
- Frequency limited by op-amps (low MHz range)
- Passive elements require significant chip area (R_s : 10-100 Ω C' : 0.25-1fF/ μm^2)
- Poor control over RC product (20%-60% variation)
- Discrete tuning possible (e.g. by employing C-arrays)

MOSFET-C Filters

Properties

- Few op-amps required
- Area efficient implementation of resistors
- Filter topologies limited (due to tuning)
- Frequency limited by op-amps (low MHz range)
- Poor linearity (due to nonlinearity of MOSFET resistors)
- MOSFET resistors require tuning
- Additional circuitry for automatic tuning

Transconductance-C (Ota-C) Filters

Properties

- Well-suited for high-frequency applications (<100MHz)
- Filter topologies limited (due to tuning)
- Many transconductance elements required
- Limited dynamic range (due to Ota nonlinearities)
- Transconductance elements require tuning
- Additional circuitry for automatic tuning

Comparison

Filter Type	Accuracy	Dynamic Range	Impl. Cost	Frequency Range
RC-Active	20%-60%	90dB	low	< 1MHz
MOSFET-C	approx. 1%	60dB	medium	< 1MHz
Transcond.-C	approx. 1%	60dB	medium	< 100MHz

2. Transconductance Elements

Voltage Controlled Current Source

Special Requirements

- High input impedance ($>M\Omega$)
- High output impedance ($>M\Omega$)
- Large input voltage swing (e.g. $1V_{p-p}$)
- Good linearity over entire range
- Wide bandwidth ($<100MHz$)
- Transconductance electrically tunable
- Wide tuning range

Basic Implementation

MOS Transistor

Major Drawback

Poor Linearity


Remedies

Fully-differential implementation


Additional compensating circuitry

Fully-differential transconductance element

Symbol

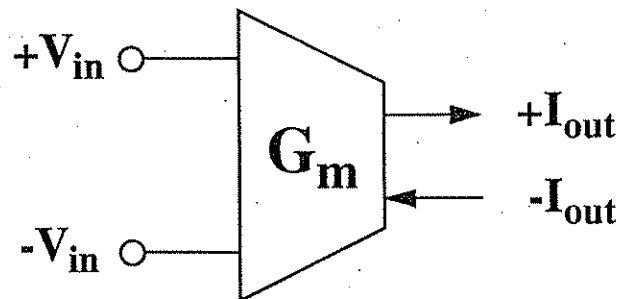


Implementation by CS Pair

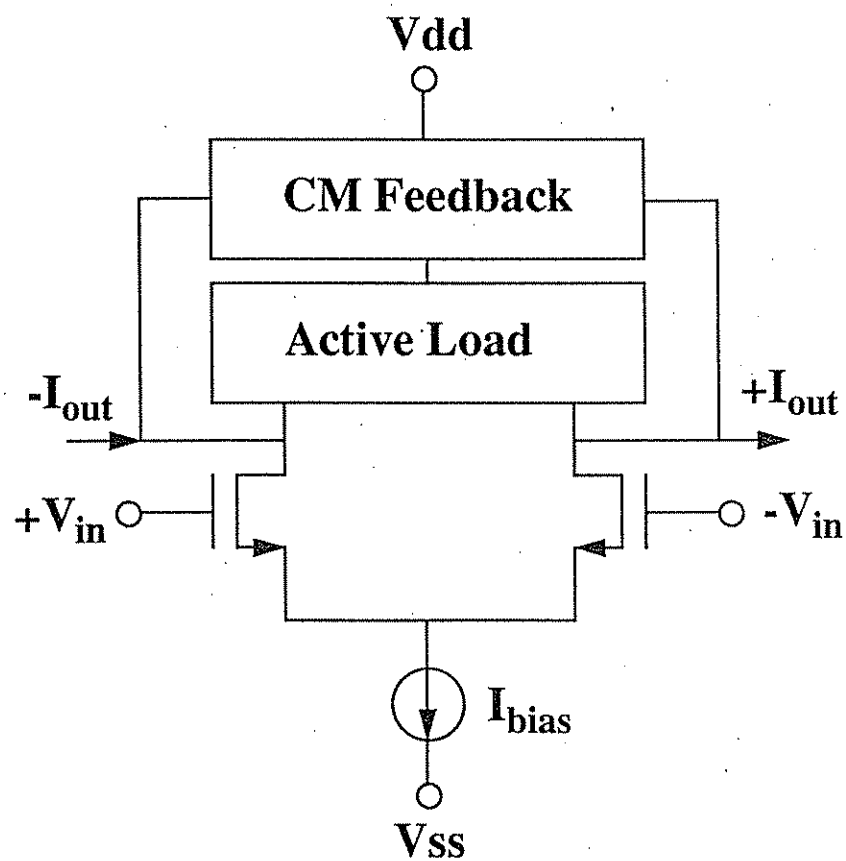


Fully-Differential Transconductance Amplifier

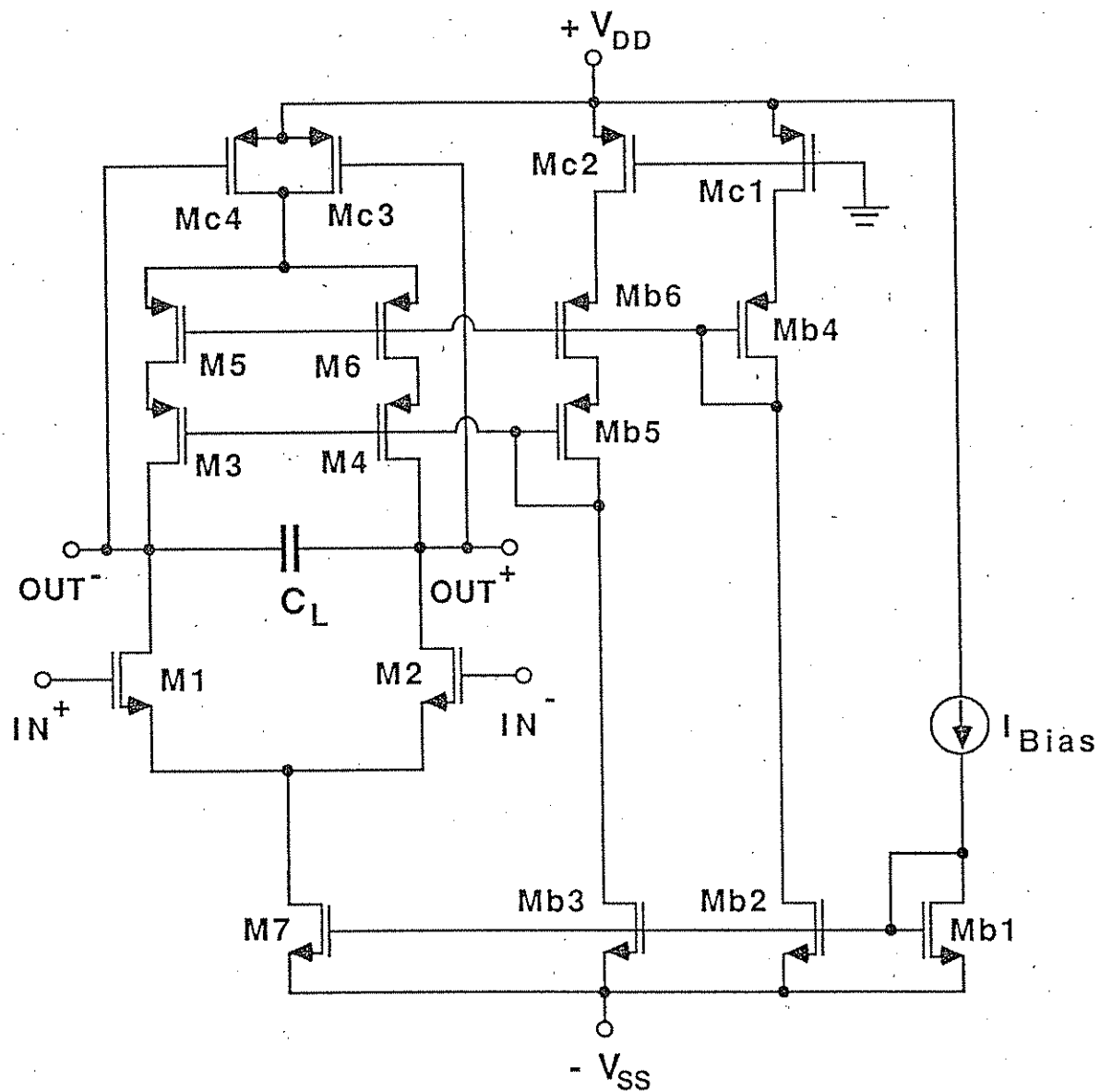Version 0: Simple Source-Coupled Differential Pair




$$G_M = \frac{1}{2} g_{m1}$$

IX-16

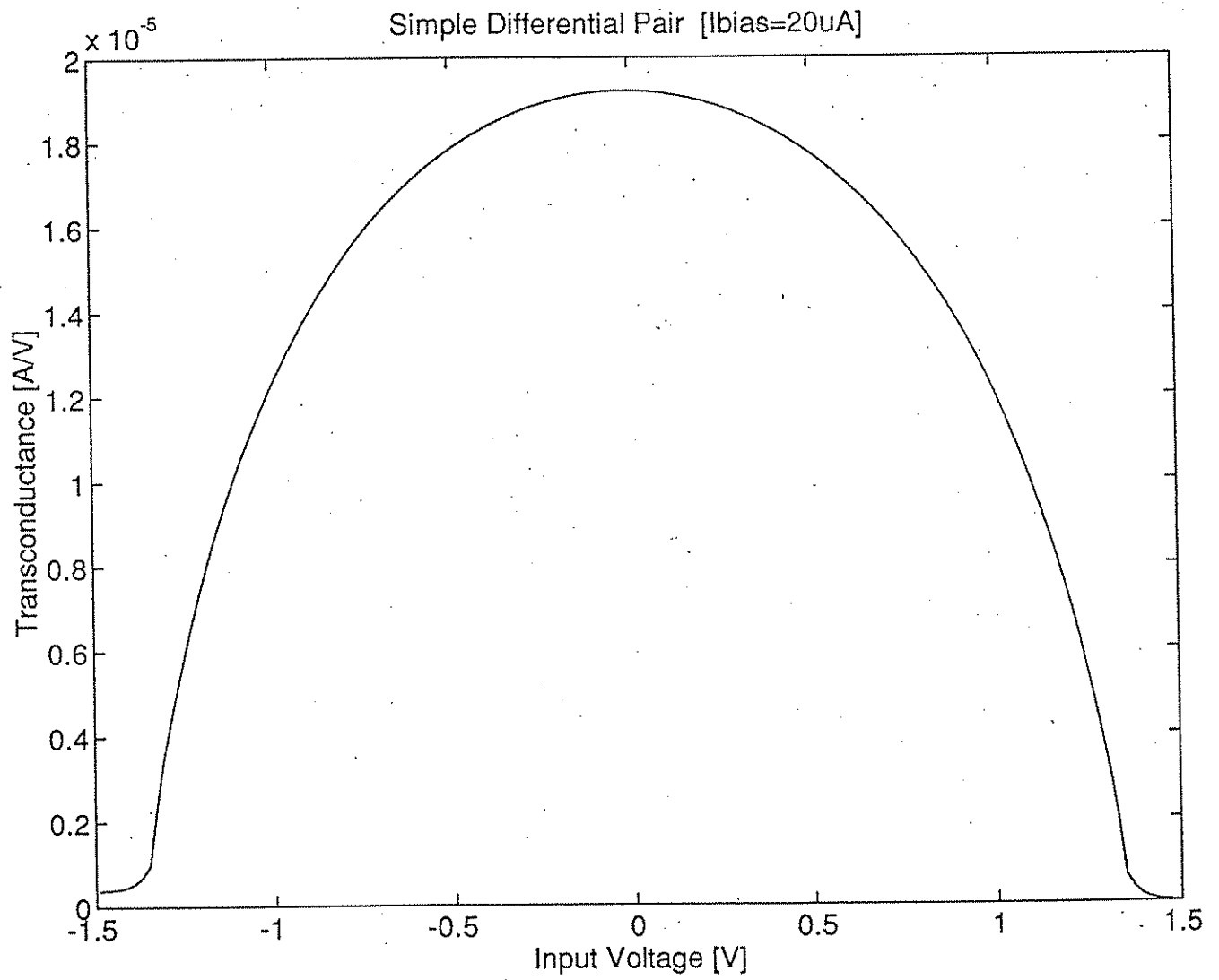


Fully-Differential Transconductance Amplifier

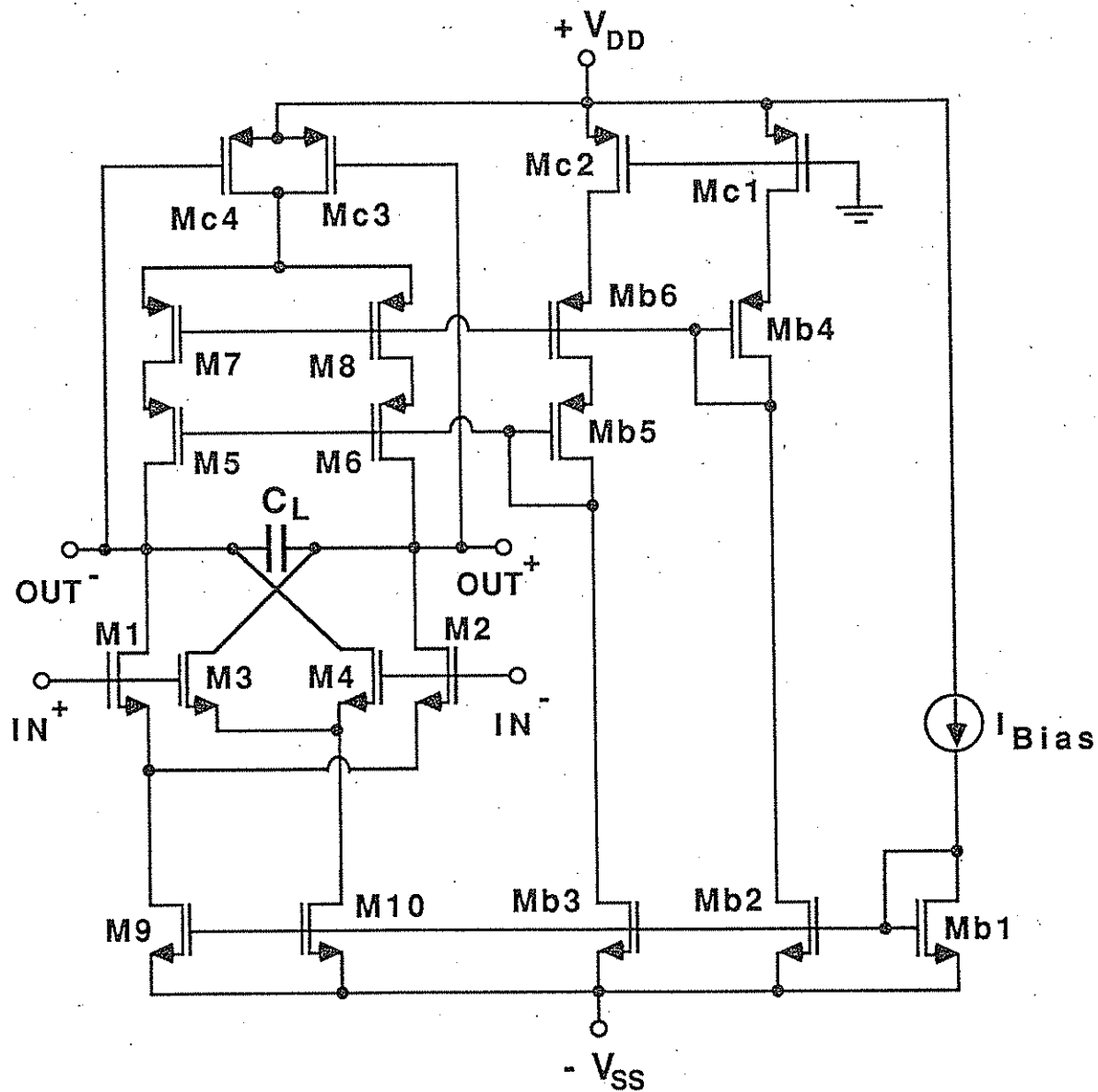Version1: Differential Pair with Cross-Coupled Inputs




$$G_M = \frac{1}{2} (g_{m1} - g_{m3})$$

IX-18

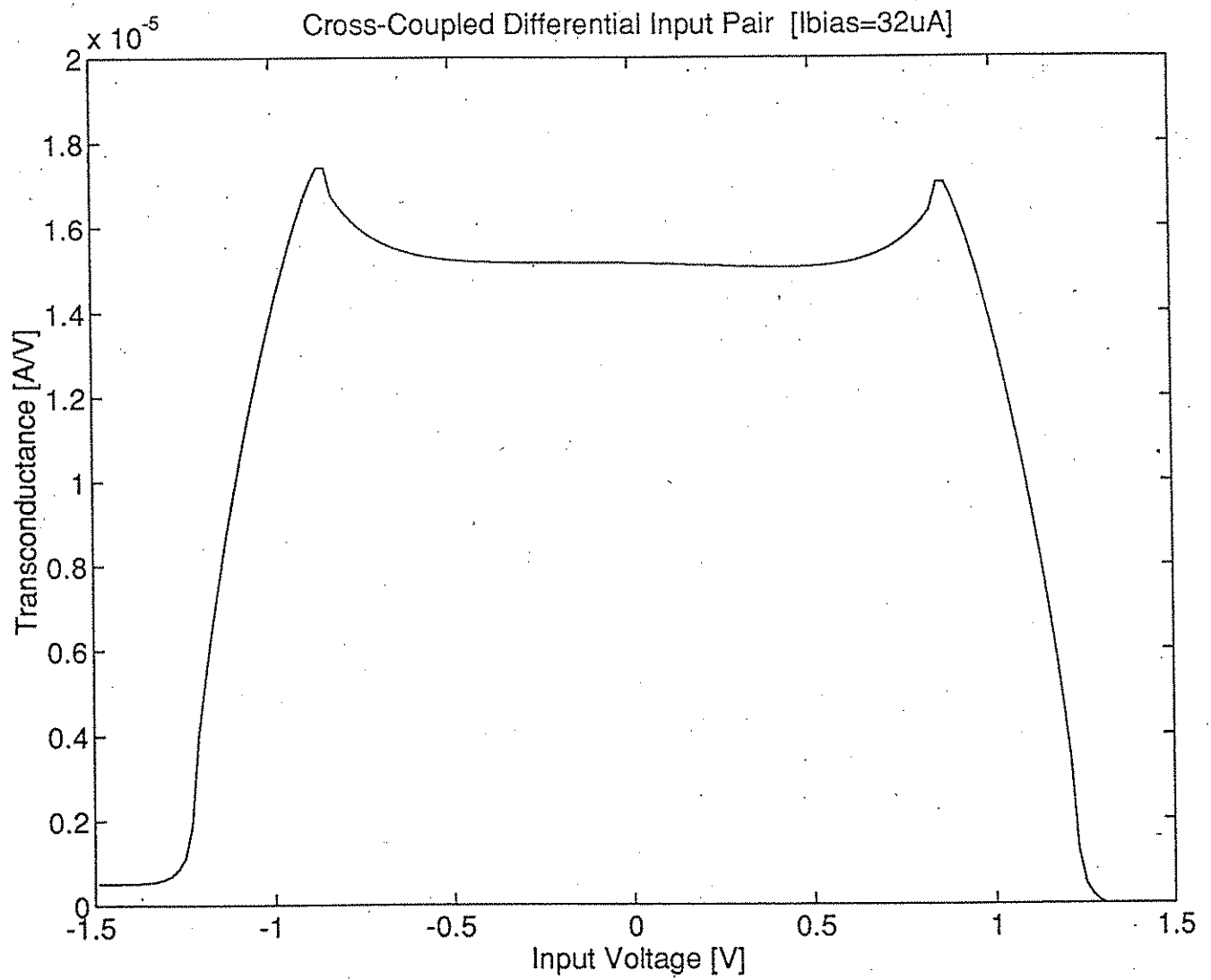

Fully-Differential Transconductance Amplifier

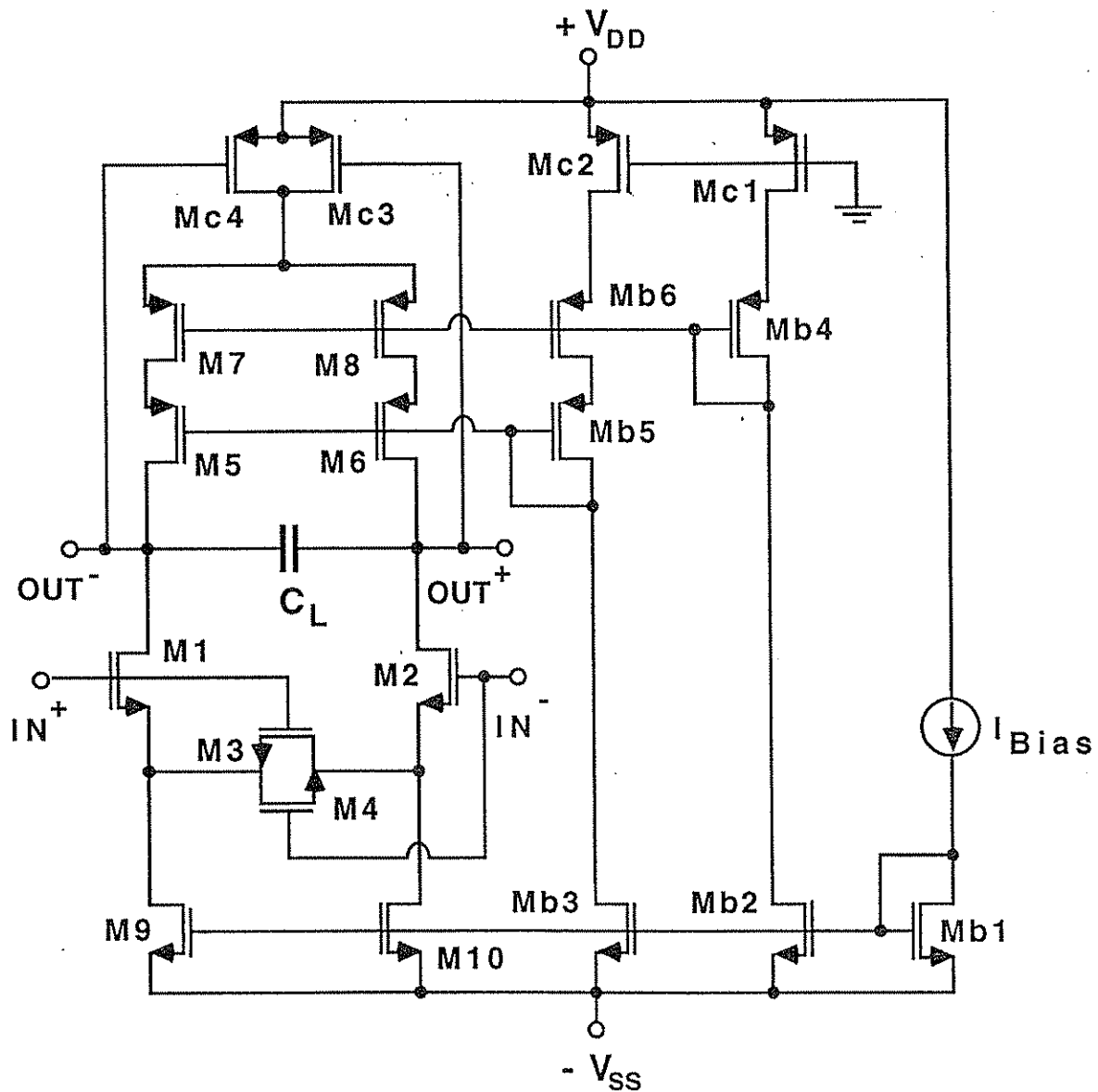
Version2: Differential Pair with Source Degeneration Devices



$$G_M = \frac{g_{m1}}{2 + g_{m1}/(g_{d3} + g_{d4})}$$

FULLY-DIFFERENTIAL TRANSCONDUCTANCE AMPLIFIER
20-OCT93 15:19:16

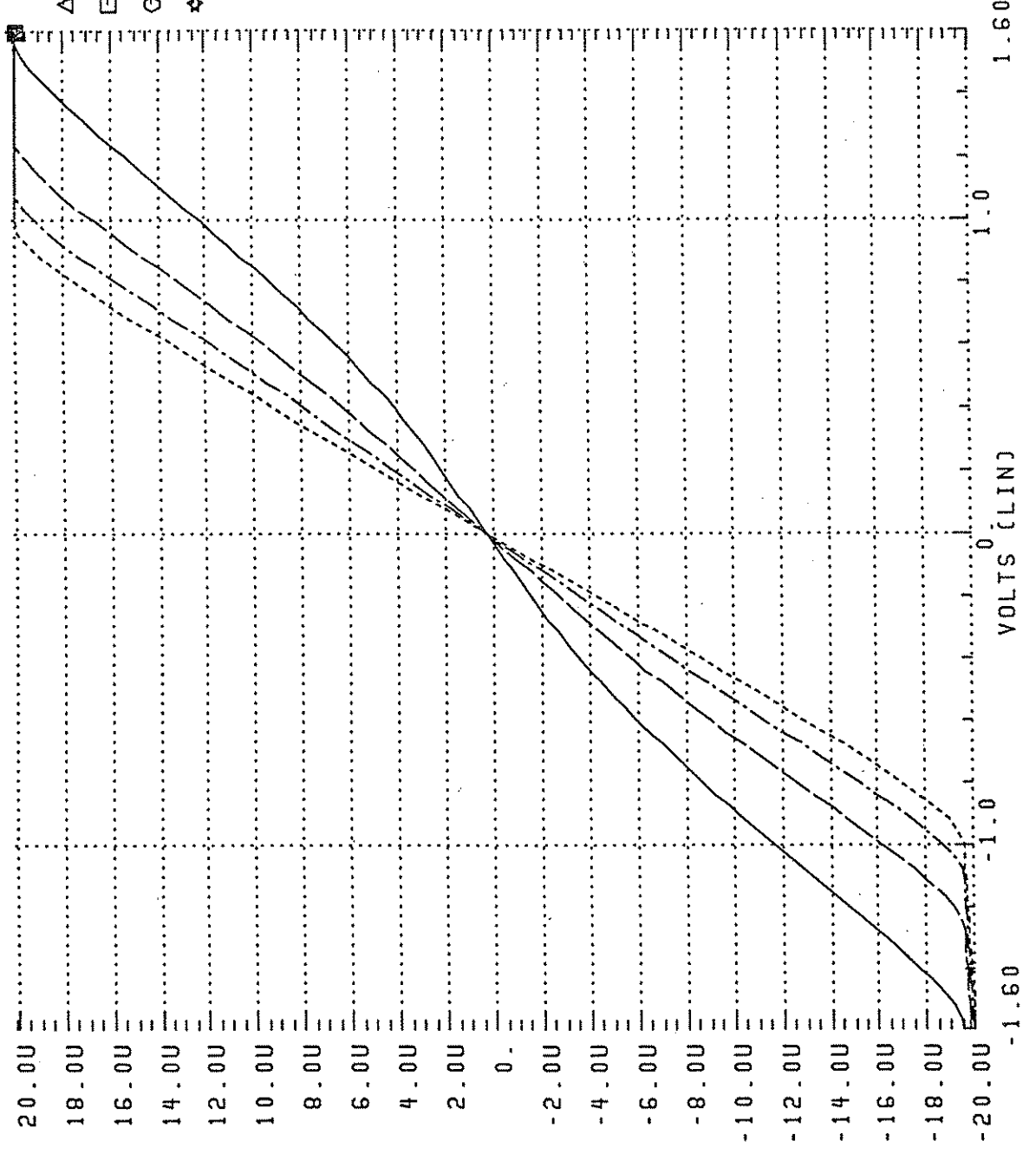
TRANSC5PAR.1
ICV1 $W_3 = 2 \mu m$
ICV2 $W_3 = 1 \mu m$
ICV3 $W_3 = 4 \mu m$
ICV4 $W_3 = 5 \mu m$



I_{OUT} ↑


AMP LIN

IX-21

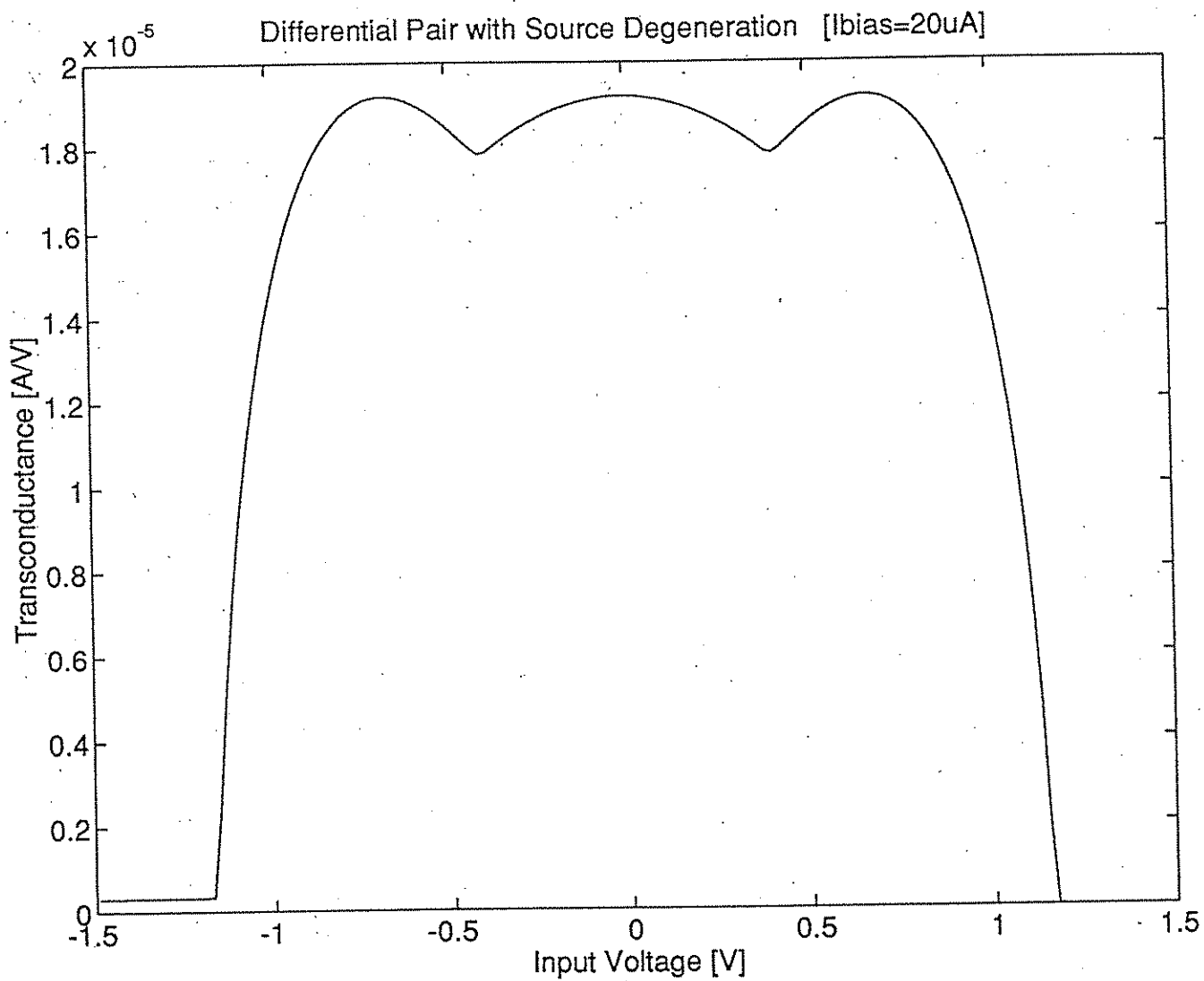

Fully-Differential Transconductance Amplifier

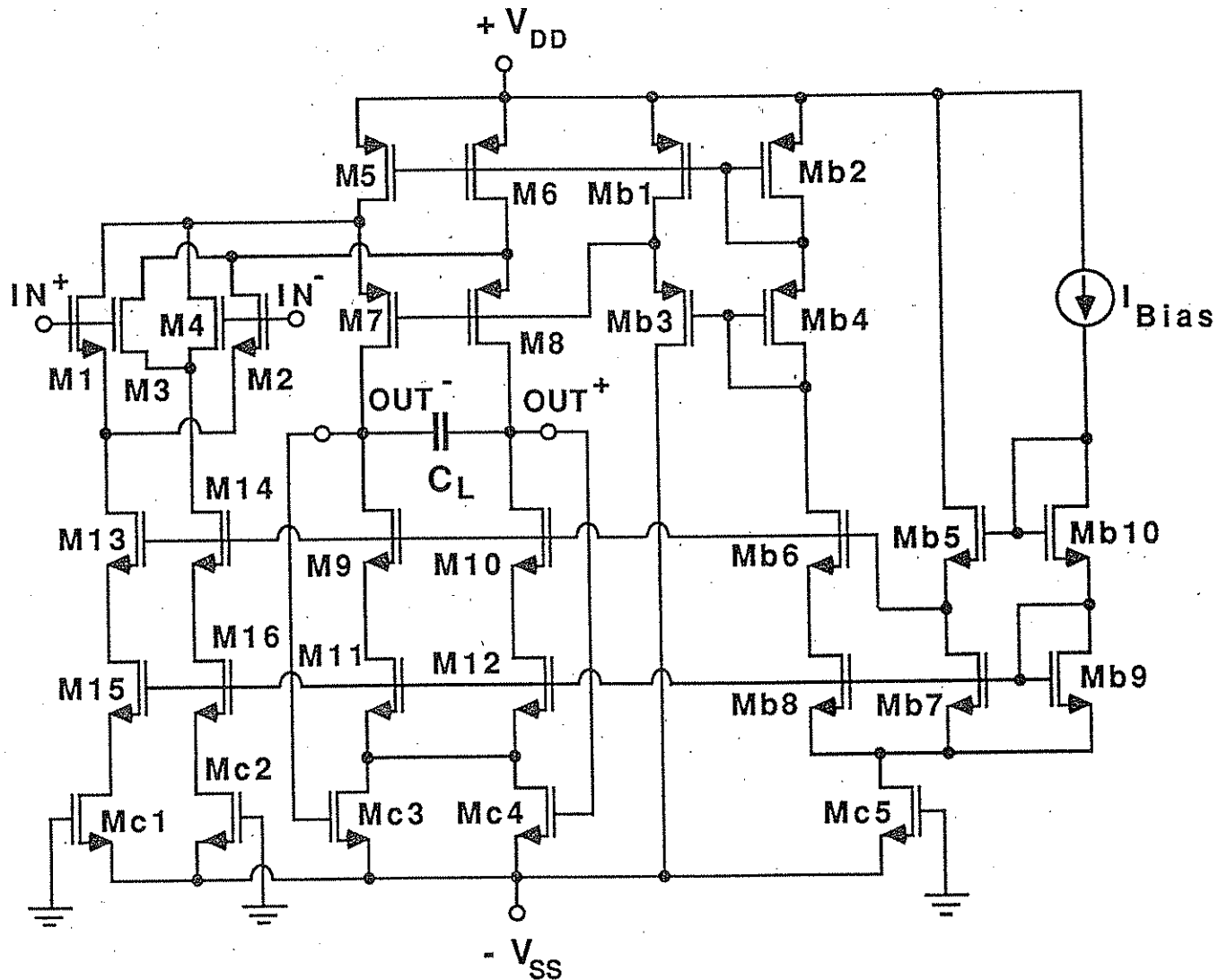
Version3: Folded Cascode with Cross-Coupled Inputs



$$G_M = \frac{1}{2} (g_{m1} - g_{m3})$$

Fully-Differential Transconductance Amplifier

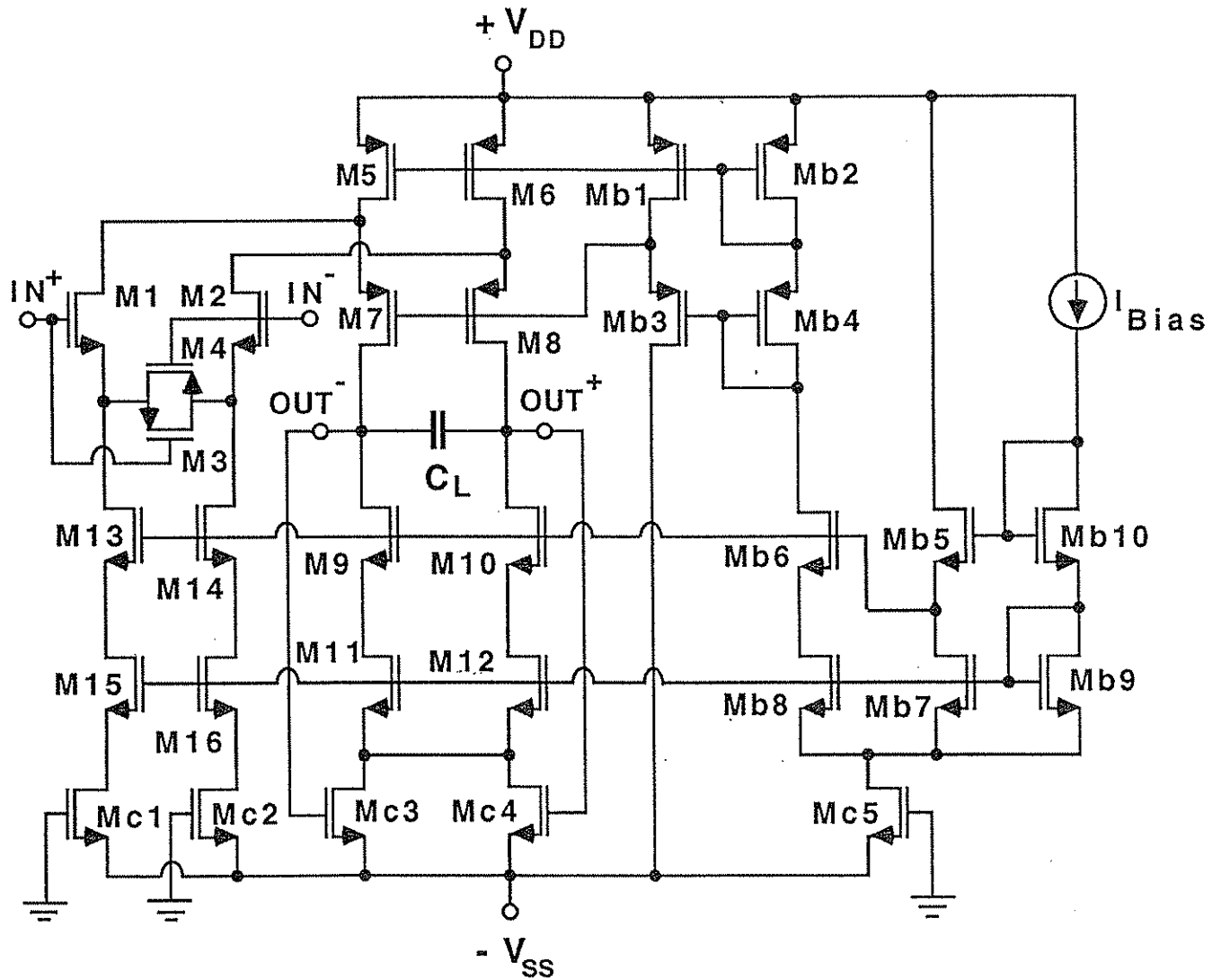Version4: Folded Cascode with Source Degeneration Devices




$$G_M = \frac{g_{m1}}{2 + g_{m1}/(g_{d3} + g_{d4})}$$

3. Filter Topologies

Basic building block

Ota-C Integrator

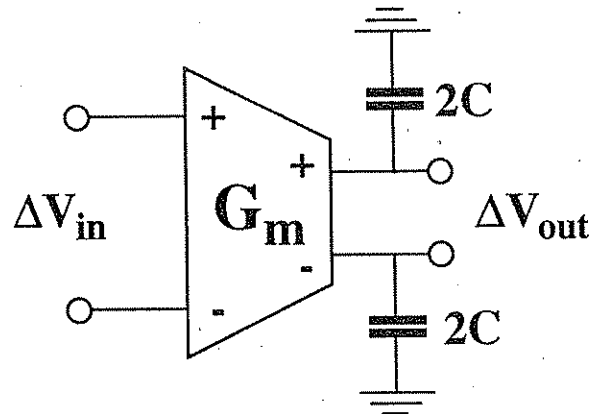


$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{G_m}{sC}$$

State-variable filter topologies


State-Variable Biquadratic Filters

General 2nd order Configuration

a) Block Diagram representation:

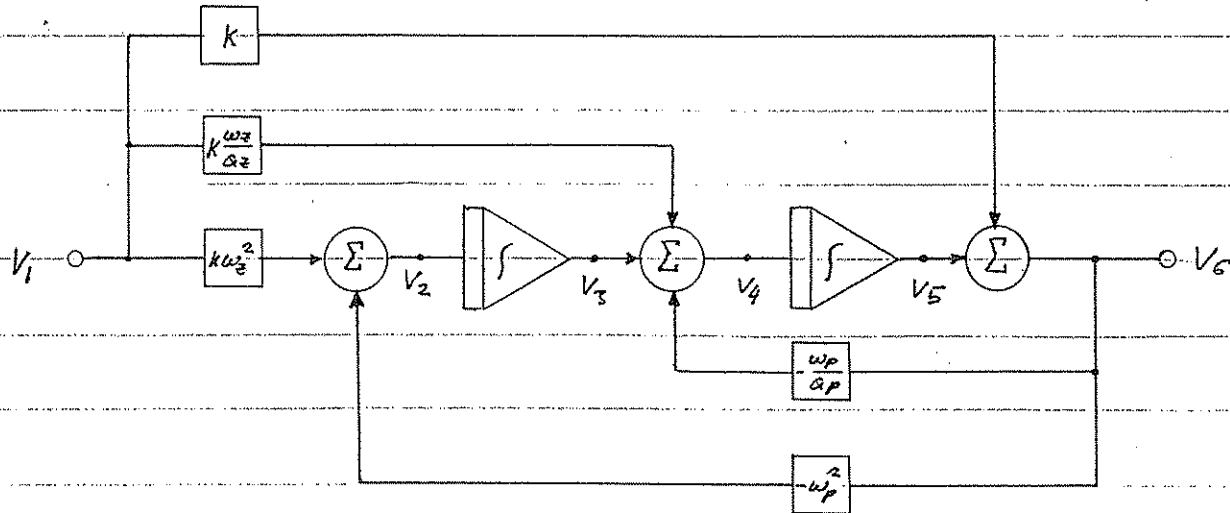

b) SFG representation: (in s-domain)

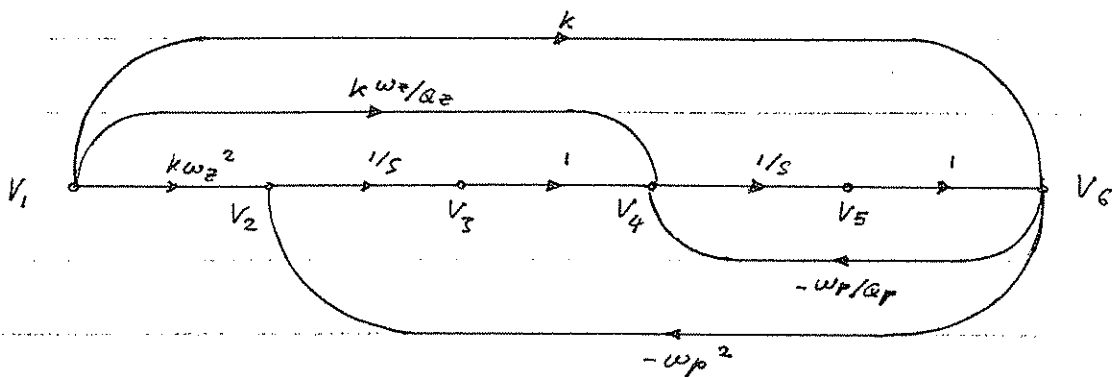

c) Voltage Transfer Function:

$$T_{16}(s) = \frac{V_6(s)}{V_1(s)} = k \frac{s^2 + s \omega_z/a_z + \omega_z^2}{s^2 + s \omega_p/a_p + \omega_p^2}$$

State-Variable Systems

The state space method is based on the description of system eq. in terms of n 1st order differential (or difference) equations, which may be combined into a 1st order vector matrix equation.

For linear, time-invariant systems, the state equation and the output equation are given by

$$\dot{\bar{x}}(t) = [A] \bar{x}(t) + [B] u(t)$$

$$\bar{y}(t) = [C] \bar{x}(t) + [D] u(t)$$

where:

$\bar{x}(t)$: state variable vector

$\bar{y}(t)$: output variable vector

$u(t)$: input vector

Example:

$$\begin{cases} \dot{x}_1 = a_1 x_1 + b_1 u \\ \dot{x}_2 = a_2 x_1 + a_3 x_2 + b_2 u \\ y = x_2 + b_5 u \end{cases}$$

where:

$$\bar{x} = (x_1, x_2)$$

$$\bar{y} = (y, 0)$$

$$\bar{u} = (u, 0)$$


$$[A] = \begin{bmatrix} 0 & a_1 \\ a_2 & a_3 \end{bmatrix}$$

$$[B] = \begin{bmatrix} a_1 b_1 + b_1 & 0 \\ a_3 b_1 + b_2 & 0 \end{bmatrix}$$

$$[C] = \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix}$$

$$[D] = \begin{bmatrix} b_5 & 0 \\ 0 & 0 \end{bmatrix}$$

2nd Order Ota-C Lowpass/Bandpass Filter

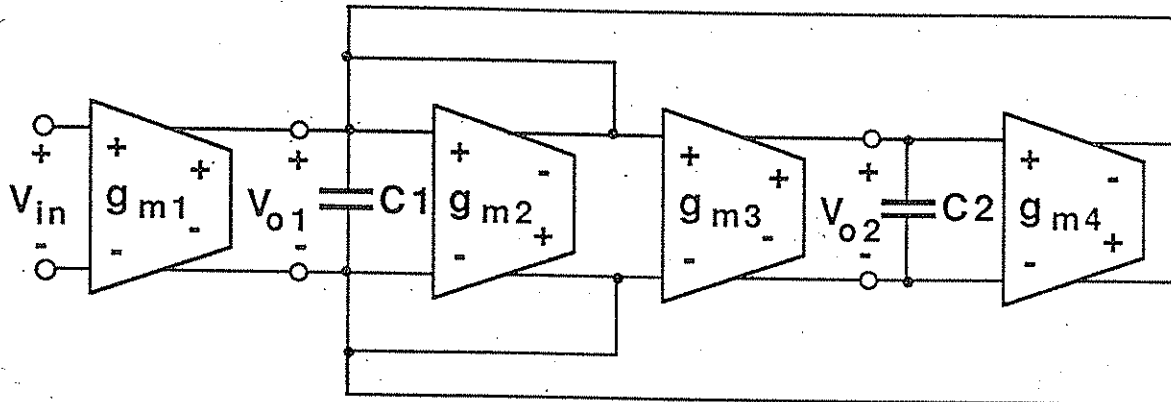

V_{o1} : Bandpass Output

V_{o2} : Lowpass Output

Pole Locations:

$$\omega_p = \sqrt{\frac{g_{m3}g_{m4}}{C_1 C_2}}$$

$$Q_p = \sqrt{\frac{g_{m3}g_{m4}C_1}{C_2}} \frac{1}{g_{m2}}$$

2nd Order OTA-C Lowpass / Bandpass Filter

a) Ideal System (R_{out} of OTA's are infinite)

Equations:

$$(1) \quad V_{o1} = V_{in} \frac{g_{m1}}{sC_1} - V_{o1} \frac{g_{m2}}{sC_1} - V_{o2} \frac{g_{m4}}{sC_1}$$

$$(2) \quad V_{o2} = V_{o1} \frac{g_{m3}}{sC_2}$$

(2) into (1) $\therefore V_{o1} = V_{in} \frac{\frac{g_{m1}}{sC_1}}{(1 + \frac{g_{m2}}{sC_1} + \frac{g_{m3}g_{m4}}{s^2C_1C_2})}$

Transfer functions:

$$\left| \begin{aligned} \frac{V_{o1}}{V_{in}} &= \frac{s \frac{g_{m1}}{C_1}}{s^2 + s \frac{g_{m2}}{C_1} + \frac{g_{m3}g_{m4}}{C_1C_2}} \right| & 2^{\text{nd}} \text{ order BP} \\ \frac{V_{o2}}{V_{in}} &= \frac{\frac{g_{m1}g_{m3}}{C_1C_2}}{s^2 + s \frac{g_{m2}}{C_1} + \frac{g_{m3}g_{m4}}{C_1C_2}} \right| & 2^{\text{nd}} \text{ order LP} \end{aligned}$$

Poles:

$$\left| \begin{aligned} \omega_p &= \sqrt{\frac{g_{m3}g_{m4}}{C_1C_2}} \\ Q_p &= \sqrt{\frac{C_1}{C_2}} \cdot \frac{\sqrt{g_{m3}g_{m4}}}{g_{m2}} \end{aligned} \right|$$

Trimming: use g_{m3} and g_{m4} for ω_p

use g_{m2} for Q_p

[illegible]
$$\frac{V_{o1}}{V_i} = \frac{\frac{g_{m1}}{C_1} (s + \frac{g_2}{C_2})}{s^2 + s \frac{g_{m2}}{C_1} [1 + \frac{g_1}{g_{m2}} + \frac{g_2 C_1}{g_{m2} C_2}] + \frac{g_{m3} g_{m4}}{C_1 C_2} [1 + \frac{g_{m2} g_2 + g_1 g_2}{g_{m3} g_{m4}}]}$$

$$\frac{V_{o2}}{V_i} = \frac{\frac{g_{m1} g_{m3}}{C_1 C_2}}{s^2 + s \frac{g_{m2}}{C_1} [1 + \frac{g_1}{g_{m2}} + \frac{g_2 C_1}{g_{m2} C_2}] + \frac{g_{m3} g_{m4}}{C_1 C_2} [1 + \frac{g_{m2} g_2 + g_1 g_2}{g_{m3} g_{m4}}]}$$

$$\omega_p = \sqrt{\frac{g_{m3} g_{m4}}{C_1 C_2}} \sqrt{1 + \frac{g_{m2} g_2 + g_1 g_2}{g_{m3} g_{m4}}}$$

$$Q_p = \sqrt{\frac{g_{m3} g_{m4}}{g_{m2}^2} \frac{C_1}{C_2}} \frac{\sqrt{1 + \frac{g_{m2} g_2 + g_1 g_2}{g_{m3} g_{m4}}}}{1 + \frac{g_1}{g_{m2}} + \frac{g_2}{g_{m2}} \frac{C_1}{C_2}}$$

$$If \quad g_1, g_2 \ll g_m$$

$$\text{If } \frac{g_i}{g_m} = \varepsilon \ll 1 \quad i=1, 2$$


$$\omega_p \approx \sqrt{\frac{g_{m3} g_{m4}}{C1 C2}}$$

$$\omega_p = \omega_{p0L} (1 + \frac{1}{2} \epsilon)$$

$$Q_p = Q_{p0L} (1 - \frac{3}{2} \epsilon)$$


Filter Tuning

Direct Tuning

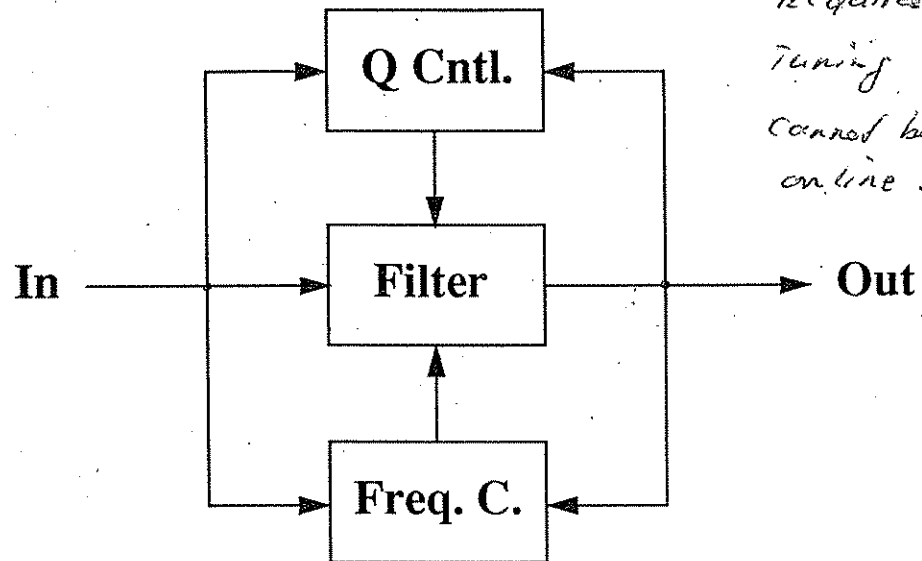

*Requires separate
tuning cycle!
cannot be done
online!*


Master-Slave Tuning

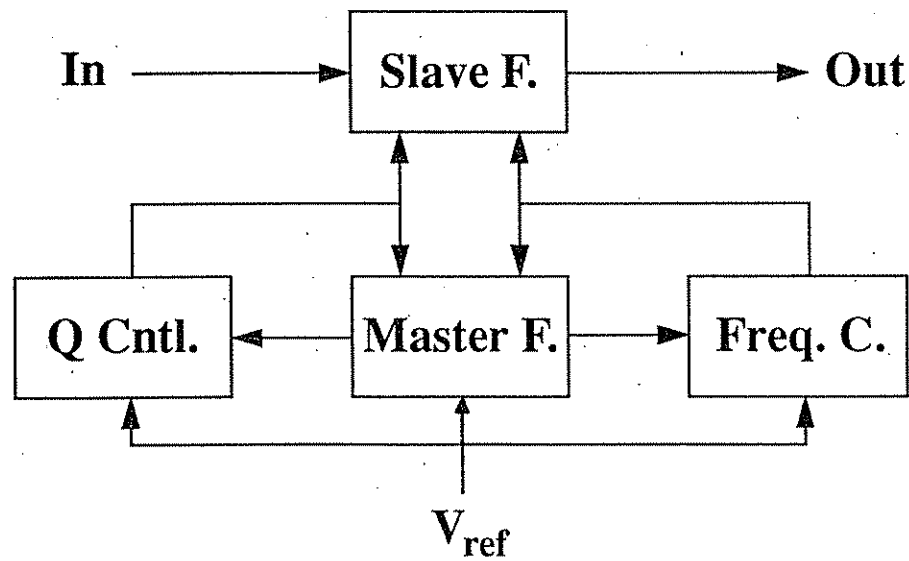

4. Simulation Results

Test Circuit

2nd Order Bandpass

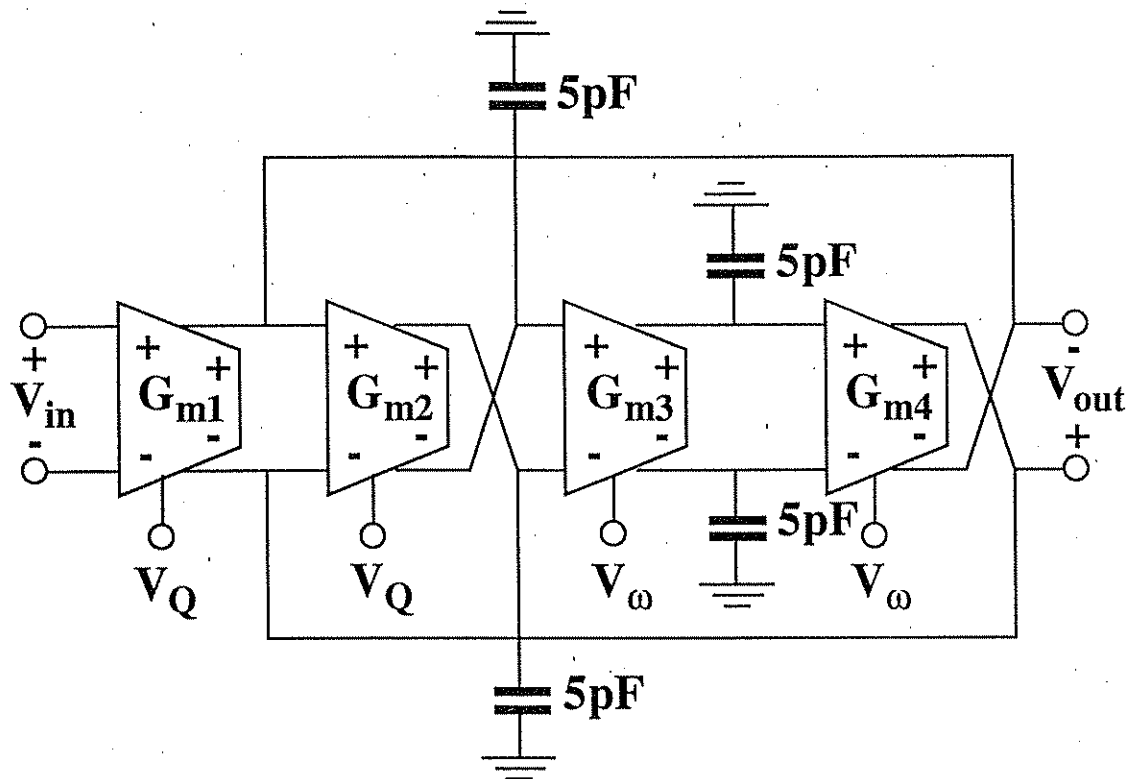



nominal bias: $G_{mi}=16\mu A/V$ $i=1,2,3,4$

$$\omega_p=2\pi*1MHz$$

$$Q_p=1$$

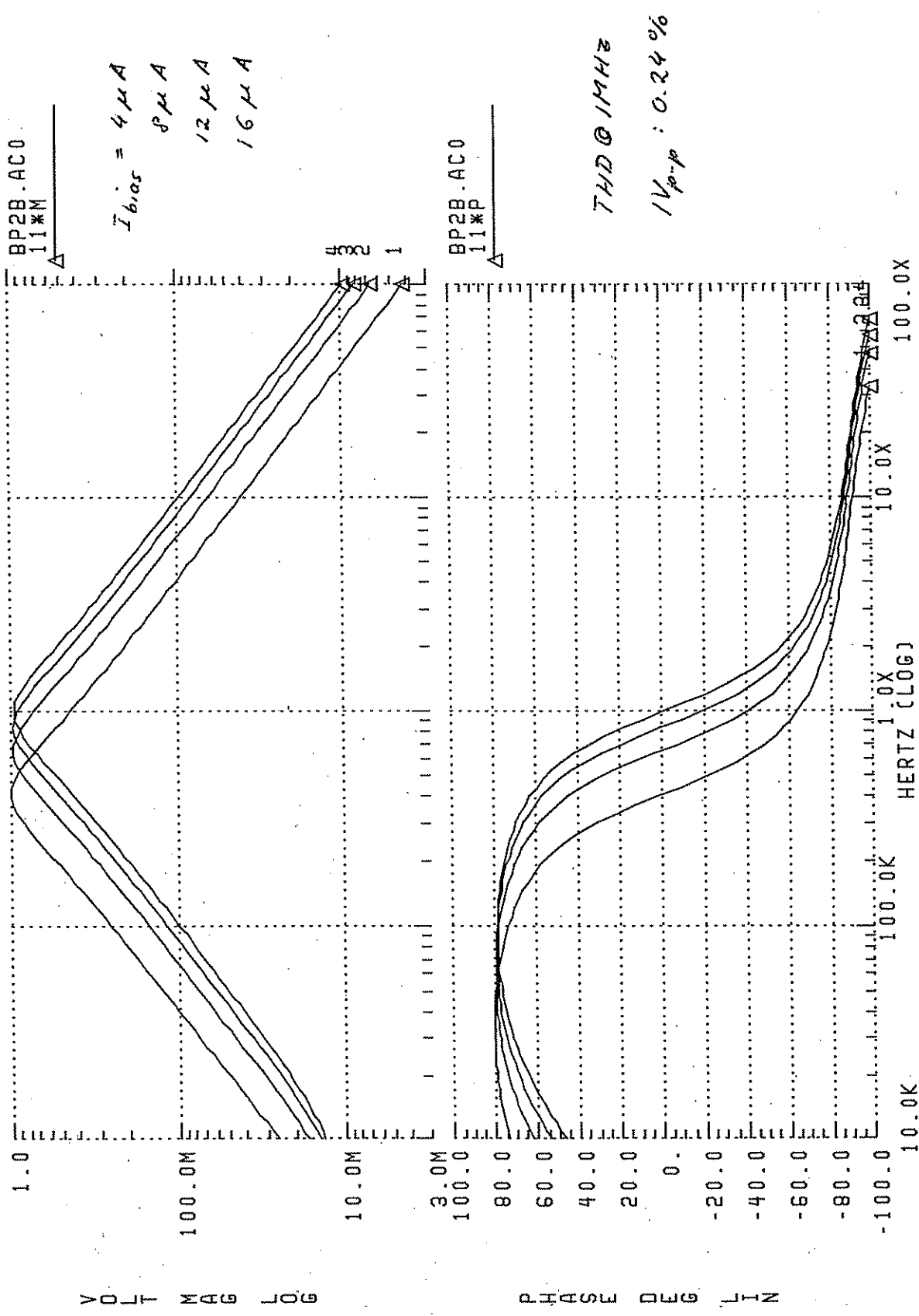
2ND ORDER OTA-C BANDPASS CIRCUIT 25-NOV93 12:21:47



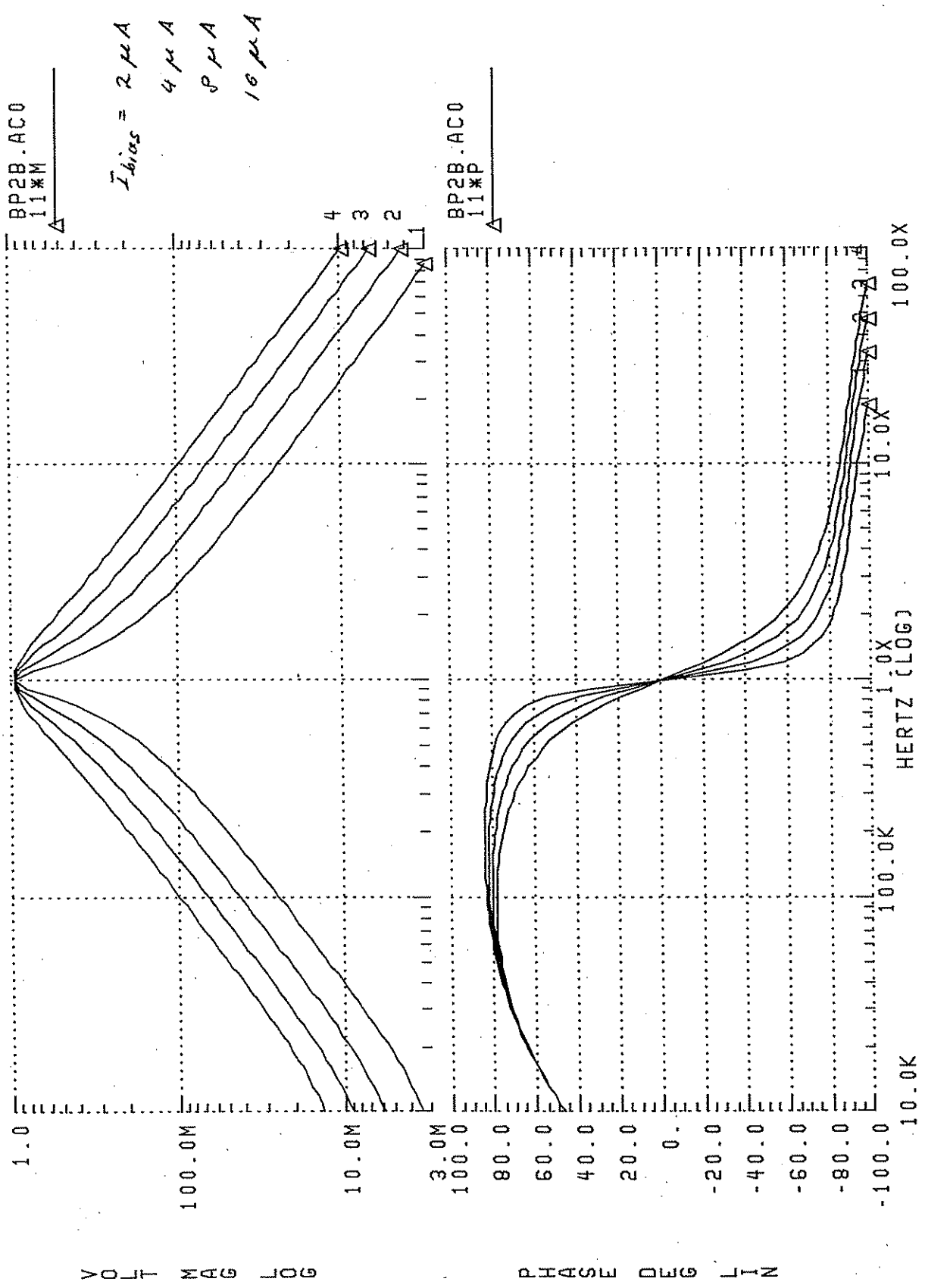

6th Order Ota-C Lowpass Filter


Passband Response

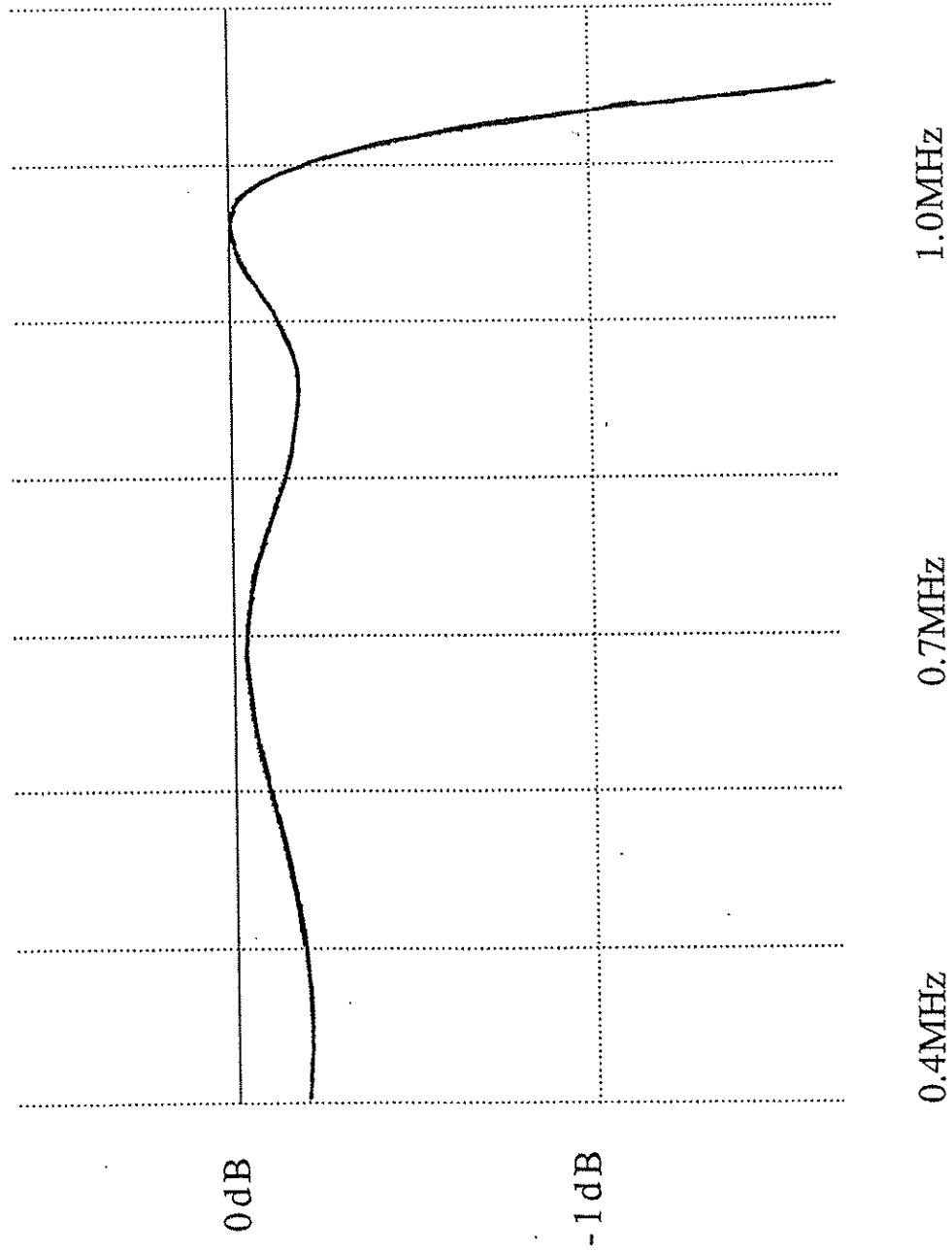


IX-34

Filter Tuning Range

Ib1=4 μ m, Ib2=16 μ m, Ib3=24 μ m,

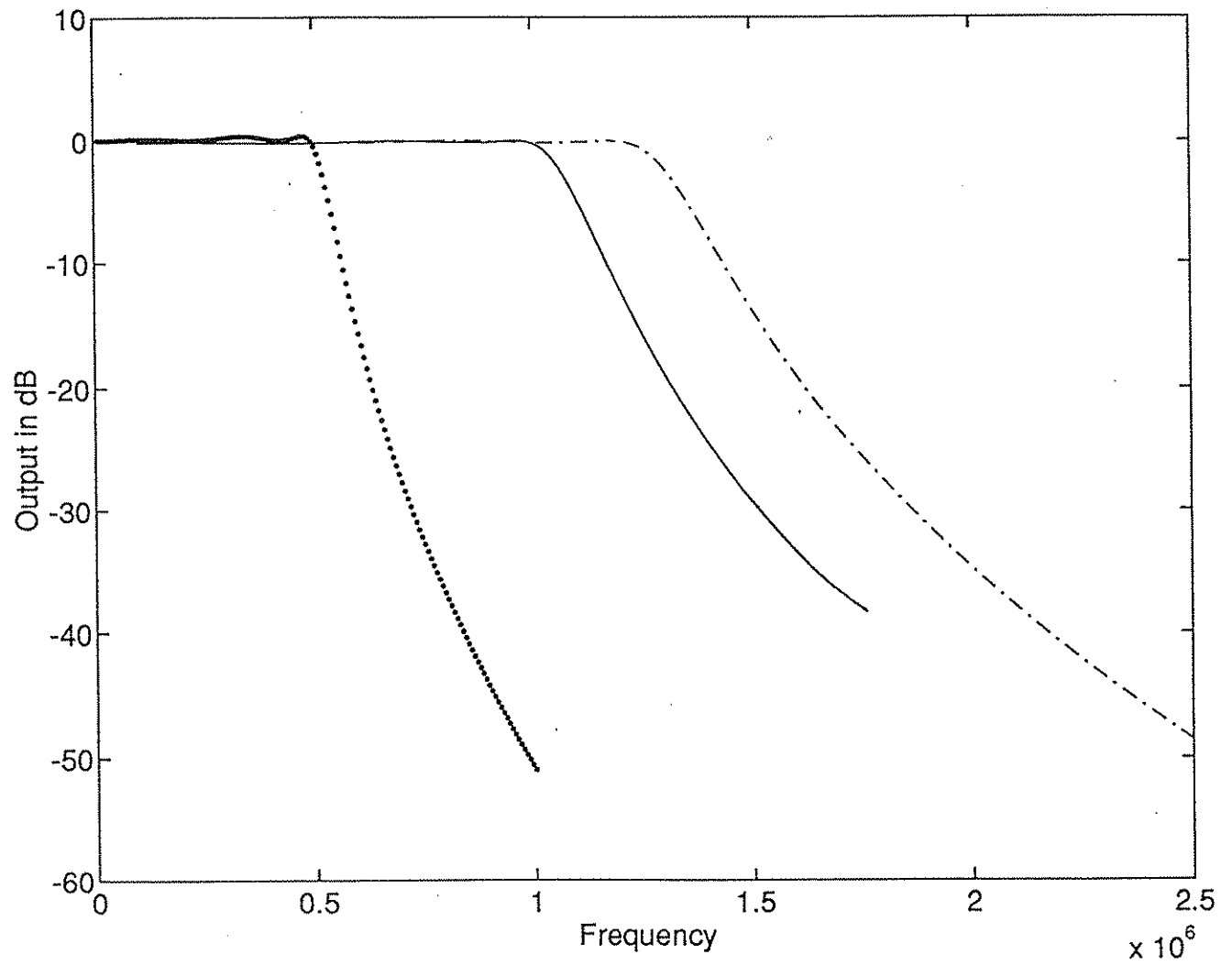


Swing Limitation

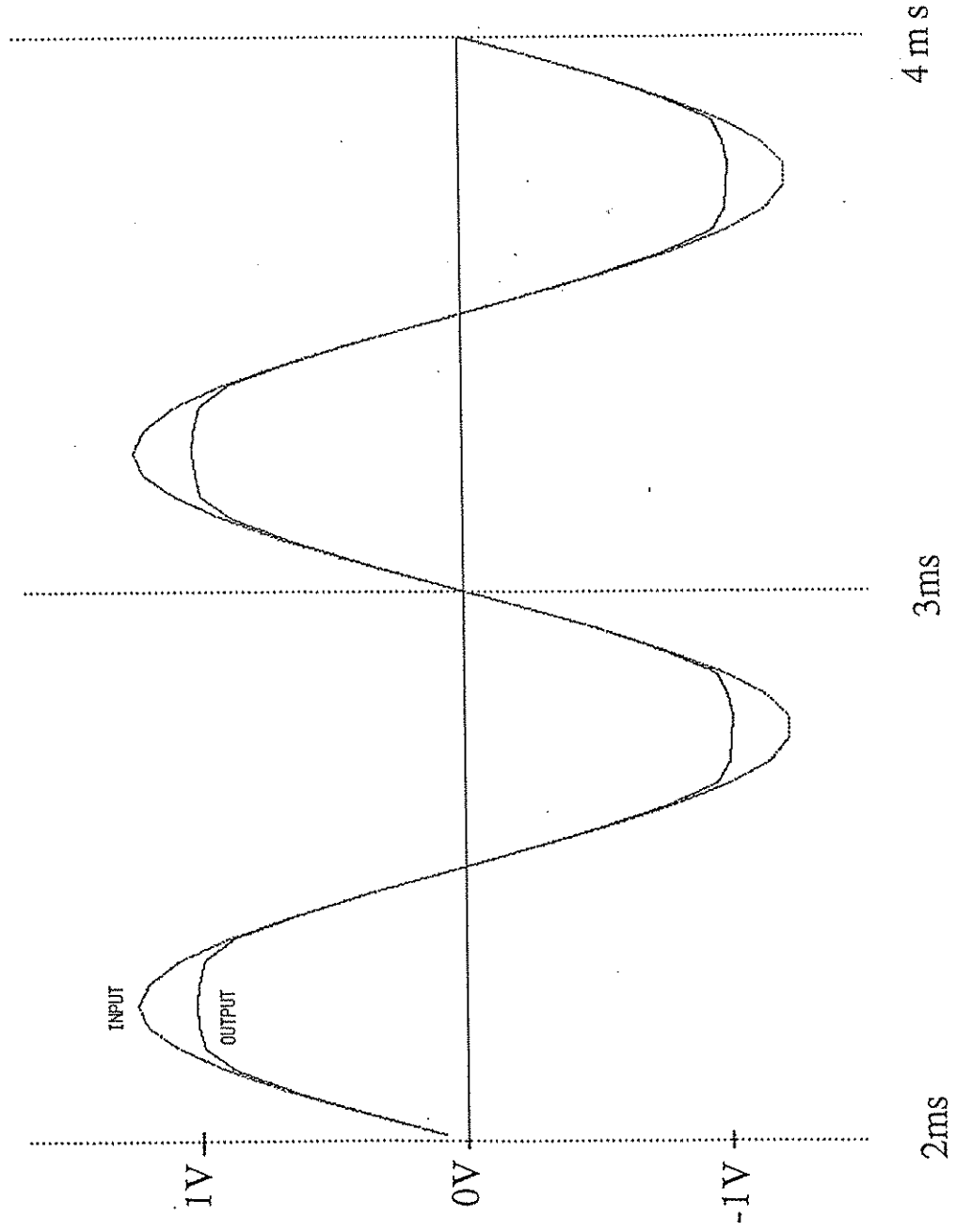

5. Layout of Prototype Filter

Transconductance Element (1.2 μm CMOS)

(size: 85 μm x 88 μm)

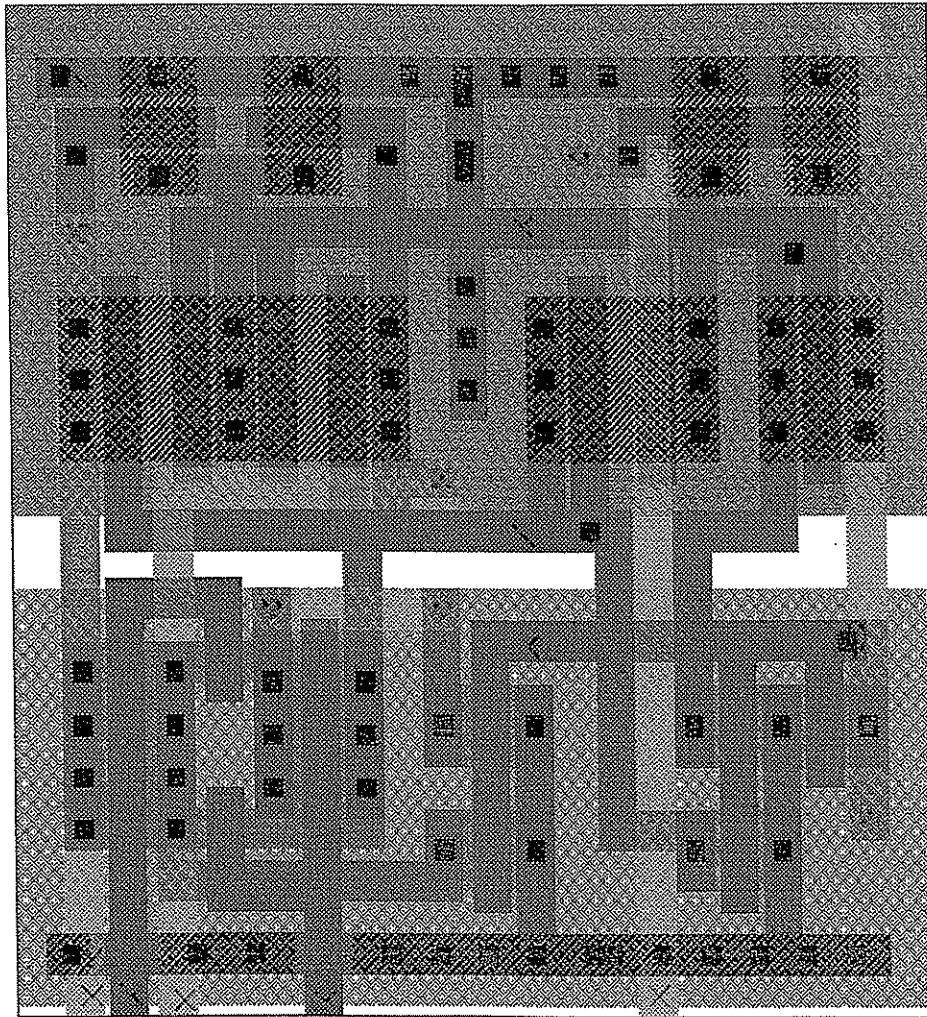

6. Conclusions

- Simple design procedure (for state variable topologies)
- Power and area efficient filter implementation
- Well suited for high frequency applications ($\omega_p = G_m/C$)
- Dynamic range limited by transconductors (Large input swing $\rightarrow$ THD $<$ 60dB)
- Transconductors require tuning
- Accuracy depending on device matching (for on-line master-slave tuning)
- Additional circuitry for automatic tuning required