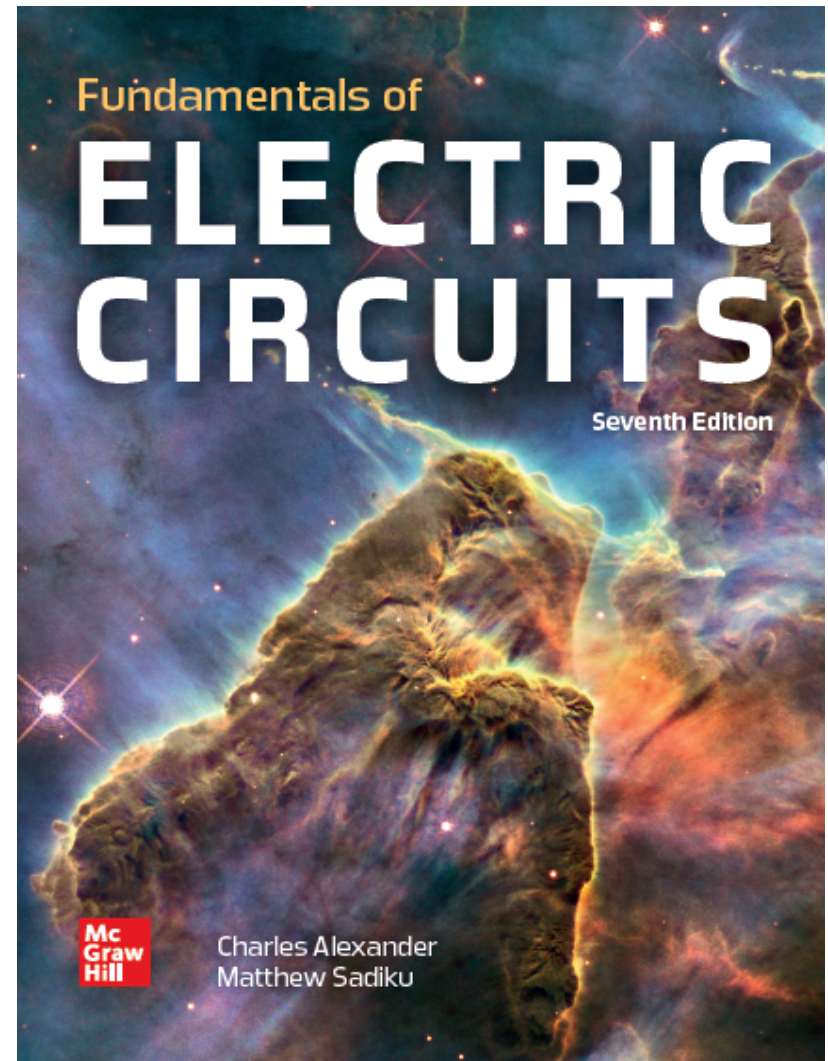


# Fundamentals of Electric Circuits

## Chapter 4

---



# Overview

- In this chapter, the concept of superposition will be introduced.
- Source transformation will also be covered.
- Thevenin and Norton's theorems will be covered.
- Examples of applications for these concepts will be presented.

# Linearity

- Linearity in a circuit means that as current is changed, the voltage changes proportionally.
- It also requires that the response of a circuit to a sum of sources will be the sum of the individual responses from each source separately.
- A resistor satisfies both of these criteria.

# Superposition

If there are two or more independent sources there are two ways to solve for the circuit parameters:

- Nodal or mesh analysis.
- Use superposition.

The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

# Applying Superposition

- Using superposition means applying one independent source at a time.
- Dependent sources are left alone.
- The steps are:
  1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using the techniques covered in Chapters 2 and 3.
  2. Repeat step 1 for each of the other independent sources.
  3. Find the total contribution by adding algebraically all the contributions due to the independent sources.


# Source Transformation

- Much like the delta-wye transformation, it is possible to transform a source from one form to another.
- This can be useful for simplifying circuits.
- The principle behind all of these transformations is equivalence.
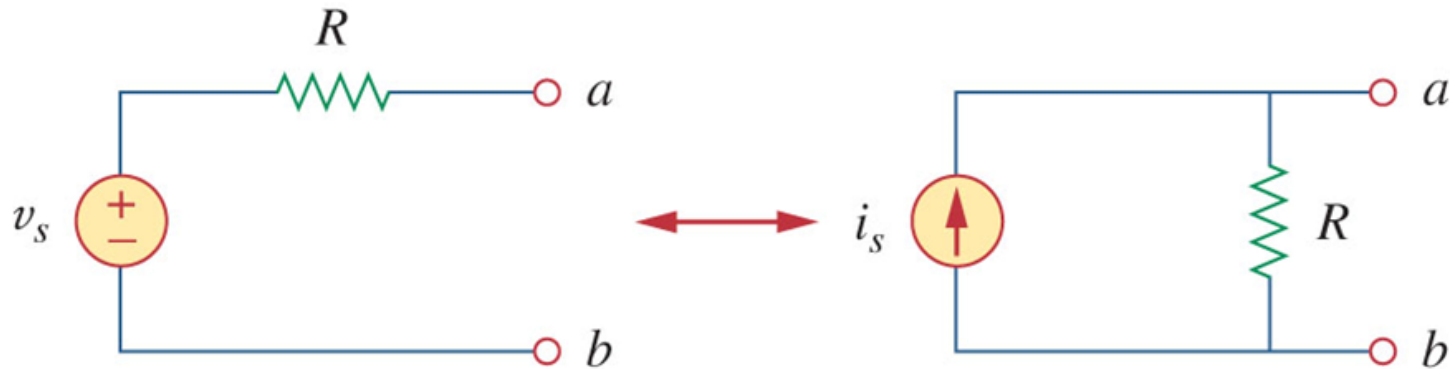
# Source Transformation II

- A source transformation is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Terminal Equivalency

- These transformations work because the two sources have equivalent behavior at their terminals.
- If the sources are turned off the resistance at the terminals are both  $R$ .
- If the terminals are short circuited, the currents need to be the same.
- From this we get the following requirement:


$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$


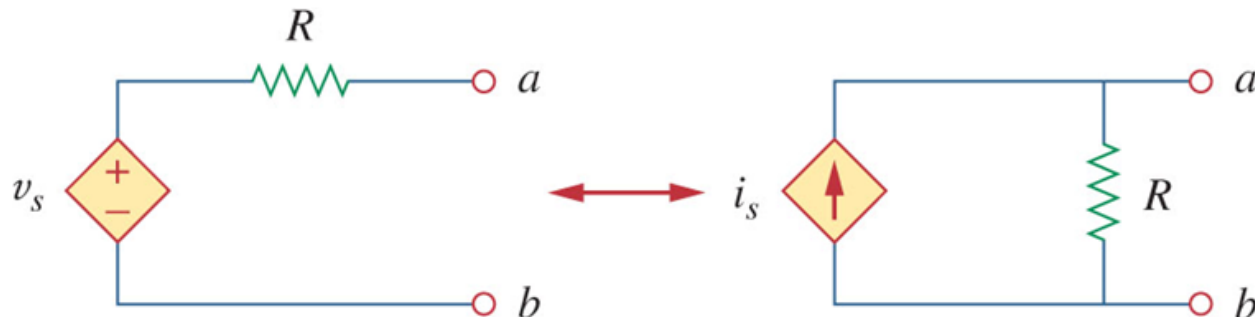
# Dependent Sources

- Source transformation also applies to dependent sources.
- But, the dependent variable must be handled carefully.
- The same relationship between the voltage and current holds here:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Source transformation rules

- Note that the arrow of the current source is directed towards the positive terminal of the voltage source.
- Source transformation is not possible when  $R = 0$  for an ideal voltage source.
- For a realistic source,  $R \neq 0$ .
- For an ideal current source,  $R = \infty$  also prevents the use of source transformation.


# Thevenin's Theorem

- In many circuits, one element will be variable.
- An example of this is mains power; many different appliances may be plugged into the outlet, each presenting a different resistance.
- This variable element is called the load.
- Ordinarily one would have to reanalyze the circuit for each change in the load.

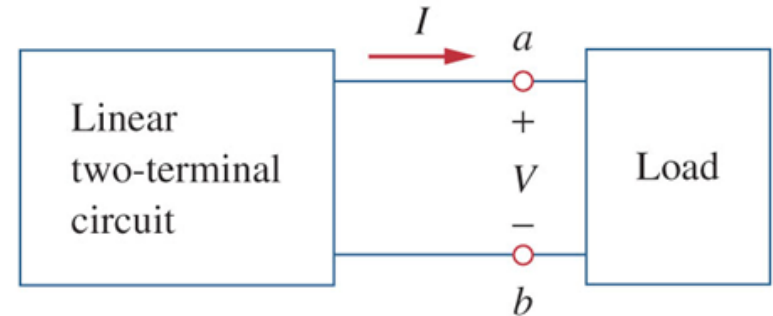
# Thevenin's Theorem II

- Thevenin's theorem states that a linear two terminal circuit may be replaced with a voltage source and resistor.
- The voltage source's value is equal to the open circuit voltage at the terminals.
- The resistance is equal to the resistance measured at the terminals when the independent sources are turned off.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

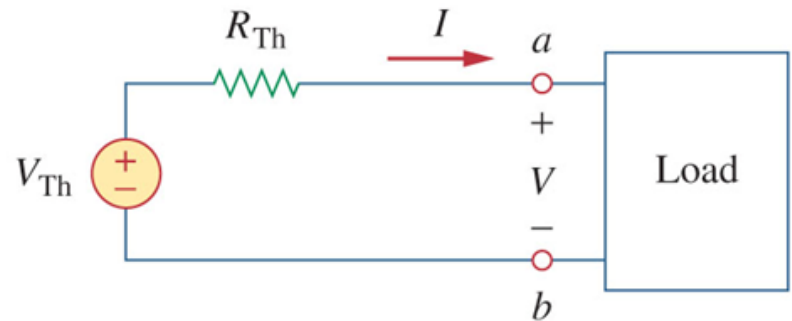


(b)
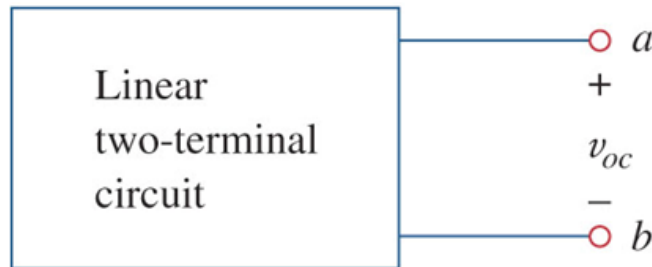
# Thevenin's Theorem III


- There are two cases to consider when finding the equivalent resistance.
- Case 1: If there are no dependent sources, then the resistance may be found by simply turning off all the sources.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$V_{Th} = v_{oc}$$

(a)

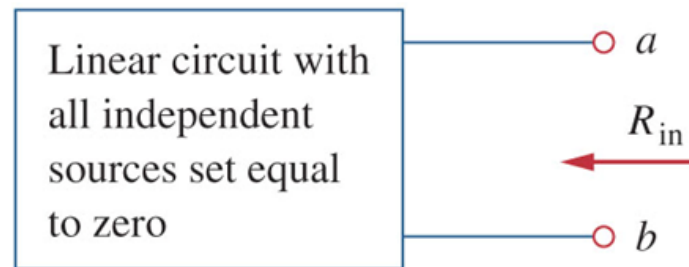


$$R_{Th} = R_{in}$$

(b)
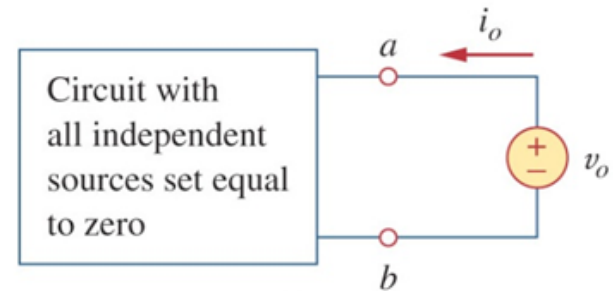
# Thevenin's Theorem IV


- Case 2: If there are dependent sources, we still turn off all the independent sources.
- Now apply a voltage  $v_o$  (or current  $i_o$ ) to the terminals and determine the current  $i_o$  (voltage  $v_o$ ).

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$R_{Th} = \frac{v_o}{i_o}$$

(a)

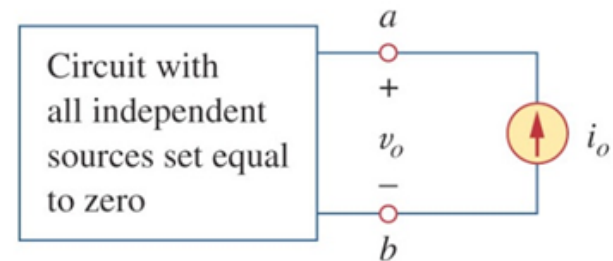

$$R_{Th} = \frac{v_o}{i_o}$$

(b)

# Thevenin's Theorem V

- Thevenin's theorem is very powerful in circuit analysis.
- It allows one to simplify a circuit.
- A large circuit may be replaced by a single independent voltage source and a single resistor.
- The equivalent circuit behaves externally exactly the same as the original circuit.

# Negative Resistance?


- It is possible for the result of this analysis to end up with a negative resistance.
- This implies the circuit is supplying power.
- This is reasonable with dependent sources.
- Note that in the end, the Thevenin equivalent makes working with variable loads much easier.
- Load current can be calculated with a voltage source and two series resistors.
- Load voltages use the voltage divider rule.



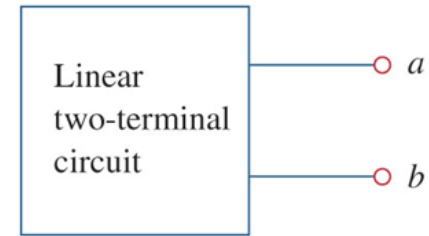
# Norton's Theorem

- Similar to Thevenin's theorem, Norton's theorem states that a linear two terminal circuit may be replaced with an equivalent circuit containing a resistor and a current source.
- The Norton resistance will be exactly the same as the Thevenin.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

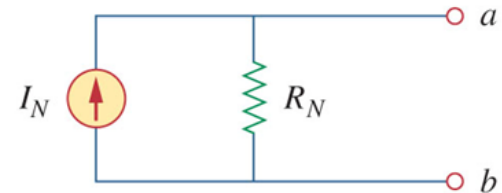


(b)

# Norton's Theorem II

- The Norton current  $I_N$  is found by short circuiting the circuit's terminals and measuring the resulting current.

$$I_N = i_{sc}$$

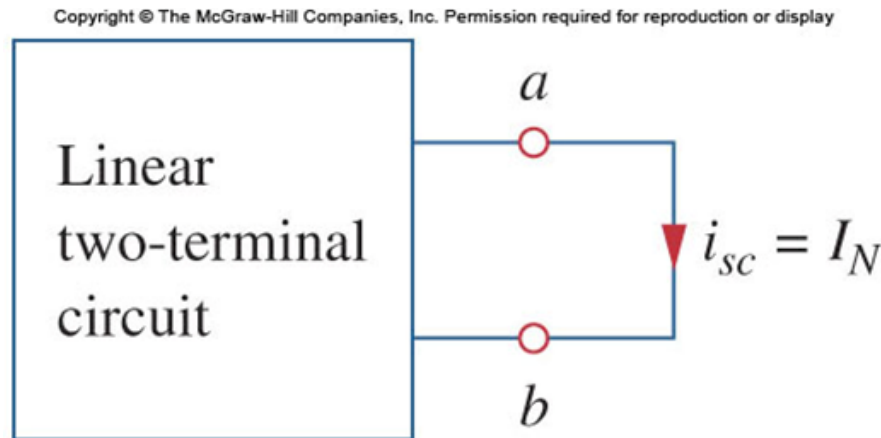

# Norton versus Thevenin

- These two equivalent circuits can be related to each other.
- One need only look at source transformation to understand this.
- The Norton current and Thevein voltage are related to each other as follows:

$$I_N = \frac{V_{Th}}{R_{Th}}$$

# Norton versus Thevenin II

- With  $V_{TH}$ ,  $I_N$ , and ( $R_{TH}=R_N$ ) related, finding the Thevenin or Norton equivalent circuit requires that we find:
- The open-circuit voltage across terminals *a and b*.
- The short-circuit current at terminals *a and b*.
- The equivalent or input resistance at terminals *a and b* when all independent sources are turned off.

# Maximum Power Transfer


- In many applications, a circuit is designed to power a load.
- Among those applications there are many cases where we wish to maximize the power transferred to the load.
- Unlike an ideal source, internal resistance will restrict the conditions where maximum power is transferred.

# Maximum Power Transfer II

- We can use the Thevenin equivalent circuit for finding the maximum power in a linear circuit.
- We will assume that the load resistance can be varied
- Looking at the equivalent circuit with load included, the power transferred is:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

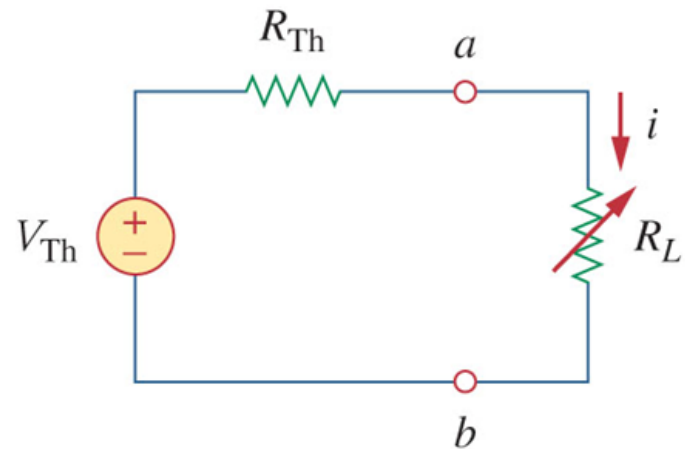
$$p = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$


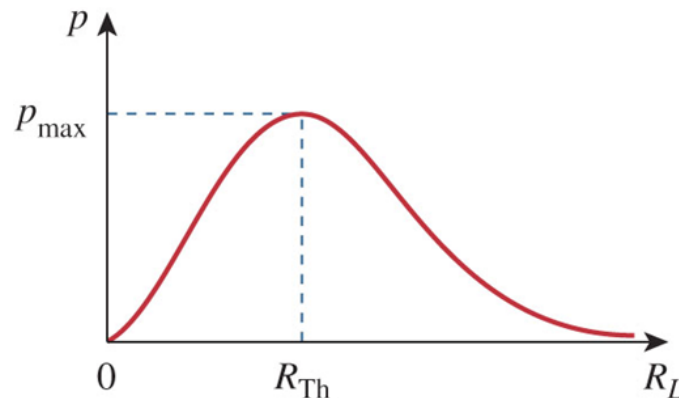
# Maximum Power Transfer III

- For a given circuit,  $V_{TH}$  and  $R_{TH}$  are fixed. By varying the load resistance  $R_L$ , the power delivered to the load varies as shown.
- You can see that as  $R_L$  approaches 0 and  $\infty$  the power transferred goes to zero.
- In fact the maximum power transferred is when  $R_L = R_{TH}$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Pspice?



- The Thevenin and Norton equivalent circuits are useful in understanding the behavior of realistic sources.
- Ideal voltage sources have no internal resistance.
- Ideal current sources have infinite internal resistance.
- The Thevenin and Norton circuits introduce deviations from these ideals.


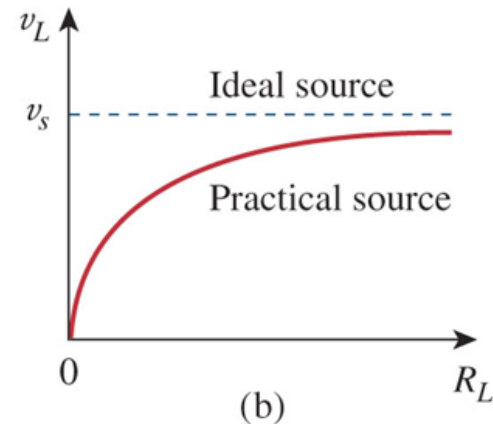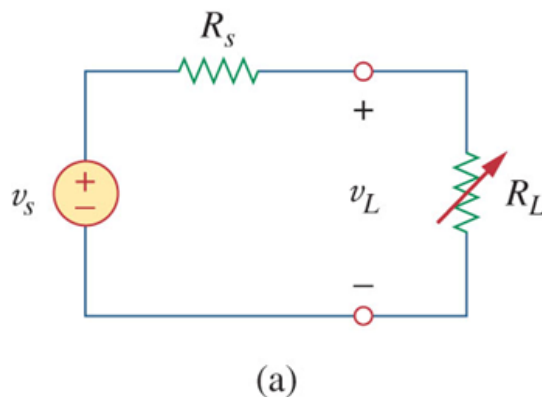
# Source Modeling

- Take the Thevenin circuit with load resistor:
- The internal resistor and the load act a voltage divider.
- The lower the load resistance, the more voltage drop that occurs in the source.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




# Source Modeling II

- This means that as the load resistance increases, the voltage source comes closer to operating like the ideal source.
- Similarly, with a realistic current source, the internal resistor in parallel with the ideal source acts to siphon away current that would otherwise go to the load.

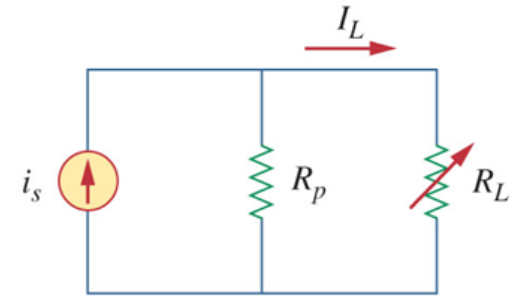
# Source Modeling III

- Here, the load and the internal resistor act as a current divider.
- From that perspective, the lower the load resistance, the more current passes through it.
- Thus lower load resistance leads to behavior closer to the ideal source.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

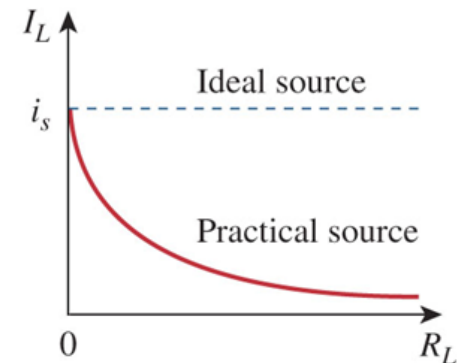


(b)
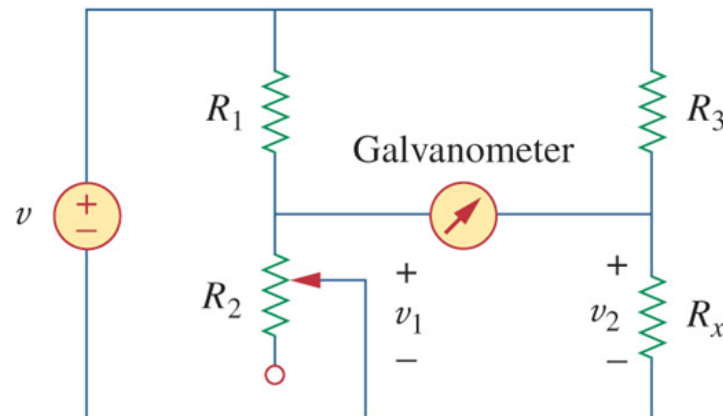
# Resistance Measurement <sub>1</sub>

- Although the ohmmeter is the most common method for measuring resistance, there is a more accurate method.
- It is called the Wheatstone bridge.
- It is based on the principle of the voltage divider.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Resistance Measurement <sub>2</sub>

- Using three known resistors and a galvanometer, an unknown resistor can be tested.
- The unknown resistor is placed at the position  $R_4$ .
- The variable resistor  $R_2$  is adjusted until the galvanometer shows zero current.
- At this point, the bridge is “balanced” and the voltages from the two dividers are equal.

# Balanced Bridge

- When balanced, the unknown resistor's value is.

$$R_x = \frac{R_3}{R_1} R_2$$

- The key to the high accuracy lies in the fact that any slight difference in the voltage dividers will lead to a current flow.

$$I = \frac{V_{Th}}{R_{Th} + R_m}$$

- Where the bridge, less the unknown resistor, is reduced to its Thevenin equivalent.

End of Main Content



Because learning changes everything.®

[www.mheducation.com](http://www.mheducation.com)