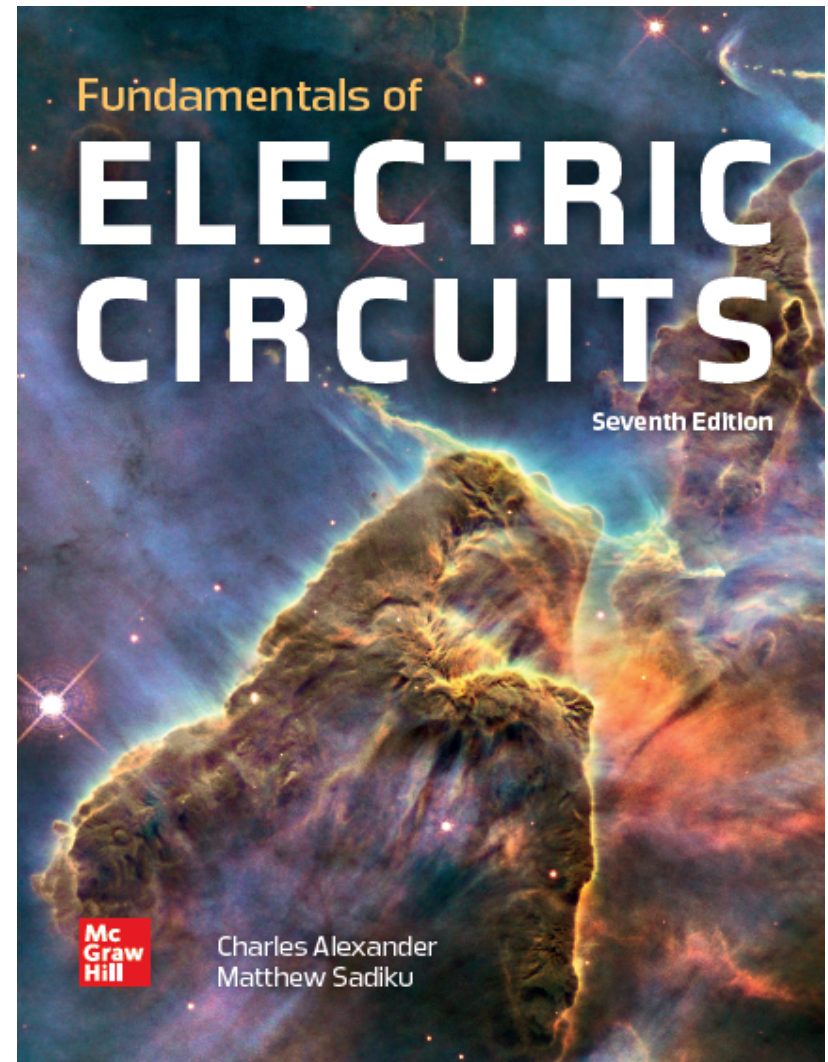


Fundamentals of Electric Circuits

Chapter 6




Overview

- This chapter will introduce two new linear circuit elements:
- The capacitor.
- The inductor.
- Unlike resistors, these elements do not dissipate energy.
- They instead store energy.
- We will also look at how to analyze them in a circuit.

Capacitors ¹

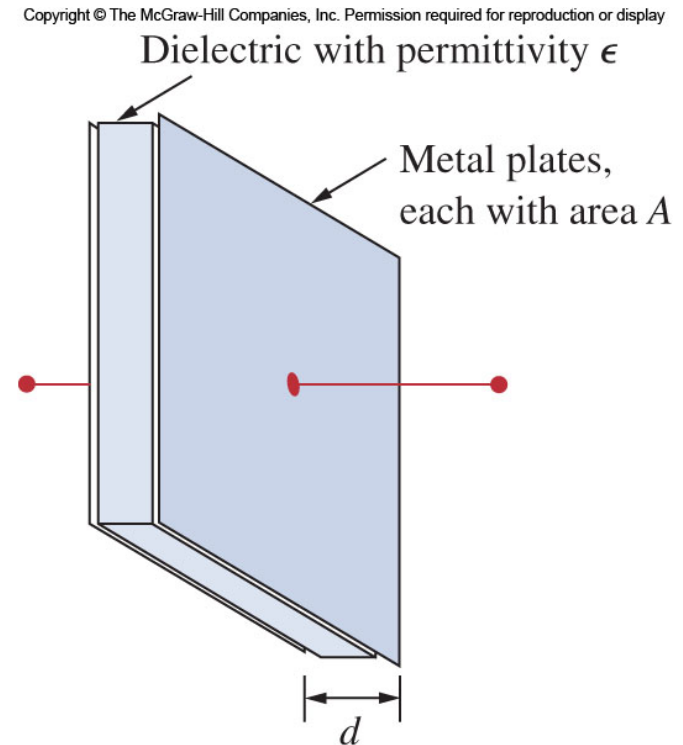- A capacitor is a passive element that stores energy in its electric field.
- It consists of two conducting plates separated by an insulator (or dielectric).
- The plates are typically aluminum foil.
- The dielectric is often air, ceramic, paper, plastic, or mica.



Capacitors ₂

- When a voltage source v is connected to the capacitor, the source deposits a positive charge q on one plate and a negative charge $-q$ on the other.
- The charges will be equal in magnitude.
- The amount of charge is proportional to the voltage:

$$q = Cv$$

- Where C is the capacitance.

Capacitors ³

The unit of capacitance is the Farad (F)

One Farad is 1 Coulomb/Volt

Most capacitors are rated in picofarad (pF) and microfarad (μF)

Capacitance is determined by the geometry of the capacitor:

- Proportional to the area of the plates (A).
- Inversely proportional to the space between them (d).


$$C = \frac{\epsilon A}{d}$$

- ϵ is the permittivity of the dielectric.

Types of Capacitors

- The most common types of capacitors are film capacitors with polyester, polystyrene, or mica.
- To save space, these are often rolled up before being housed in metal or plastic films.
- Electrolytic caps produce a very high capacitance.
- Trimmer caps have a range of values that they can be set to.
- Variable air caps can be adjusted by turning a shaft attached to a set of moveable plates.

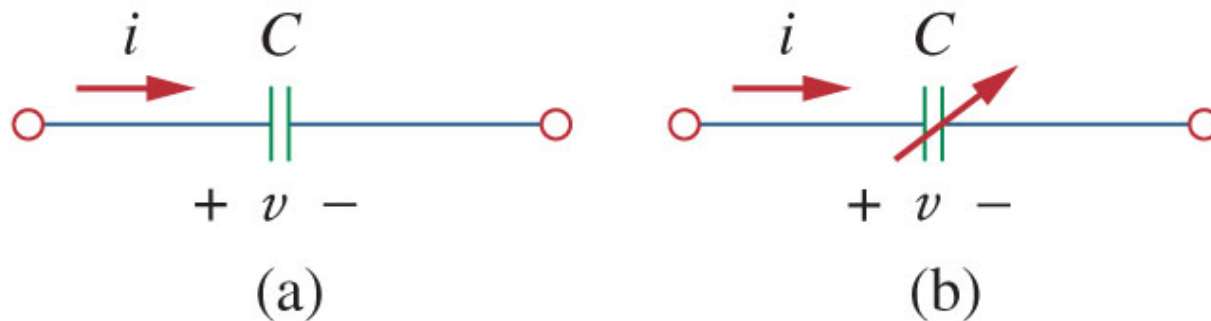
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Applications for Capacitors

Capacitors have a wide range of applications, some of which are:

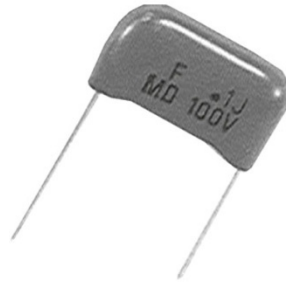- Blocking DC.
- Passing AC.
- Shift phase.
- Store energy.
- Suppress noise.
- Start motors.



(a)



(b)

Courtesy of Tech America



(c)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Current Voltage Relationship

- Using the formula for the charge stored in a capacitor, we can find the current voltage relationship.
- Take the first derivative with respect to time gives:

$$i = C \frac{dv}{dt}$$

- This assumes the passive sign convention.

Stored Charge

- Similarly, the voltage current relationship is:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

- This shows the capacitor has a memory, which is often exploited in circuits.
- The instantaneous power delivered to the capacitor is.

$$p = vi = Cv \frac{dv}{dt}$$

- The energy stored in a capacitor is:

$$w = \frac{1}{2} Cv^2$$

Properties of Capacitors ¹

- Ideal capacitors all have these characteristics:
- When the voltage is not changing, the current through the cap is zero.
- This means that with DC applied to the terminals no current will flow.
- Except, the voltage on the capacitor's plates can't change instantaneously.
- An abrupt change in voltage would require an infinite current!
- This means if the voltage on the cap does not equal the applied voltage, charge will flow and the voltage will finally reach the applied voltage.


Properties of Capacitors ²

- An ideal capacitor does not dissipate energy, meaning stored energy may be retrieved later.
- A real capacitor has a parallel-model leakage resistance, leading to a slow loss of the stored energy internally.
- This resistance is typically very high, on the order of 100 M Ω and thus can be ignored for many circuit applications.


Parallel Capacitors ¹

- We learned with resistors that applying the equivalent series and parallel combinations can simplify many circuits.
- Starting with N parallel capacitors, one can note that the voltages on all the caps are the same.
- Applying KCL:

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

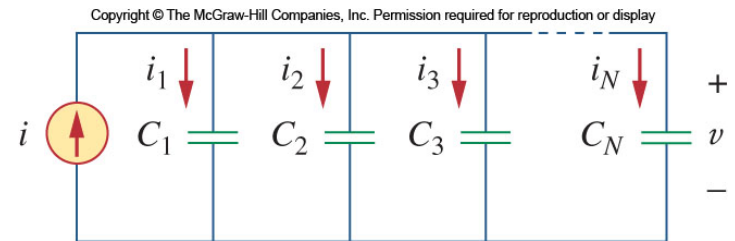

(a)

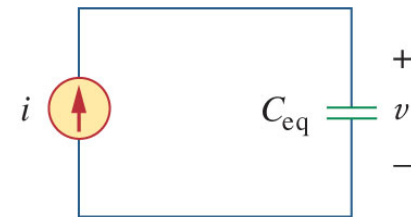

(b)

Parallel Capacitors ²

- Taking into consideration the current voltage relationship of each capacitor:

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \cdots + C_N \frac{dv}{dt}$$
$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$

- Where

$$C_{eq} = C_1 + C_2 + C_3 + \cdots + C_N$$


- From this we find that parallel capacitors combine as the sum of all capacitance.

Series Capacitors ¹


- Turning our attention to a series arrangement of capacitors:
- Here each capacitor shares the same current.
- Applying KVL to the loop:

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$

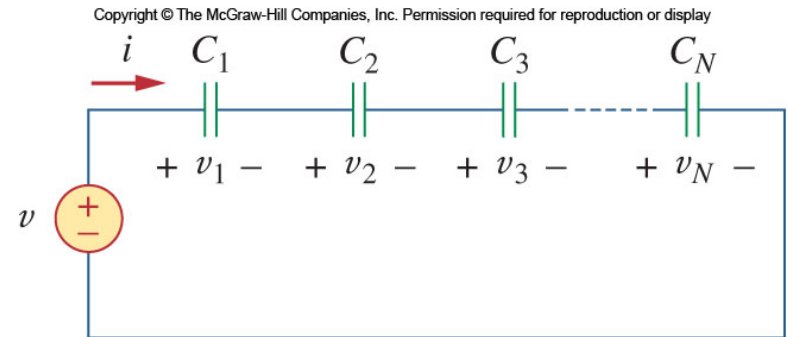- Now apply the voltage current relationship.



(a)

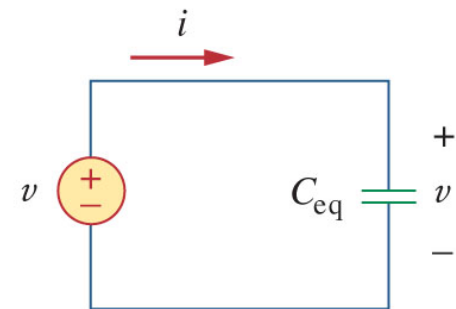

(b)

Series Capacitors ²

$$\begin{aligned} v &= \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) + \frac{1}{C_3} \int_{t_0}^t i(\tau) d\tau + v_3(t_0) + \cdots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0) \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0) + v_3(t_0) + \cdots + v_N(t_0) \\ &= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0) \end{aligned}$$

- Where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots + \frac{1}{C_N}$$

- From this we see that the series combination of capacitors resembles the parallel combination of resistors.

Series and Parallel Caps

- Another way to think about the combinations of capacitors is this:
- Combining capacitors in parallel is equivalent to increasing the surface area of the capacitors:
- This would lead to an increased overall capacitance (as is observed).
- A series combination can be seen as increasing the total plate separation.
- This would result in a decrease in capacitance (as is observed).


Inductors ¹

- An inductor is a passive element that stores energy in its magnetic field.
- They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any conductor has inductance, but the effect is typically enhanced by coiling the wire up.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

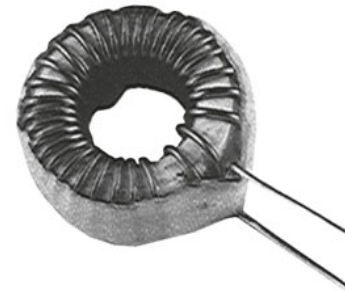

(b)



(c)

Courtesy of Tech America

Inductors ²

- If a current is passed through an inductor, the voltage across it is directly proportional to the time rate of change in current.

$$v = L \frac{di}{dt}$$


- Where, L , is the unit of inductance, measured in Henries, H.
- One Henry is 1 volt-second per ampere.
- The voltage developed tends to oppose a changing flow of current.

Inductors ³

- Calculating the inductance depends on the geometry:
- For example, for a solenoid the inductance is:

$$L = \frac{N^2 \mu A}{l}$$

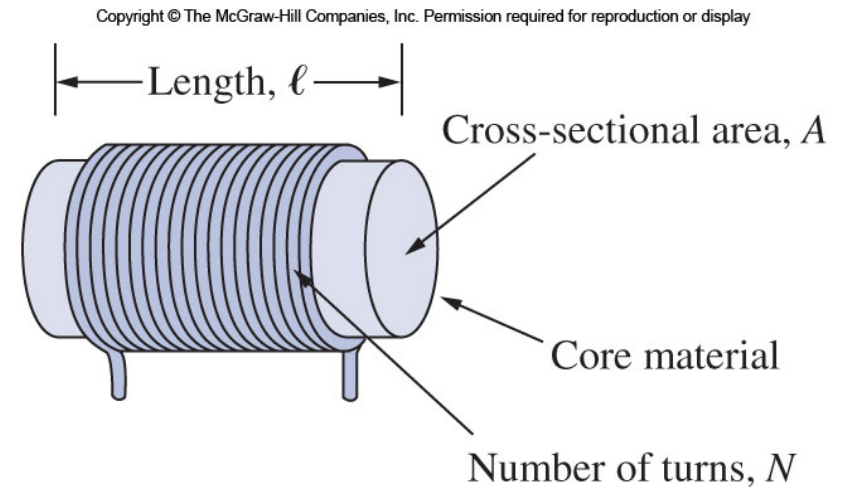- Where N is the number of turns of the wire around the core of cross sectional area A and length l .
- The material used for the core has a magnetic property called the permeability, μ .



Current in an Inductor

- The current voltage relationship for an inductor is:

$$I = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

- The power delivered to the inductor is:

$$p = vi = \left(L \frac{di}{dt} \right) i$$

- The energy stored is:

$$w = \frac{1}{2} Li^2$$

Properties of Inductors ¹

- If the current through an inductor is constant, the voltage across it is zero.
- Thus an inductor acts like a short for DC.
- The current through an inductor cannot change instantaneously.
- If this did happen, the voltage across the inductor would be infinity!
- This is an important consideration if an inductor is to be turned off abruptly; it will produce a high voltage.


Properties of Inductors ²

- Like the ideal capacitor, the ideal inductor does not dissipate energy stored in it.
- Energy stored will be returned to the circuit later.
- In reality, inductors do have internal resistance due to the wiring used to make them.
- A real inductor thus has a winding resistance in series with it.
- There is also a small winding capacitance due to the closeness of the windings.
- These two characteristics are typically small, though at high frequencies, the capacitance may matter.


Series Inductors ¹

- We now need to extend the series parallel combinations to inductors.
- First, let's consider a series combination of inductors.
- Applying KVL to the loop:

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$

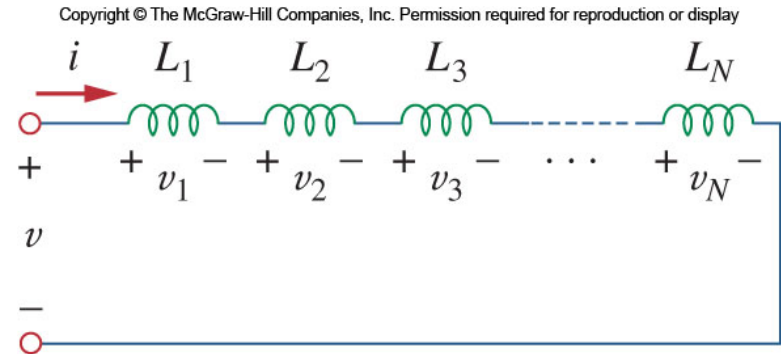

(a)

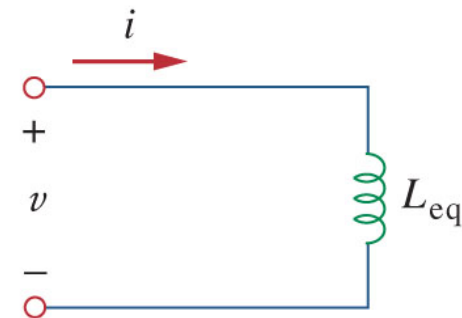

(b)

Series Inductors ²

- Factoring in the voltage current relationship.

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \cdots + L_N \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

- Where

$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_N$$

- Here we can see that the inductors have the same behavior as resistors.



Parallel Inductors ¹

- Now consider a parallel combination of inductors:
- Applying KCL to the circuit:

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

- When the current voltage relationship is considered, we have:
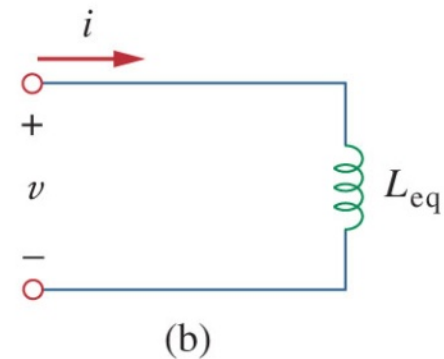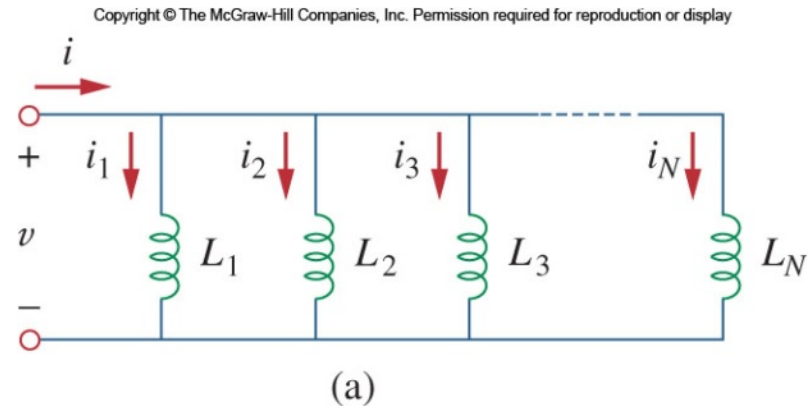
$$i = \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_0^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_0^t v dt + i(t_0)$$



Parallel Inductors ²

- The equivalent inductance is thus:

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

- Once again, the parallel combination resembles that of resistors.
- On a related note, the Delta-Wye transformation can also be applied to inductors and capacitors in a similar manner, as long as all elements are the same type.

Summary of Capacitors and Inductors

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

TABLE 6.1

Important characteristics of the basic elements.[†]

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v - i :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
i - v :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Applications


- Due to their bulky size, inductors are less frequently used as compared to capacitors, however they have some applications where they are best suited.
- They can be used to create a large amount of current or voltage for a short period of time.
- Their resistance to sudden changes in current can be used for spark suppression.
- Along with capacitors, they can be used for frequency discrimination.

Integrator

- Capacitors, in combination with op-amps can be made to perform advanced mathematical functions.
- One such function is the integrator.
- By replacing the feedback resistor with a capacitor, the output voltage from the op-amp is:

$$v_o = -\frac{1}{RC} \int v_i(\tau) d\tau$$

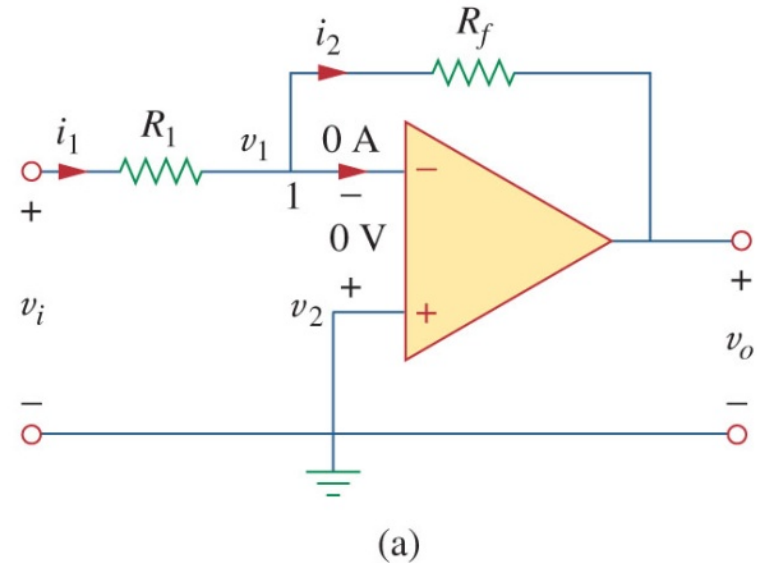Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Differentiator

- The previous circuit functions as an integrator with time.
- If the capacitor is used in place of the input resistor instead of the feedback resistor, there will only be current flowing if the voltage is changing.
- The output voltage in this case will be:

$$v_o = -RC \frac{dv_i}{dt}$$

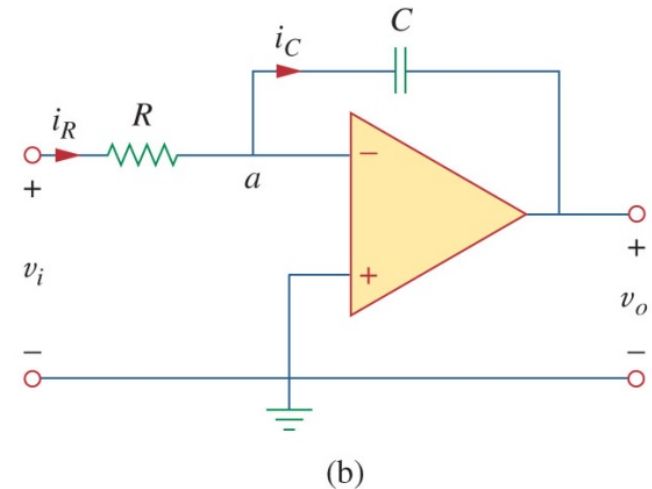- From this it is clear this circuit performs differentiation with time.



End of Main Content



Because learning changes everything.®

www.mheducation.com