

Homework 2

1) MOS I/V Characteristics HSpice

- Use HSpice to plot the I/V characteristics of an n-channel device ($W=6\mu\text{m}$, $L=1.2\mu\text{m}$) for three gate-source voltages of 1 V, 2 V and 3V, respectively. Use the **dc analysis** and sweep the drain voltage from 0 V to 5 V while the source remains grounded.
- Repeat the above exercise for a p-channel device of equal size.
- Use your plots to find the equivalent transconductance values g_m and output resistances r_o of the 2 devices under the various bias conditions.

2) MOS Model parameters

- Use the BSIM parameters listed on the next page to calculate I_d , g_m , g_{mb} , r_o and λ for the n-channel MOS transistor described in problem 1a).
- Repeat your calculations for the p-channel device described in problem 1b).
- Compare your results for g_m and r_o with the equivalent values derived from your HSpice plots. Comment on the differences.

3) Common-Source Gain Stage

An n-channel common-source amplifier with $W=6\mu\text{m}$ and $L=1.2\mu\text{m}$ is featuring a bias current of $I_{DQ}=50\mu\text{A}$.

- Find the load resistance so that you achieve a dc voltage gain of 50.
- Can you find a value for the dc current gain?
- How would you realize the load resistance computed above? Explain!

SPICE BSIM3 VERSION 3.1 PARAMETERS

```

.MODEL nfet NMOS (
+VERSION = 3.1          TNOM = 27          LEVEL = 49
+XJ = 1.5E-7           NCH = 1.7E17       TOX = 1.39E-8
+K1 = 0.8857752       K2 = -0.0935679      VTH0 = 0.6398186
+K3B = -7.6711263    W0 = 1E-8           K3 = 22.1010569
+DVT0W = 0            DVT1W = 0           NLX = 1E-9
+DVT0 = 2.7950058    DVT1 = 0.4085592   DVT2W = 0
+U0 = 453.2010286    UA = 2.494433E-13  DVT2 = -0.1237812
+UC = 2.022743E-11   VSAT = 1.730467E5   UB = 1.488658E-18
+AGS = 0.1151449     B0 = 2.792031E-6    A0 = 0.5543744
+KETA = -1.371458E-3 A1 = 0              B1 = 5E-6
+RDSW = 1.319508E3   PRWG = 0.0381943   A2 = 0.3560219
+WR = 1              WINT = 2.507126E-7 PRWB = 0.0141195
+XL = 0              XW = 0              LINT = 2.304464E-8
+DWB = 4.946821E-8   VOFF = 0            DWG = -1.755808E-8
+CIT = 0             CDSC = 2.4E-4       NFACTOR = 0.7910748
+CDSCB = 0           ETA0 = 0.0051332   CDSCD = 0
+DSUB = 0.1945608   PCLM = 2.253484    ETAB = -1.252309E-3
+PDIBLC2 = 2.440187E-3 PDIBLCB = -0.1294159 PDIBLC1 = -1
+PSCBE1 = 5.348212E8 PSCBE2 = 3.233314E-5 DROUT = 0.6751288
+DELTA = 0.01        RSH = 80.3         PVAG = 0
+PRT = 0             UTE = -1.5         MOBMOD = 1
+KT1L = 0            KT2 = 0.022        KT1 = -0.11
+UB1 = -7.61E-18    UC1 = -5.6E-11    UA1 = 4.31E-9
+WL = 0              WLN = 1            AT = 3.3E4
+WWN = 1             WWL = 0            WW = 0
+LLN = 1             LW = 0             LL = 0
+LWL = 0             CAPMOD = 2         LWN = 1
+CGDO = 2.12E-10    CGSO = 2.12E-10   XPART = 0.5
+CJ = 4.279445E-4   PB = 0.9616445    CGBO = 1E-9
+CJSW = 3.492439E-10 PBSW = 0.1         MJ = 0.4374524
+CJSWG = 1.64E-10   PBSWG = 0.1       MJSW = 0.1245165
+CF = 0             PVTH0 = 0.0431719 MJSWG = 0.1245165
+PK2 = -0.0350028   WKETA = -0.0230093 PRDSW = -30.376525
*                   LKETA = 2.090253E-3)

.MODEL pfet PMOS (
+VERSION = 3.1          TNOM = 27          LEVEL = 49
+XJ = 1.5E-7           NCH = 1.7E17       TOX = 1.39E-8
+K1 = 0.5429357       K2 = 9.433657E-3   VTH0 = -0.9488171
+K3B = -0.8567156    W0 = 1E-8           K3 = 3.2656684
+DVT0W = 0            DVT1W = 0           NLX = 1.48542E-8
+DVT0 = 2.530444     DVT1 = 0.5291909   DVT2W = 0
+U0 = 220.9301068    UA = 3.049951E-9   DVT2 = -0.1040273
+UC = -5.63429E-11   VSAT = 2E5         UB = 1E-21
+AGS = 0.1506017     B0 = 9.121548E-7   A0 = 0.9085767
+KETA = -2.819843E-3 A1 = 0              B1 = 5E-6
+RDSW = 3E3          PRWG = -0.0464229  A2 = 0.3
+WR = 1              WINT = 2.90101E-7 PRWB = -0.0398483
+XL = 0              XW = 0              LINT = 4.254314E-8
+DWB = 1.788287E-8   VOFF = -0.0659109 DWG = -2.169468E-8
+CIT = 0             CDSC = 2.4E-4       NFACTOR = 0.8188201
+CDSCB = 0           ETA0 = 1.380153E-3 CDSCD = 0
+DSUB = 0.7658995   PCLM = 2.0797597   ETAB = -0.0429727
+PDIBLC2 = 4.521707E-3 PDIBLCB = -0.0437905 PDIBLC1 = 0.1113965
+PSCBE1 = 1.25116E10 PSCBE2 = 1.227353E-9 DROUT = 0.3065171
+DELTA = 0.01        RSH = 104.9        PVAG = 8.477076E-6
+PRT = 0             UTE = -1.5         MOBMOD = 1
+KT1L = 0            KT2 = 0.022        KT1 = -0.11
+UB1 = -7.61E-18    UC1 = -5.6E-11    UA1 = 4.31E-9
+WL = 0              WLN = 1            AT = 3.3E4
+WWN = 1             WWL = 0            WW = 0
+LLN = 1             LW = 0             LL = 0
+LWL = 0             CAPMOD = 2         LWN = 1
+CGDO = 2.25E-10    CGSO = 2.25E-10   XPART = 0.5
+CJ = 7.308538E-4   PB = 0.9416073    CGBO = 1E-9
+CJSW = 2.852637E-10 PBSW = 0.99        MJ = 0.4948413
+CJSWG = 6.4E-11    PBSWG = 0.99       MJSW = 0.3001719
+CF = 0             PVTH0 = 5.98016E-3 MJSWG = 0.3001719
+PK2 = 3.73981E-3   WKETA = 4.127712E-3 PRDSW = 14.8598424
*                   LKETA = -2.567864E-3)

```