


Basics – 6

circuit analysis; dependent sources


Circuit Analysis


- Noted in the last class that sometimes we can do a full analysis using series/parallel combining, voltage/current division
- Let's do another example or two

Example: find I and V_o

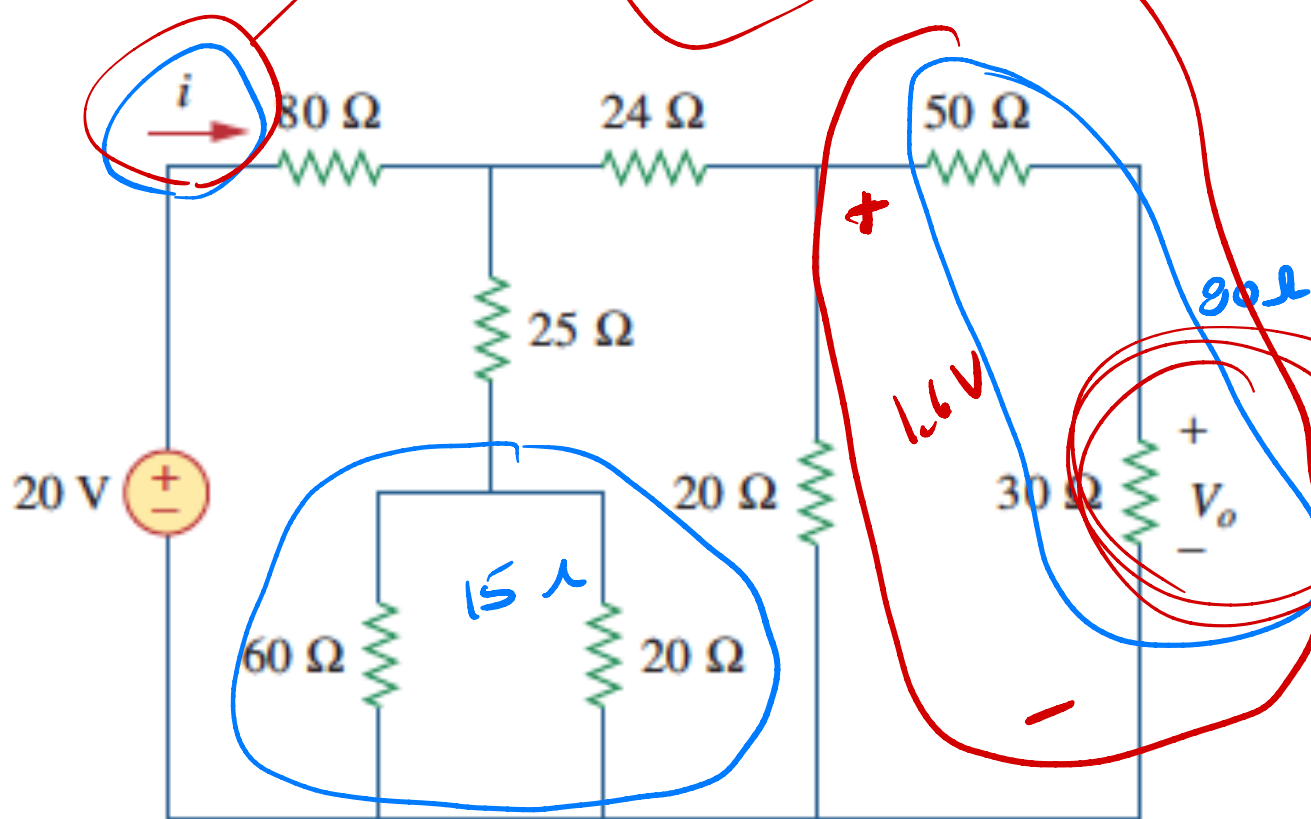


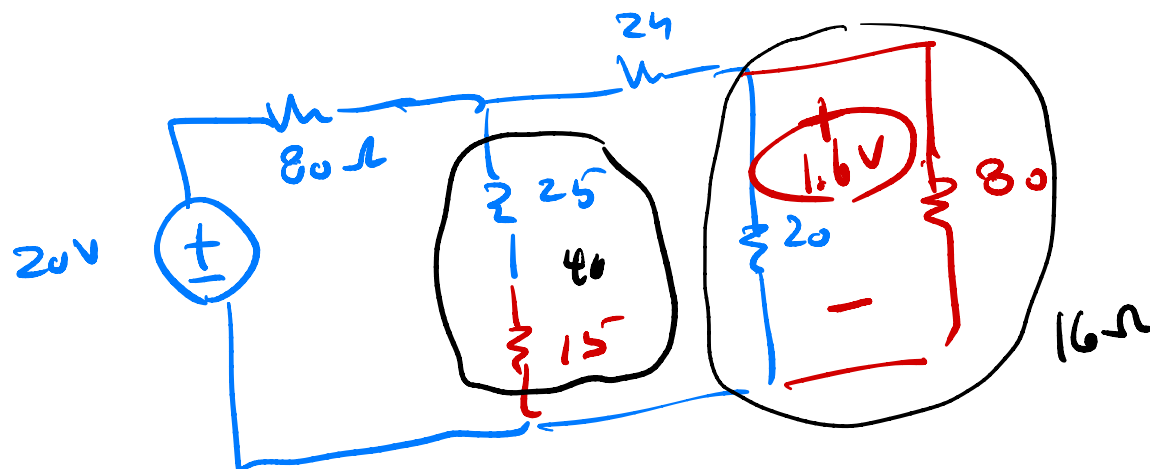
- 1- parallel 60, 20
- 2- series 50, 30
- 3- par. 20, 80
- 4- series 25, 15



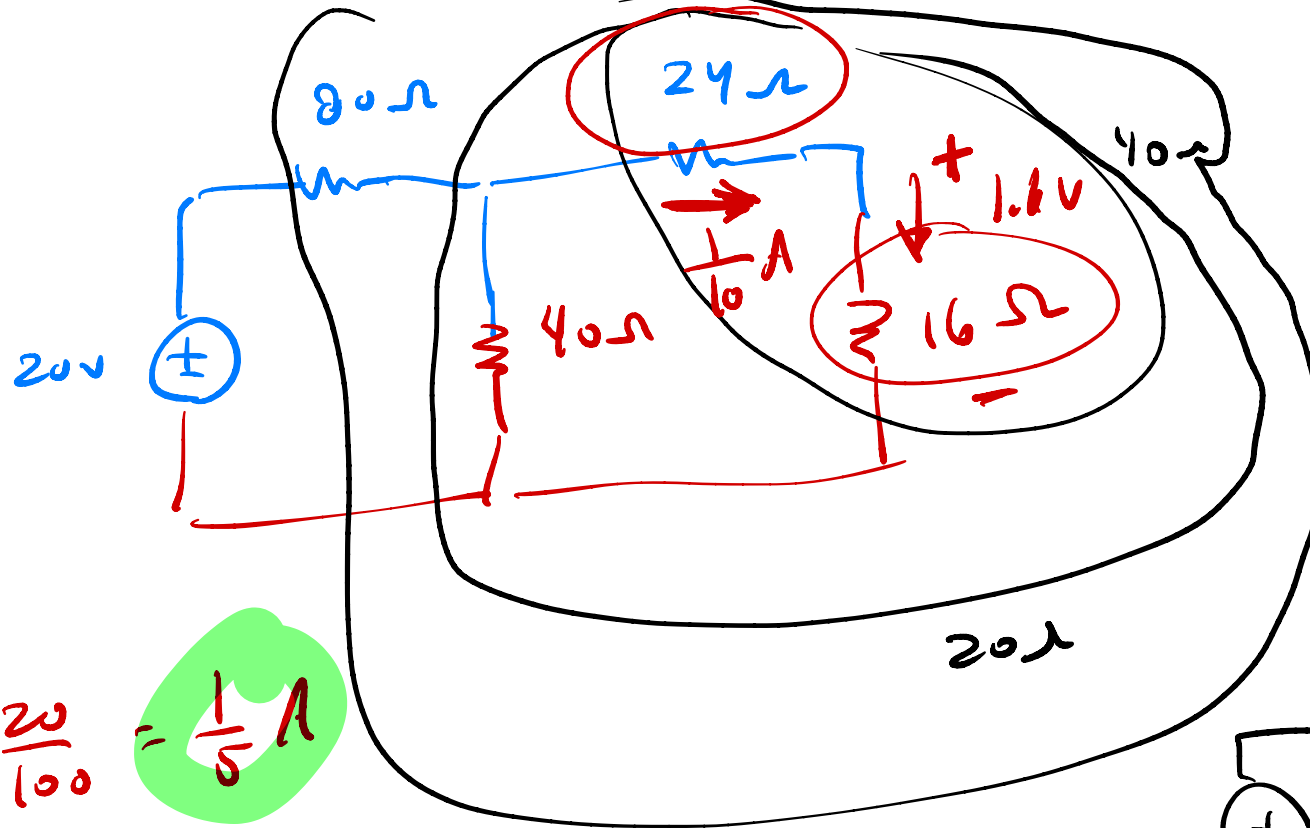


- 5 - series 24, 16
- 6 - par. 40, 40
- 7 - series 20, 30

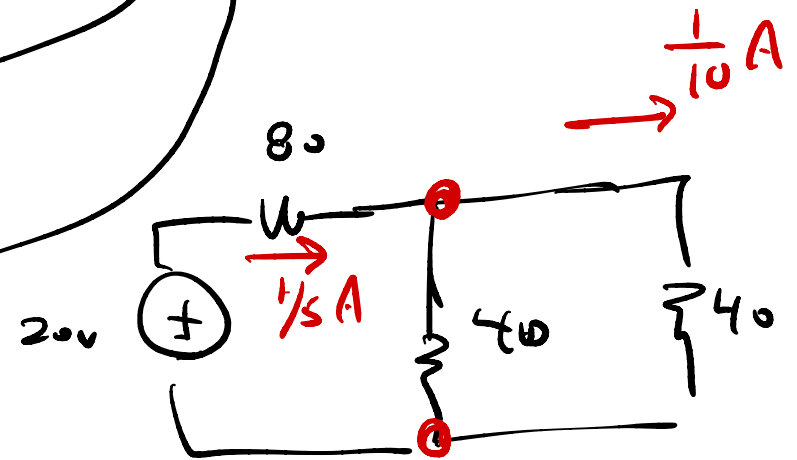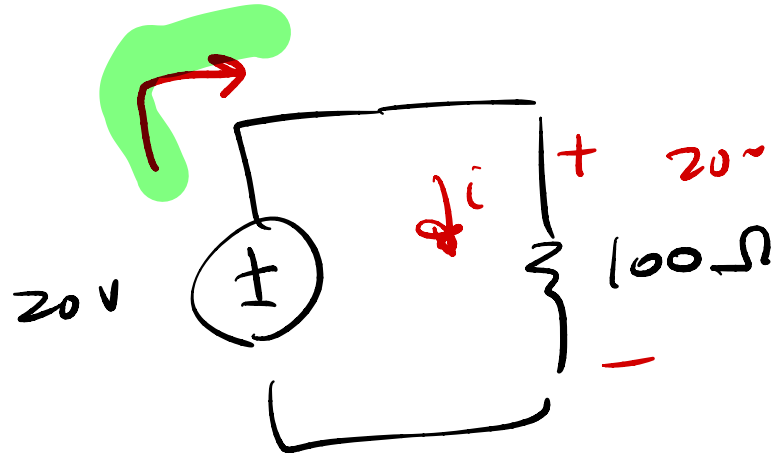
$$i = \frac{20}{100} = \frac{1}{5} \text{ A}$$



Example: find V_o and I_o

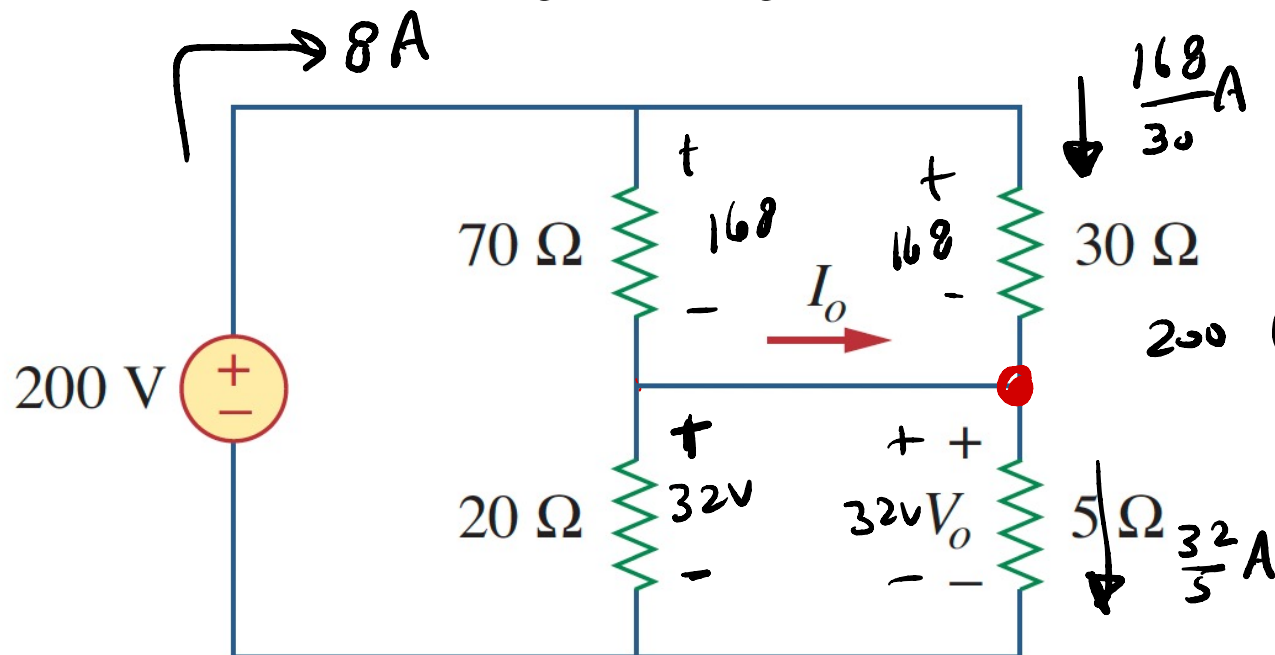

1- parallel twice

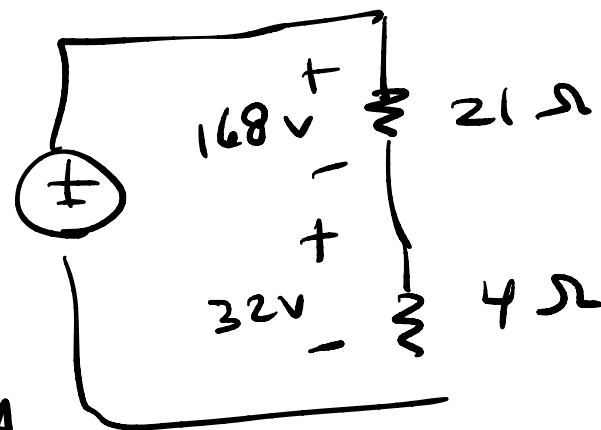

2- volt. div

3- Ohm's law twice


4- KCL at node

$$I + \frac{168}{30} = \frac{32}{5}$$

$$I = \frac{32}{5} - \frac{168}{30}$$

$$I = \frac{6.4}{10} - \frac{5.6}{15} = \frac{19.2}{30} - \frac{11.2}{30} = \frac{8}{30} = \frac{4}{15} = 0.267 \text{ A}$$

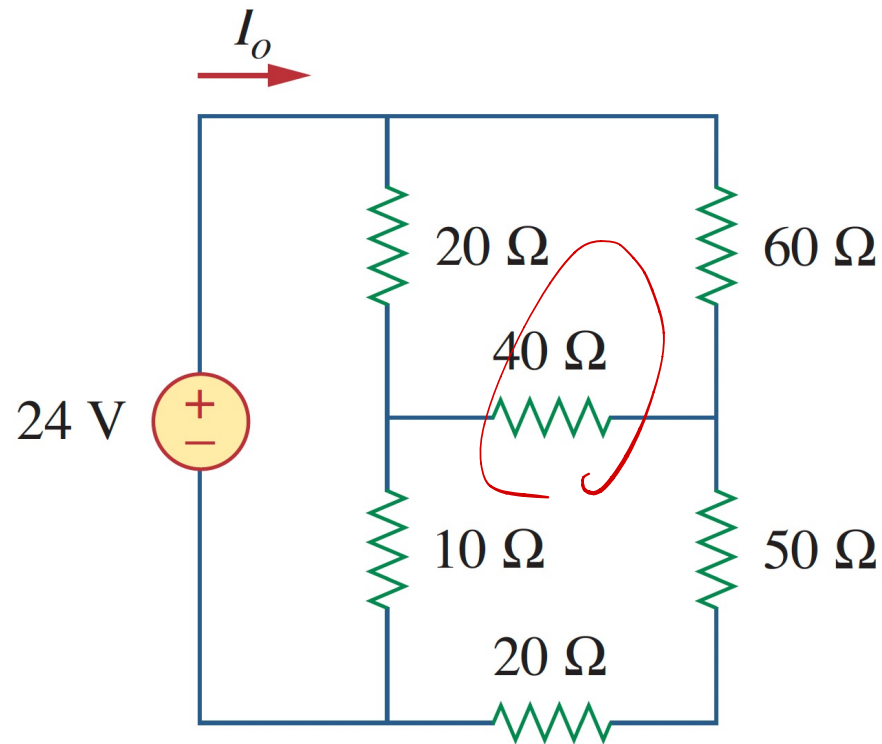
But sometimes you cannot: how do you find the current I_o now?







Watch/read materials on Delta-Wye on the course website

Dependent Sources

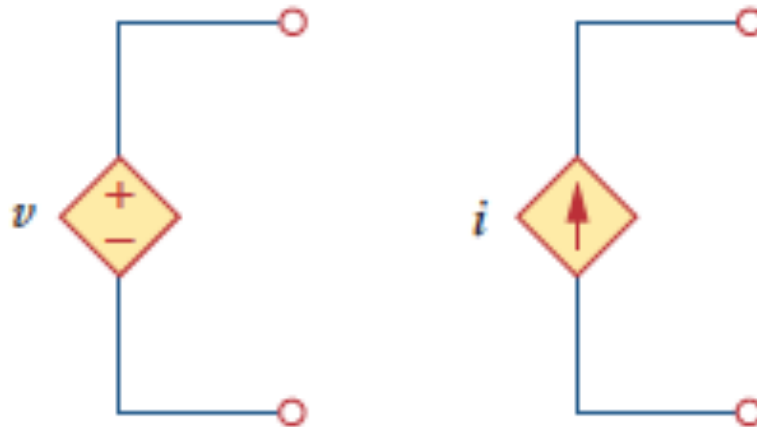
- The voltage or current is dependent upon some other circuit variable
- Drawn as a diamond or rhombus



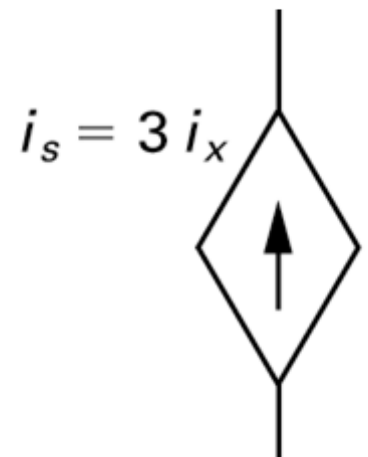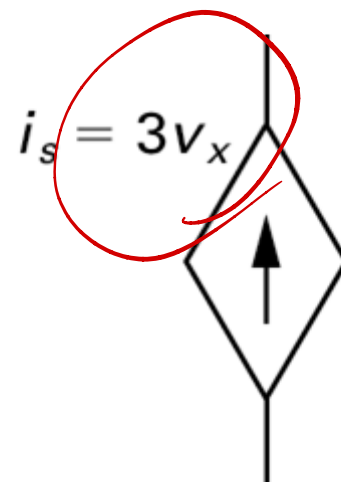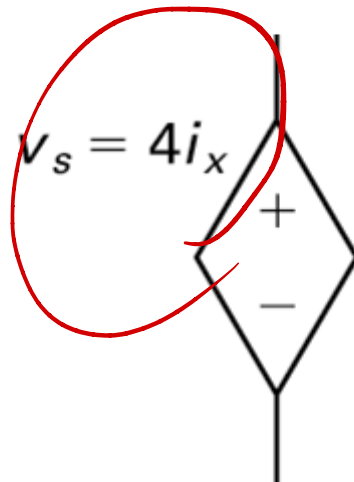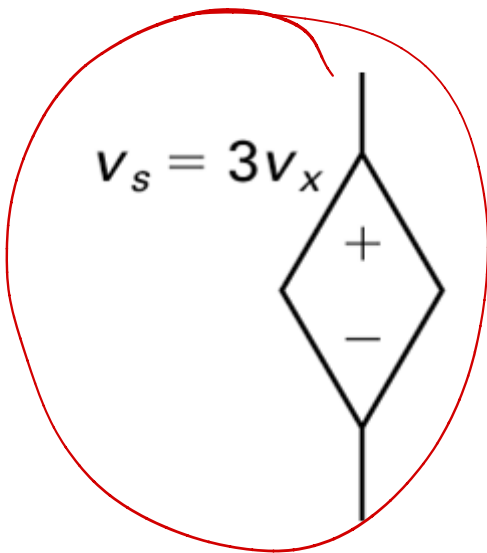- A linear relationship to some other circuit variable is common
 - What units does the entire label have?
 - What units does the multiplier have?




Example:

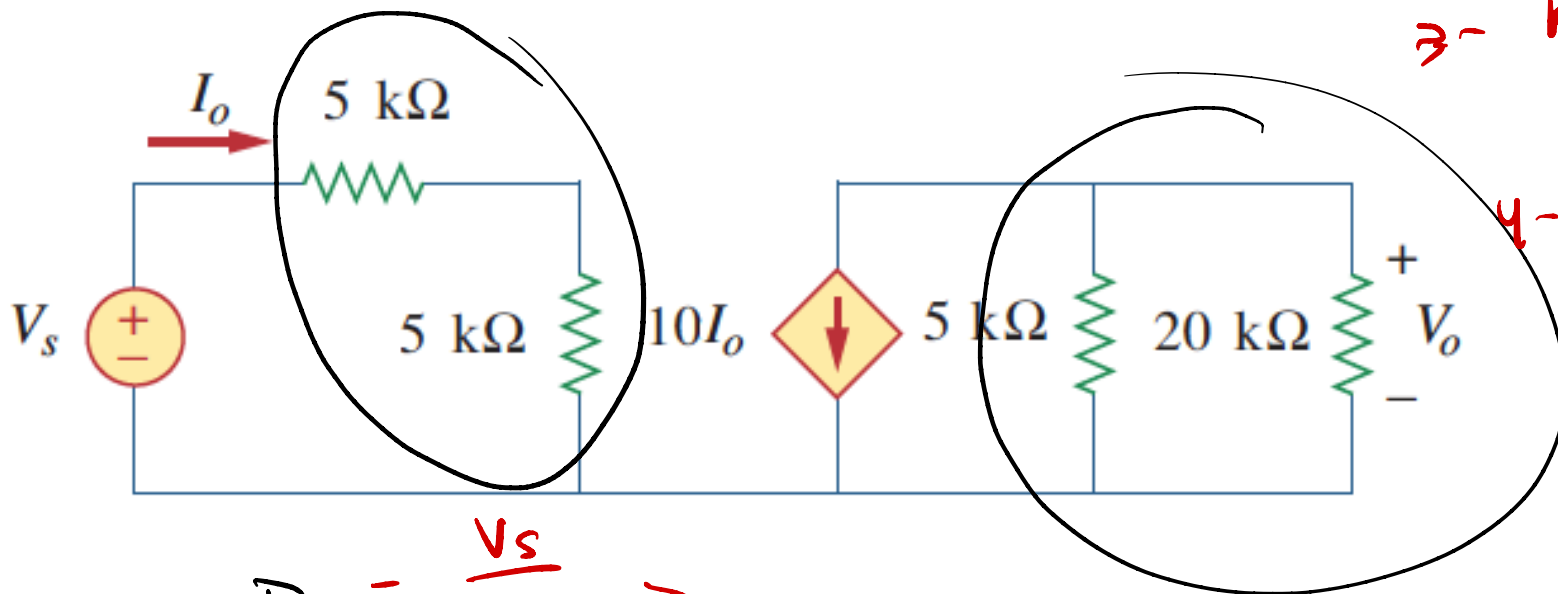

- 1- series 5.5
- 2- parallel 5, 20
- 3- KVL left to find I_o

4- KCL on right to get I_4

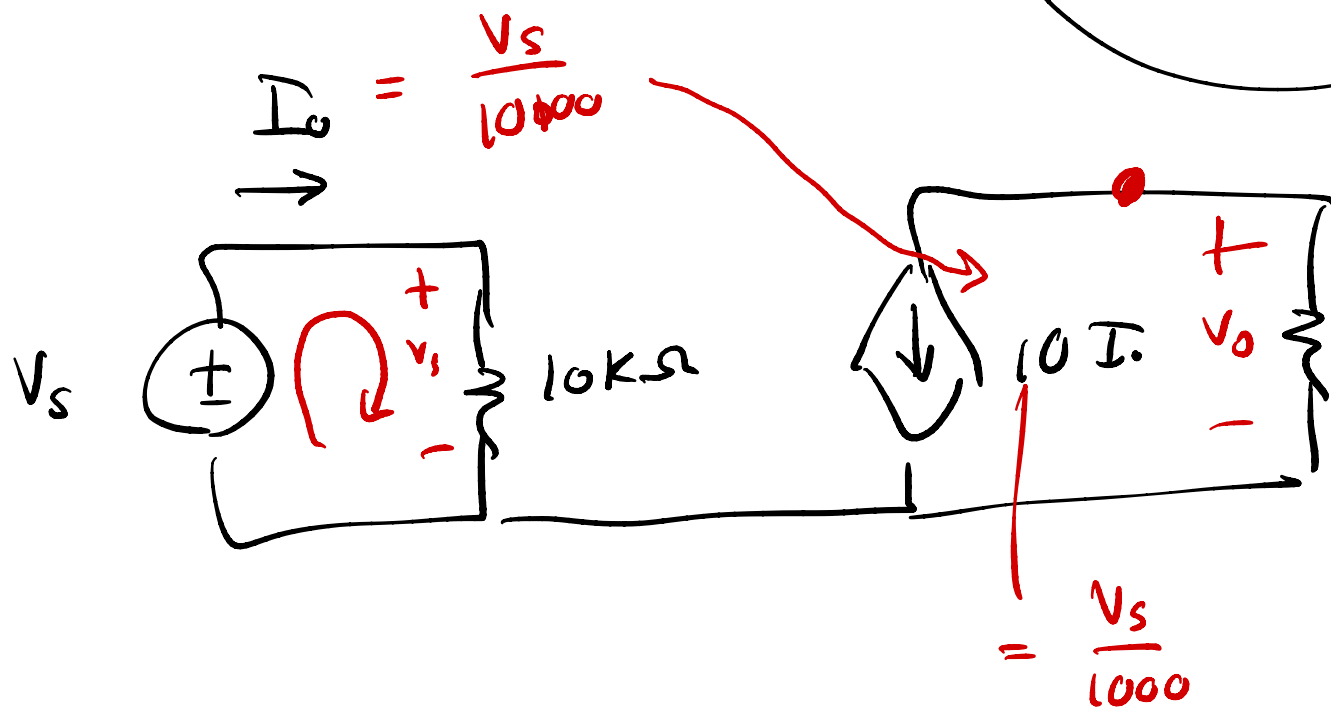

$$I_4 = -\frac{V_s}{1000}$$

4 kΩ


5- Ohm's Law

$$V_o = 4000 \cdot \frac{-V_s}{1000}$$

$$= -4V_s$$

Example:

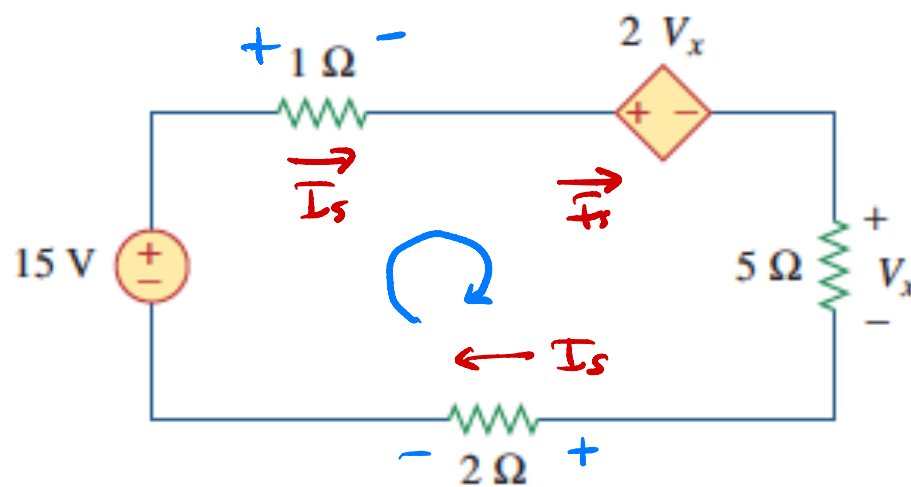2.21 Find V_x in the circuit of Fig. 2.85.



1- define I_s

2- use KCL

3- use KVL

4- ohm

$$V_x = 5 I_s$$

3- ohm

$$V_x = 5 \cdot \frac{15}{18}$$

$$= \frac{75}{18} \text{ V}$$

Figure 2.85


$$\text{KVL: } 15 - 1 \cdot I_s - 2V_x - V_x - 2I_s = 0$$

$$15 = 3I_s + 3V_x \Rightarrow 15 = 18I_s$$

$$I_s = \frac{15}{18} \text{ A}$$

2 A
 $2\text{ A} - 60\text{ W}$

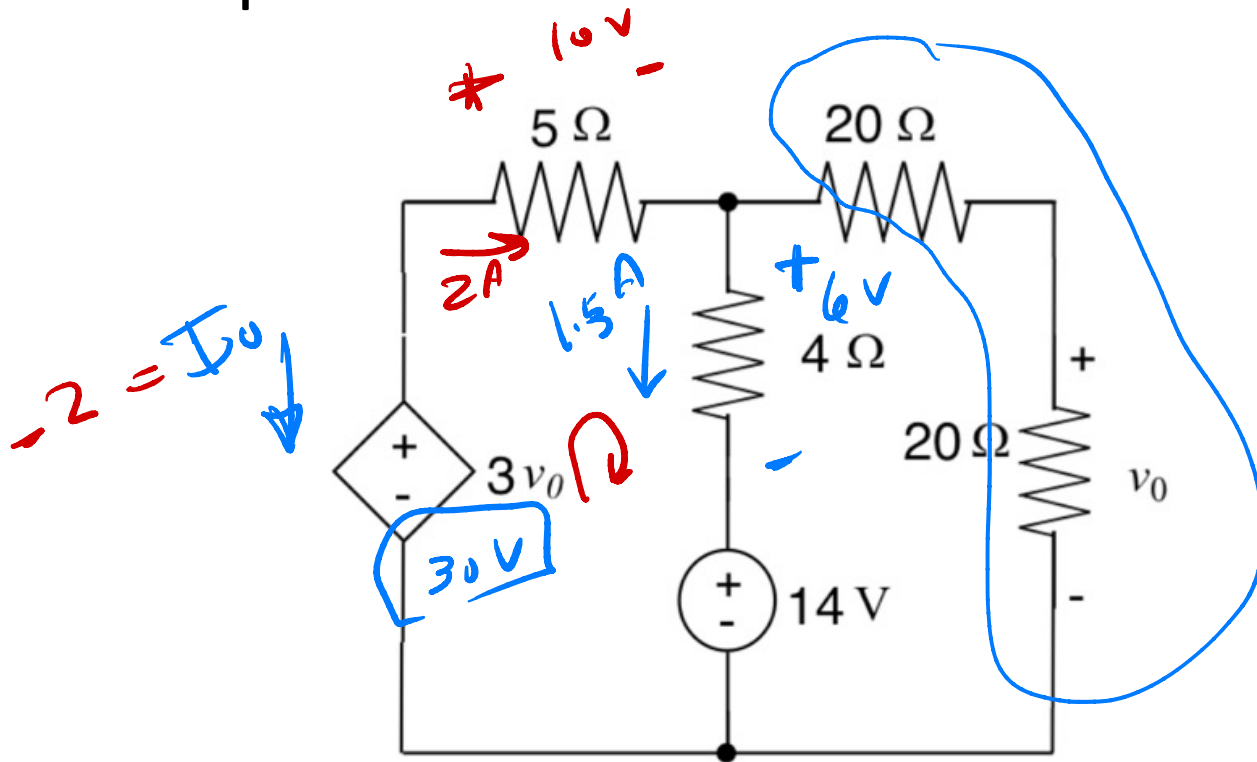Example: given that the current in the 4 ohm resistor is 1.5 A going down, find the current and power of the dependent source




- 1- Ohm law on 4Ω
- 2- KVL on right
- 3- Use volt div
 $V_o = 10\text{ V}$
- 4- $3V_o = 30\text{ V}$
- 5- KVL on left hand loop

$V_{5\Omega} = 10\text{ V}$
 6- Ohm's Law


2.5 A

Practice problem: find i_o

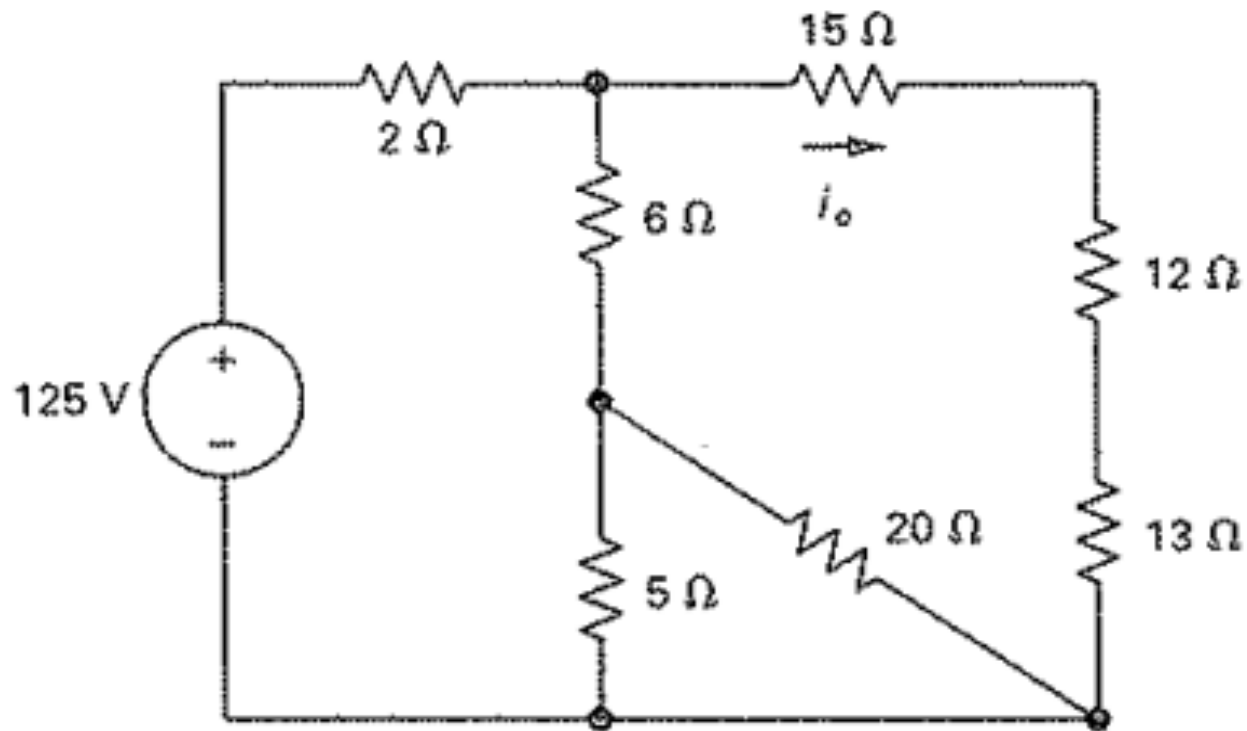

5 V, 5 W

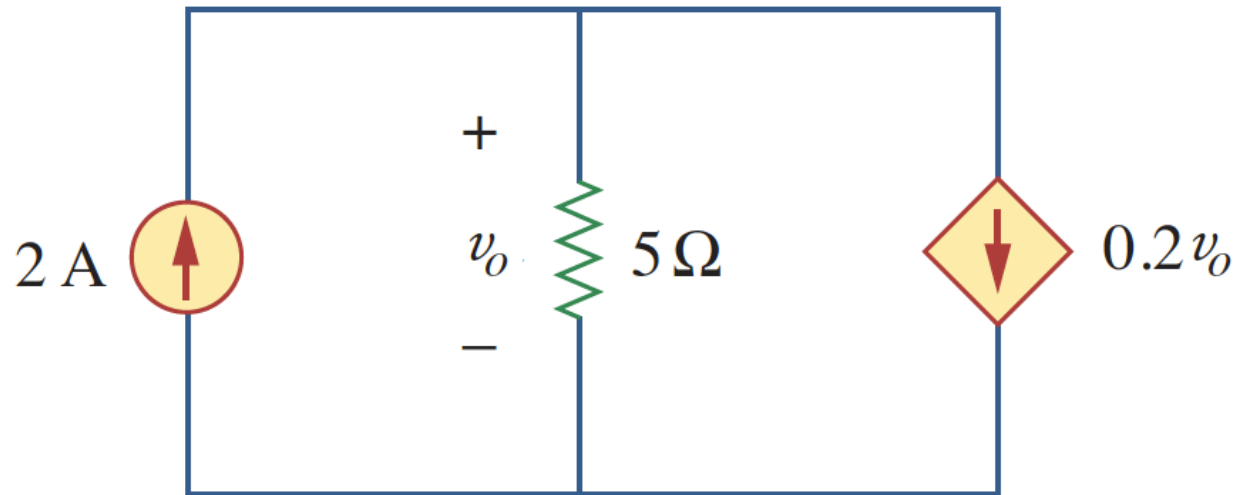Practice problem: Find v_o and the power of the dependent source



57 V

Practice problem: find v_o

