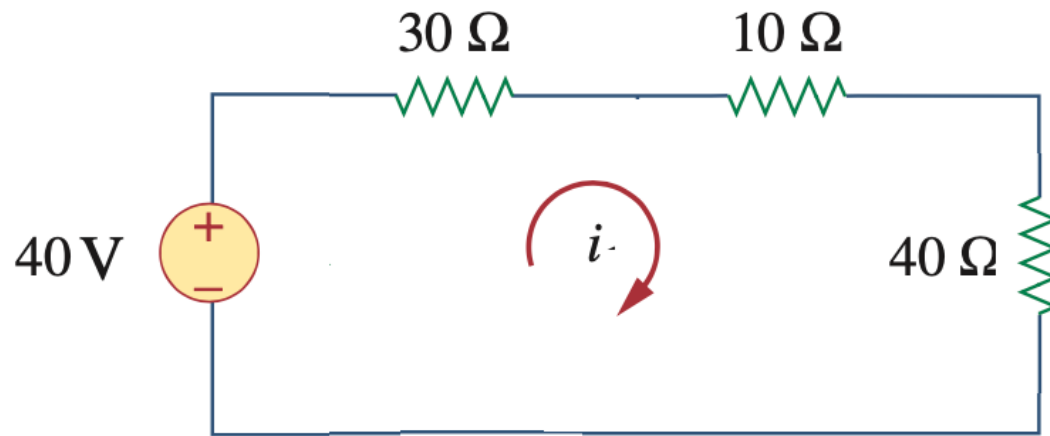


Phasors – 7

AC power


Power – DC Resistive Circuits

- General expression: $P = v i$



- Solve for clockwise current: $i = \frac{40 \text{ V}}{80 \Omega} = 0.5 \text{ A}$

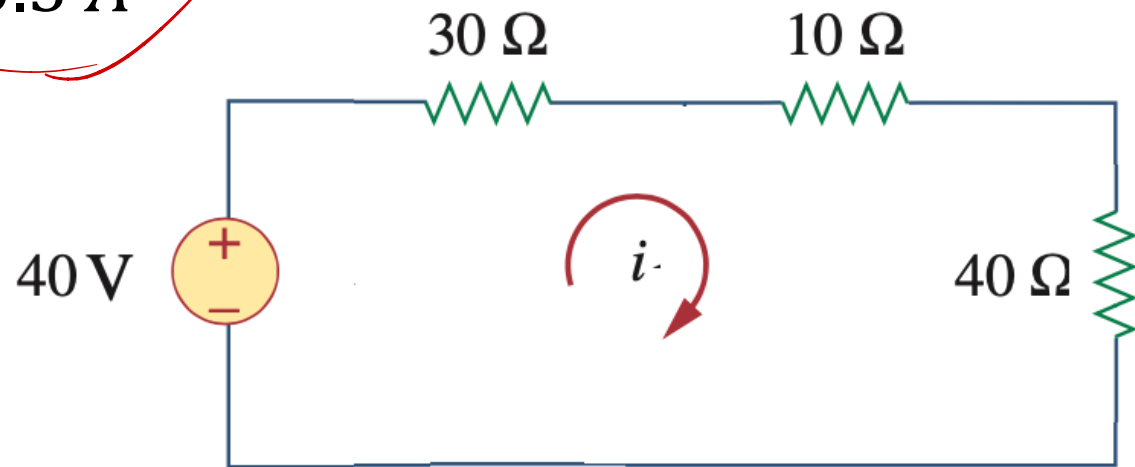- With $i = \frac{40\text{ V}}{80\ \Omega} = 0.5\text{ A}$



- Using $v = R i$ and $P = v i$

$$\begin{aligned} \rightarrow v_{30} &= 15\text{ V} \\ \rightarrow v_{10} &= 5\text{ V} \\ \rightarrow v_{40} &= 20\text{ V} \end{aligned}$$

$$i_{\text{source}} = -0.5\text{ A}$$

$$P_{30} = 7.5\text{ W}$$


$$\mathbf{P_{10} = 2.5\text{ W}}$$

$$P_{40} = 10\text{ W}$$

$$P_{\text{source}} = -20\text{ W}$$


Power
sums to
zero

Sinusoidal Source

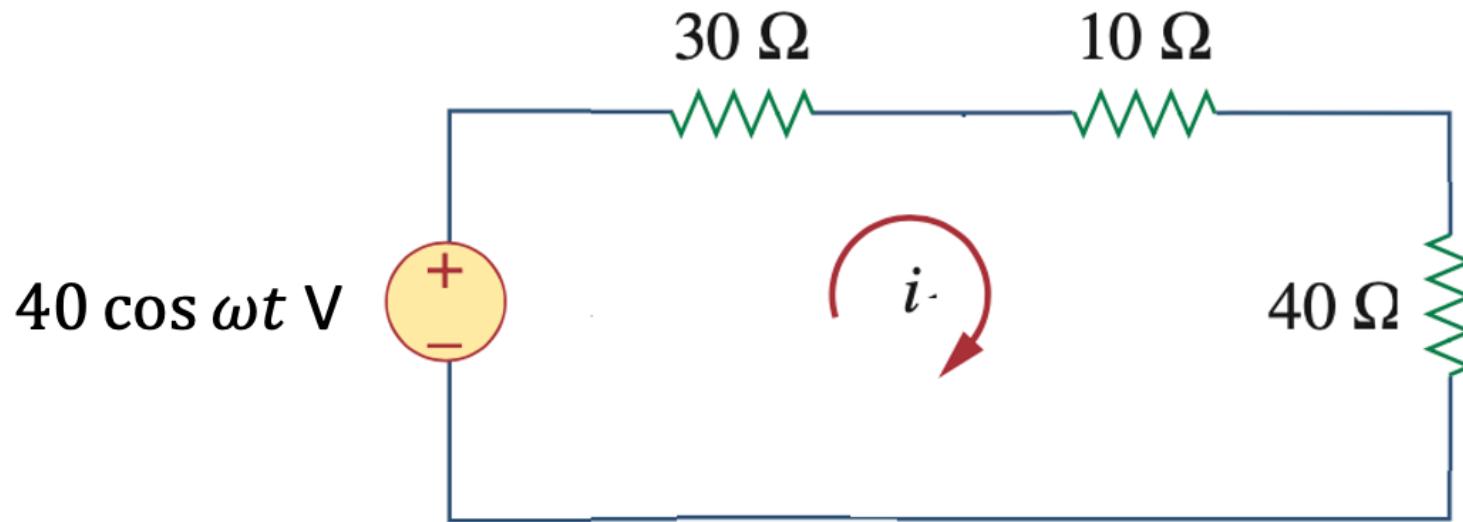

- Using phasors, clockwise current phasor is $\mathbf{I} = \frac{40}{80} = 0.5$ so $i(t) = 0.5 \cos \omega t \text{ A}$

- With $i(t) = 0.5 \cos \omega t$

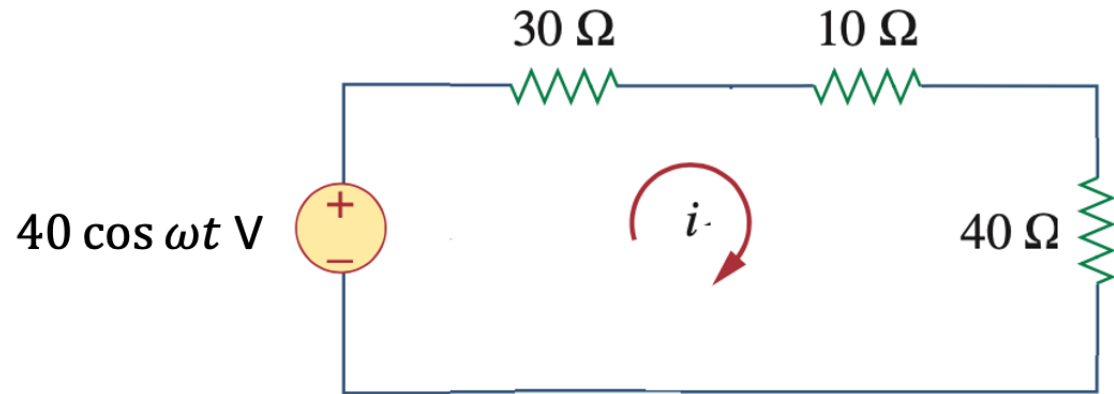

- Consider the 10Ω resistor:


$$i_{10}(t) = 0.5 \cos \omega t \text{ A}$$

$$v_{10}(t) = 10 i_{10}(t) = 5 \cos \omega t \text{ V}$$

$$p_{10}(t) = v_{10}(t) i_{10}(t) = 2.5 \cos^2 \omega t \text{ W}$$

$$= 1.25 + 1.25 \cos 2\omega t \text{ W}$$


- Graphically:

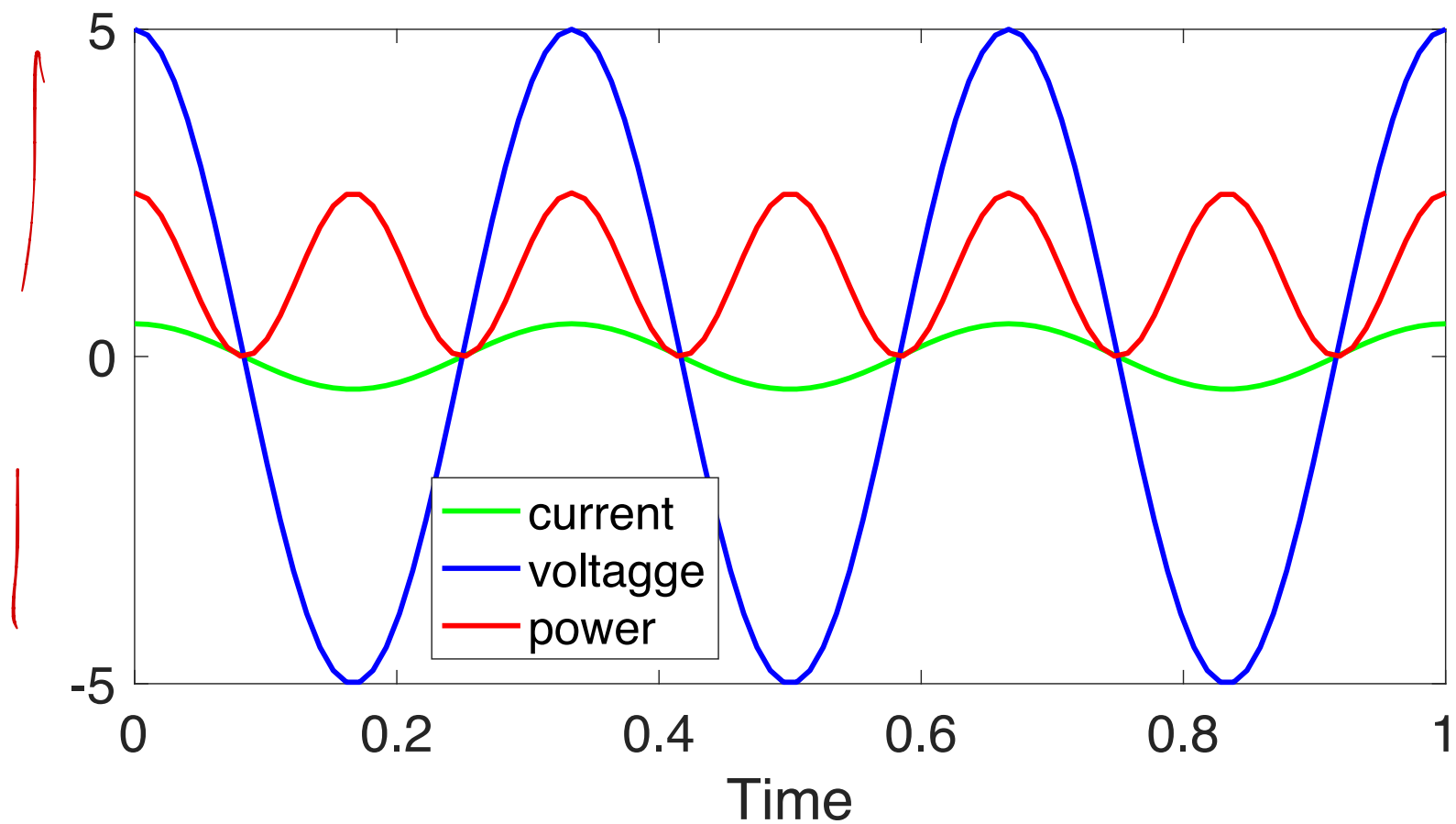

- To simplify, keep just the average value
 - Since periodic, average over 1 period

$$P = \frac{1}{T} \int_t^{t+T} v(t)i(t)dt$$

- For our example

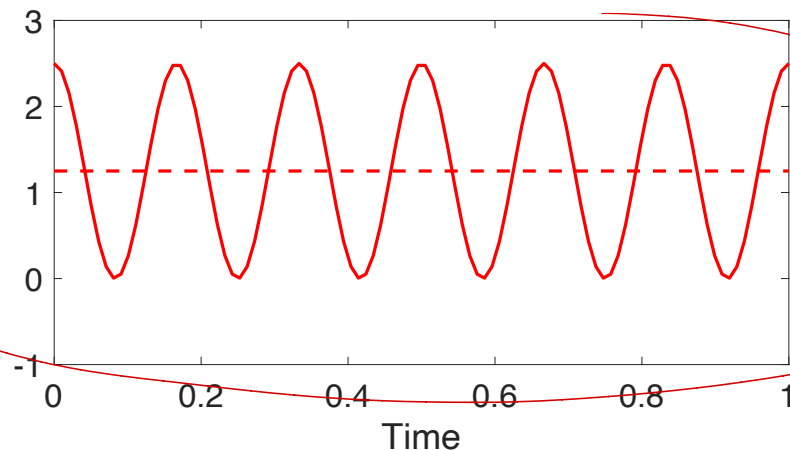

$$P_{4\Omega} = \frac{1}{T} \int_0^T \underbrace{(1.25 + 1.25 \cos 2\omega t)}_{\text{average value}} dt = \underline{\underline{1.25 \text{ W}}}$$

5 volts, 0.5 amps, but not 2.5 watts

- In general, for AC and resistors $V = I R$

$$v(t) = V \cos \omega t$$

$$i(t) = I \cos \omega t$$

$$P(t) = v(t) i(t) = V I \cos^2 \omega t$$


$$= \frac{V I}{2} + \frac{V I}{2} \cos 2\omega t = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} + \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos 2\omega t$$

$$P_{average} = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} = V_{RMS} I_{RMS}$$

What the DMM reads!


What about an RLC Load?

- Consider

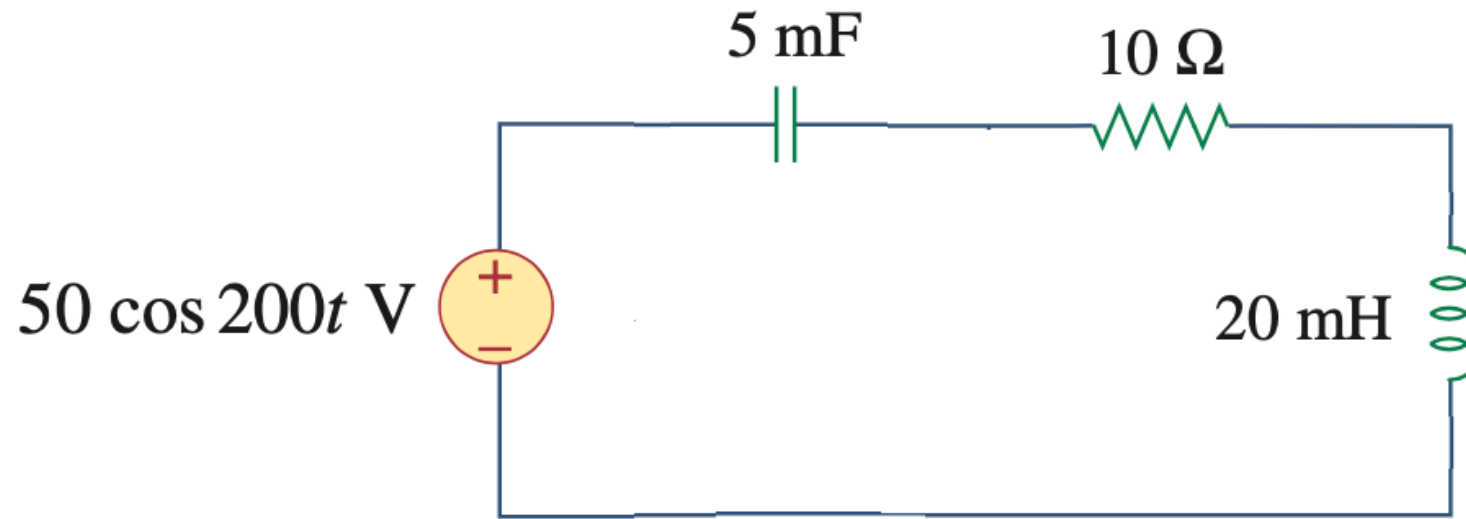

- Solve for the current and voltages using phasors


- Convert to phasors and impedances

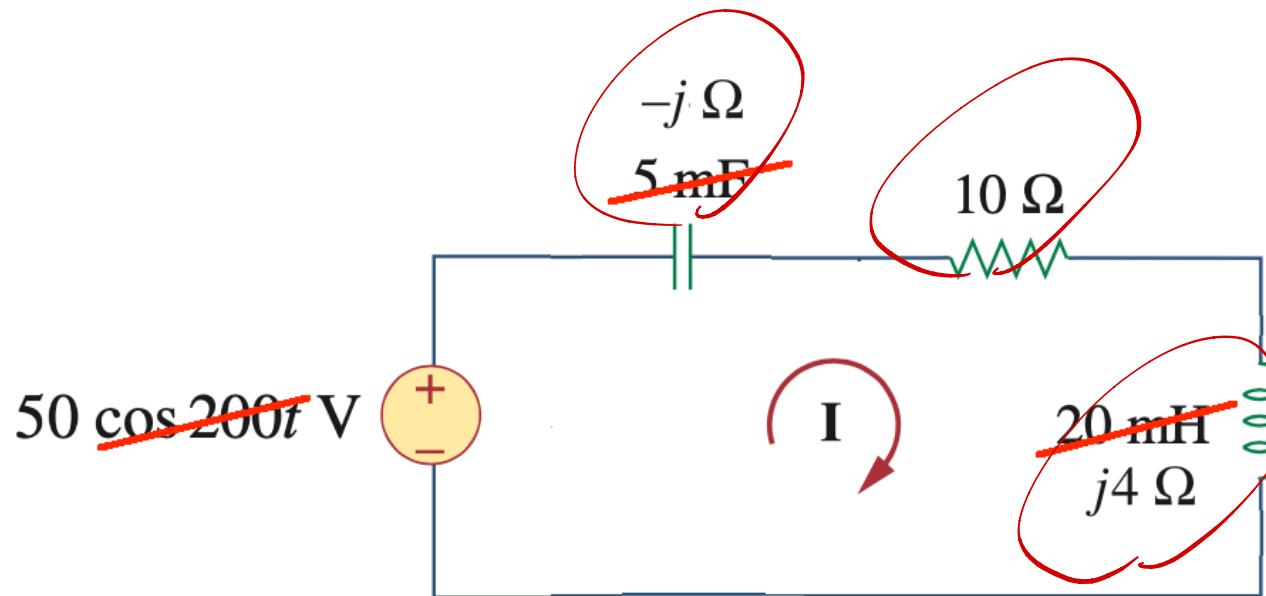


- The clockwise current is

$$\mathbf{I} = \frac{50}{-j1 + 10 + j4} = \frac{50}{10 + j3} = 4.59 - j1.38$$
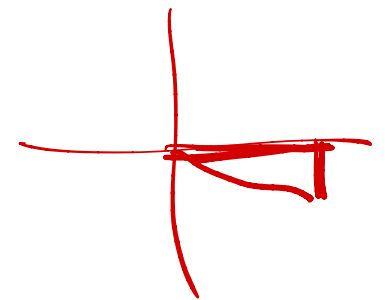
$$i(t) = 4.79 \cos(200t - 16.7^\circ) \text{ A}$$



- Resistor:

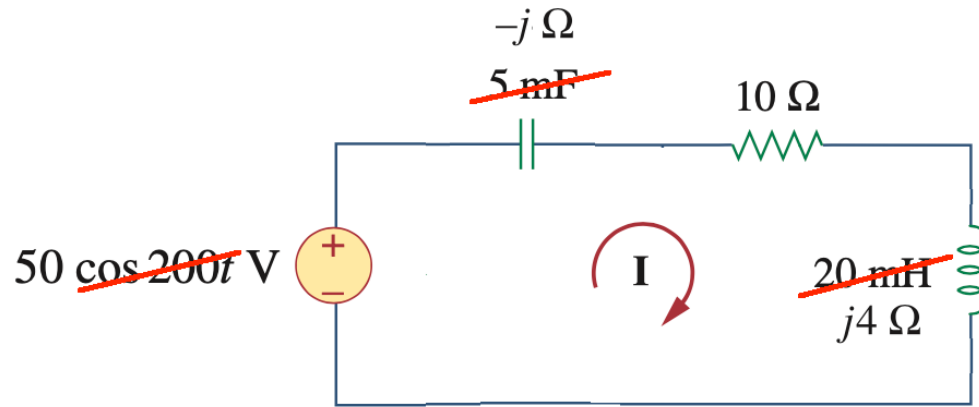

$$\mathbf{I} = 4.59 - j1.38$$

$$i(t) = 4.79 \cos(200t - 16.7^\circ) \text{ A}$$

$$\mathbf{V} = 10 \mathbf{I} = 45.9 - j13.8$$

$$v_R(t) = 47.9 \cos(200t - 16.7^\circ) \text{ V}$$


$$p(t) = v(t) i(t)$$

$$= 229 \cos^2(200t - 16.7^\circ) \text{ W}$$

$$= 115 + 115 \cos(400t - 33.4^\circ) \text{ W}$$

$$\text{So } P_{\text{average}} = 115 \text{ W}$$

- Inductor:

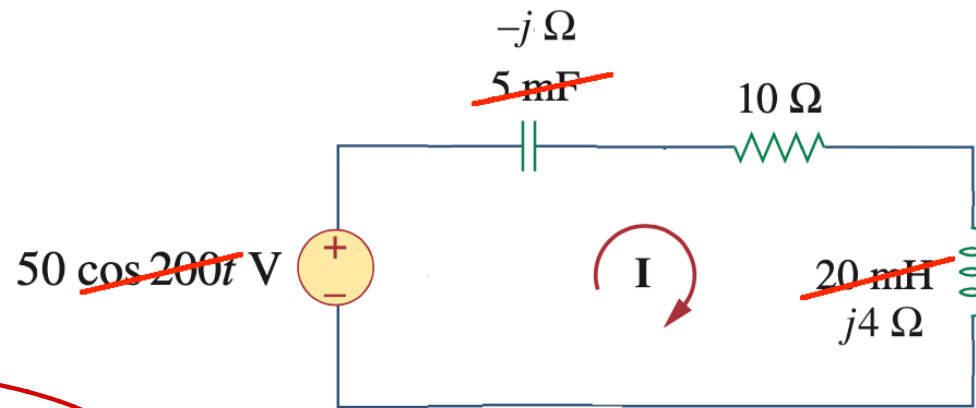

$$\mathbf{I} = 4.59 - j1.38$$

$$i(t) = 4.79 \cos(200t - 16.7^\circ) \text{ A}$$

$$\mathbf{V} = j4 \mathbf{I} = 5.50 + j18.3$$

$$v_L(t) = 19.2 \cos(200t + 73.3^\circ) \text{ V}$$


$$p(t) = v(t) i(t)$$

$$= 92.0 \cos(200t - 16.7^\circ) \cos(200t + 73.3^\circ) \text{ W}$$

$$= 46.0 \cos(400t + 56.6^\circ) \text{ W}$$

$$\text{So } P_{\text{average}} = 0$$

- Capacitor:

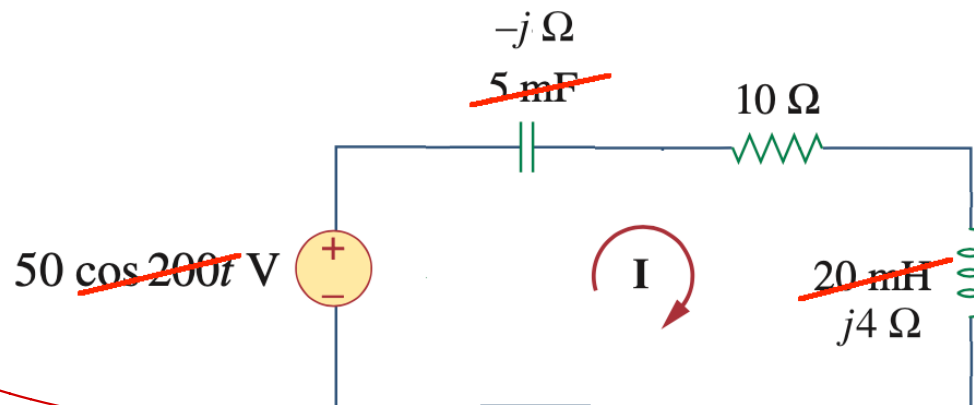

$$\mathbf{I} = 4.59 - j1.38$$

$$i(t) = 4.79 \cos(200t - 16.7^\circ) \text{ A}$$

$$\mathbf{V} = -j1 \mathbf{I} = -1.38 - j4.59$$

$$v_C(t) = 4.79 \cos(200t - 107^\circ) \text{ V}$$


$$p(t) = v(t) i(t)$$

$$= 22.9 \cos(200t - 16.7^\circ) \cos(200t - 107^\circ) \text{ W}$$

$$= 11.5 \cos(400t - 124^\circ) \text{ W}$$

So $P_{\text{average}} = 0$

- The source:

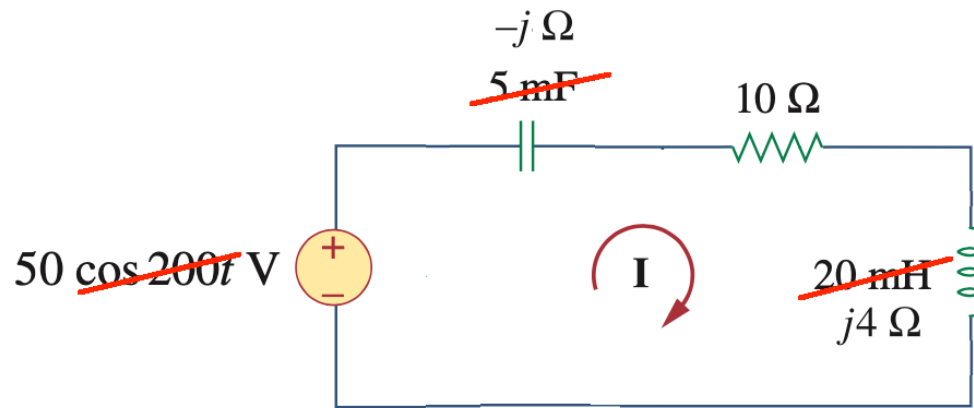

$$\mathbf{I} = 4.59 - j1.38$$

$$i(t) = 4.79 \cos(200t - 16.7^\circ) \text{ A}$$


$$\mathbf{V} = -50$$

$$V_s(t) = 50 \cos 200t \text{ V}$$

$$\begin{aligned} p(t) &= V_s(t) i(t) \\ &= -239 \cos 200t \cos(200t - 16.7^\circ) \text{ W} \\ &= -115 - 120 \cos(400t - 16.7^\circ) \text{ W} \end{aligned}$$

So $P_{\text{average}} = -115 \text{ W}$

- Summary:

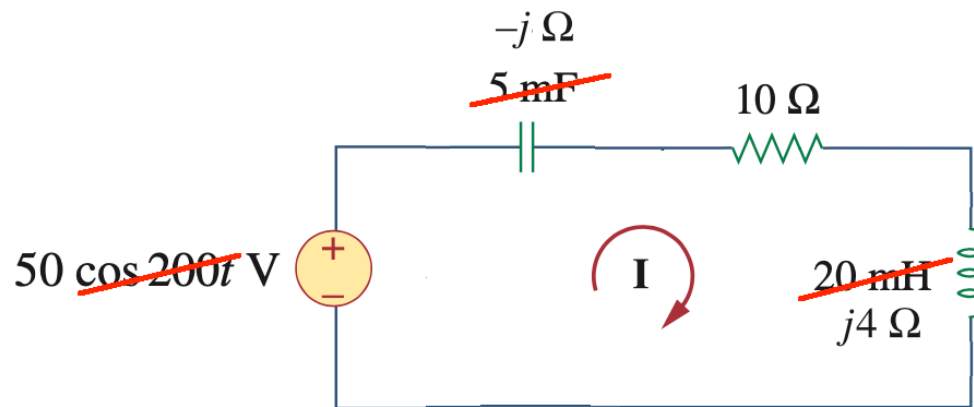

Real power
 $P = 115 \text{ Watts}$

$$P_R(t) = 115 + 115 \cos(400t - 33.4^\circ) \text{ W}$$

$$P_L(t) = 46.0 \cos(400t + 56.6^\circ) \text{ W}$$

$$P_C(t) = 11.5 \cos(400t - 124^\circ) \text{ W}$$

$$P_S(t) = -115 + 120 \cos(400t - 16.7^\circ) \text{ W}$$

Reactive power
 $Q = 34.5 \text{ VARs}$

Time varying portions sum to zero

Complex Power

$$S = P + jQ$$

Complex Power

- Can get these quantities directly from phasors

$$S = P + jQ = \frac{\mathbf{V} \mathbf{I}^*}{2} = \begin{cases} \frac{(\mathbf{Z} \mathbf{I}) \mathbf{I}^*}{2} = \frac{\mathbf{Z} \mathbf{I} \mathbf{I}^*}{2} = \frac{|\mathbf{I}|^2}{2} \mathbf{Z} \\ \frac{\mathbf{V} (\mathbf{V}/\mathbf{Z})^*}{2} = \frac{\mathbf{V} \mathbf{V}^*}{2 \mathbf{Z}^*} = \frac{|\mathbf{V}|^2}{2 \mathbf{Z}^*} \end{cases}$$

- Our example


$$S = \frac{50 (4.59 - j1.38)^*}{2} = 115 + j34.5$$

- Consider a load $\mathbf{Z} = |Z|e^{j\theta}$ and that we have the phasor relationship $\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}}$
 - The angle between the current and voltage phasors (vectors) is θ
- Further, recall the vector dot product so that the average power is

$$P = \frac{\mathbf{V} \mathbf{I}^*}{2} = \frac{|\mathbf{V}| |\mathbf{I}| \cos \theta}{2} = \frac{|\mathbf{V}|}{\sqrt{2}} \frac{|\mathbf{I}|}{\sqrt{2}} \cos \theta$$
$$= V_{RMS} I_{RMS} \cos \theta$$

“power factor”

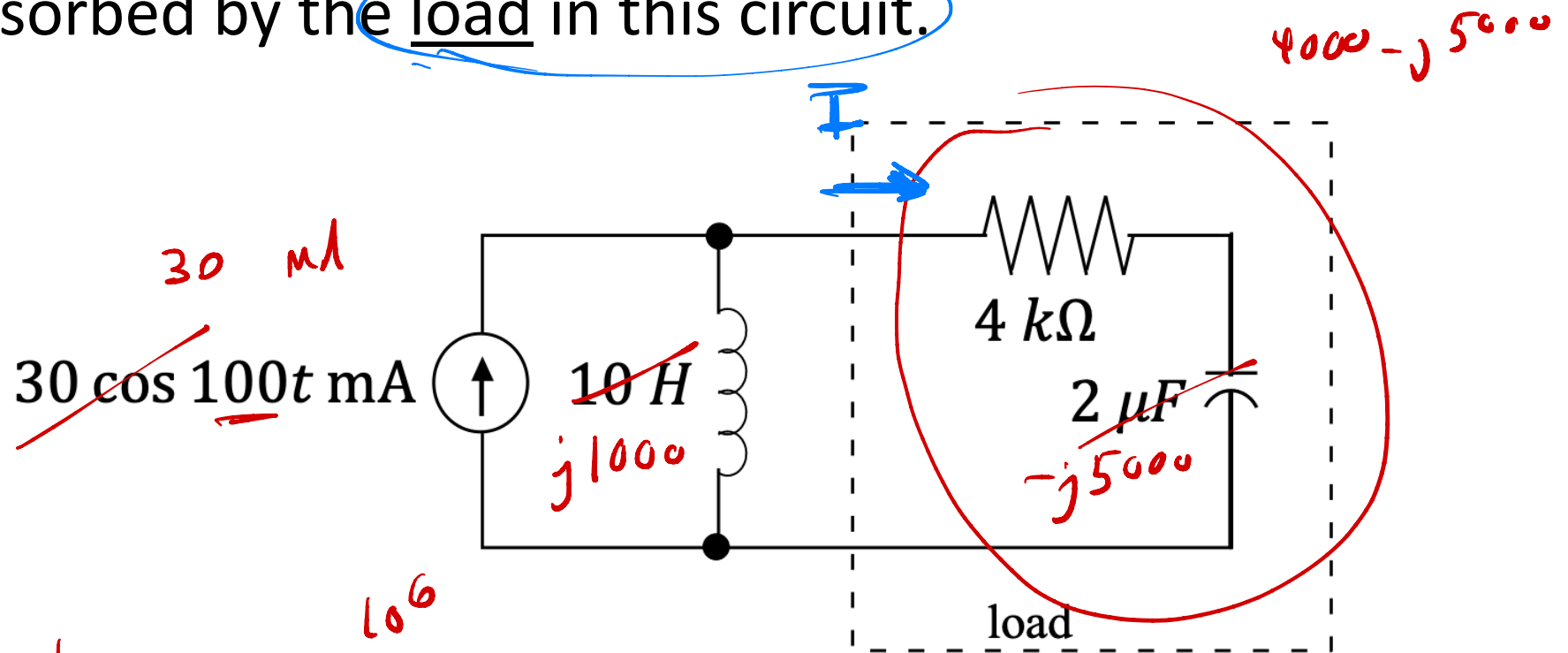Example problem: Find the real and reactive powers absorbed by the load in this circuit.



$$-j \frac{1}{\omega C} = -j \frac{10^6}{100 \cdot 2}$$

$$I = .03 \frac{j1000}{4000 - j5000 + j1000} = \frac{j1000}{4000 - j4000}$$

$$= \frac{j}{4(1-j)} \cdot \frac{17}{17} = \frac{-1+j}{8}$$

$$P = \frac{(|I|^2}{2} Z = \frac{\frac{2}{64} (4000 - j5000)}{2}$$

$$I = \frac{-1+j}{8}$$

$$|I| = \frac{\sqrt{2}}{8}$$

$$Z = 4000 - j5000$$



56.25 mW, 56.25 mVARs