


2nd Order Transients – 2

Form; more resistances;
initial and final conditions

So far, for “simple” RLC circuits


- Step 1 – identify type and form characteristic polynomial

Parallel

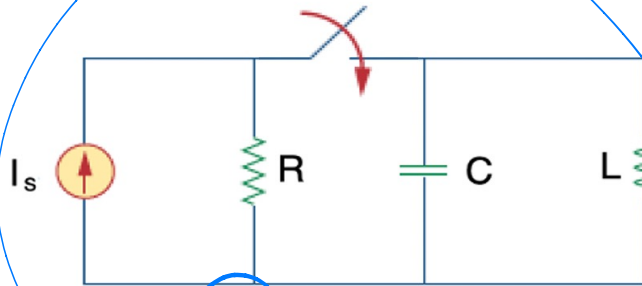

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Series

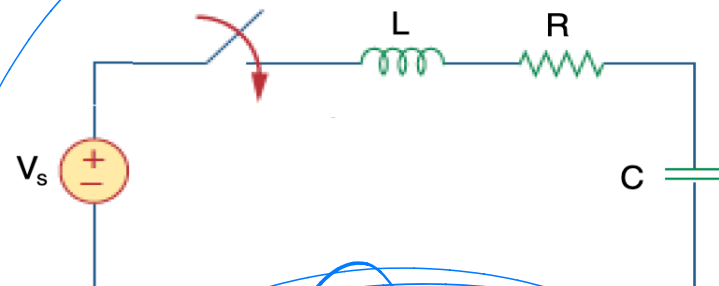

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- Step 2 – based on real vs complex roots, identify form of solution

Real roots:


$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

Complex roots:

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

- Step 3 – use final value to evaluate x_∞
- Step 4 – the other constants?

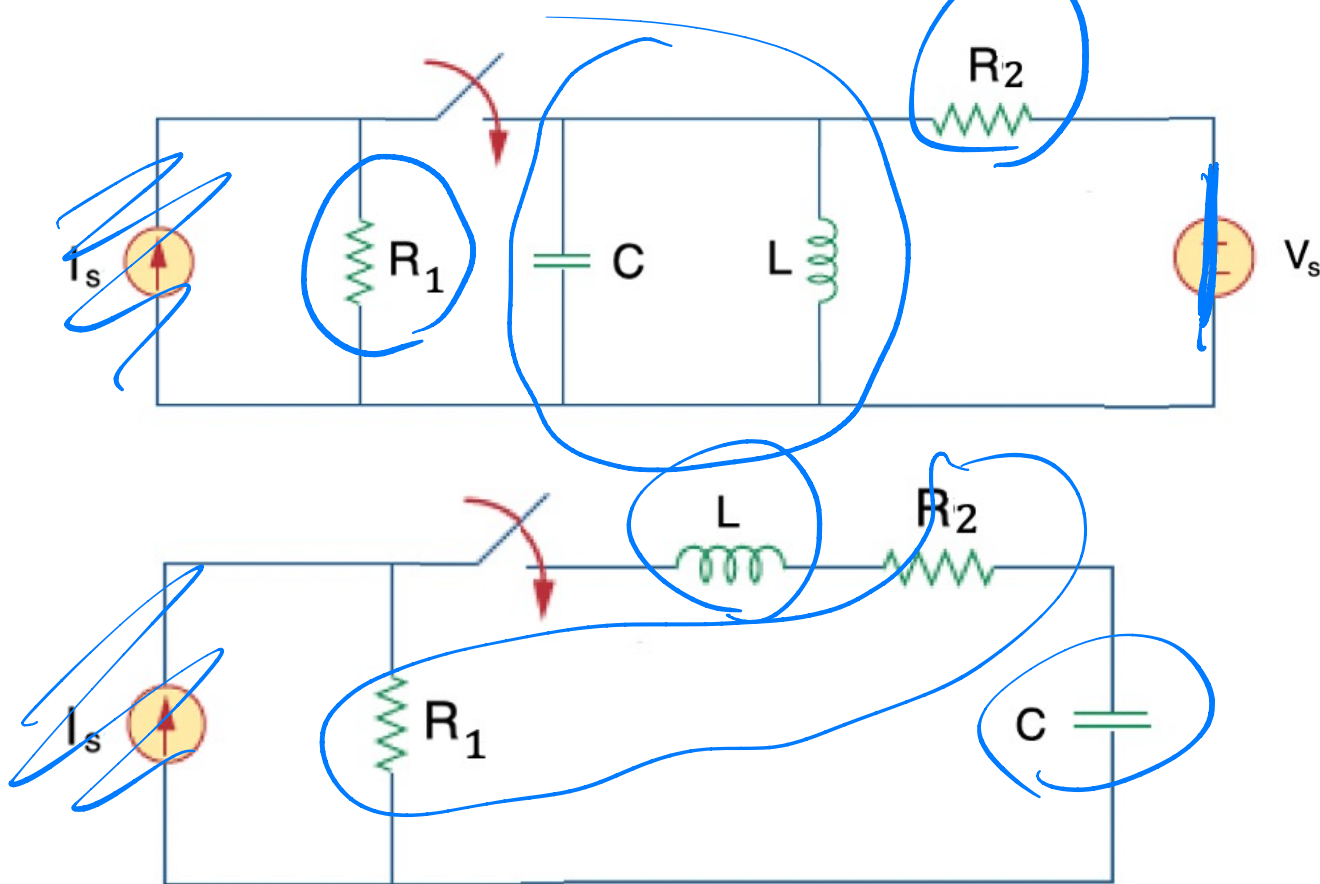- Aside – what if we add an extra resistor?



Parallel form



$$R = R_1 \parallel R_2$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC}$$


$$R = R_1 + R_2$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- Or several?

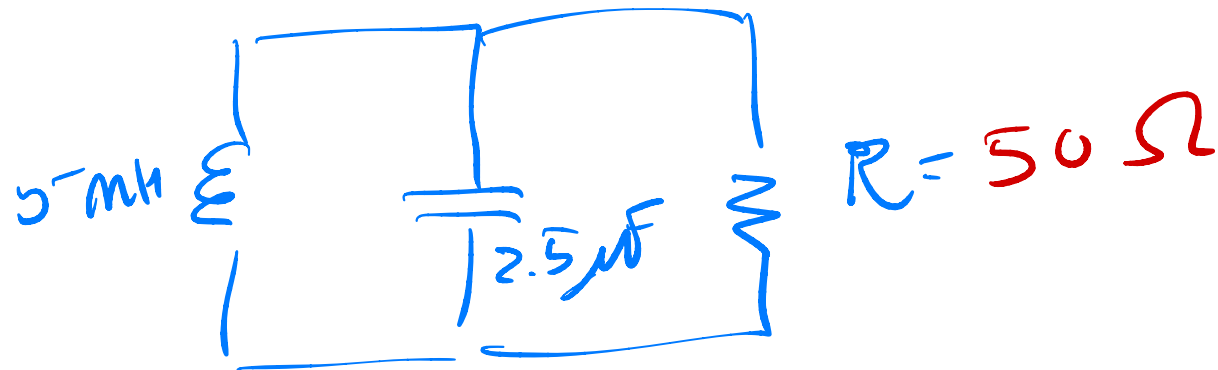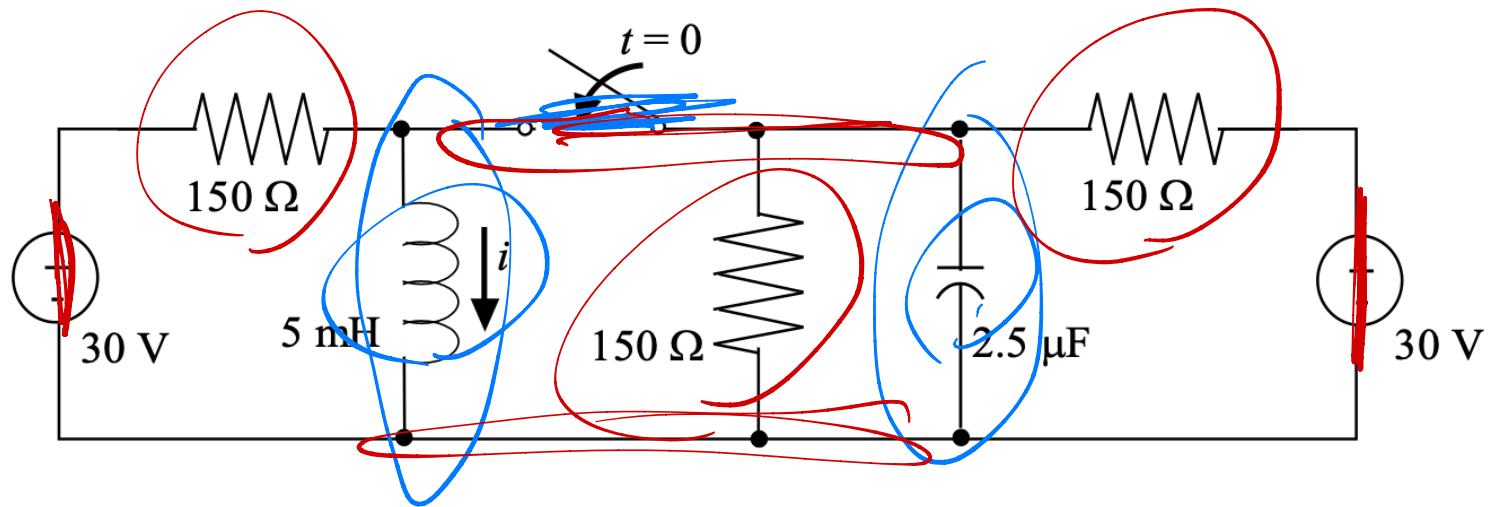

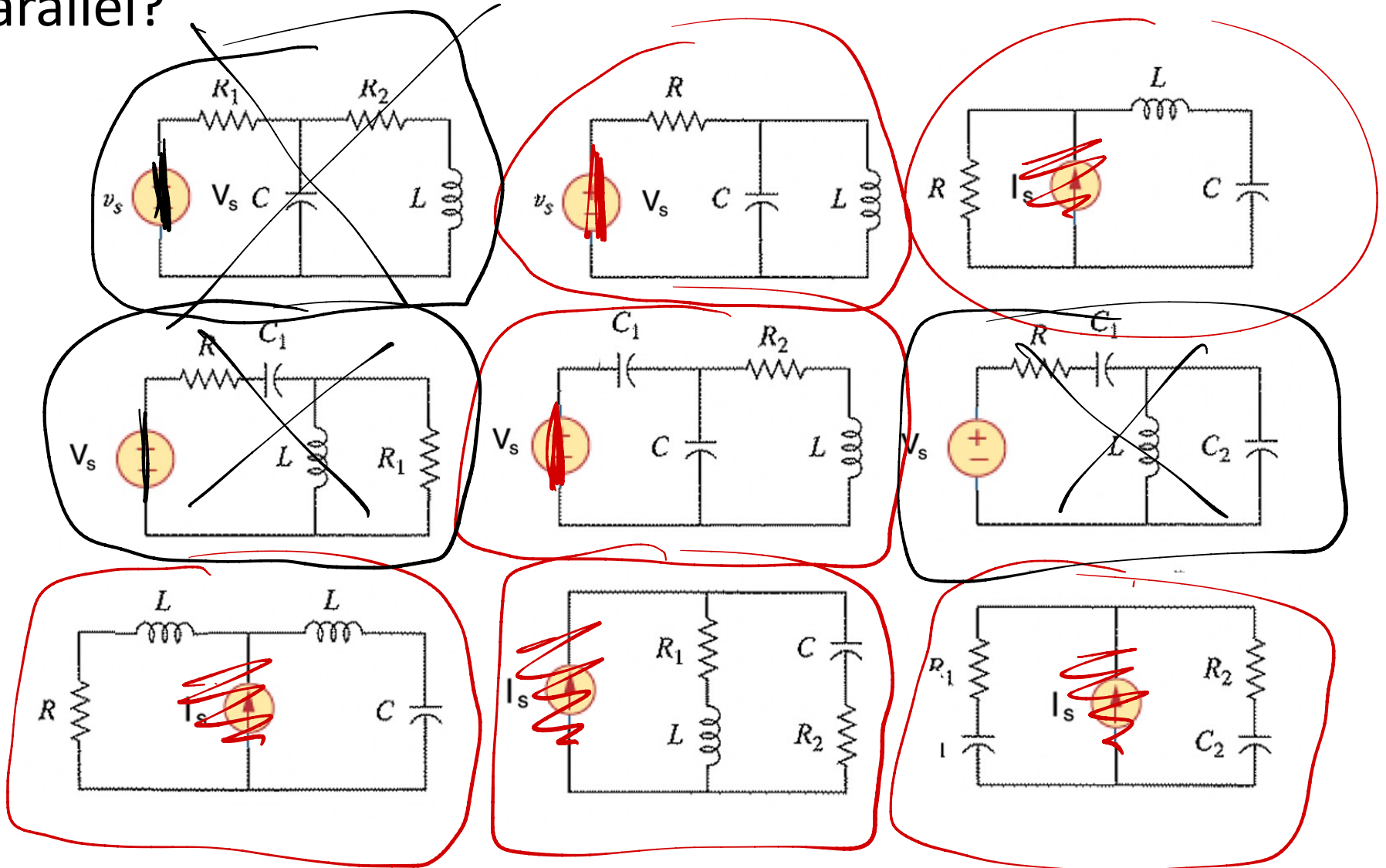
Question: Which of these circuits match our assumed 2nd order RLC circuit form? If yes, which form, series or parallel?



Initial and Final Conditions

- Just like the 1st order case:
 - From a DC analysis based on “open” or “short” models for C and L both before and after the switch event
 - Before switching event yields initial values
 - After switching event yields final values

Example:

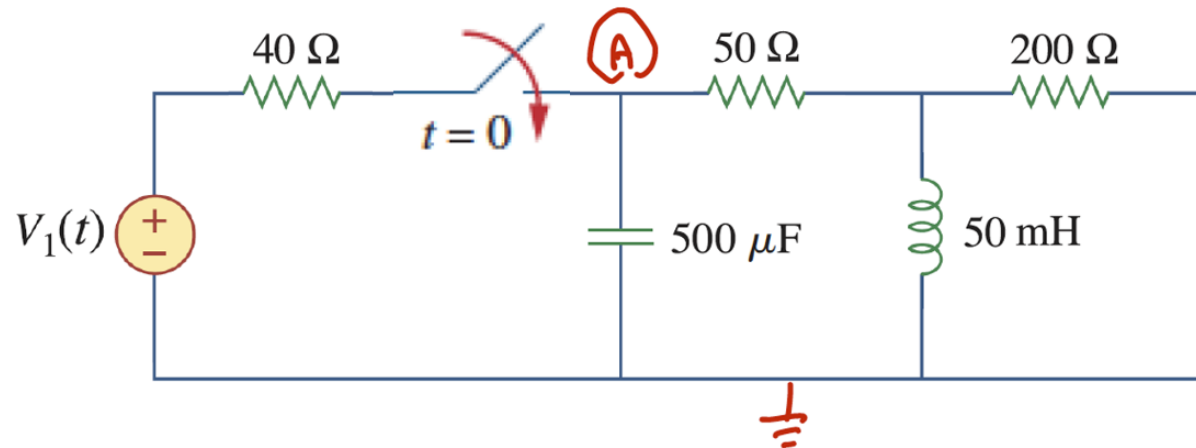

$$A(t) = a_0 + a_1 e^{-94.3t} + a_2 e^{-764t}$$

- $A(0) = 0$
- $A(\infty) = \frac{5}{9} V_1$


$$a_0 = \frac{5}{9} V_1$$

$$a_0 + a_1 + a_2 = 0$$


$$t \rightarrow \infty$$

$$t = 0^-$$

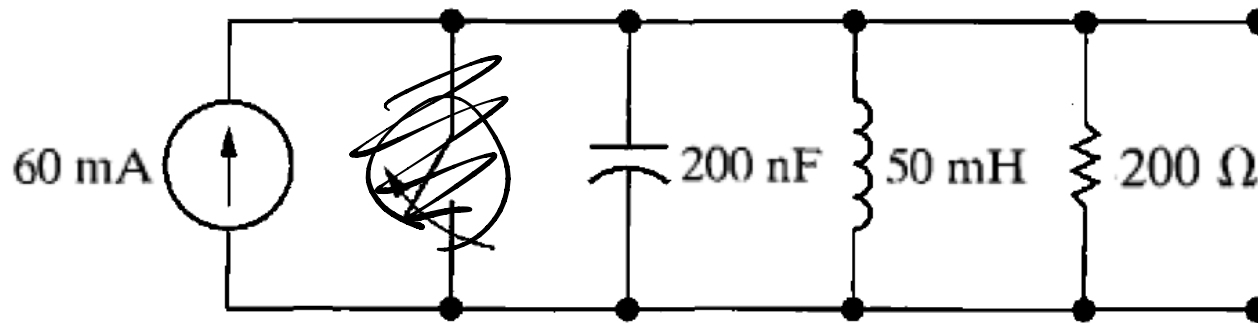Example: Find the initial/final conditions




$$t \rightarrow \infty$$

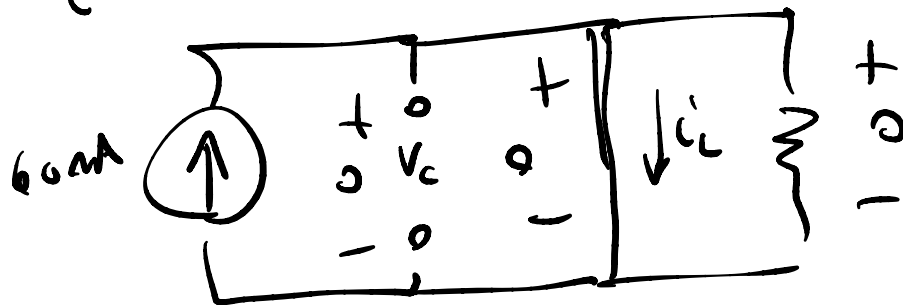

$$v_C(\infty) = 0$$

$$i_L(\infty) = 60 \text{ mA}$$


$$t = 0^-$$

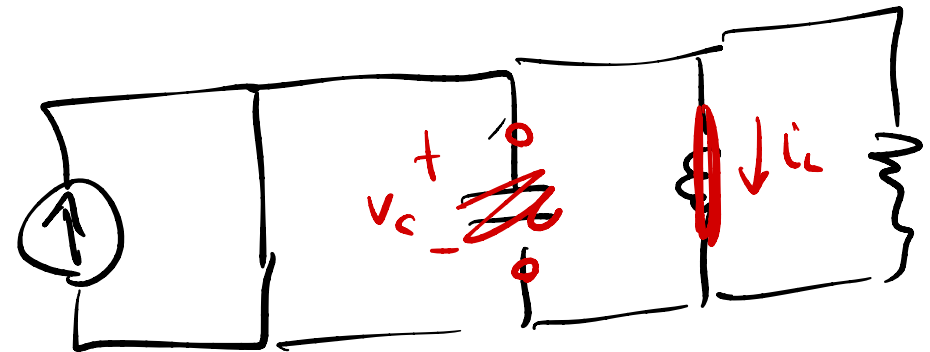

$$i_L(0^-) = 0$$

$$v_C(0^-) = 0$$

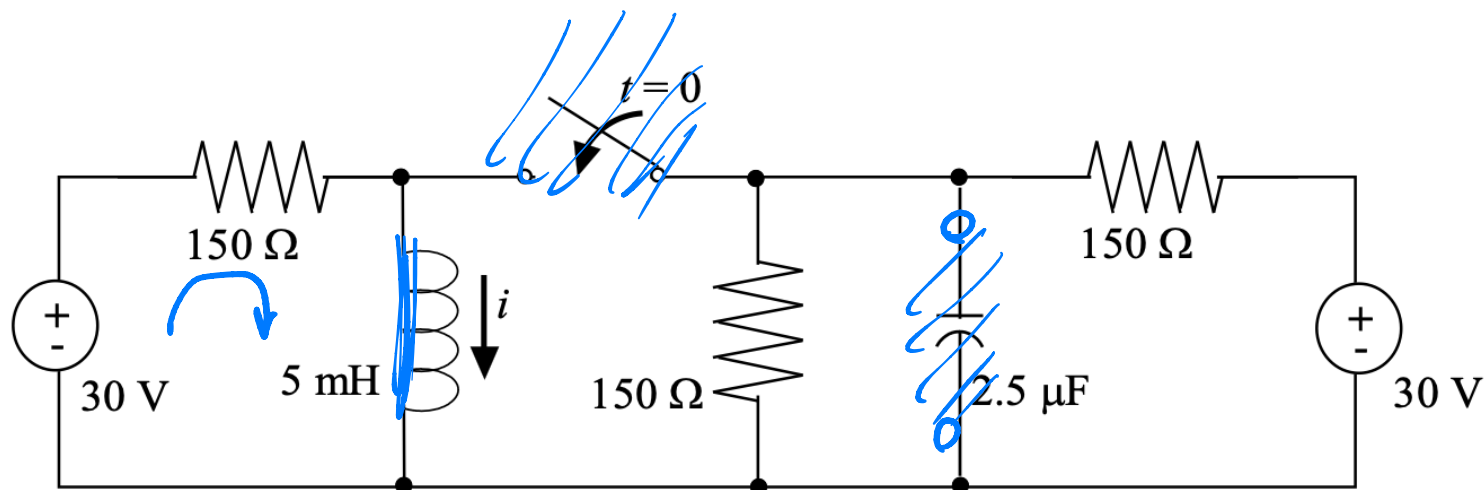Example: Find the initial/final conditions




$t \rightarrow \infty$

$$i_L(\infty) = .4 \text{ A}$$

$$v_C(\infty) = 0$$


$t = 0^-$

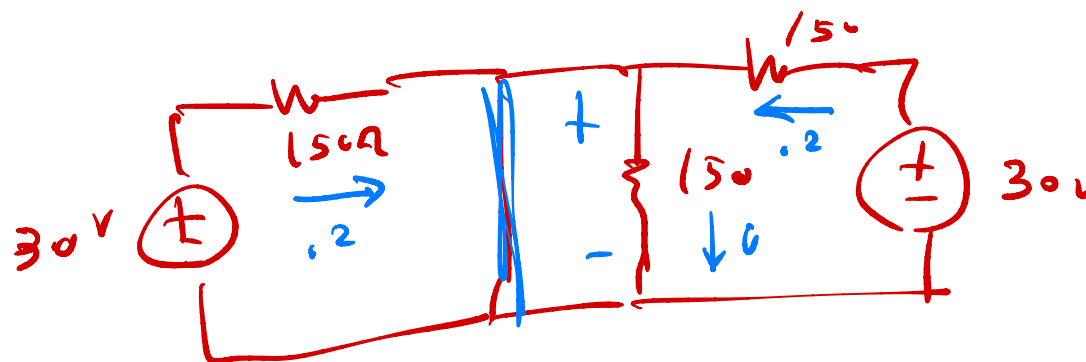

$$i_L(0^-) = \frac{30}{150} = .2 \text{ A}$$

$$v_C(0^-) = 15 \text{ V}$$

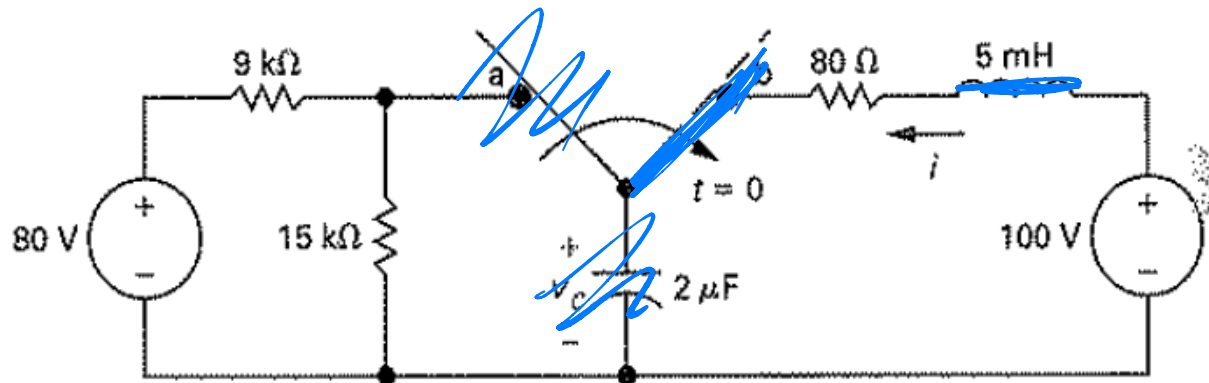Example: Find the initial/final conditions




$$i_L(0^-) = 0 \text{ A}$$


$$v_C(0^-) = 80 \cdot \frac{15}{15+9}$$

$$i_L(\infty) = 0 \text{ A}$$

$$v_C(\infty) = 100 \text{ V}$$

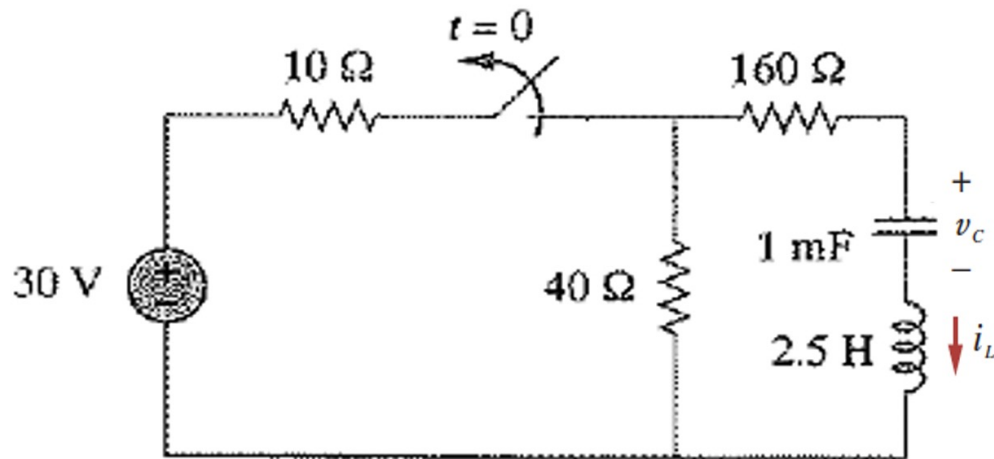Practice problem: Find the form of solution and the initial/final conditions



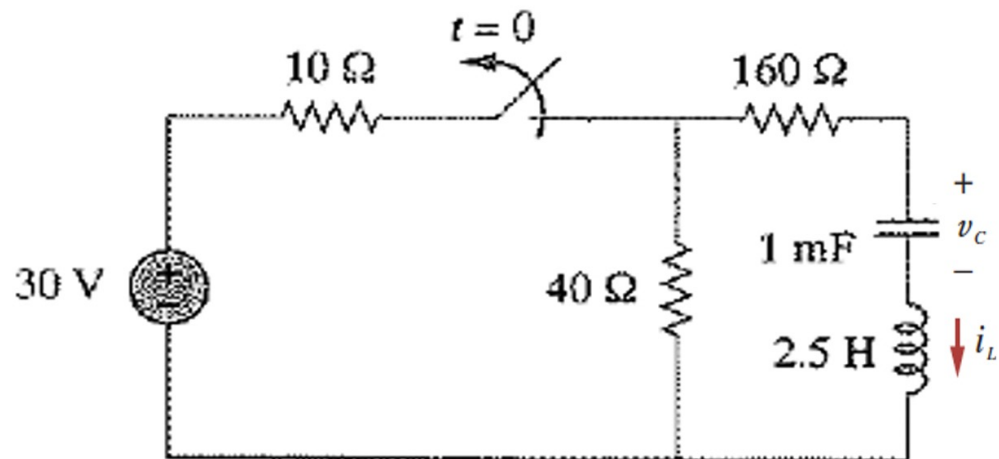

$$x(t) = A_1 e^{-5.36t} + A_2 e^{-74.6t} + x_\infty$$


$$i_L(0) = 0 \text{ A}$$


$$i_L(\infty) = 0 \text{ A}$$

$$v_C(0) = 24 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

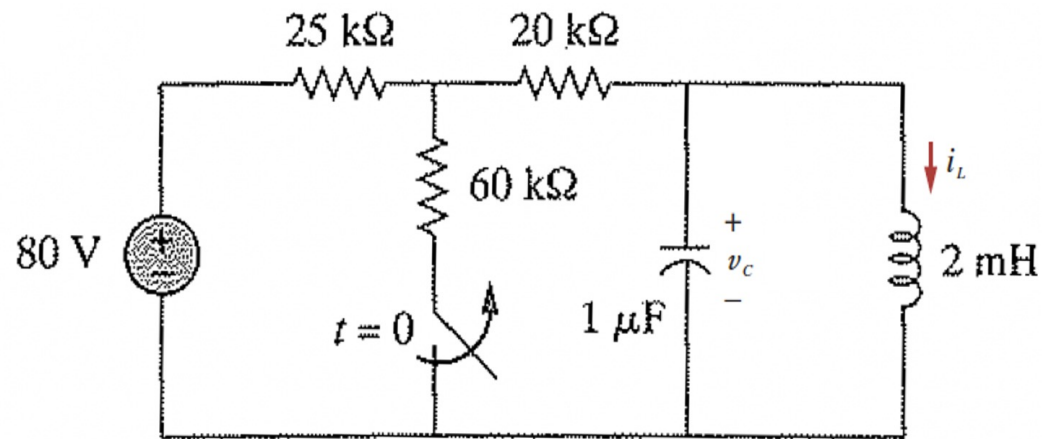Practice problem: Find the form of solution and the initial/final conditions



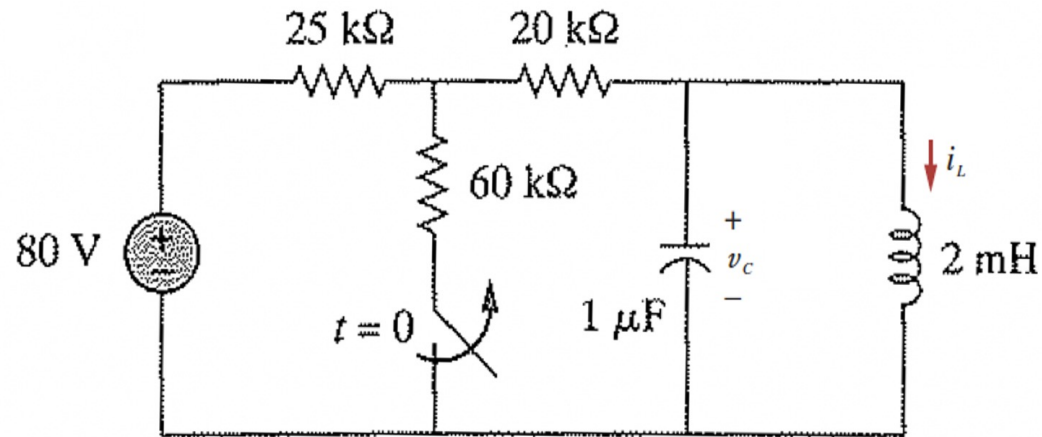

$$x(t) = B_1 e^{-11.1t} \cos 22361t + B_2 e^{-11.1t} \sin 22361t + x_\infty$$


$$i_L(0) = 1.5 \text{ A}$$


$$i_L(\infty) = \frac{16}{9} \text{ A}$$

$$v_C(0) = 0 \text{ V}$$

$$v_C(\infty) = 0 \text{ V}$$

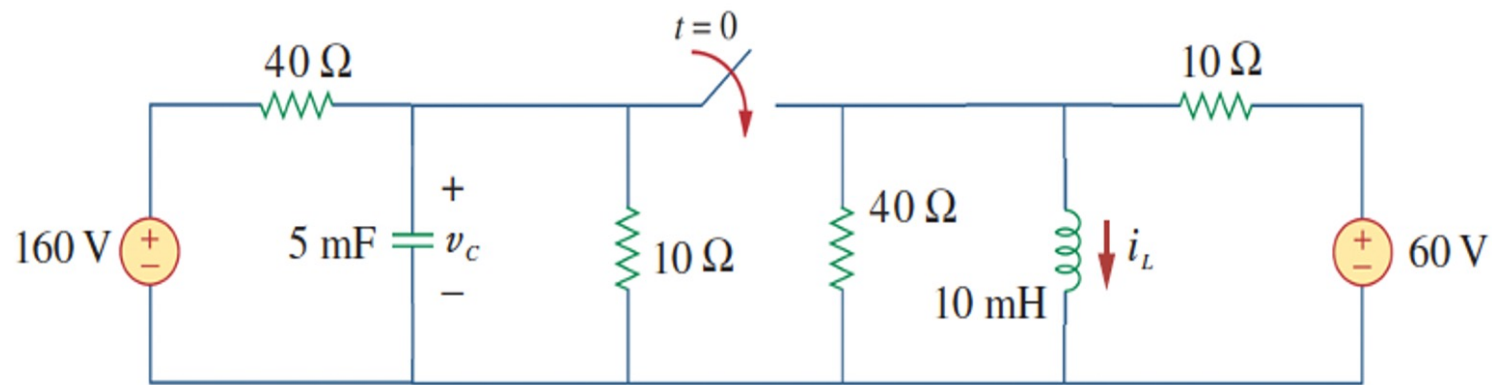Practice problem: Find the form of solution and the initial/final conditions



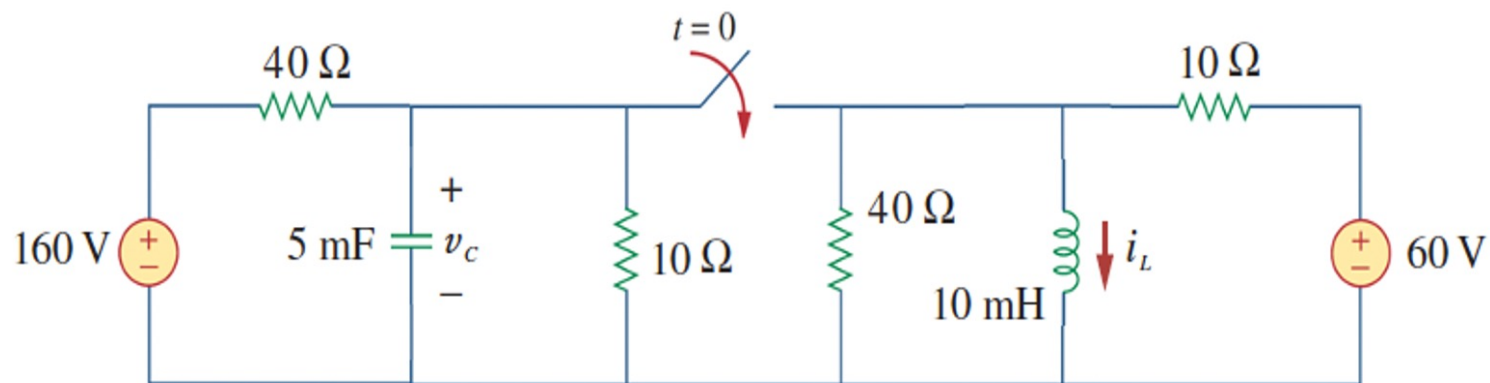

$$x(t) = B_1 e^{-25t} \cos 139t + B_2 e^{-25t} \sin 139t + x_\infty$$

$$i_L(0) = 6 \text{ A}$$

$$i_L(\infty) = 10 \text{ A}$$

$$v_c(0) = 32 \text{ V}$$

$$v_c(\infty) = 0 \text{ V}$$