

2nd Order Transients – 3

the full solution

How to find the constants?

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

- x_∞ is easy
 - Short inductor, open capacitor, solve DC problem
- Initial condition ($v_C(0)$ or $i_L(0)$) is not enough

$$x(0) = A_1 + A_2 + x_\infty$$

$$x(0) = B_1 + x_\infty$$

Approach: include a derivative condition at time 0

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$x'(t) = s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}$$

$$x'(0) = s_1 A_1 + s_2 A_2$$

use with $x(0) = A_1 + A_2 + x_\infty$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

$$x'(t) = -\alpha B_1 e^{-\alpha t} \cos \omega_d t - \alpha B_2 e^{-\alpha t} \sin \omega_d t \\ - \omega_d B_1 e^{-\alpha t} \sin \omega_d t + \omega_d B_2 e^{-\alpha t} \cos \omega_d t$$

$$x'(0) = -\alpha B_1 + \omega_d B_2$$

use with $x(0) = B_1 + x_\infty$

Solving

- Overdamped (2 real roots, s_1, s_2):

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$A_1 = \frac{x'(0) - s_2 [x(0) - x_\infty]}{s_1 - s_2}$$
$$A_2 = \frac{s_1 [x(0) - x_\infty] - x'(0)}{s_1 - s_2}$$

- Underdamped (complex roots, $-\alpha \pm j\omega_d$):

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

$$B_1 = x(0) - x_\infty$$

$$B_2 = \frac{x'(0) + \alpha [x(0) - x_\infty]}{\omega_d}$$

Question – how do we get the derivative's value?

- Answer – Recall

For a capacitor


$$i = C \frac{dv}{dt}$$
$$\text{so } v'(0) = \frac{1}{C} i(0)$$


For an inductor

$$v = L \frac{di}{dt}$$
$$\text{so } i'(0) = \frac{1}{L} v(0)$$

Use KVL, KCL to get the capacitor current or inductor voltage

- Example – the parallel case

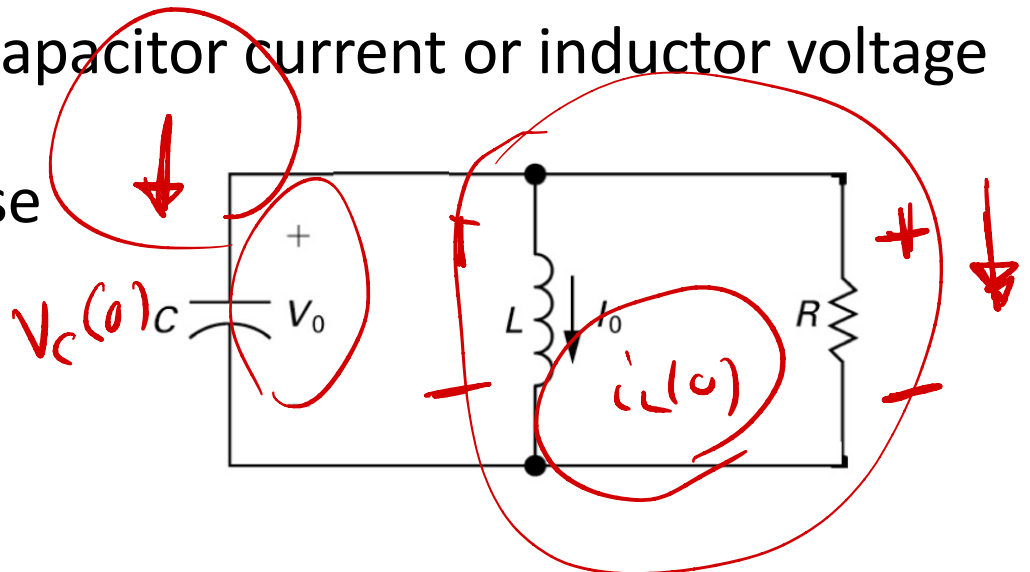

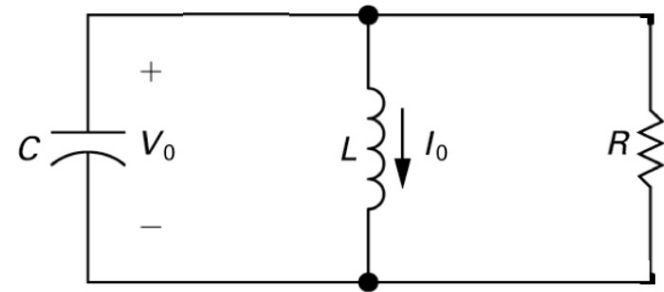

- Use KCL to find $v_C'(0)$

$$i_C(t) + i_R(t) + i_L(t) = 0 \quad \rightarrow \quad C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} + i_L(t) = 0$$

$$v_C'(0) = -\frac{v_C(0)}{RC} - \frac{i_L(0)}{C}$$

- Use KVL to find $i_L'(0)$


$$v_L(t) = v_C(t) \quad \rightarrow \quad L \frac{di_L(t)}{dt} = v_C(t)$$

$$i_L'(0) = \frac{v_C(0)}{L}$$

Example: Find the derivative conditions

$$i_L'(0) = 10,000 \text{ A/s}$$

$$v_C'(0) = 0 \text{ V/s}$$

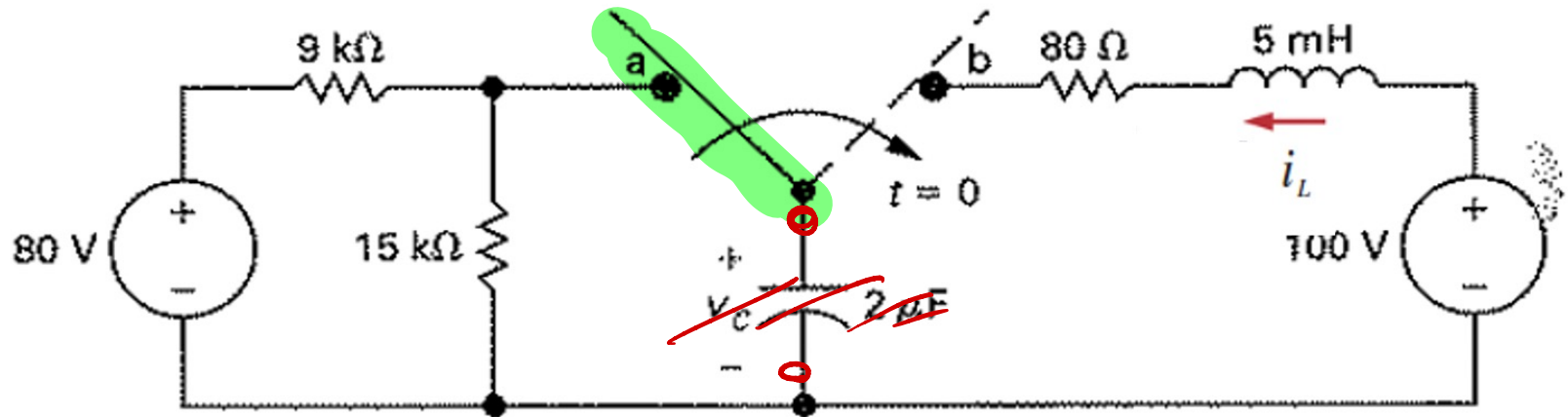

$$t \rightarrow \infty$$

$$i_L(\infty) = 0$$

$$v_C(\infty) = 100 \text{ V}$$

$$t = 0^-$$

$$v_C(0^-) = 50 \text{ V}$$

$$i_L(0^-) = 0$$

$$t = 0$$

$$v_C(0) = 50 \text{ V}$$

$$i_L(0) = 0$$


$$v_C'(0) = 0$$

$$i_L'(0) = 10^4$$

Example: Find the derivative conditions

$$i_L'(0) = 0 \text{ A/s}$$

$$v_C'(0) = -300,000 \text{ V/s}$$

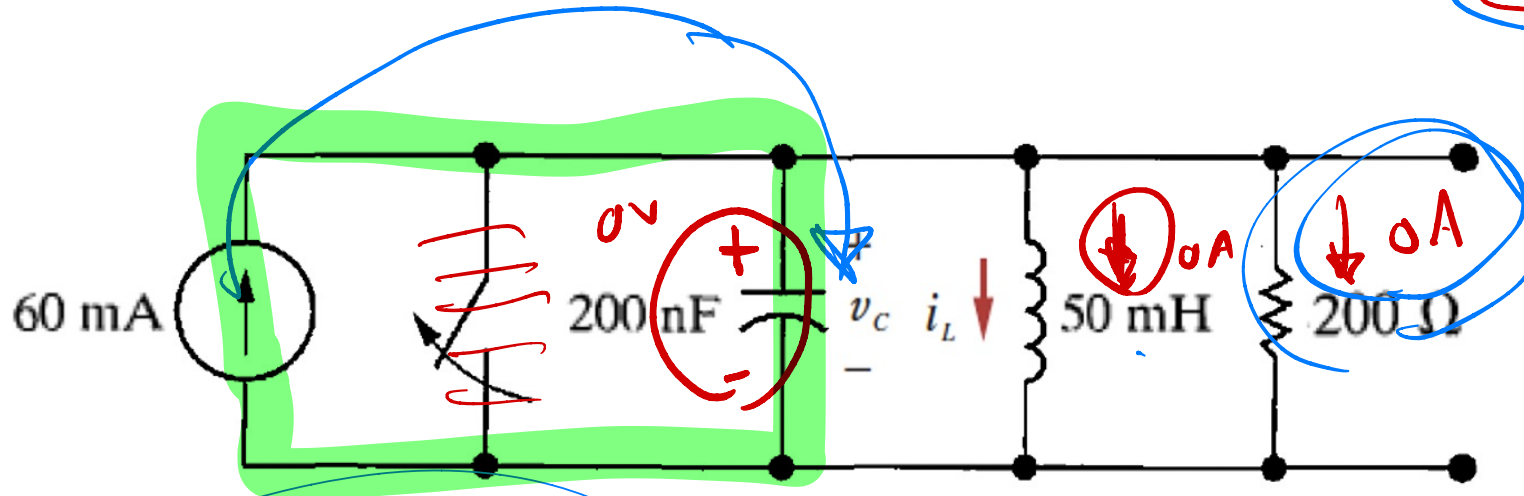

$t = 0^-$

$$v_C(0^-) = v_C(0) = 0$$

$$i_L(0^-) = i_L(0) = 0$$

$t = 0$

$$v_C'(0) = \frac{1}{C} i_L(0)$$

$$= \frac{1}{C} [60 \cdot 10^{-3}]$$


$$i_L'(0) = \frac{1}{L} v_C(0) = 0$$

Total Solution

1. Identify type (series/parallel) and values of R,L,C
2. Root characteristic equation, to find form
3. Find $i_L(0)$ and $v_C(0)$
4. For variable of interest, find $x(0)$, $x'(0)$, and $x(\infty)$
5. Assemble answer

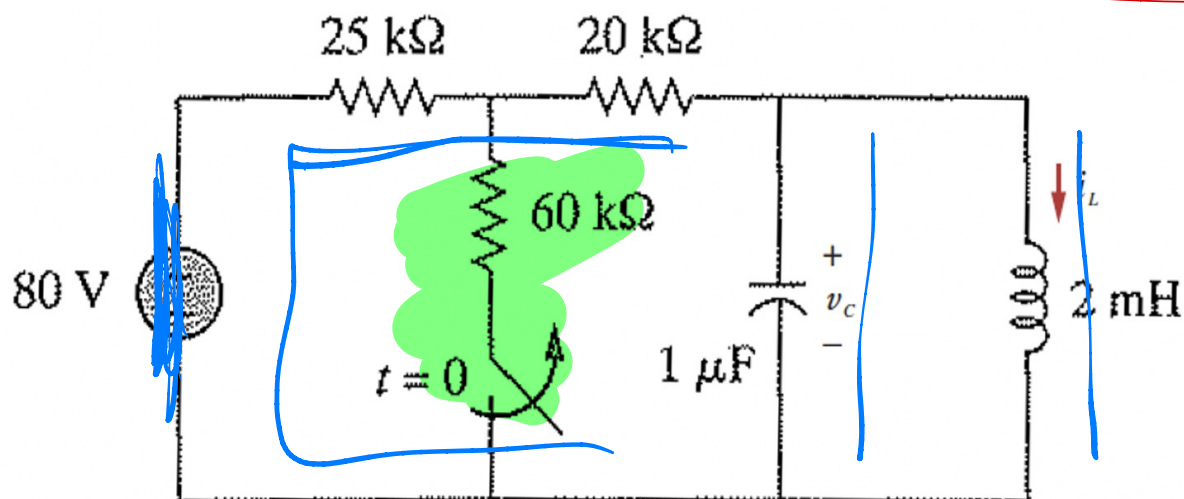Example: Find $v_C(t)$

$$v_C(t) = -7.45 e^{-11.1t} \sin 22361t \text{ V}$$



parallel

$$R = 45 \text{ k}\Omega$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC}$$

$$s^2 + 222s + 5 \cdot 10^8 = 0$$

$$s = -11.1 \pm j 22361$$

$$v_C(t) = \cancel{B_1} e^{-11.1t} \cos 22361t + B_2 e^{-11.1t} \sin 22361t + \cancel{v_C(\infty) = 0}$$

$$v_C(\infty) = 0$$

$$v_C(0) = 0$$

$$v'_C(0) = \frac{5}{18} \cdot 10^6$$

Cheat Sheet

Parallel:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Series:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Overdamped:

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x_\infty$$

$$A_1 = \frac{x'(0) - s_2[x(0) - x_\infty]}{s_1 - s_2} \quad A_2 = \frac{s_1[x(0) - x_\infty] - x'(0)}{s_1 - s_2}$$

Underdamped:


$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t + x_\infty$$

$$B_1 = x(0) - x_\infty$$

$$B_2 = \frac{x'(0) + \alpha[x(0) - x_\infty]}{\omega_d}$$


$\frac{5}{10} \cdot 10^4 -$
 22361

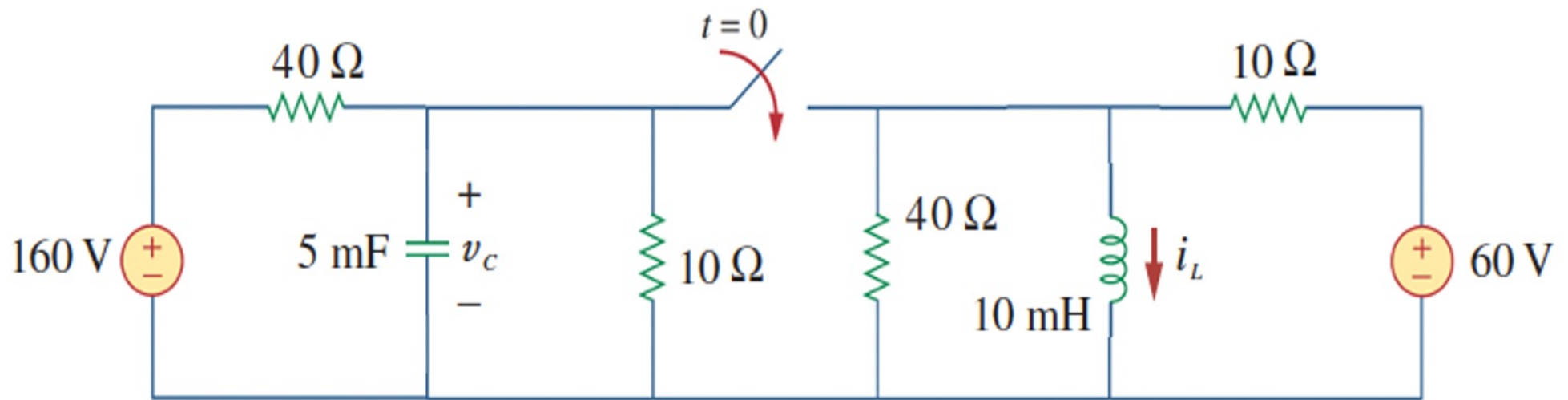Practice problem: Find the derivative conditions




$$\begin{aligned}i_L'(0) &= 3200 \text{ A/s} \\v_c'(0) &= -800 \text{ V/s}\end{aligned}$$

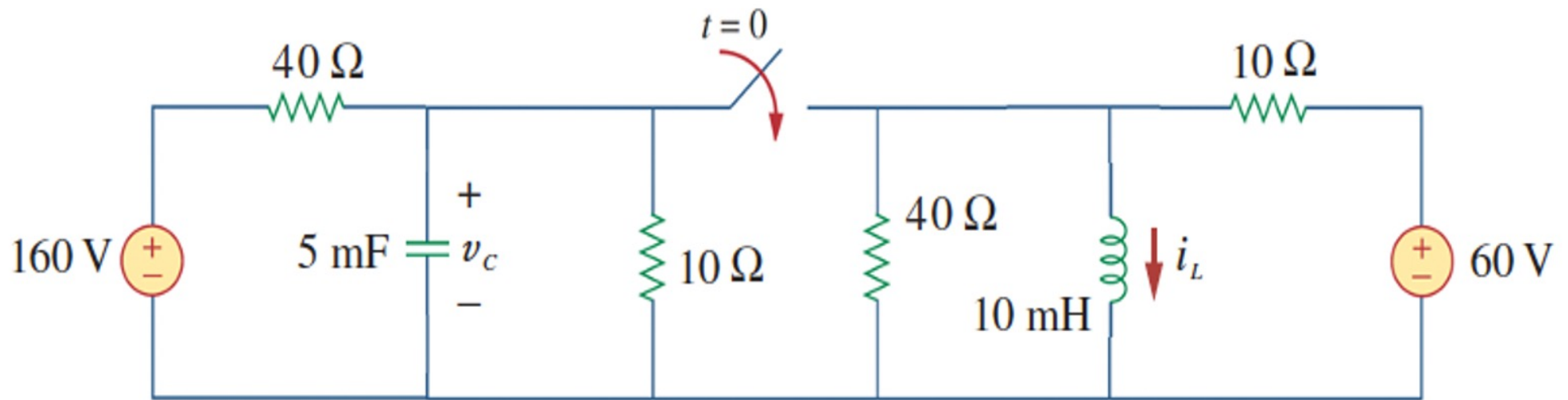Practice problem: Find the final form for $i_L(t)$




$$i_L(t) = -4 e^{-25t} \cos 139t + 22.3 e^{-25t} \sin 139t + 10 \text{ A}$$

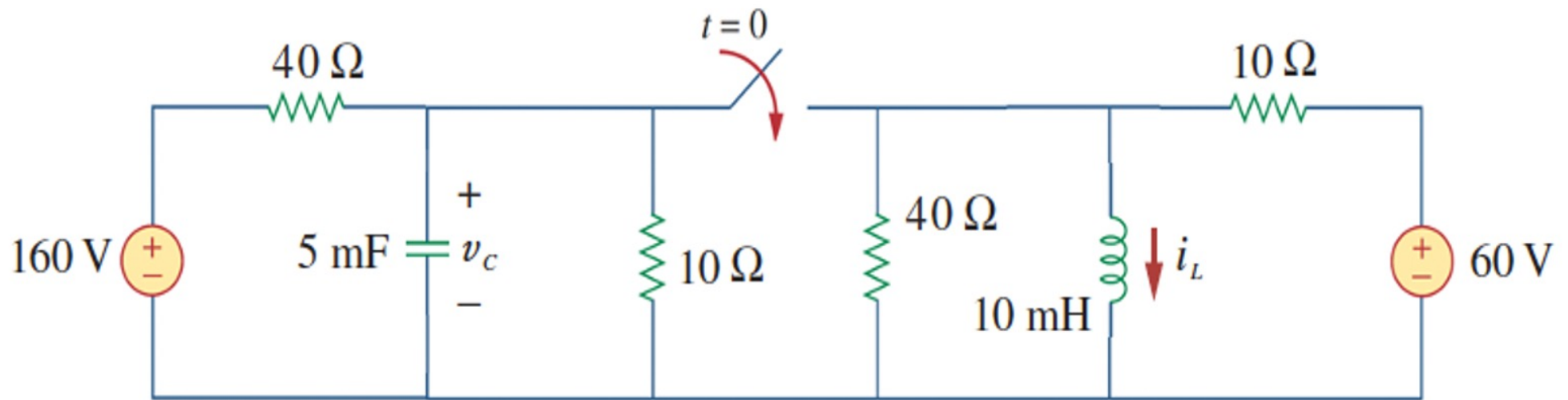Practice problem: Find the final form for $v_C(t)$



$$v_C(t) = 32 e^{-25t} \cos 139t \text{ V}$$

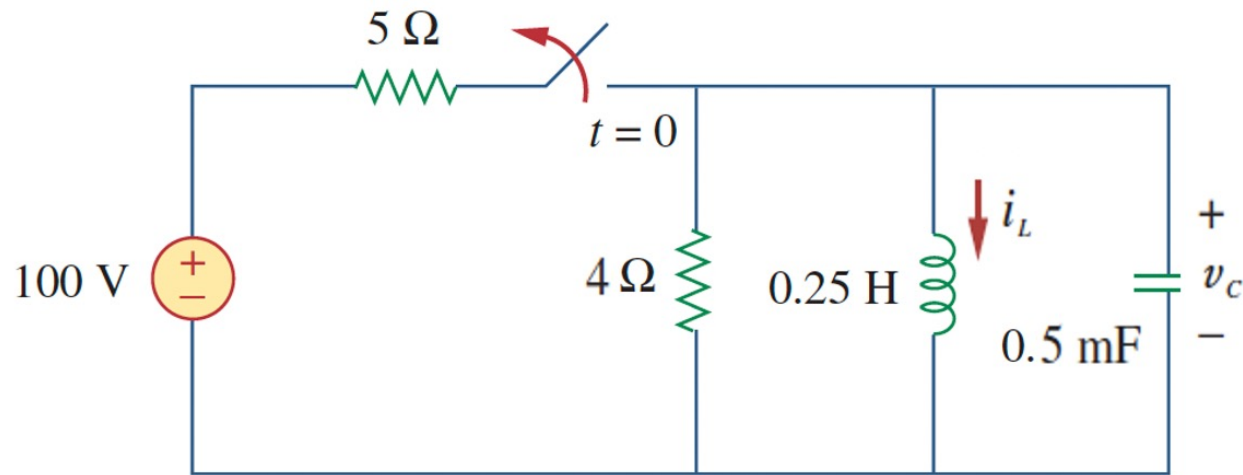
Practice problem: Find form and the initial, final, and derivative conditions



$$x(t) = A_1 e^{-16.6t} + A_2 e^{-483t} + x_\infty$$


$$\begin{aligned} i_L(0) &= 20 \text{ A} \\ i_L(\infty) &= 0 \text{ A} \\ i_L'(0) &= 0 \text{ A/s} \\ v_C(0) &= 0 \text{ V} \\ v_C(\infty) &= 0 \text{ V} \\ v_C'(0) &= -40,000 \text{ V/s} \end{aligned}$$

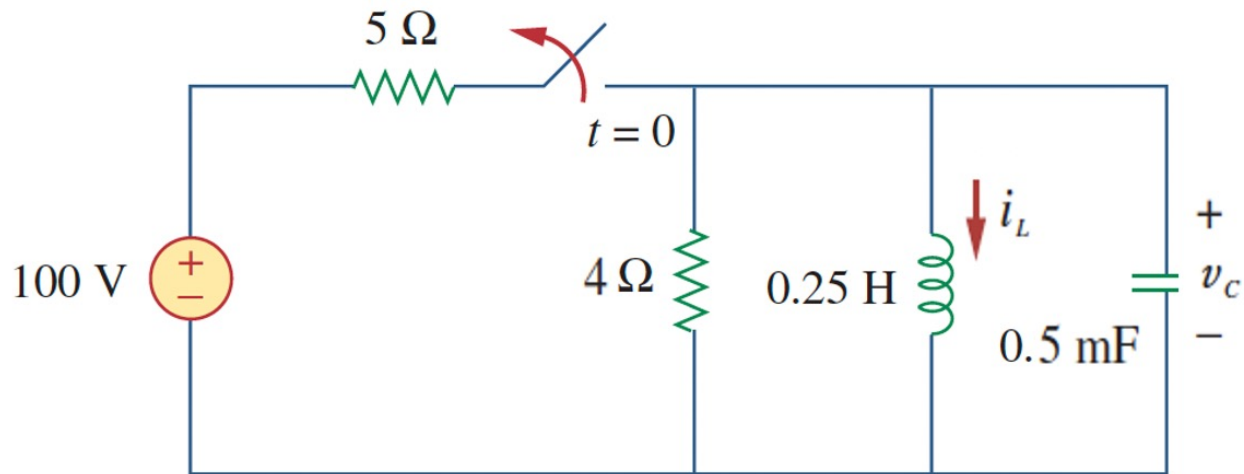Practice problem: Find the final form for $i_L(t)$




$$i_L(t) = 20.7e^{-16.6t} - 0.709e^{-483t} \text{ A}$$

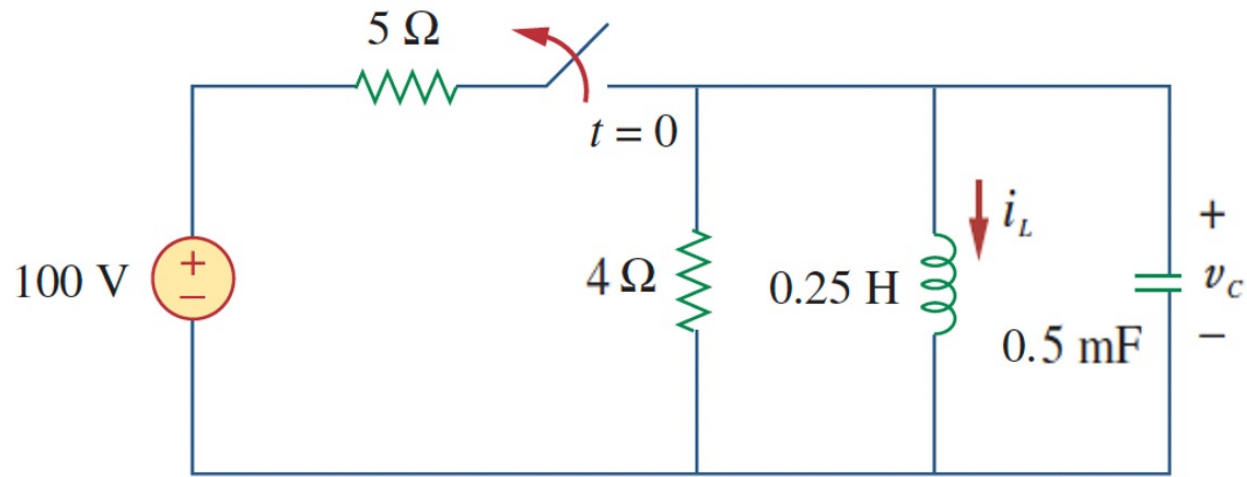Practice problem: Find the final form for $v_C(t)$




$$v_C(t) = -85.7 e^{-16.6t} + 85.7 e^{-483t} \text{ V}$$

Practice problem: Find $i_o(t)$

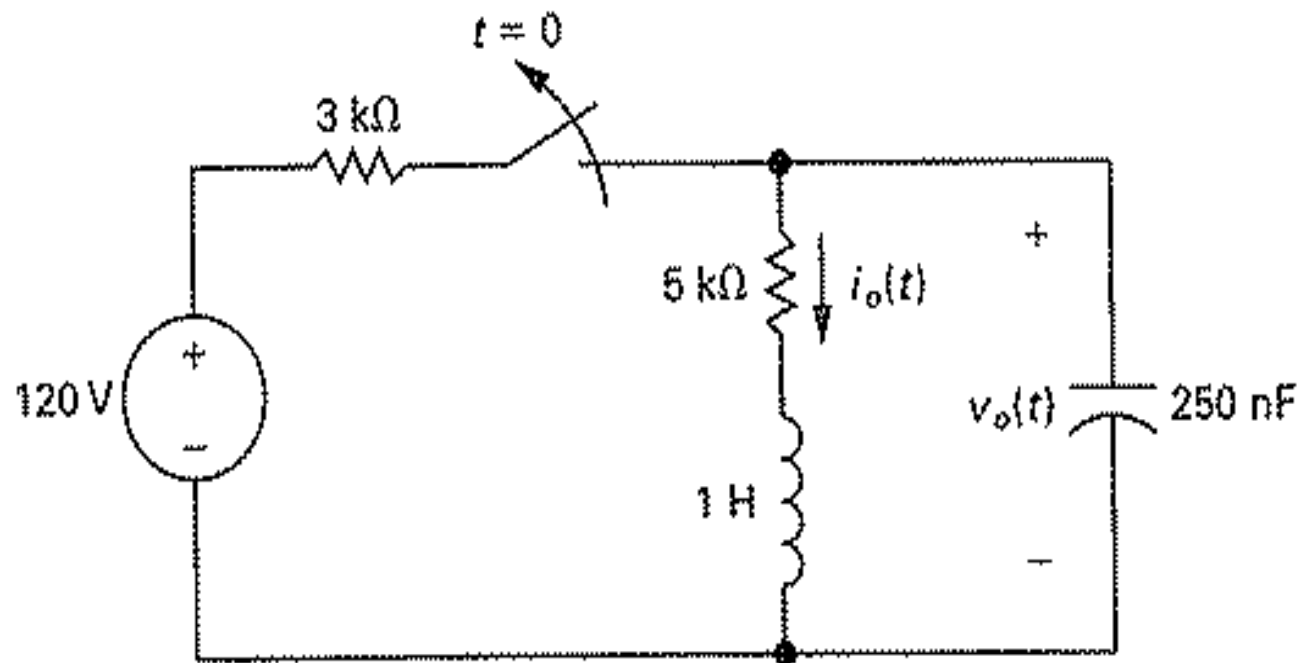

$$i_o(t) = 20 e^{-1000t} - 5 e^{-4000t} \text{ mA}$$

Practice problem: Find $v(t)$

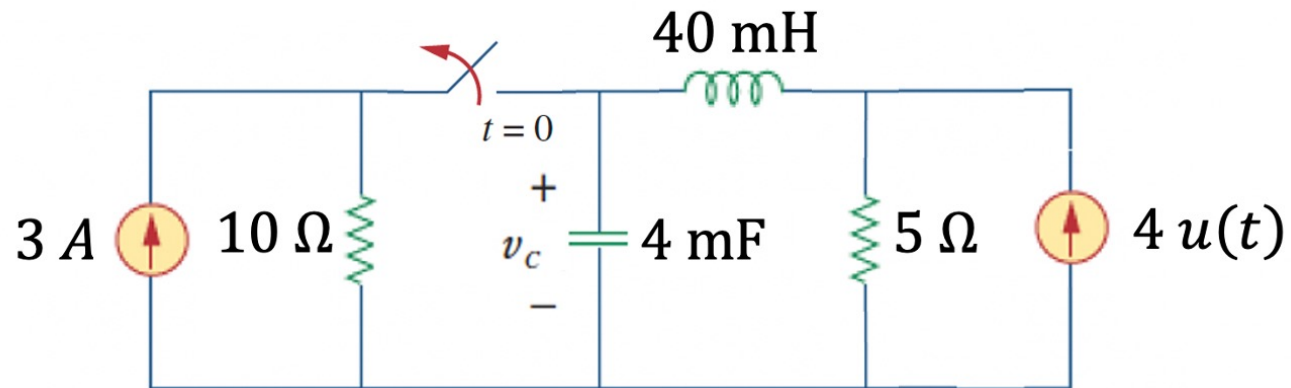

$$v(t) = 10 e^{-62.5t} \cos 48.4t + 2.58. e^{-25t} \sin 48.4t + 20\text{ A}$$