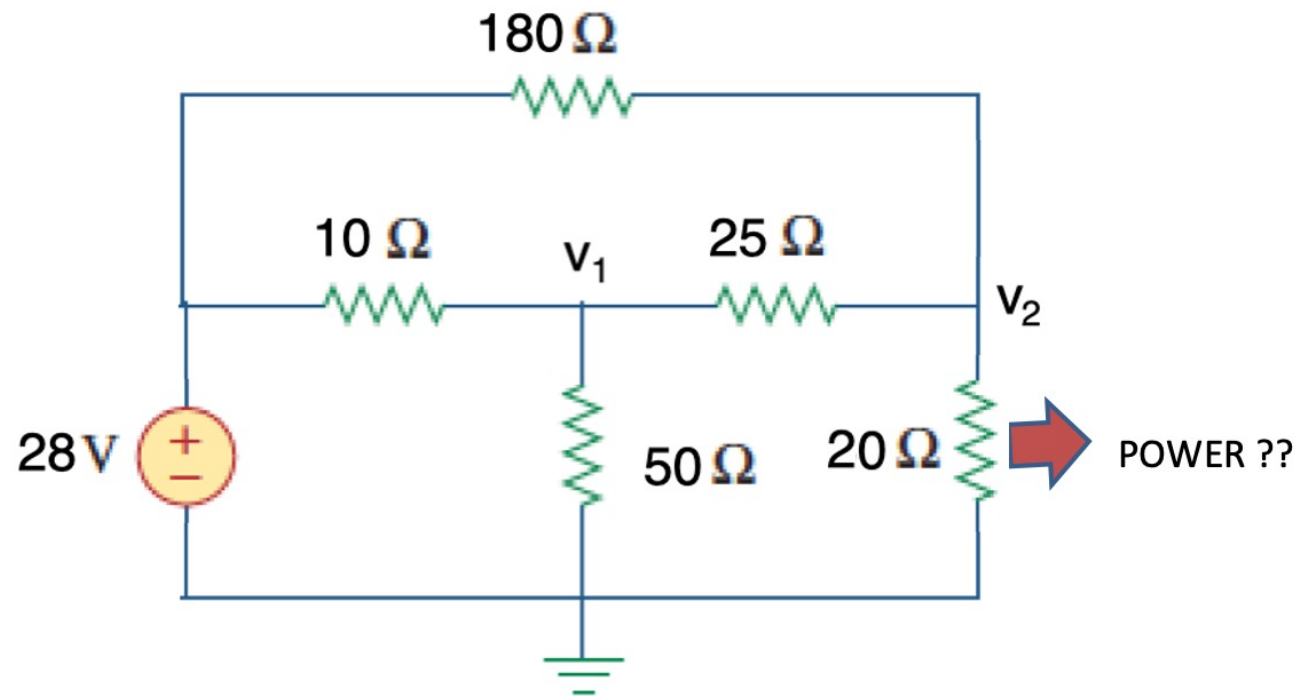


Theorems – 4


maximum power transfer

Power Transfer




- How much power is dissipated in the 20 Ω resistor?
 - Method: node analysis $\rightarrow v_2 = 10 \text{ V}$
 - Power calculation $P = \frac{v_2^2}{20} = \frac{10^2}{20} = 5 \text{ W}$

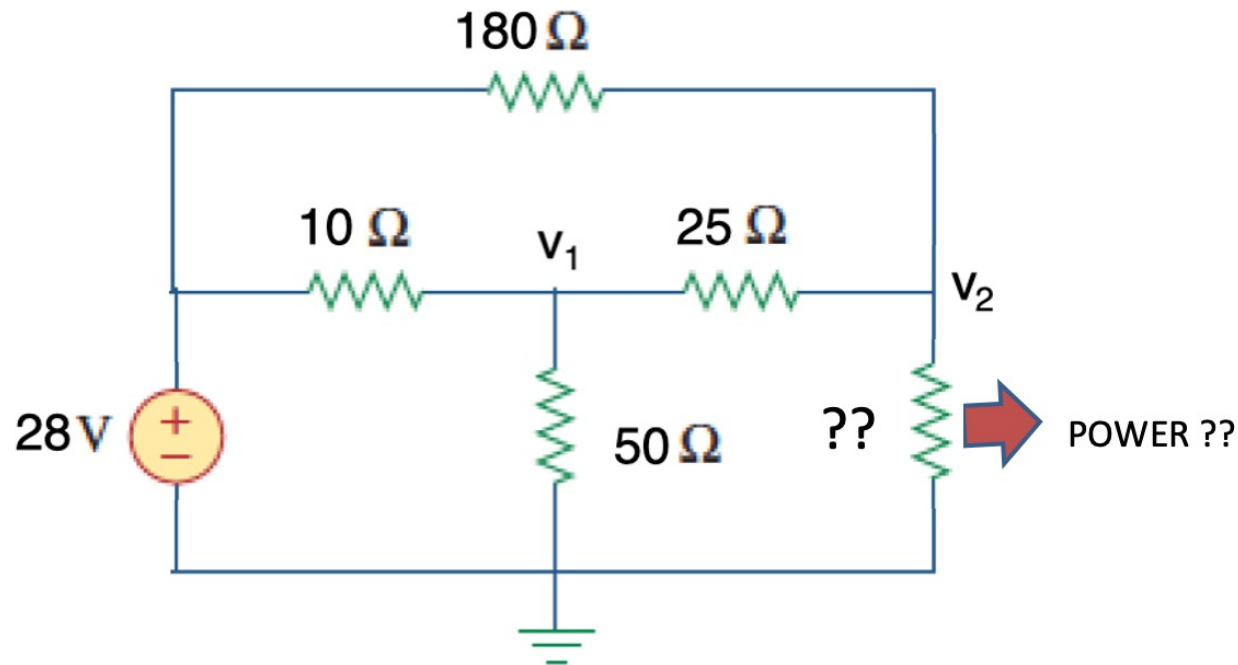- Question – if the resistance was larger/smaller than $20\ \Omega$ could it take more power from the circuit?



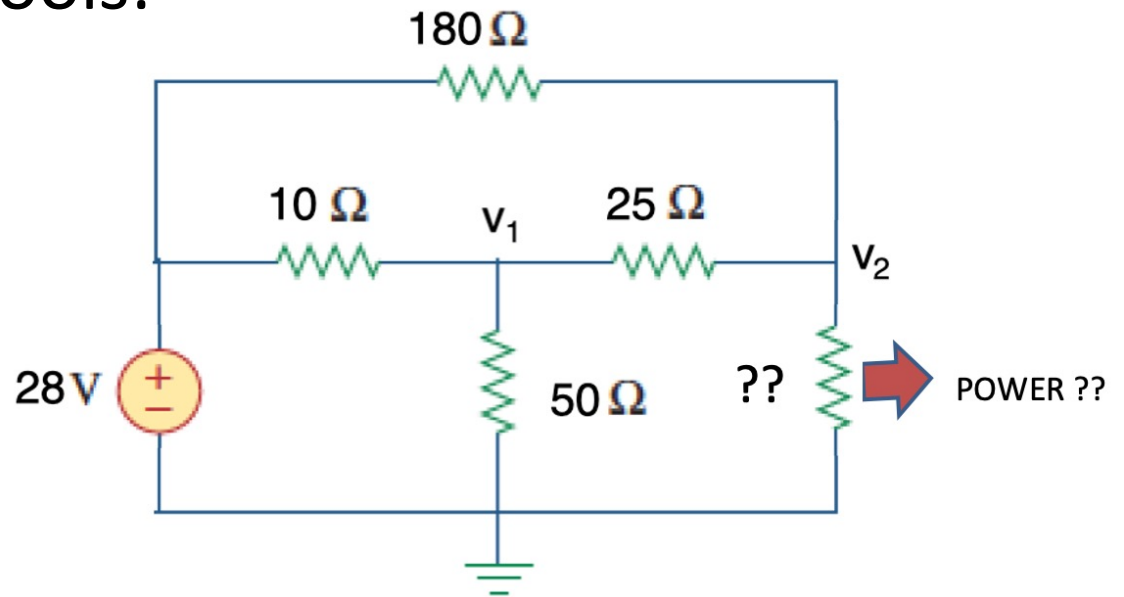- Approach 1 – solve for power in terms of R
 - MatLab symbolic tools:



%% setup problem

`syms v1 v2 R`

`[s1,s2] = solve(v1/50+(v1-28)/10+(v1-v2)/25==0, ...`

`v2/R+(v2-v1)/25+(v2-28)/180==0,v1,v2)`

`pow = s2^2/R;`

%% check for R = 20 ohms

`subs(s2,R,20)`

`subs(pow,R,20)`

`ans =`

`10`

`ans =`

`5`


- Optimize

% optimize over R

`dpow = diff(pow,R);`

`Rstar = solve(dpow)`

`eval(subs(pow,R,Rstar))`

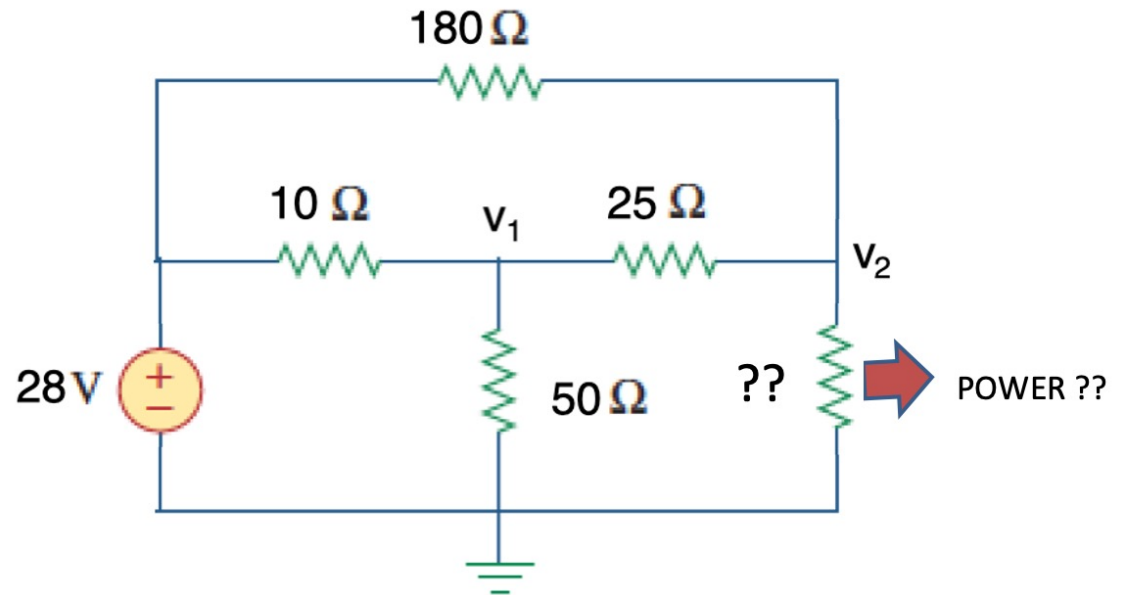

`Rstar =`

`225/8`

`ans =`



`5.1467e+00`

$$R^* = \frac{225}{8} = 28.1 \, \Omega$$

$$P_{max} = 5.15 \, W$$

- What's going on?


$$P = \frac{148225 R}{4 (8R + 225)^2}$$

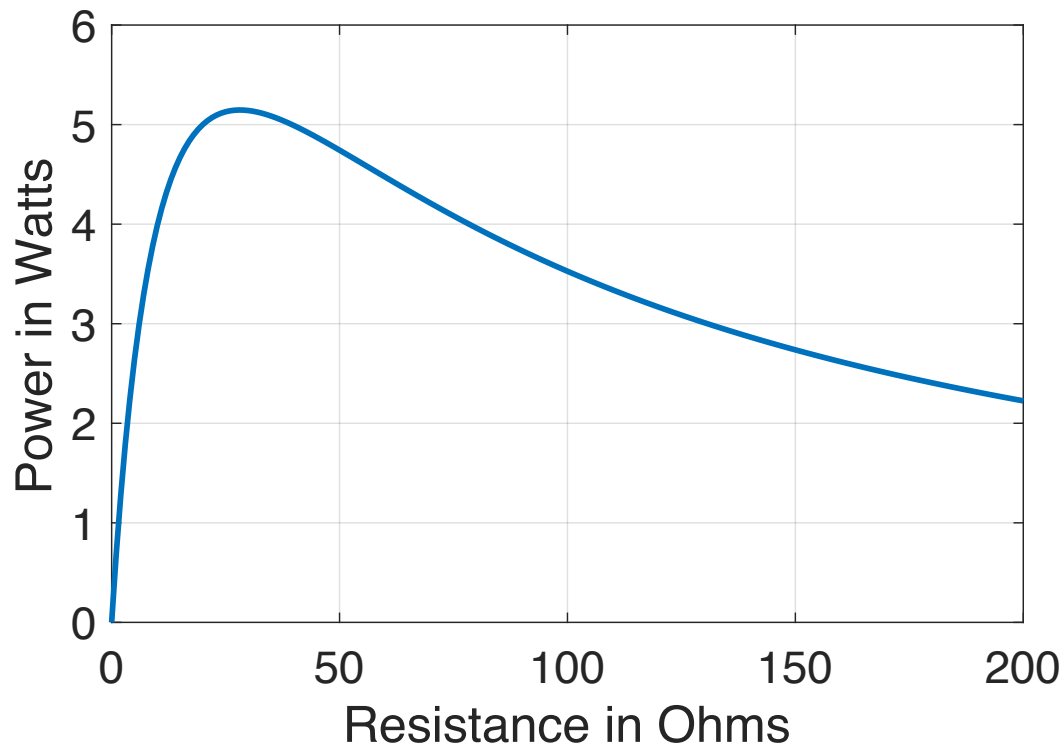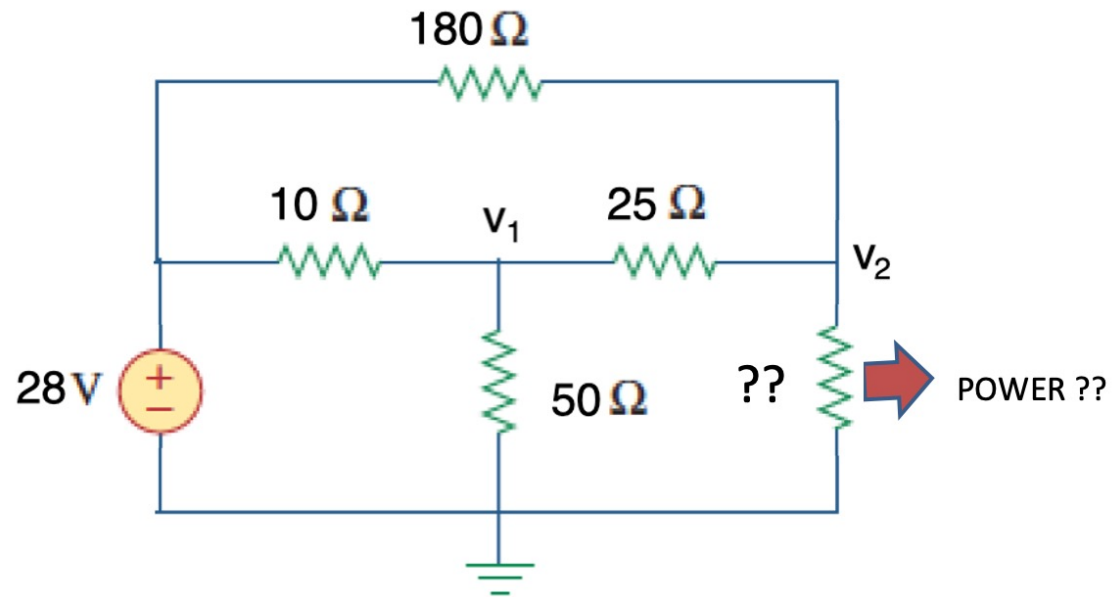



```
Rv = 0:200;
Pv = subs(pow,Rv);
plot(Rv,Pv)
```

Maximum Power Transfer

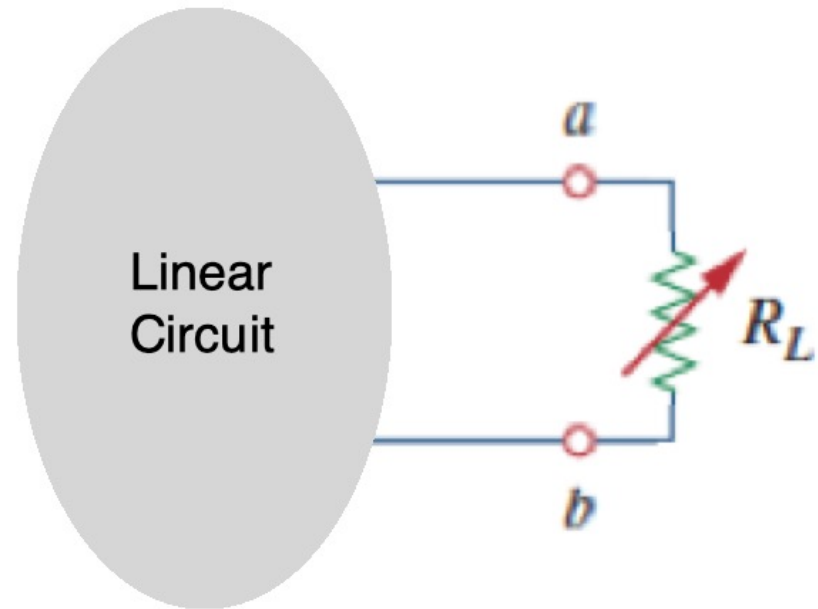- Consider connecting a “load” resistance, R_L , across two points of a circuit
- What happens as it varies?
 - Current
 - Voltage
 - Power



- Use the Thevenin model

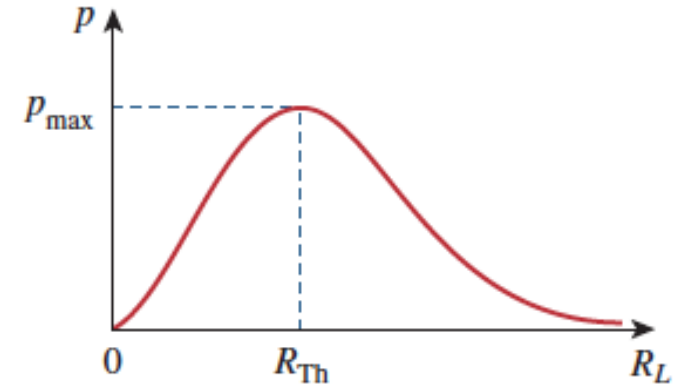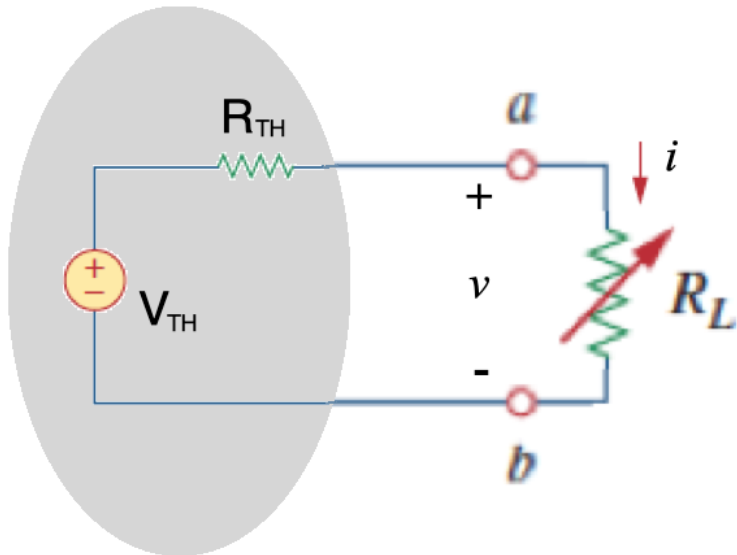


$$v = \frac{R_L}{R_L + R_{th}} v_{th}$$

$$p = \frac{v^2}{R_L} = \frac{R_L}{(R_L + R_{th})^2} v_{th}^2$$


- $\frac{\partial p}{\partial R_L} = 0$ yields a max of $P_{max} = \frac{V_{th}^2}{4R_{th}}$ when $R_L = R_{th}$


Example: find a load resistance to dissipate maximum power

$20\ \Omega, 20\ W$

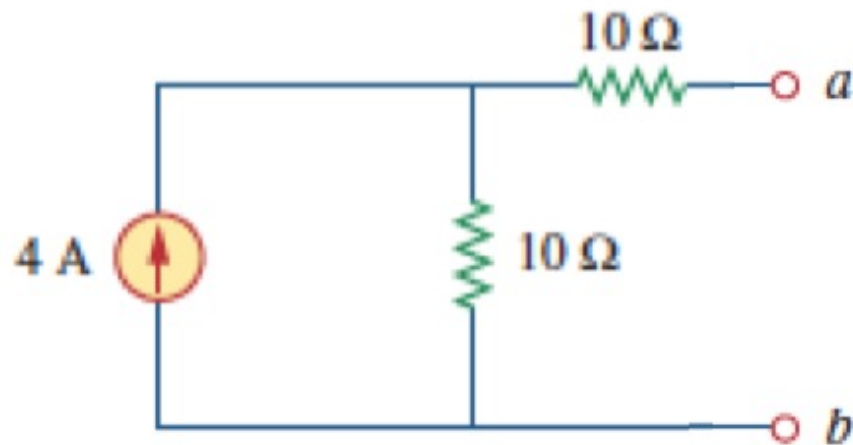

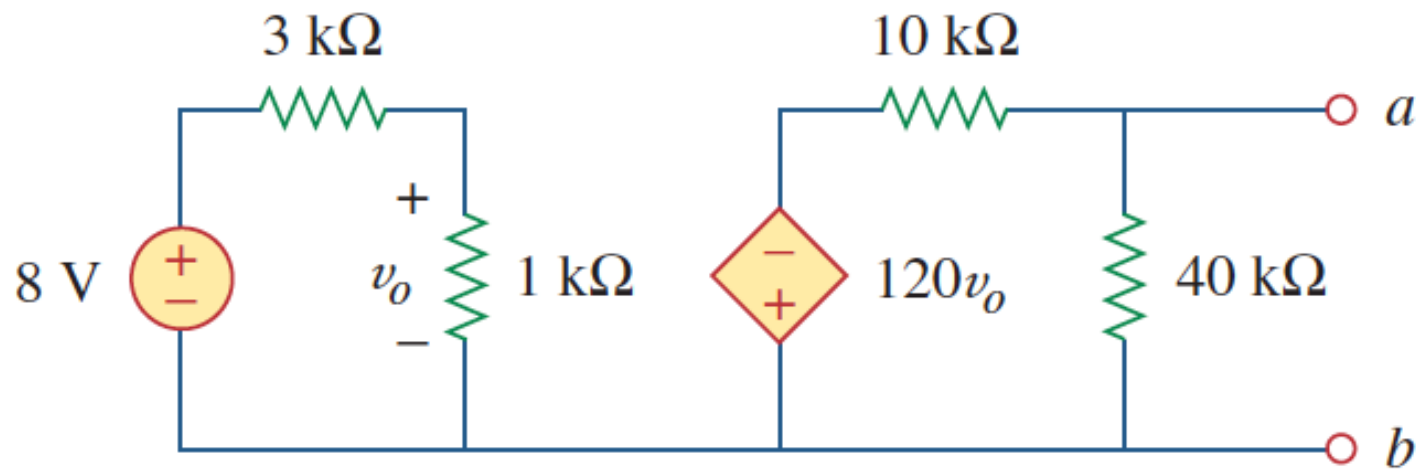
Example: find the load that dissipates maximum power



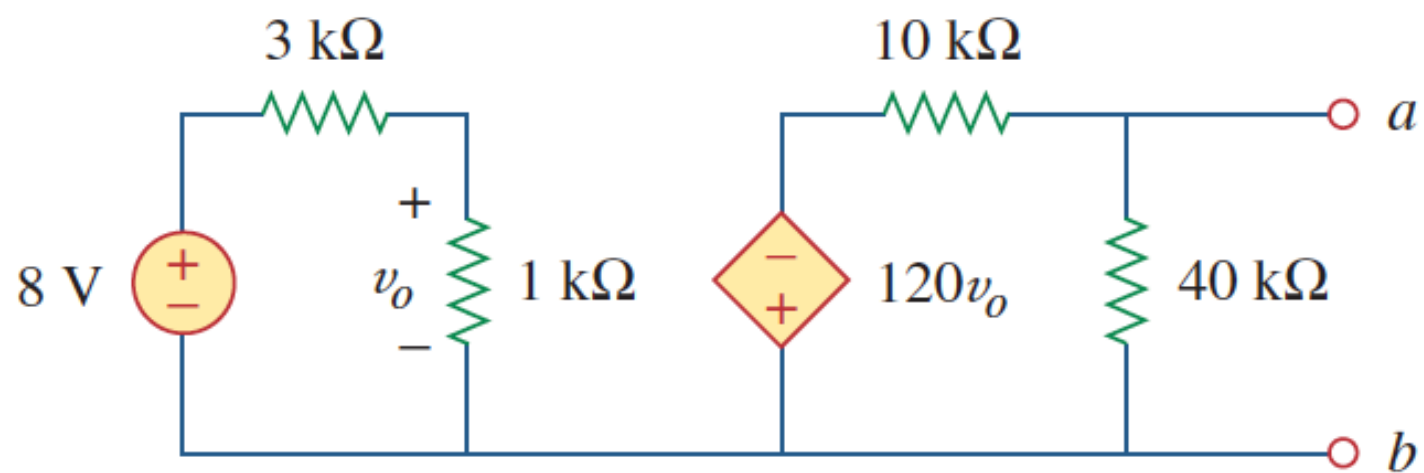


$8\text{ k}\Omega$

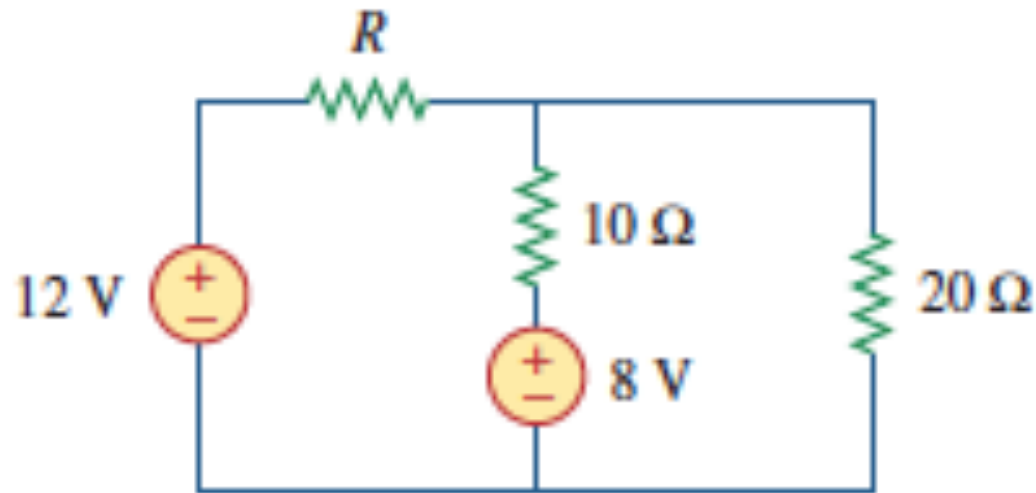Example (trick): find R to maximum the power delivered to the $10\ \Omega$ resistor




Maximum AC Power

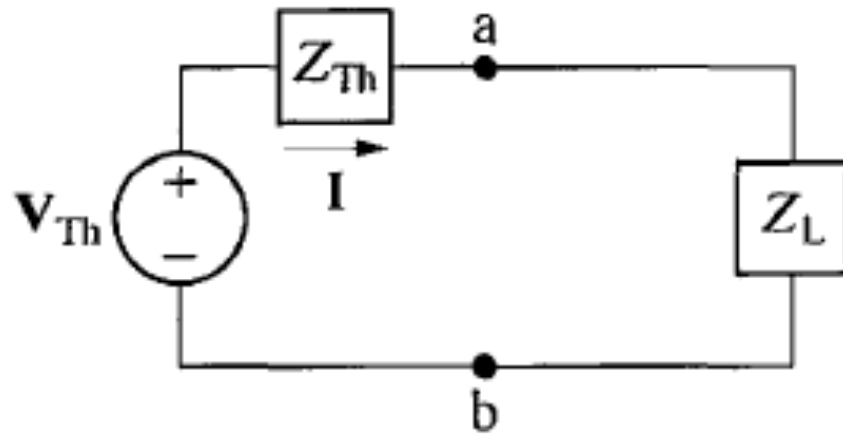- Given a phasor Thevenin model, how do we get maximum power to Z_L ?




- For sinusoidal sources and RLC circuits, power is

$$S = \frac{|\mathbf{I}|^2}{2} Z_L \quad P = \frac{|\mathbf{I}|^2}{2} R_L$$

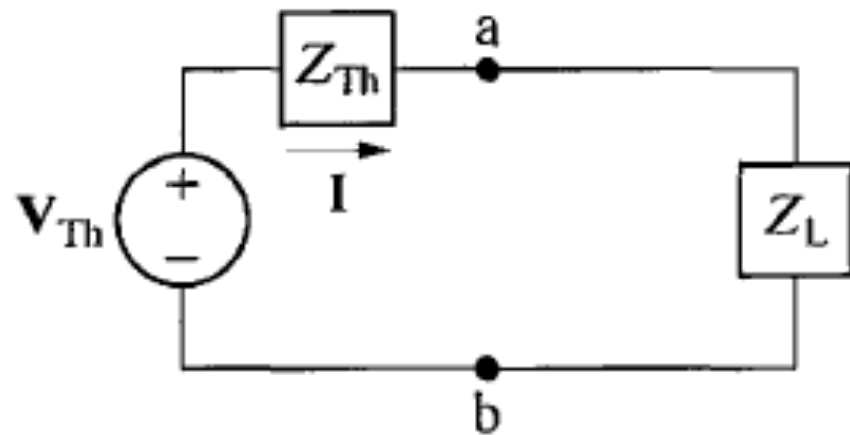

- For our problem
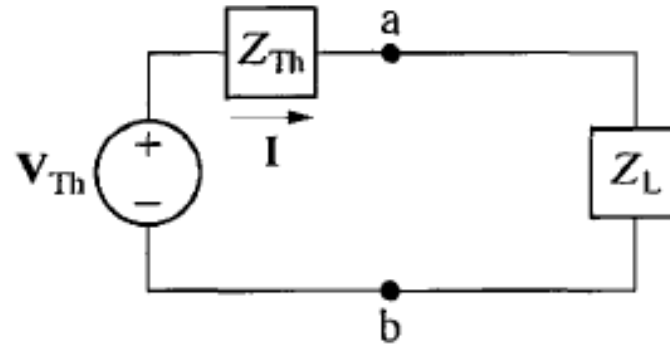
$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{Z_{Th} + Z_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$$



- So

$$P = \frac{|I|^2}{2} R_L = \frac{1}{2} \frac{|V_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- We can optimize this using calculus
- How depends upon which parameters we can change

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Example 1 (unusual): both R_L and X_L are free to choose

$$\frac{\partial P}{\partial X_L} = 0 \qquad \frac{\partial P}{\partial R_L} = 0$$

$$Z_L = Z_{Th}^*$$

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Example 2 (more common): X_L is fixed, but R_L is free to choose

$$\frac{\partial P}{\partial R_L} = 0$$


$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$


$$P_{max} = \dots$$

$$P = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Other scenarios:
 - Fixed angle on Z_L
 - Limits on R_L and X_L

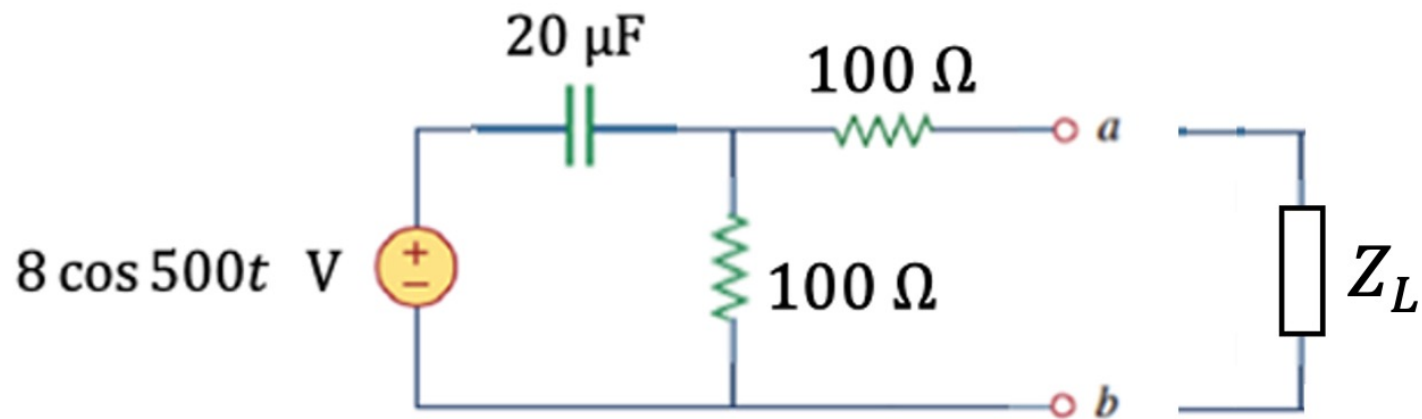Example: find Z_L to maximize the power transfer




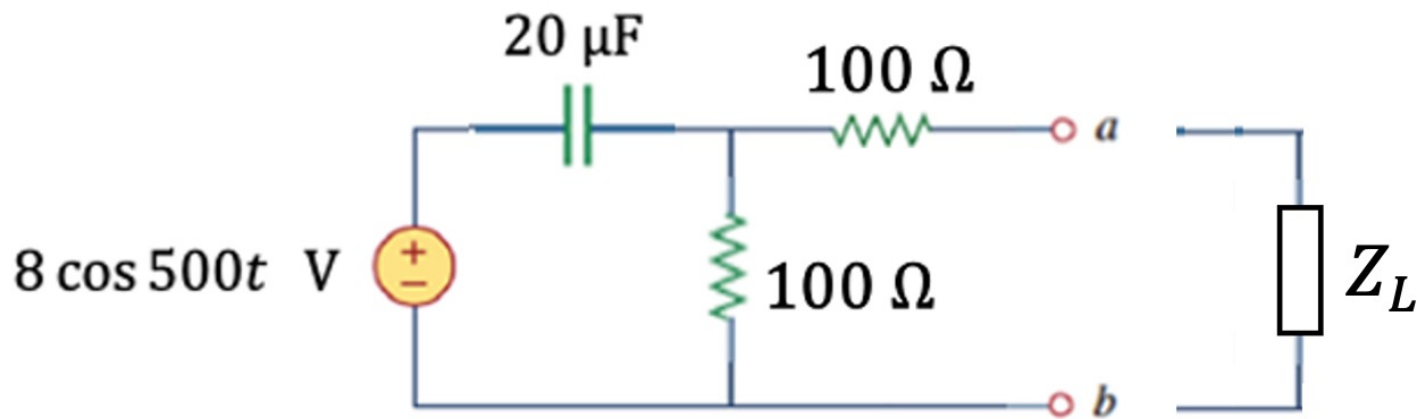

Since $V_{Th} = 4\sqrt{2} \cos(500t + 45^\circ) \text{ V}$ and $Z_{Th} = 150 - j50 \Omega$,
 then $Z_{Th} = 150 + j50 \Omega = 150 \Omega, 0.1 \text{ H}$, and $P = 26.7 \text{ mW}$


$$1.6 \, \Omega, \frac{5}{8} \, W$$

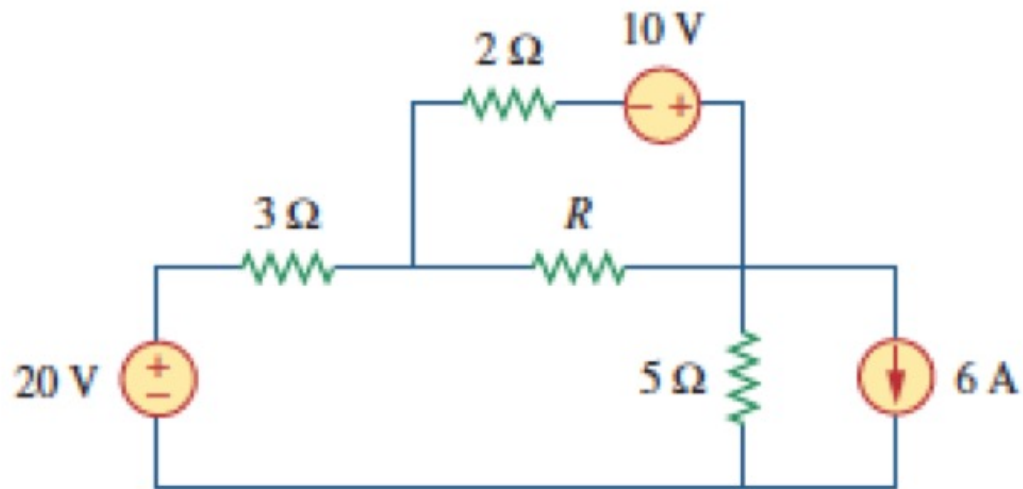Practice problem: maximize the power to R




$3\text{ k}\Omega, 468\text{ mW}$

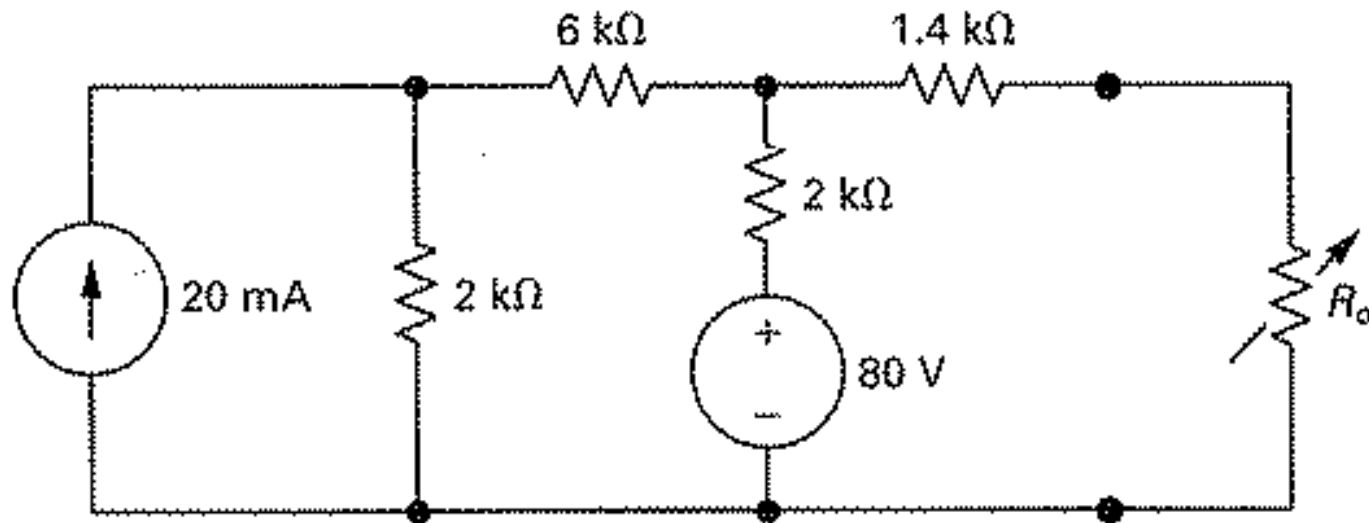Practice problem: maximize the power to R_o



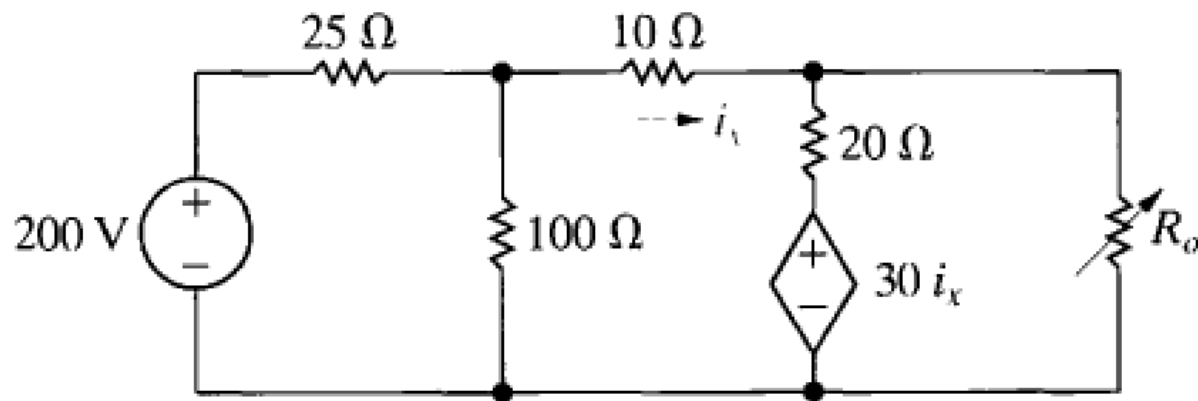
7.5 Ω , 333 W

Practice problem: maximize the power to R_o



$3\ \Omega, 1.2\ \text{kW}$

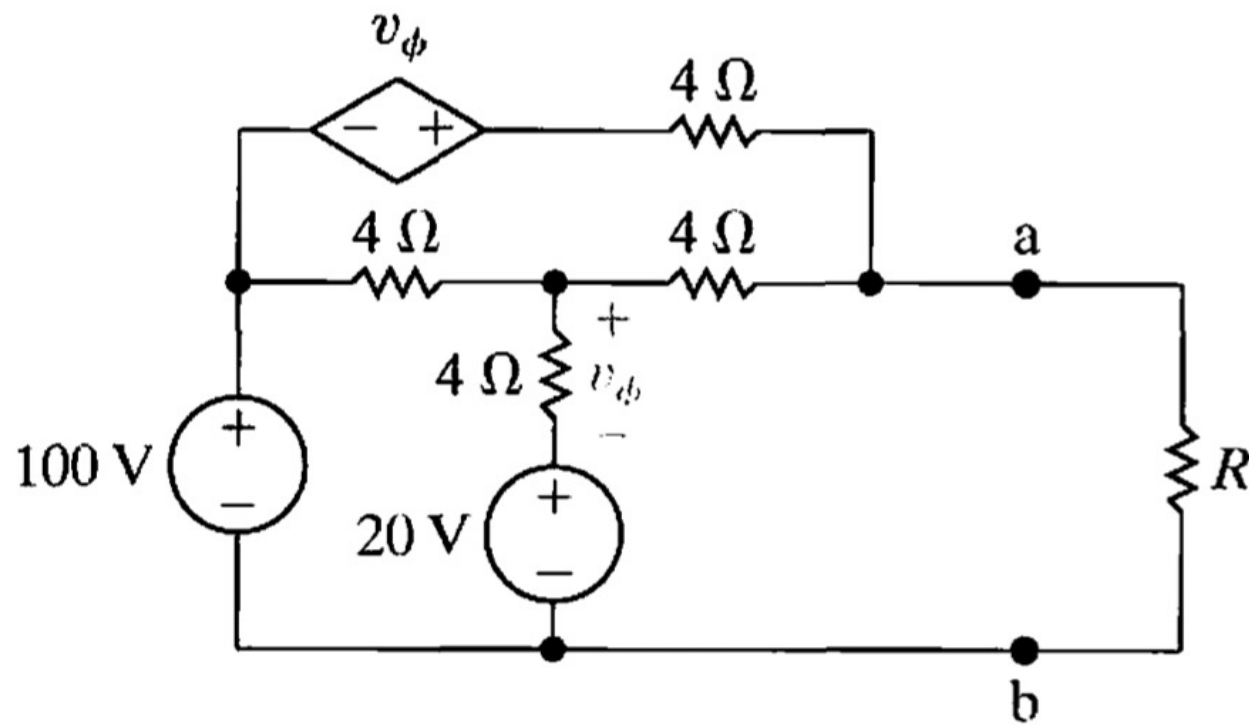Practice problem: maximize the power to R



$4\text{ k}\Omega, 9\text{ mW}$

Practice problem: maximize the power to R_L

